



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612

# DIGITAL ELECTRONICS

EC-EE


Date of Test : 20/02/2025

## ANSWER KEY >

- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (d)  | 13. (b) | 19. (b) | 25. (a) |
| 2. (c) | 8. (a)  | 14. (b) | 20. (c) | 26. (a) |
| 3. (b) | 9. (c)  | 15. (b) | 21. (a) | 27. (c) |
| 4. (d) | 10. (c) | 16. (c) | 22. (a) | 28. (b) |
| 5. (c) | 11. (b) | 17. (c) | 23. (c) | 29. (c) |
| 6. (b) | 12. (b) | 18. (d) | 24. (b) | 30. (a) |

**DETAILED EXPLANATIONS**

1. (c)

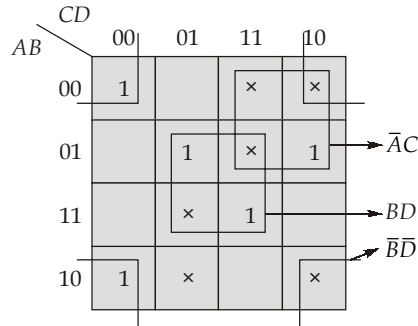

The function is  $BD + \bar{B}\bar{D} + \bar{A}C$

2. (c)

$$\% \text{ Resolution} = \frac{1}{2^N - 1} \times 100\% = \frac{1}{2^4 - 1} \times 100\% = \frac{100}{15} = 6.67\%$$

3. (b)

Given that,

$$\begin{array}{r} 1011001111 \\ + 1 \\ \hline 1011010000 \\ \hline \end{array}$$

Complemented output

∴ No. of flip flop = 5

4. (d)

The flip-flop is connected in toggle mode. Thus,  $Q_{n+1} = \bar{Q}_n$ .

5. (c)

The excitation table of a J-K flip-flop can be given as

$Q_n$	$Q_{n+1}$	J	K	
0	0	0	x	
0	1	1	x	
1	0	x	1	← Required excitation
1	1	x	0	

6. (b)

In the given digital circuit each multiplexer is working as a NOT gate thus it is a ring oscillator

with five NOT gates. The frequency of oscillation will be  $f = \frac{1}{2N t_{pd}}$ .

$N$  = number of NOT gates in cascade

$t_{pd}$  = propagation delay of each NOT gate.

$$\therefore f = \frac{1}{2 \times 5 \times 25ns} = 4 \times 10^6 \text{ Hz} = 4 \text{ MHz.}$$

7. (d)

As  $A, B$  is the select line and  $C$  is the input,

	$I_0$	$I_1$	$I_2$	$I_3$
$\bar{C}$	0	②	④	⑥
$C$	1	③	5	⑦
	0	1	$\bar{C}$	1

So,  $\Sigma m(2, 3, 4, 6, 7) = \text{Total no. of min-terms} = 5$

8. (a)

In general, the range of numbers that can be represented by an  $n$ -bit number with 2's complement representation is  $(-2^{n-1})$  to  $(+2^{n-1} - 1)$ . The 2's complement is the standard representation used for signed binary representation.

9. (c)

The Karnaugh map for POS form can be given by


	$AB$			
$CD$	00	01	11	10
00	0			0
01		0	0	
11		0	0	
10	0			0

POS form of  $f$  is given as,

$$f(A, B, C, D) = (B + D)(\bar{B} + \bar{D})$$

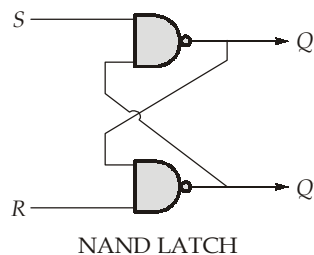10. (c)

SR latch by cross-coupling two NAND gates




If the both  $S$  and  $R$  inputs are set 0 then the result will be as follows:

Truth table for the SR latch using the NAND gates

$S$	$R$	$Q$
0	0	Invalid state ( $Q = Q' = 1$ )
0	1	1
1	0	0
1	1	Previous state

$\therefore Q = 1$   
and  $Q' = 1$

11. (b)

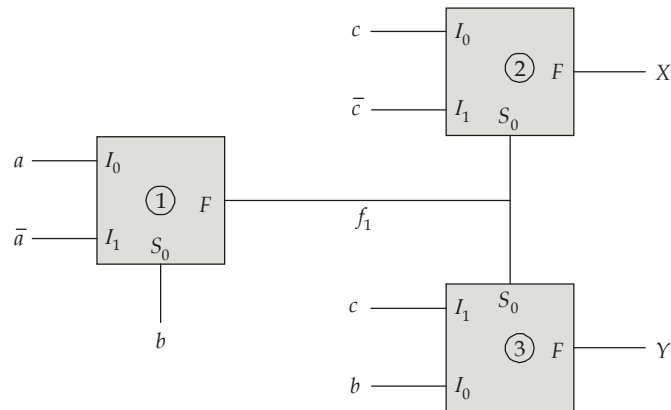

The output of 1<sup>st</sup> MUX,  $f_1 = (\bar{a}b + a\bar{b})$

Thus, 
$$\begin{aligned} \text{Output } X &= (\bar{a}\bar{b} + \bar{a}b)c + (a\bar{b} + \bar{a}b)\bar{c} \\ &= a \oplus b \oplus c \end{aligned}$$

and 
$$\begin{aligned} \text{Output } Y &= (\bar{a}\bar{b} + \bar{a}b)b + (a\bar{b} + \bar{a}b)c \\ &= ab + \bar{a}bc + \bar{a}bc = (ab + \bar{a}bc) + (ab + \bar{a}bc) \\ &= a(b + \bar{b}c) + b(a + \bar{a}c) = ab + bc + ca \end{aligned}$$

So, the given circuit can act as a full-adder.

12. (b)

For  $A = 1,$   
 $B = 0$

the output of ex-or gate will be 1.

So,  $I_0 = 1$   
 $I_1 = 0$   
 $I_2 = B = 0$   
 $I_3 = A = 1$   

$$Y = \bar{C}\bar{D}I_0 + \bar{C}DI_1 + C\bar{D}I_2 + CDI_3 = \bar{C}\bar{D} + CD$$
  

$$Y = C \odot D$$

13. (b)

Initial input to  $J_1K_1$  will be 1 1  
 Input to  $J_0K_0$  will be 1 0  
 After 1<sup>st</sup> clock pulse  $Q_0Q_1$  will be 1 1  
 Input to  $J_1K_1$  after 1<sup>st</sup> clock pulse will be 0 0  
 Input to  $J_0K_0$  after 1<sup>st</sup> clock pulse will be 0 1  
 After 2<sup>nd</sup> clock pulse  $Q_0Q_1$  will be 0 1

14. (b)

The K-map of the given function will be as shown below.

	$yz$	00	01	11	10
$wx$	00	0	0		x
	01	0	0		
	11				
	10	0	0	0	x

$$\text{So, } F(w, x, y, z) = (w + y)(\bar{w} + x)$$

15. (b)

Present State		Next State		$T_B$	$T_A$
$Q_B$	$Q_A$	$Q_B^+$	$Q_A^+$		
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	0	1	0
1	1	0	1	1	0

$$T_B = 1;$$

$$T_A = \bar{Q}_B \bar{Q}_A + \bar{Q}_B Q_A$$

$$T_A = \bar{Q}_B$$

16. (c)

$$\begin{aligned} wx + w(x + y) + x(x + y) &= wx + wx + wy + x + xy \\ &= x(1 + y + w + w) + wy \\ &= x + wy \end{aligned}$$

$\therefore$  option (a) is correct

$$\begin{aligned} \overline{w\bar{x}(y + \bar{z})} + \bar{w}x &= \overline{w\bar{x} + y + \bar{z}} + \bar{w}x \\ &= (\bar{w} + x) + (\bar{y}z) + \bar{w}x \\ &= \bar{w} + x + \bar{y}z \end{aligned}$$

$\therefore$  option (b) is correct

$$\begin{aligned} (w\bar{x}(y + x\bar{z}) + \bar{w}\bar{x})y &= (w\bar{x}y + w\bar{x} \cdot x\bar{z} + \bar{w}\bar{x})y \\ &= w\bar{x}y + \bar{w}\bar{x}y \\ &= (w + \bar{w})\bar{x}y \\ &= \bar{x}y \end{aligned}$$


$\therefore$  option (c) is **incorrect**

$$\begin{aligned} (w + y)(wxy + wyz) &= wxy + wyz + wxxy + wyzy \\ &= wxy + wyz \end{aligned}$$

option (d) is correct

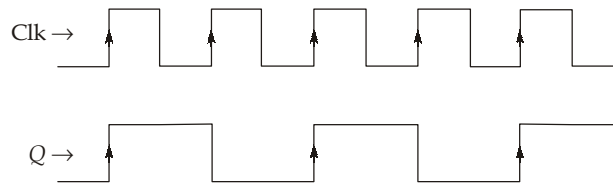17. (c)

J-K flip flop is in toggle mode so after every clock pulse output  $Q$  toggles so output  $Q$  will be as



and Q is clock to MOD-3 down counter then after 5 clock pulses of input clk there are 3 +ve edge of clock pulses applied to counter

∴ output of counter goes to

	<b>A</b>	<b>B</b>
Initially	→ 0	0
1 <sup>st</sup> clk	→ 1	1
2 <sup>nd</sup> clk	→ 1	0
3 <sup>rd</sup> clk	→ 0	1

∴ So the states of Q, A, B respectively are 101.

18. (d)

	A	B	Y	X	T <sub>A</sub>
Initially	1	1	1	1	0
1 <sup>st</sup> CLK →	1	0	1	0	1
2 <sup>nd</sup> CLK →	0	0	0	1	1
3 <sup>rd</sup> CLK →	1	1	1	1	0
4 <sup>th</sup> CLK →	1	0	1	0	

∴  $(ABY)_2 = (101)_2 = 5$

19. (b)

$$Y = \overline{\overline{Q_1 Q_3} \cdot \overline{Q_2 Q_3}}$$

$$= Q_1 Q_3 + Q_2 Q_3$$

$$Y = Q_3(Q_1 + Q_2)$$

To reset the counter output Y must be one

$$Y = Q_3(Q_1 + Q_2)$$

Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
1	0	1	0
1	1	0	0
1	1	1	0

when the counter output  $Q_3 Q_2 Q_1 Q_0 = 1010$ . Then the output Y will give output 1 and it will be given to inverter, so it will reset the counter and again counting will start and it will not go for further combinations.

20. (c)

$$S = (\overline{P+Q} + \overline{P+\overline{P+Q}})(\overline{P+\overline{P+Q}})$$

Consider,  $\overline{P+Q} = X$

and  $\overline{P+(\overline{P+Q})} = Y$

Then,


$$S = (X + Y)Y = XY + Y = Y$$

$$S = \overline{P + (\overline{P + Q})} = \overline{P} \cdot (P + Q) = \overline{P}Q$$

So

for,  $S = 1$ ,  $P$  should be '0' and  $Q$  should be '1'.

21. (a)

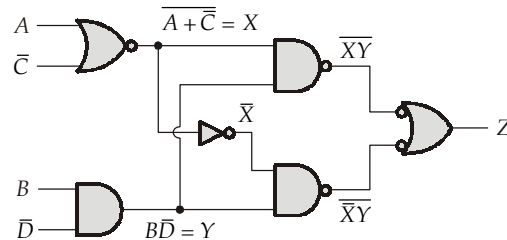

$$\begin{aligned} Z &= XY + \overline{X}Y \\ &= Y = B\overline{D} \end{aligned}$$

22. (a)

$$\begin{aligned} A\overline{C} + \overline{A}C &= A(\overline{A\overline{B} + \overline{A}B}) + \overline{A}(A\overline{B} + \overline{A}B) \\ &= A(\overline{A} + B)(A + \overline{B}) + \overline{A}A\overline{B} + \overline{A}\overline{A}B \\ &= (A\overline{A} + AB)(A + \overline{B}) + \overline{A}B \\ &= AB + AB\overline{B} + \overline{A}B \\ &= AB + \overline{A}B \\ &= B(A + \overline{A}) \\ &= B \end{aligned}$$

**Alternate Solution:**

$$\begin{aligned} A\overline{B} + \overline{A}B &= C = A \oplus B \text{ (Given)} \\ \overline{A}C + A\overline{C} &= C = A \oplus C = A \oplus (A \oplus B) \\ &= 0 \oplus B = B \quad (\because A \oplus A = 0, 0 \oplus A = A) \end{aligned}$$

23. (c)

$$\begin{aligned} S_1 &= A \oplus B \\ C_1 &= AB \\ S &= (A \oplus B) \oplus AB \\ &= (A \oplus B) \cdot \overline{AB} + \overline{(A \oplus B)} \cdot AB \\ &= (\overline{A\overline{B} + \overline{A}B})(\overline{A} + \overline{B}) + (A\overline{B} + \overline{A}B)(AB) \\ &= \overline{A\overline{B} + \overline{A}B} + AB = A + B \\ C &= (A \oplus B) \cdot AB = (\overline{A\overline{B} + \overline{A}B})AB \\ &= 0 \end{aligned}$$

**Alternate Solution:**


A	B	S <sub>1</sub>	C <sub>1</sub>	S (S <sub>1</sub> ⊕ C <sub>1</sub> )	C (S <sub>1</sub> C <sub>1</sub> )
0	0	0	0	0	0
0	1	1	0	1	0
1	0	1	0	1	0
1	1	0	1	1	0

∴ C = 0  
 and S = A + B


24. (b)

Q <sub>n</sub>	D	Q <sub>n+1</sub>	Excitation inputs	
			J	K
0	0	0	0	×
0	1	1	1	×
1	0	0	×	1
1	1	1	×	0

Excitation map for J

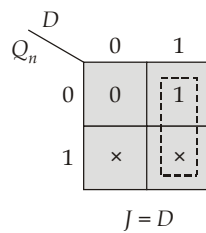


Excitation map for K

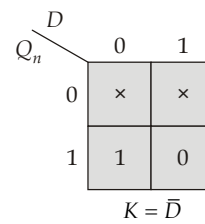

25. (a)


We know,

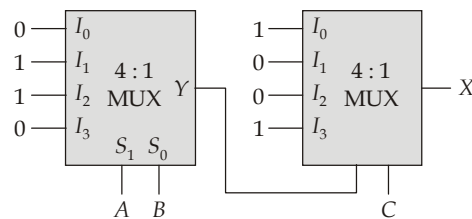

$$\begin{aligned}
 Y &= \bar{A}B + A\bar{B} = A \oplus B \\
 X &= Y \odot C = (\bar{A} \cdot B + A\bar{B}) \cdot \bar{C} + (\bar{A} \cdot B + A\bar{B}) \cdot C \\
 &= (\bar{A} \oplus B) \cdot \bar{C} + \bar{A} \cdot B \cdot C + A\bar{B}C \\
 &= (A \odot B)\bar{C} + \bar{A} \cdot BC + A\bar{B}C \\
 &= (A \cdot B + \bar{A} \cdot \bar{B})\bar{C} + \bar{A} \cdot BC + A\bar{B}C \\
 &= A \cdot B \cdot \bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A} \cdot B \cdot C + A\bar{B}C
 \end{aligned}$$




26. (a)  
Time period,

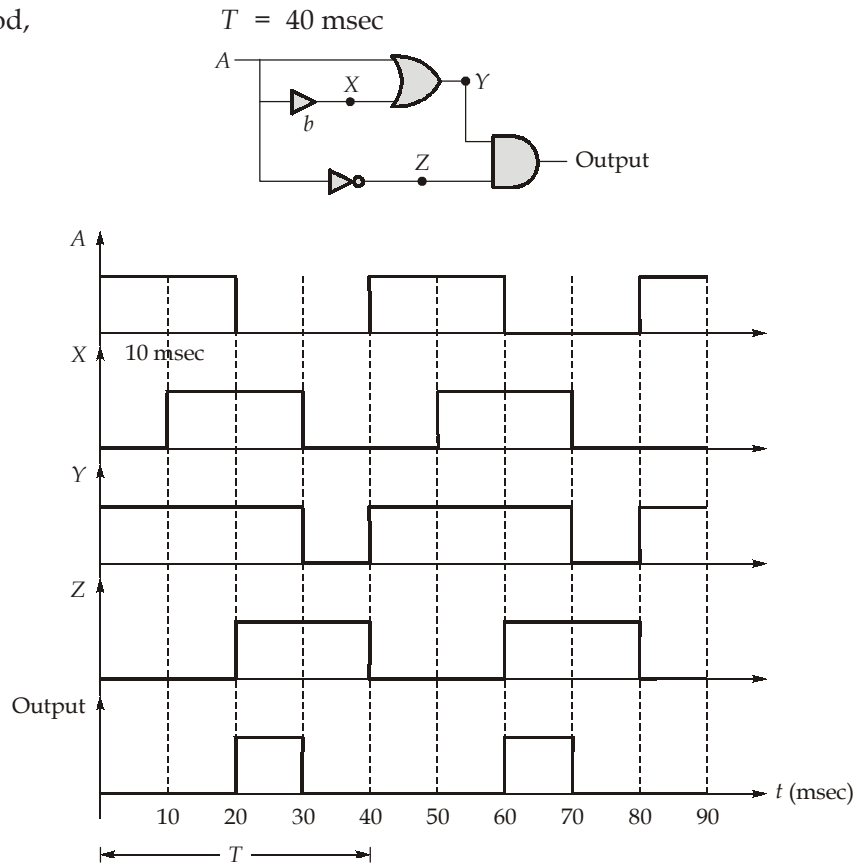

27. (c)  
Given, Boolean function,

$$F = m_0 + m_2 + m_3 + m_5 + m_7$$


Using K-map for minimization

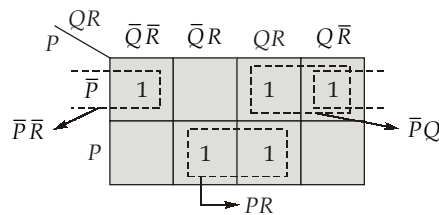

$$F = \bar{P}\bar{R} + \bar{P}Q + PR$$

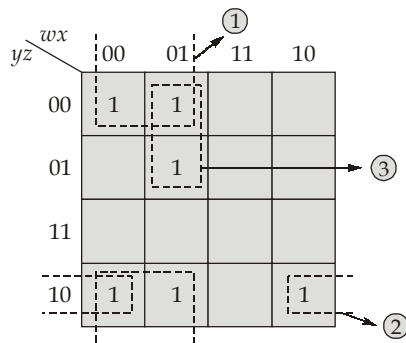28. (b)

$$f(w, x, y, z) = \Sigma(0, 2, 4, 5, 6, 10)$$



∴ 3 essential prime implicants.

29. (c)

By truth table

Number of clock pulse	$D_{in} = A \oplus D$	A	B	C	D
initial	-	1	1	0	1
1	0	0	1	1	0
2	0	0	0	1	1
3	1	1	0	0	1
4	0	0	1	0	0
5	0	0	0	1	0
6	0	0	0	0	1
7	1	1	0	0	0
8	1	1	1	0	0

Hence 8 clock cycles are required for state 1100.

30. (a)

Given configuration is MOD-10 up counter

$$\therefore \text{Frequency at output} = \frac{\text{Clock frequency}}{10} = \frac{20\text{K}}{10} = 2 \text{ kHz}$$

