



**OFFLINE  
TEST SERIES**

# MADE EASY

India's Best Institute for IES, GATE & PSUs

## ESE-2017 : Prelims Exam

UPSC Engineering Services Examination

## E & T

## ENGINEERING

Answer Key & Solutions

Test 3: Part Syllabus Technical  
Electronics Devices and Circuits

- |         |         |         |         |         |
|---------|---------|---------|---------|---------|
| 1. (c)  | 16. (d) | 31. (a) | 46. (a) | 61. (c) |
| 2. (c)  | 17. (b) | 32. (d) | 47. (d) | 62. (a) |
| 3. (d)  | 18. (d) | 33. (b) | 48. (a) | 63. (c) |
| 4. (d)  | 19. (d) | 34. (c) | 49. (c) | 64. (c) |
| 5. (d)  | 20. (b) | 35. (c) | 50. (c) | 65. (b) |
| 6. (c)  | 21. (c) | 36. (a) | 51. (d) | 66. (a) |
| 7. (d)  | 22. (c) | 37. (b) | 52. (b) | 67. (d) |
| 8. (d)  | 23. (c) | 38. (a) | 53. (c) | 68. (a) |
| 9. (a)  | 24. (b) | 39. (a) | 54. (c) | 69. (b) |
| 10. (b) | 25. (b) | 40. (d) | 55. (a) | 70. (d) |
| 11. (b) | 26. (c) | 41. (d) | 56. (b) | 71. (a) |
| 12. (d) | 27. (a) | 42. (c) | 57. (b) | 72. (a) |
| 13. (b) | 28. (d) | 43. (c) | 58. (b) | 73. (a) |
| 14. (a) | 29. (a) | 44. (c) | 59. (c) | 74. (a) |
| 15. (d) | 30. (c) | 45. (c) | 60. (c) | 75. (c) |

**DETAILED EXPLANATIONS**

2. (c)

In a metal, all electrons are free electrons. Therefore, electron concentration remains same even if the temperature is raised. On increasing the temperature, the mobility of electrons decreases due to the more thermal agitation. Therefore, electrical conductivity of a metal has negative temperature coefficient.

3. (d)

Potential barrier now becomes  $(V_0 + V_r)$  increase

where  $V_r$  is applied reverse bias voltage

space charge layer width  $W \propto \sqrt{V_0 + V_r}$

so, increase electric field

$$E \propto x_{no} N_D$$

or

$$E \propto x_{po} N_A$$

where,  $x_{no}$  - part of depletion width on  $n$ -side increases as  $W$  increases with ' $V_r$ '.

$x_{po}$  - part of depletion width on  $p$ -side increases as  $W$  increases with ' $V_r$ '.

so, electric field  $E$  increase.


5. (d)

From the given diagram  $V_{GS} = 0$

since  $V_{GS} < V_T$ , MOSFET will be in OFF state.

hence  $V_D = 6\text{ V}$  and  $I_D = 0$

6. (c)

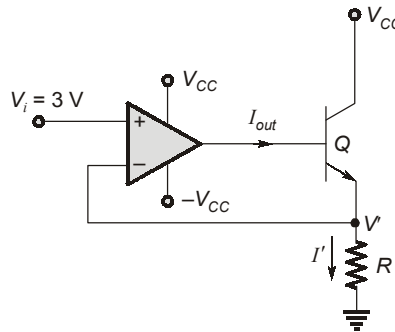

since op-amp draws no current, 
$$I_{out} = I_B$$

$$V' = V_i = 3\text{ V}$$

$$\therefore \text{Current } I' = \frac{V'}{R} = \frac{3}{10}\text{ A}$$


$$\therefore I' = I_E = \frac{3}{10}\text{ A}$$

$$I_E = (1 + 99)I_B$$

$$\frac{3}{10} = 100 I_B \text{ (or) } \frac{3}{10} = 100 I_{out}$$

$$\therefore I_{out} = \frac{3}{1000} = 3\text{ mA}$$

11. (b)

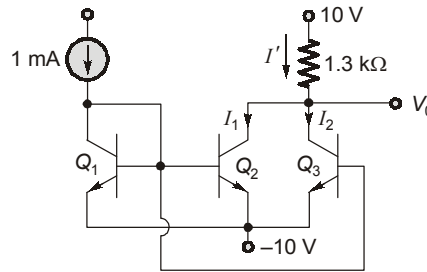

Assume current  $I'$  flows through the resistor  $1.3 \text{ k}\Omega$ .

Also given  $Q_1$ ,  $Q_2$  and  $Q_3$  are identical and  $\beta$  is large

From the given diagram,  $Q_1, Q_2$  is pair of transistors form current mirror circuit. Therefore the current  $I_1 = 1 \text{ mA}$

Similarly  $Q_2, Q_3$  pair of transistors also form current mirror circuit. Hence the current  $I_2 = 1 \text{ mA}$ .

$\therefore$  The current  $I' = I_1 + I_2 = 1 + 1 = 2 \text{ mA}$

$$\begin{aligned} \text{output voltage } V_0 &= 10 \text{ V} - 1.3 \text{ k}\Omega \times (2 \text{ mA}) \\ &= (10 - 1.3 \times 2) \text{ V} \\ &= (10 - 2.6) \text{ V} \\ V_0 &= 7.4 \text{ V} \end{aligned}$$

12. (d)

Given  $I_{DSS} = 10 \text{ mA}$ ,  $V_P = -4 \text{ V}$

$$I_D = I_{DSS} \left[ 1 - \frac{V_{GS}}{V_P} \right]^2$$

by KVL in the input loop

$$\begin{aligned} -2.5 - V_{GS} &= 0 \\ \Rightarrow V_{GS} &= -2.5 \\ I_D &= 10 \times 10^{-3} \left[ 1 - \frac{-2.5}{-4} \right]^2 \text{ A} \\ I_D &= 1.4 \text{ mA} \\ 15 - I_D \times 2 \text{ k}\Omega - V_{DS} &= 0 \\ \therefore V_{DS} &= 15 - I_D \times 2 \text{ k}\Omega = 15 - 2.8 \\ V_{DS} &= 12.2 \text{ V} \end{aligned}$$

13. (b)

We know that

$$\begin{aligned} I_{CEO} &= (1 + \beta) I_{CBO} \\ &= (49 + 1) 20 \times 10^{-6} \\ I_{CEO} &= 1 \text{ mA} \end{aligned}$$

Now, by applying KVL around the loop that includes  $V_{CC}$ ,  $R_B$  and ground

$$\begin{aligned} I_{BQ} &= \frac{V_{CC} - V_{BEQ}}{R_B} = \frac{10 - 0.7}{100 \text{ k}\Omega} = 93 \mu\text{A} \\ \therefore I_{CQ} &= \beta I_{BQ} + I_{CEO} \\ &= 49 \times 93 \times 10^{-6} + 1 \times 10^{-3} \text{ A} \\ I_{CQ} &= 5.557 \text{ mA} \end{aligned}$$

22. (c)

By voltage division rule at inverting terminal of op-amp

$$V_f = \frac{V_0 \cdot R_1}{R_1 + R_2}$$

The feedback factor  $\beta = \frac{R_1}{R_1 + R_2} = \frac{10}{11}$

closed loop gain  $A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} = \frac{10^4}{1 + 10^4 \times \frac{10}{11}}$

$\therefore A_{CL} \approx 1.1$

25. (b)

Here,

$$V_i = 2V$$

$\therefore D_1 \rightarrow$  OFF and  $D_2, D_3, D_4$  are ON

$$V_0 = 0.6 \times 3 = 1.8V$$

$$I = \frac{10 - 1.8}{2k} = 4.1mA$$

27. (a)


For four-point method

$$R = 4.53 \times \frac{V}{I} = 4.53 \times \frac{0.22}{10 \times 10^{-3}} \text{ } \Omega/\text{square}$$

$\therefore R = 100 \Omega/\text{square}$

29. (a)

As LED is forward bias,

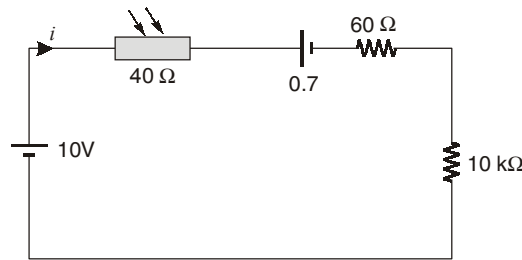

$$i = \frac{10 - 0.7}{(10k + 100)} = 9.2079 \times 10^{-4} \text{ A}$$

$\therefore$

$$V_{10k\Omega} = 10k \times 9.2079 \times 10^{-4} \approx 9.21 \text{ V}$$

30. (c)

$$n = 1 \times \frac{10^{16}}{m^3} = 1 \times \frac{10^{16}}{10^6 \text{ cm}^3} = 1 \times \frac{10^{10}}{\text{cm}^3}$$

$$J_n = 50 \text{ A/cm}^2$$

$$E = 15 \text{ V/cm}$$

$$\mu_n = \frac{J_n}{neE} = \frac{50}{1 \times 10^{10} \times 1.6 \times 10^{-19} \times 15}$$

$$\mu_n = 2.083 \times 10^9 \text{ cm}^2/\text{V-s}$$

34. (c)

During an electron transition across the energy gap in an indirect energy gap material, both momentum and energy of electron change.

38. (a)

$$V_z = V_{BE} + I \times 1.8 \text{ k}\Omega$$

$$6.2 = 0.7 + 1.8 \text{ k} \times I$$

$$I = \frac{6.2 - 0.7}{1.8} \text{ mA} = 3.06 \text{ mA}$$

39. (a)

Given  $\beta = 100$

Let the transistor be in active region

At the input loop

$$2.7 - 40 \times 10^3 I_B - 0.7 = 0$$

$$I_B = \frac{1}{20} \text{ mA}$$

$$I_C = \beta I_B$$

$$= 5 \text{ mA}$$

$$V_{CE} = 10 - 2.5 \times 10^3 \times 5 \times 10^{-3}$$


$$V_{CE} = -2.5 \text{ V}$$

Transistor is in saturation region

42. (c)

Pinch off voltage in JFET depends on dimensions of device.

43. (c)

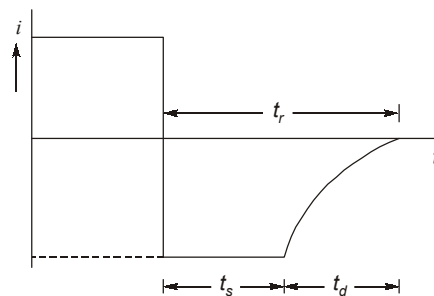


Reverse recovery time  $t_r = t_s + t_d$

$t_s$  = storage time (to remove stored minority carriers)

$t_d$  = to bring the diode in reverse biased condition (i.e.  $V_D = V_R$ ) and current  $i = 0$ .

44. (c)

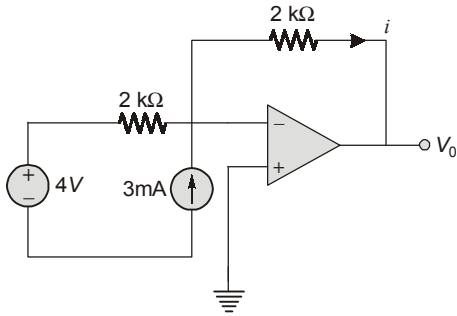

$$i = 3\text{ mA} + \frac{4}{2}\text{ mA} = 5\text{ mA}$$

∴

$$V_0 = -(2\text{ k}\Omega)(5\text{ mA}) = -10\text{ volts}$$

45. (c)

$$V_0 = \left(1 + \frac{20}{10}\right)6.3 = 18.9\text{ volts}$$

46. (a)

Variable capacitance diodes are used under reverse-bias condition.

47. (d)

In a MOSFET operating in the saturation region, the channel length modulation effect causes a decrease in the output resistance.

48. (a)


Oscillator is a feedback amplifier which satisfies the Barkhausen criterion given below:

(i) Loop gain  $A\beta$  must be slightly greater than 1.

(ii) Loop phase shift must be multiple of  $360^\circ$ .

Emitter follower is common-collector amplifier which has voltage series feedback.

49. (c)

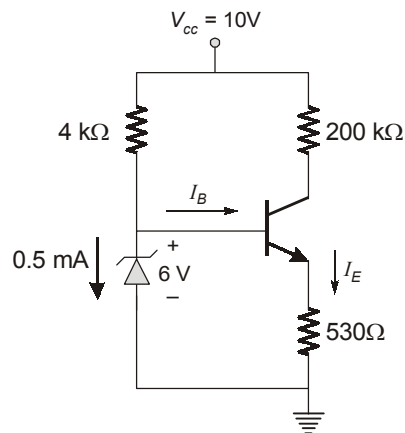

From KVL,

$$0.7 + 530 I_E = 6$$

$$\begin{aligned} \therefore I_E &= \frac{5.30}{530} = 10 \text{ mA} \\ \text{So, } I_{4 \text{ k}\Omega} &= \frac{10 - 6}{4 \times 10^3} = 1 \text{ mA} \\ \therefore I_B &= 0.5 \text{ mA} \\ \text{Now, } 1 + \beta &= \frac{I_E}{I_B} = \frac{10}{0.5} = 20 \\ \therefore \beta &= 19 \end{aligned}$$

**52. (b)**

We shall assume that both diodes are conducting. It follows that  $V_B = 0$  and  $V_0 = 0$ . The current through  $D_2$  can now be determined from

$$I_{D2} = \frac{10 - 0}{10 \times 10^3} = 1 \text{ mA}$$

Writing node equation at  $B$ ,

$$\begin{aligned} I + (1 \times 10^{-3}) &= \frac{0 - (-10)}{5 \times 10^3} \\ I &= 1 \text{ mA} \end{aligned}$$

Thus  $D_1$  and  $D_2$  are conducting as originally assumed, and the final result is  $I = 1 \text{ mA}$  and  $V_0 = 0 \text{ V}$ .

**54. (c)**

Photodiode is always operated in reverse bias and when light is off current flowing through this diode is reverse saturation current as working as a normal diode when light is off.

**56. (b)**

$$I_0 = \frac{V_0 - V_S}{R_L} \quad \text{where } V_0 = \left(1 + \frac{R_L}{R_S}\right) V_S$$

**57. (b)**

An op-amp based non-inverting amplifier is voltage series feedback amplifier. Voltage series feedback is also known as series-shunt feedback.

**59. (c)**

$$\text{Generation rate} = \frac{\Delta n}{\tau_n} = \frac{\Delta p}{\tau_p}$$

Excess carrier concentration,  $\Delta n = \Delta p$

$$\text{generation rate} = \frac{10^{15}}{10 \times 10^{-6}} = 10^{20} \text{ pair/cm}^3/\text{sec}$$

60. (c)

$$n_i^2 \propto T^3$$

$$\left(\frac{n_i}{2n_i}\right)^2 = \left(\frac{T_1}{T_2}\right)^3$$

$$T_2 = \sqrt[3]{4} T_1$$

$$T_2 = 1.587 T_1$$

61. (c)

$$I_{D\text{sat}} = \frac{W \mu_n C_{ox}}{2L} (V_{GS} - V_T)^2$$

$$4 \times 10^{-3} = \left(\frac{W}{L}\right) 25 \times 10^{-6} (4)^2$$

$$\frac{W}{L} = 10$$

$$W = 10L = 12.5 \mu\text{m}$$

63. (c)

$$P_{D(\text{derate})} = P_{D(\text{max})} - [(\text{derating factor}) \times \Delta T]$$

$$= 400 \text{ mW} - (3.2 \text{ mW}/^\circ\text{C}) [90^\circ\text{C} - 50^\circ\text{C}]$$

$$= 400 \text{ mW} - 128 \text{ mW}$$

$$= 272 \text{ mW}$$

$$\therefore P_{D(\text{derate})} = 272 \text{ mW}$$

64. (c)

Common base current gain

$$\alpha = \frac{\Delta I_C}{\Delta I_E} = \frac{0.995 \times 10^{-3}}{1.0 \times 10^{-3}} = 0.995$$

 $\therefore$  Common emitter current gain is

$$\beta = \frac{\alpha}{1 - \alpha} = \frac{0.995}{1 - 0.995} = 199$$

65. (b)

Given  $I = 5 \text{ mA}$ ,  $T = 300 \text{ K}$ forward resistance of a PN junction diode  $r_f = \frac{\eta V_T}{I}$ 

$$V_T = \frac{T}{11600}$$

$$r_f = \frac{2 \times \frac{T}{11600}}{5 \times 10^{-3}} = \frac{2 \times 300}{11600 \times 5 \times 10^{-3}}$$

$$\therefore r_f = 10.34 \Omega$$



73. (a)

A device can be used as oscillator if it exhibits negative resistance property and tunnel diode exhibited this property so, A and R both are true and R is correct explanation.

75. (c)

For the feedback amplifier to oscillate its loop gain is unity and phase shift is zero.

○○○○