

Try to avoid
calculation
mistake



MADE EASY

Leading Institute for ESE, GATE & PSUs

Highlights final
answers
use Headings

ESE 2025 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

Electrical Engineering

Test-1 : Electric Circuits + Engineering Mathematics

Name :

Roll No :

Test Centres

Delhi ☒ Bhopal ☐ Jaipur ☐
Pune ☐ Kolkata ☐ Hyderabad ☐

Student's Signature

Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	39
Q.2	45
Q.3	
Q.4	48
Section-B	
Q.5	33
Q.6	34
Q.7	
Q.8	
Total Marks Obtained	199

Signature of Evaluator

Cross Checked by

Sourabh
kumar

Try to avoid
calculation
mistake



MADE EASY

Leading Institute for ESE, GATE & PSUs

Highlights final
answers
use Headings

ESE 2025 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

Electrical Engineering

Test-1 : Electric Circuits + Engineering Mathematics

Name : Rajat Dixit

Roll No : E E 2 5 M T D L A D 1 1

Test Centres

Delhi ☒ Bhopal ☐ Jaipur ☐
Pune ☐ Kolkata ☐ Hyderabad ☐

Student's Signature

Rajat

Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	39
Q.2	45
Q.3	
Q.4	48
Section-B	
Q.5	33
Q.6	34
Q.7	
Q.8	
Total Marks Obtained	199

Signature of Evaluator

Cross Checked by

Sourabh
umar

IMPORTANT INSTRUCTIONS

CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.

DONT'S


1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

DO'S

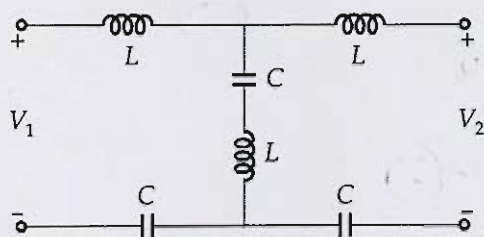
1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

Section A : Electric Circuits

1 (a) Determine Z-parameters for network shown



[12 marks]

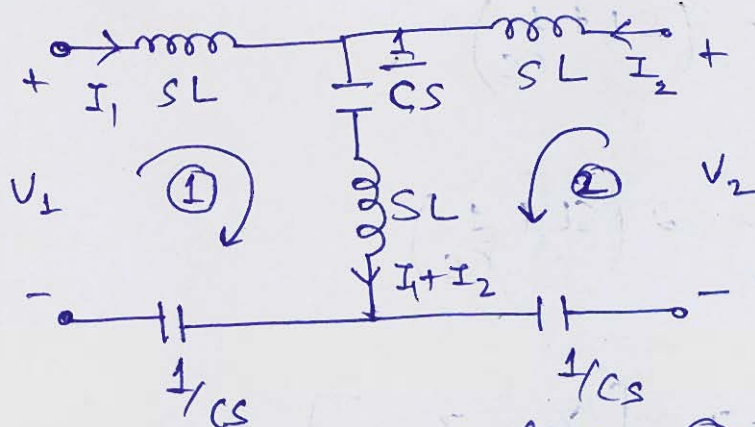

Applying KVL in loop - ①

$$V_1 = SL I_1 + \left(SL + \frac{1}{CS} \right) I_1 + \left(SL + \frac{1}{CS} \right) I_2 + \frac{1}{CS} I_1$$

$$V_1 = 2 \left(SL + \frac{1}{CS} \right) I_1 + \left(SL + \frac{1}{CS} \right) I_2 \quad \text{--- (1)}$$

Similarly, Applying KVL in loop - ②, we get

$$V_2 = SL I_2 + \left(SL + \frac{1}{CS} \right) I_1 + \left(SL + \frac{1}{CS} \right) I_2 + \frac{1}{CS} I_2$$

$$V_2 = \left(SL + \frac{1}{CS} \right) I_1 + 2 \left(SL + \frac{1}{CS} \right) I_2 \quad \text{--- (2)}$$

from eqn. (1)

$$Z_{11} = \left. \frac{V_1}{I_1} \right|_{I_2=0} = 2 \left(SL + \frac{1}{CS} \right)$$

$$Z_{12} = \left. \frac{V_1}{I_2} \right|_{I_1=0} = \left(sL + \frac{1}{Cs} \right)$$

Similarly, From eqn-②

$$Z_{21} = \left. \frac{V_2}{I_1} \right|_{I_2=0} = \left(sL + \frac{1}{Cs} \right)$$

$$Z_{22} = \left. \frac{V_2}{I_2} \right|_{I_1=0} = 2 \left(sL + \frac{1}{Cs} \right)$$

Z parameter; $[Z] = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix}$


$$[Z] = \begin{bmatrix} 2 \left(sL + \frac{1}{Cs} \right) & sL + \frac{1}{Cs} \\ \left(sL + \frac{1}{Cs} \right) & 2 \left(sL + \frac{1}{Cs} \right) \end{bmatrix}$$

Ans

Good
Approach

11

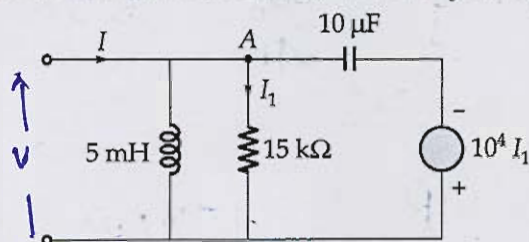- 1 (b) Determine the resonant frequency, quality factor Q_0 and bandwidth of the given circuit.



[12 marks]

from ckt. as shown in figure -

$$I = \frac{V}{j\omega L} + \frac{V}{R} + \frac{V + 10^4 I_1}{\frac{1}{j\omega C}} \quad \text{--- (1)}$$

from fig:- $I_1 = \frac{V}{R}$

Given $\rightarrow R = 15 \text{ k}\Omega$
 $L = 5 \text{ mH}$
 $C = 10 \mu\text{F}$

$$I = \frac{V}{j\omega L} + \frac{V}{R} + j\omega C \left[V + 10^4 \frac{V}{R} \right]$$

$$Y_{in} = \frac{I}{V} = \frac{1}{j\omega L} + \frac{1}{R} + j\omega C \left[1 + \frac{10^4}{R} \right]$$

$$= -\frac{j}{\omega L} + \frac{1}{R} + j\omega C \left[1 + \frac{10^4}{R} \right]$$

At resonance $Y_{in}(\text{imag.}) = 0$

$$-\frac{1}{\omega L} + \omega C \left[1 + \frac{10^4}{R} \right] = 0$$

Substituting the values of R, L, C

$$-\frac{1}{5 \times 10^{-3} \omega} + \omega \times 10 \times 10^{-6} \left[1 + \frac{10^4}{15 \times 10^3} \right] = 0$$

$$-200 + \omega^2 \times 1.67 \times 10^{-5} = 0$$

$$\omega^2 = \frac{200}{1.67 \times 10^{-5}} \Rightarrow \omega_0 = 3460.64 \text{ rad/sec}$$

$$\text{Resonant frequency} = \frac{\omega_0}{2\pi} = 550.77 \text{ Hz}$$

Ans

$$\text{Quality factor} = \frac{R}{\omega_0 L} = \frac{15 \times 10^3}{3460.64 \times 5 \times 10^{-3}}$$

$$Q = 866.89$$

Ans

$$\text{Bandwidth} = \frac{\omega_0}{Q} = \frac{3460.64}{866.89} = 3.99 \text{ rad/sec}$$


$$B.W = 3.99 \approx 4 \text{ rad/sec}$$

Ans

11


Good
Approach

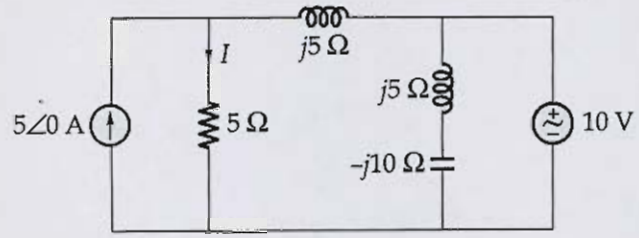1 (c) (i) Determine the current 'I' in the network shown using principle of superposition.



[6 marks]

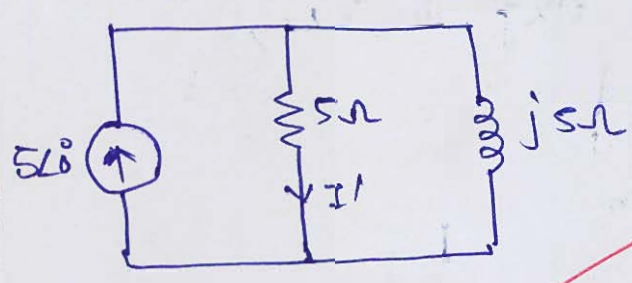Current I' in 5Ω resistor due to only independent current source $5\angle 0^\circ$ Amp.




Applying current division rule -

$$I' = \frac{5\angle 0^\circ \times 5\angle 90^\circ}{5 + j5}$$

$$I' = 3.53 \angle 45^\circ \text{ Amp}$$

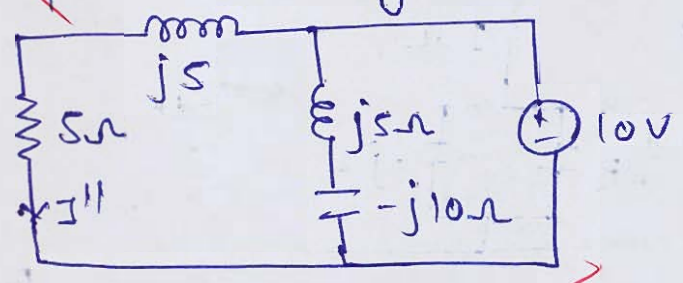Current I'' in 5Ω resistance due to only independent voltage source 10V.



$$I'' = \frac{10}{5 + j5}$$

$$= 1.414 \angle -45^\circ \text{ Amp}$$

According to principle of superposition →

$$I = I' + I''$$

$$= 3.53 \angle 45^\circ + 1.414 \angle -45^\circ$$


$$I = 3.80 \angle 23.16^\circ \text{ Amp}$$

5

Good Approach

Ans


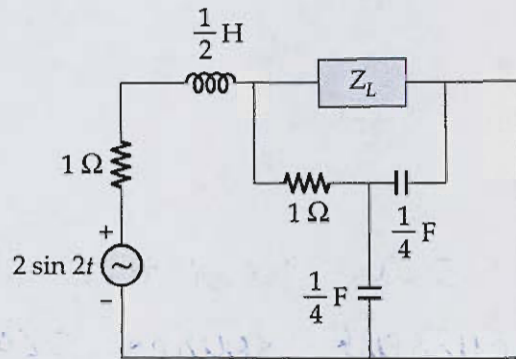
- Q.1 (c) (ii) Determine the value of impedance Z_L for maximum power transfer, in Z_L , in the given network.



[6 marks]

Soln:for maximum power txf. in Z_L ,

$$Z_L = Z_{th}^*$$

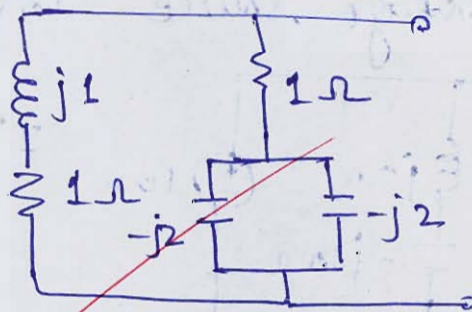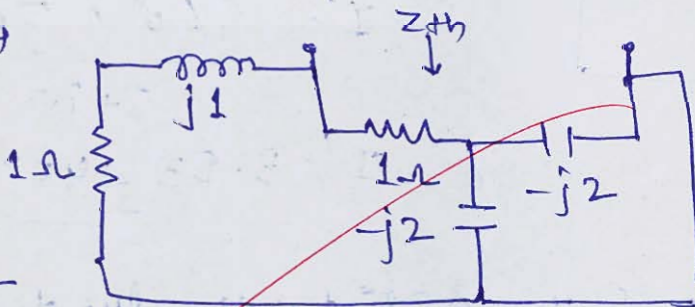 $Z_{th} \rightarrow$ 

5


Good Approach

$$\begin{aligned}
 Z_{th} &= (1+j1) \parallel (1-j2) = \sqrt{2} \angle 45^\circ \times \sqrt{2} \angle -45^\circ \\
 &= \frac{5.83 \angle -30.96^\circ}{3.60 \angle -56.305^\circ} = \frac{2}{2} \sqrt{2} \angle -45^\circ \\
 &= 1.616 \angle 25.34^\circ \Omega = 1 \Omega
 \end{aligned}$$

$$Z_L = Z_{th}^* = 1.616 \angle -25.34^\circ = 1.416 - 0.69j \Omega$$

Ans


1 (d) Consider the following circuit:

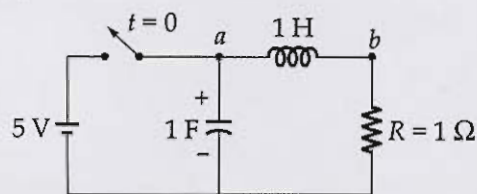

The switch is initially closed. After steady state is reached the switch is opened. Determine the nodal voltage $V_a(t)$ and $V_b(t)$.

[12 marks]

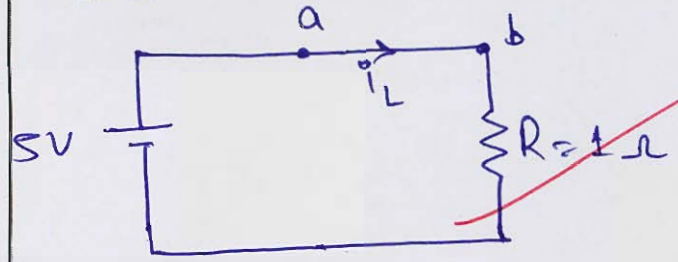At steady state, capacitor acts as ∞ and inductor acts as short circuit.




So, $V_a = V_c(0^-) = 5V$

$V_b = 5V$

$i_L(0^-) = 5A$

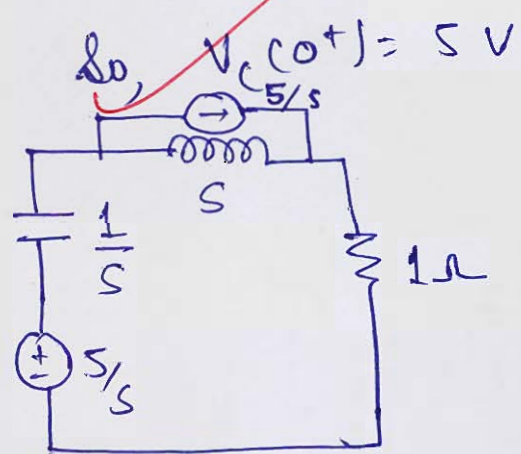At instant $t=0$, switch is opened, the voltage on capacitor doesn't change instantaneously.



So, $V_c(0^+) = 5V$

hly $i_L(0^+) = 5A$

3

In complete solution

The first part of the question is to find the value of x in the following equation:

$$2x + 3 = 7$$

 To solve for x , we need to isolate x on one side of the equation. We can do this by subtracting 3 from both sides:

$$2x + 3 - 3 = 7 - 3$$

$$2x = 4$$

 Now, we divide both sides by 2 to solve for x :

$$\frac{2x}{2} = \frac{4}{2}$$

$$x = 2$$

 Therefore, the value of x is 2.

Q. 1. A circuit diagram is shown below. Find the value of R if the power dissipated in the 10Ω resistor is $10W$.

Sol. Given, $P = 10W$, $R_1 = 10\Omega$, $R_2 = 20\Omega$, $R_3 = 5\Omega$, $V = 30V$

Let the current through the 10Ω resistor be I .

Power dissipated in 10Ω resistor is given by

$$P = I^2 R$$
$$10 = I^2 \times 10$$
$$I^2 = 1$$
$$I = 1A$$

Since the 10Ω resistor is in series with the parallel combination, the current through the parallel combination is also $1A$.

Let the voltage across the parallel combination be V_p .

The voltage across the 20Ω resistor is V_1 and the voltage across the branch containing 5Ω and R is V_2 .

Since $V_1 + V_2 = 30V$ and $V_1 = I R_1 = 1 \times 20 = 20V$, we have

$$V_2 = 30 - 20 = 10V$$

The current through the 5Ω resistor is I_1 and the current through R is I_2 .

Since $I_1 + I_2 = 1A$ and $I_1 = \frac{V_2}{R_3} = \frac{10}{5} = 2A$, we have

$$I_2 = 1 - 2 = -1A$$

The negative sign indicates that the current through R is in the opposite direction to the assumed direction.


The voltage across R is $V_R = I_2 R = -1 \times R = -R$.

Since $V_2 = 10V$, we have

$$-R = 10$$
$$R = -10\Omega$$


The negative sign indicates that the resistor R is not a passive resistor but an active component like a dependent current source.

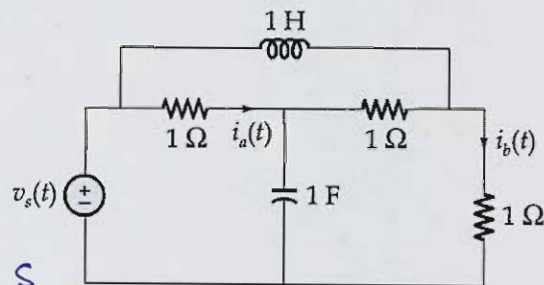- Q.1 (e) For the bridged T-network of the figure given below the source voltage is $v_s(t) = 2 \cos t$. The circuit is in steady state condition. Determine: (i) $i_a(t)$ and (ii) $i_b(t)$.



[12 marks]

Sol:-

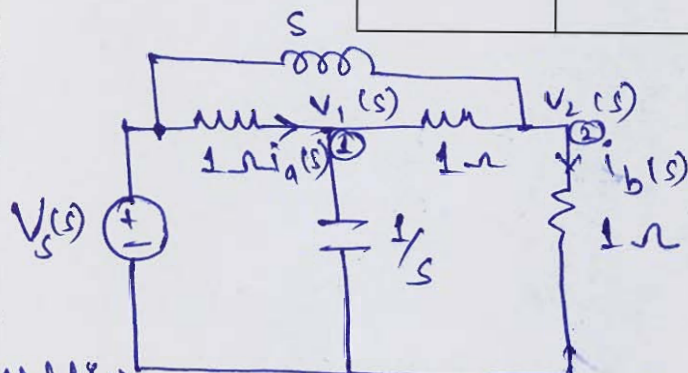

$$V_s(s) = \frac{2s}{s^2 + 1}$$

Applying KCL at node (1)

$$\frac{V_s - V_1}{1} = \frac{V_1}{1/s} + \frac{V_1 - V_2}{1}$$

$$V_s - V_1 = sV_1 + V_1 - V_2$$

$$V_s = (s+2)V_1 - V_2 \quad \text{--- (1)}$$

Applying KCL at node (2)

$$\frac{V_s - V_2}{s} + \frac{V_1 - V_2}{1} = 0$$

$$V_s - V_2 + sV_1 - sV_2 = 0$$

$$V_s = -sV_1 + V_2 + sV_2 + sV_2 = -sV_1 + (2s+1)V_2 \quad \text{--- (2)}$$

from eqn. (1) & (2)

$$(s+2)V_1 - V_2 = -sV_1 + (2s+1)V_2$$

$$(2s+2)V_1 = (2s+2)V_2 \Rightarrow V_1 = V_2$$

Substituting in eqn. (1) & (2)

$$V_s = (S+2) V_1 - V_1$$

$$V_s = (S+2-1) V_1$$

$$V_1 = \frac{V_s}{(S+1)}$$

$$\Rightarrow I_a(s) = \frac{V_s - V_1}{1}$$

$$= V_s - \frac{V_s}{S+1} = V_s \left[\frac{S}{S+1} \right]$$

$$I_a(s) = \frac{2S^2}{(S^2+1)(S+1)} = \frac{A}{(S+1)} + \frac{BS+C}{S^2+1}$$

$$2S^2 = AS^2 + A + BS^2 + BS + CS + C$$

$$A+B=2, \quad B+C=0, \quad A+C=0$$

$$\text{on solving: } A=1, \quad B=1, \quad C=-1$$

$$I_a(s) = \frac{1}{S+1} + \frac{S-1}{S^2+1} \Rightarrow I_a(t) = e^{-t} u(t) + \cos t u(t) - \sin t u(t)$$

Inverse Laplace transform

$$I_a(t) = (e^{-t} + \cos t - \sin t) u(t)$$

$$\text{Hly } I_b(s) = \frac{V_2}{1} = \frac{V_1}{1} = \frac{V_s}{S+1} = \frac{2S}{(S^2+1)(S+1)} = \frac{A}{(S+1)} + \frac{BS+C}{S^2+1}$$

$$2S = AS^2 + A + BS^2 + BS + CS + C$$

$$A+B=0, \quad B+C=2, \quad A+C=0$$

$$A=-1, \quad B=1, \quad C=1$$


$$I_b(s) = \frac{-1}{S+1} + \frac{S+1}{S^2+1}$$

$$\Rightarrow I_b(t) = (-e^{-t} + \cos t + \sin t) u(t)$$

4

Ans.

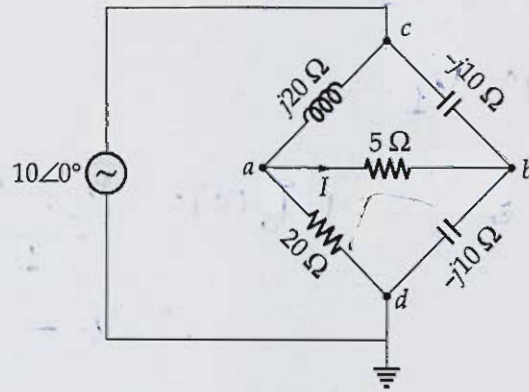
- Q.2 (a) (i) Determine current I in the network using Thevenin's theorem.



Solⁿ:

Calculation of Z_{th} →

[10 marks]

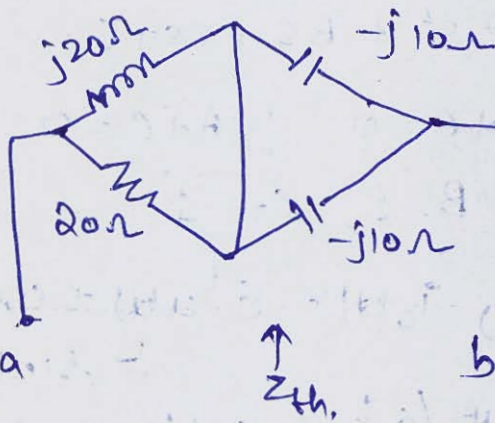


$$\begin{aligned}
 Z_{th} &= (j20 \parallel 20) + (-j10 \parallel -j10) \\
 &= 14.142 \angle 45^\circ + 5 \angle -90^\circ \\
 &= 11.180 \angle 26.56^\circ \Omega
 \end{aligned}$$

Calculation of V_{oc} →

$$V_{oc} = V_a - V_b$$

$$V_a = \frac{10 \angle 0^\circ \times 20}{20 + j20}$$
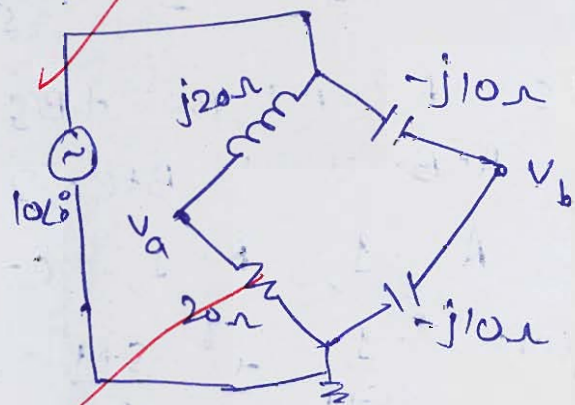
$$= 5\sqrt{2} \angle -45^\circ \text{ V}$$




$$\begin{aligned}
 \text{Hence } V_b &= \frac{10 \angle 0^\circ \times -j10}{-j10 - j10} = \frac{10 \angle 0^\circ \times -j10}{-j20} \\
 &= 5 \text{ V}
 \end{aligned}$$

$$V_{oc} = V_a - V_b = 5\sqrt{2} \angle -45^\circ - 5$$

$$= 5 \angle -90^\circ \text{ V}$$

Thevenin equivalent ckt:-

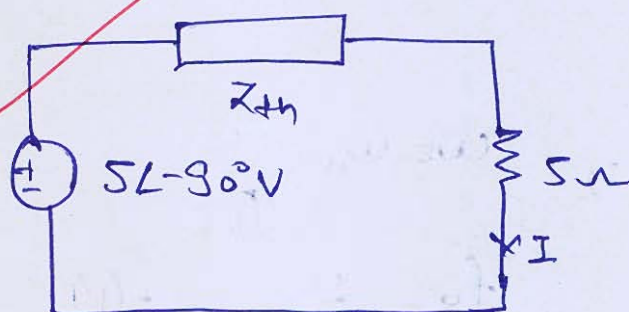


$$I = \frac{5 \angle -90^\circ}{11.18 \angle 26.56^\circ + 5} = 0.316 \angle -108.43^\circ \text{ Amp}$$

9

Good
Approach

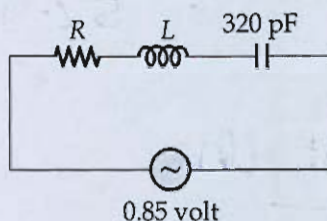- Q.2 (a) (ii) For the circuit shown determine the value of inductance for resonance if $Q = 50$ and $f_0 = 175 \text{ kHz}$. Also find the circuit current, the voltage across the capacitor and the bandwidth of the circuit.



[10 marks]

Soln?

At resonance

$$\omega L = \frac{1}{\omega C} \Rightarrow \omega = \omega_0 = \frac{1}{\sqrt{LC}}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}} \quad \text{--- (1)}$$

Given: - $f_0 = 175 \text{ kHz}$ $Q = 50$, $C = 320 \text{ pF}$

Substituting in eqn. (1)

$$175 \times 10^3 = \frac{1}{2\pi\sqrt{L \times 320 \times 10^{-12}}}$$

$$3.0625 \times 10^{10} = \frac{1}{4\pi^2 \times L \times 320 \times 10^{-12}}$$

$$L = 2.58 \times 10^{-3}$$

$$\boxed{L = 2.58 \text{ mH}} \quad \text{Ans}$$

$$Q = \frac{\omega_0 L}{R} \Rightarrow R = \frac{\omega_0 L}{Q} = \frac{2\pi \times 175 \times 10^3 \times 2.58 \times 10^{-3}}{50}$$

$$\boxed{R = 56.84 \Omega}$$

Circuit current

$$I = \frac{V}{R} = \frac{0.85}{56.84}$$

$$\boxed{I = 0.01495 \text{ A}} \quad \text{Ans}$$

Voltage across capacitor

$V_c = QV = 50 \times 0.85$

$V_c = 42.5V$ Ans

Bandwidth $= \frac{\omega_0}{Q} = \frac{2\pi \times 175 \times 10^3}{50}$


B.W = 7000π rad/sec
= 3500 Hz

Ans


9

Good Approach

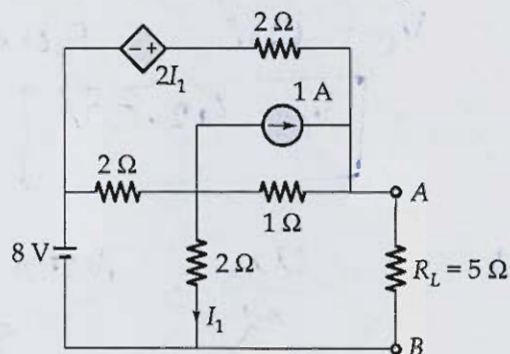- Q.2 (b) Determine the current through the load resistance $R_L = 5 \Omega$ across the terminals A-B of the circuit shown in figure below, using Thevenin's theorem. Also, find the maximum power that can be transferred to the load resistance R_L .



[20 marks]

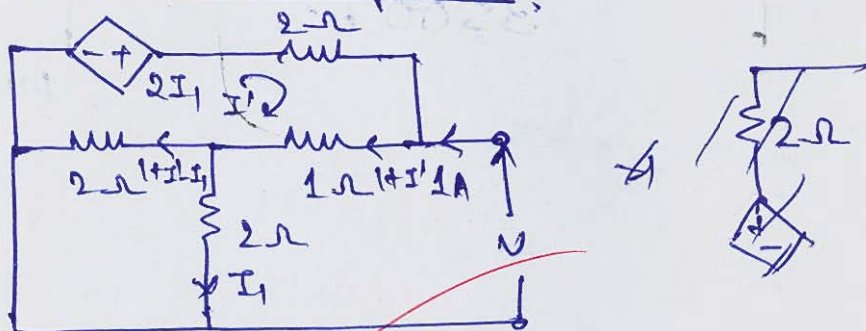Soln:-Calculation of $R_{th} \rightarrow$ 

$$V = 1(1 + I') + 2I_2 \quad \rightarrow (a)$$

$$2I_2 = 2I' + (1 + I') + 2(1 + I' - I_1)$$

$$2I_2 = 2I' + 1 + I' + 2 + 2I' - 2I_1$$

$$-3 = 5I' - 4I_2 \quad \rightarrow (1)$$

$$\text{Also, } 2I_1 = 2(1 + I' - I_1)$$

$$I_1 = 1 + I' - I_1$$


$$2I_1 - I' = 1 \quad \rightarrow (2)$$

On solving $I' = -\frac{1}{3} \text{ Amp}$, $I_1 = \frac{1}{3} \text{ Amp}$
Substituting in eqn. (a)

$$V = \left(1 - \frac{1}{3}\right) + 2 \times \frac{1}{3} = \frac{2}{3} + \frac{2}{3} = \frac{4}{3} \text{ V}$$

$R_{th} = \frac{V}{I} = \frac{3}{1} = 3 \Omega$

Calculation of V_{oc} -

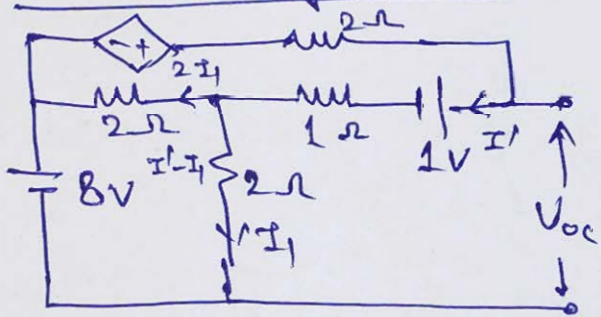

18

Good Approach

$V_{oc} = 1 + I' + 2I_1 \quad \text{--- (6)}$


$2I_1 = 2I' + 1 + I' + 2I' - 2I_1$

$8 = -2(I' - I_1) + 2I_1 \Rightarrow -1 = 5I' - 4I_1 \rightarrow \text{--- (7)}$

$8 = -2I' + 2I_1 + 2I_1 = -2I' + 4I_1 \rightarrow \text{--- (8)}$

On solving:- $I' = \frac{7}{3} A, \quad I_1 = \frac{19}{6} A$

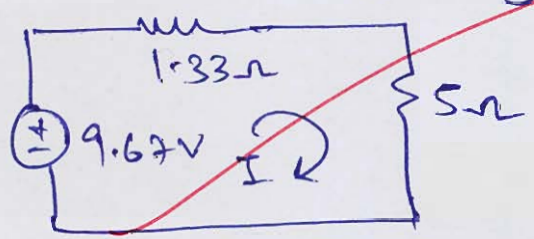$V_{th} = V_{oc} = 1 + \frac{7}{3} + \frac{19}{3} = 9.67 V$



$I = \frac{9.67}{1.33 + 5} = 1.526 A$

Maxm power transferred


$= \frac{V_{th}^2}{4R_{th}} = \frac{(9.67)^2}{4 \times 1.33}$

$P_{max} = 17.53 W$

[Faint handwritten notes and diagrams are visible on the page, including a flowchart and various mathematical expressions.]

- 2 (c) (i) Derive expression for frequency for maximum voltage across inductor in series RLC resonant circuit.
- (ii) Calculate the maximum voltage across the inductor using result of part (i) with constant voltage and variable frequency. Assume $R = 50 \Omega$, $L = 0.05\text{H}$, $C = 20 \mu\text{F}$ and $V = 100 \text{ V}$.

[13 + 7 marks]

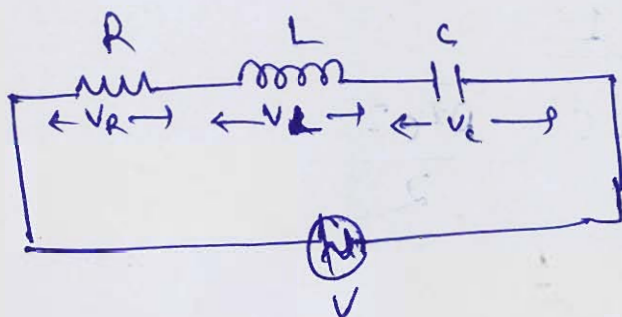

Applying voltage division rule -

$$V_L = V \times \frac{j\omega L}{R + j(\omega L - \frac{1}{\omega C})}$$

$$V_L = V \times \frac{j\omega L}{R^2 + (\omega L - \frac{1}{\omega C})^2} \times R - j(\omega L - \frac{1}{\omega C})$$

$$V_L = V \times \left[\frac{j\omega L R + \omega L (\omega L - \frac{1}{\omega C})}{R^2 + (\omega L - \frac{1}{\omega C})^2} \right]$$

$$= V \times \left[\frac{j\omega L R + \omega^2 L^2 - \frac{L}{C}}{R^2 + (\omega L - \frac{1}{\omega C})^2} \right] \quad \text{--- (1)}$$

Differentiating and equating V_L with respect to ω to zero
i.e. $\frac{dV_L}{d\omega} = 0$

On differentiating eqn. (1) & equating it to zero, we get

$$\omega = \frac{1}{\sqrt{LC - \frac{R^2 C^2}{2}}}$$

$$\text{i.e.; } \omega = \frac{1}{\sqrt{LC} \sqrt{1 - \frac{R^2 C}{2L}}}$$

$$\text{or } f_L = \frac{1}{2\pi\sqrt{LC} \sqrt{1 - \frac{R^2 C}{2L}}}$$

expression for frequency for maximum voltage across inductor.

(ii) Given $R = 50 \Omega$
 $L = 0.05 \text{ H}$
 $C = 20 \mu\text{F}$

We know that $Q = \frac{\omega_0 L}{R}$

$$Q = \frac{1}{\sqrt{LC}} \times \frac{L}{R} = \frac{1}{R} \sqrt{\frac{L}{C}}$$


$$\text{So, } Q = \frac{1}{50} \sqrt{\frac{0.05}{20 \times 10^{-6}}} = 1$$

Maximum voltage across inductor

$$V_L = QV = 1 \times 100$$


$$(V_L)_{\max} = 100 \text{ V}$$

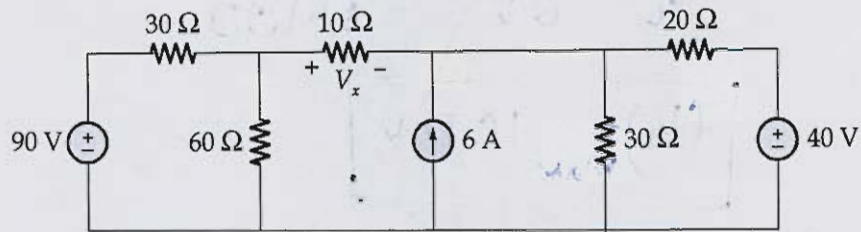- Q.3 (a) (i) The circuit shown in the figure below consists of three independent sources. Determine the value of the voltage across $10\ \Omega$ resistance using superposition theorem.




[10 marks]

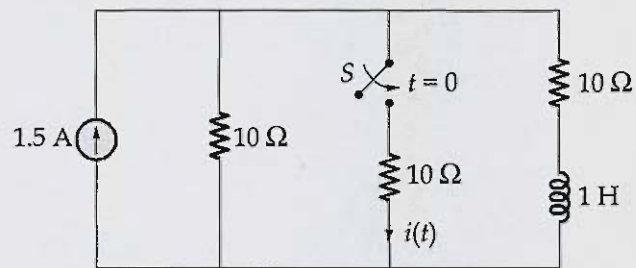Q.3 (a) (ii) Consider the network shown below:




If switch S is closed at $t = 0$, calculate $i(t)$ for $t > 0$ by using Laplace transform approach.
[10 marks]

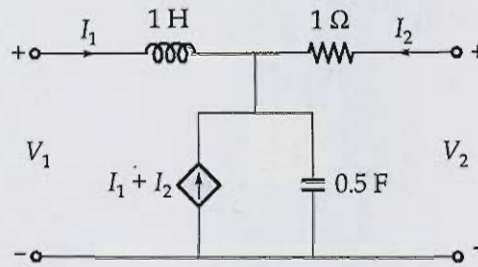Q.3 (b) Determine the transmission parameters matrix for the two port network shown below.



[20 marks]

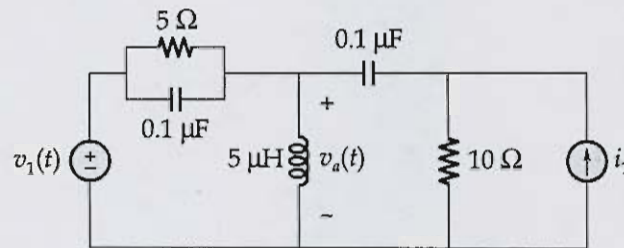- Q.3 (c) (i) For the circuit shown below, $v_1(t) = 10 \sin 10^6 t$ V and $i_1(t) = 10 \cos 10^6 t$ A and the circuit is operating in steady state condition. Determine the node to datum voltage $v_a(t)$.



[10 marks]

- Q.3 (c) (ii) A certain practical dc voltage source can provide a current of 2.5 A when it is (momentarily) short circuited and can provide a power of 80 W to $20\ \Omega$ load.


Find:

1. The open circuit voltage.
2. The maximum power it could deliver to a well-chosen R_L .
3. What is the value of that R_L ?


[10 marks]



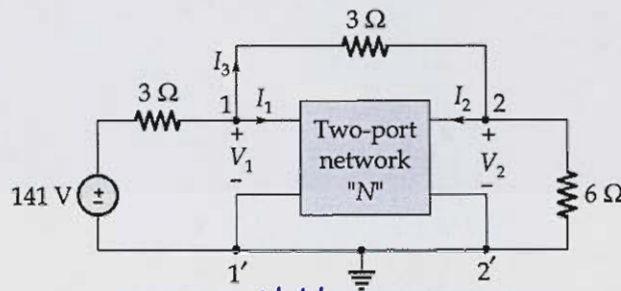- Q.4 (a) (i) The z-parameters of the two port network-N shown in the figure below are given as $z_{11} = 2 \Omega$, $z_{12} = z_{21} = 1 \Omega$ and $z_{22} = 4 \Omega$. Find the values of currents I_1 , I_2 and I_3 .



[12 marks]

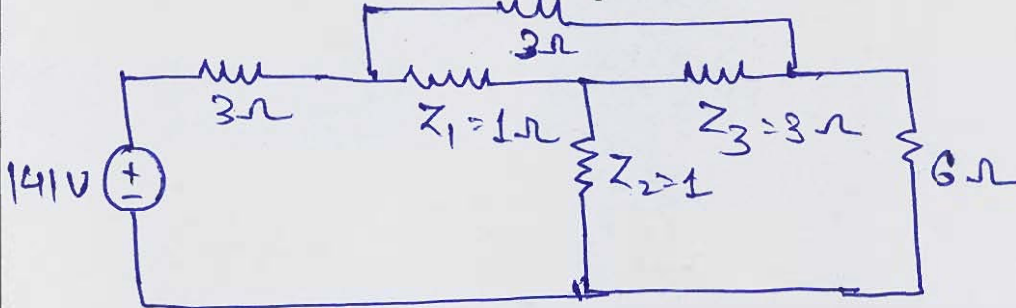



$$z_{11} = 2 \Rightarrow z_1 + z_2 = 2$$

$$z_2 = z_{12} = z_{21} = 1 \Omega$$

$$\text{So, } z_1 = 1 \Omega$$

$$z_{22} = z_3 + z_2 = 4 \Rightarrow z_3 = 3 \Omega$$

Applying Y-Δ trans.

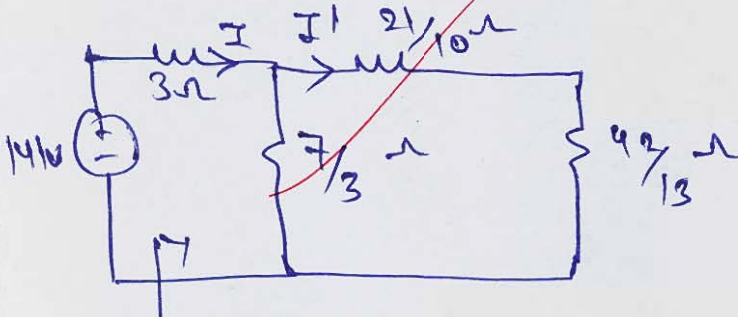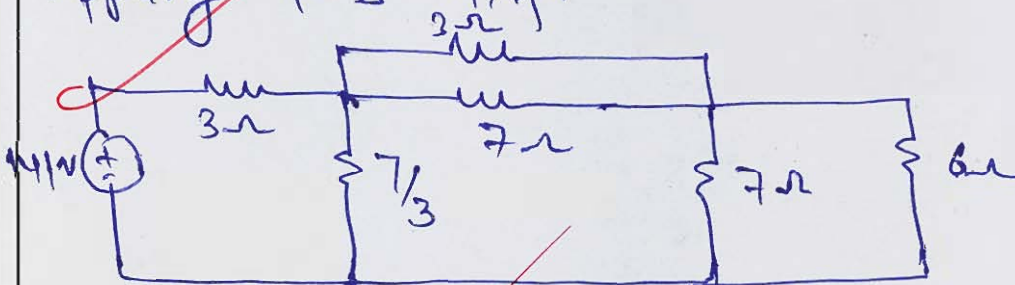

$$I = \frac{141}{Z_{eq}} = 4.622 \text{ Amp.}$$

$$\frac{691}{130}$$

$$I' = \frac{4.622 \times 7}{3} = 1.4074 \text{ Amp}$$


$$\frac{7}{3} + \frac{693}{130}$$

$$I_3 = \frac{1.4074 \times 7}{10} = 0.9852 \text{ Amp}$$


$$I_1 = I' - I_3 = 0.422 \text{ Amp}$$

3

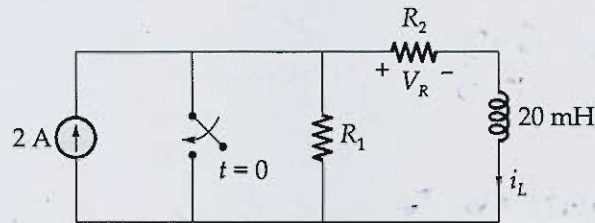- Q.4 (a) (ii) Determine values of R_1 and R_2 in the circuit of figure such that $V_R(0^+) = 10$ V and $V_R(1 \text{ msec}) = 5$ V.



[8 marks]

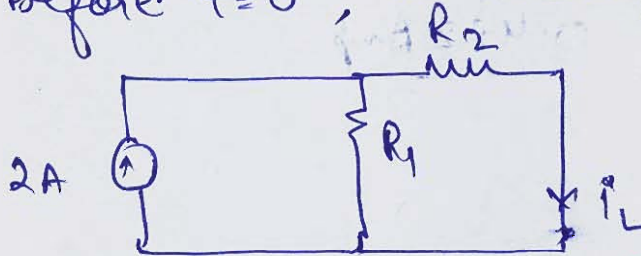Soln:-Before $t=0$, at steady state

$$i_L = \frac{2 \times R_1}{R_1 + R_2} = \frac{2R_1}{R_1 + R_2} \quad [\text{By current division rule}]$$

$$V_R = \frac{2R_1 R_2}{R_1 + R_2} \quad \text{--- (1)}$$

at $t=0$, switch closed, $i_L(0^+) = i_L(0) = i_L(0^+)$

$$= \frac{2R_1}{R_1 + R_2}$$

$$V_R(0^+) = \frac{2R_1 R_2}{R_1 + R_2} = 10$$

$$i_L = i_L(0) \cdot e^{-t/\tau}$$

$$i_L = \frac{2R_1}{R_1 + R_2} \cdot e^{-t/L/R_1} = \frac{2R_1}{R_1 + R_2} \cdot e^{-\frac{R_1 t}{L}}$$

$$V_R(t) = R_2 \cdot i_L = \frac{2R_1 R_2}{R_1 + R_2} \cdot e^{-\frac{R_1 t}{L}} \quad \text{--- (2)}$$

$$V_R(t) = V_R(0) \cdot e^{\frac{-R_1 t}{L}} \quad [\text{from (1) \& (2)}]$$

$$5 = 10 \cdot e^{\frac{-R_1 \times 10^{-3}}{20 \times 10^{-3}}}$$

$$-0.693 = \frac{-R_1 \times 10^{-3}}{20 \times 10^{-3}}$$

$$R_1 = 13.86 \, \Omega$$

Substituting R_1 in eqn (1)

$$10 = \frac{2 \times 13.86 \times R_2}{13.86 + R_2}$$


$$13.86 = 1.77 R_2$$

$$R_2 = 7.819 \, \Omega$$


8

Good
APPROACH

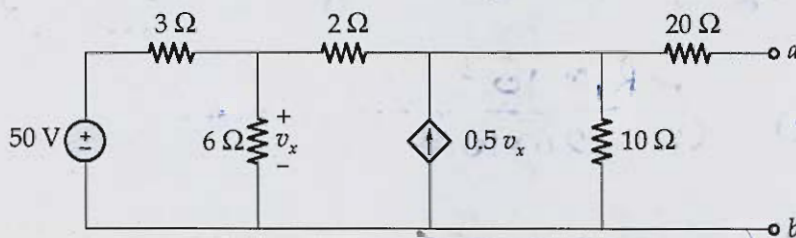- Q.4 (b) Determine the Thevenin's equivalent network and Norton's current at terminals $a-b$ for the circuit shown below and draw the two equivalent circuits.



[20 marks]

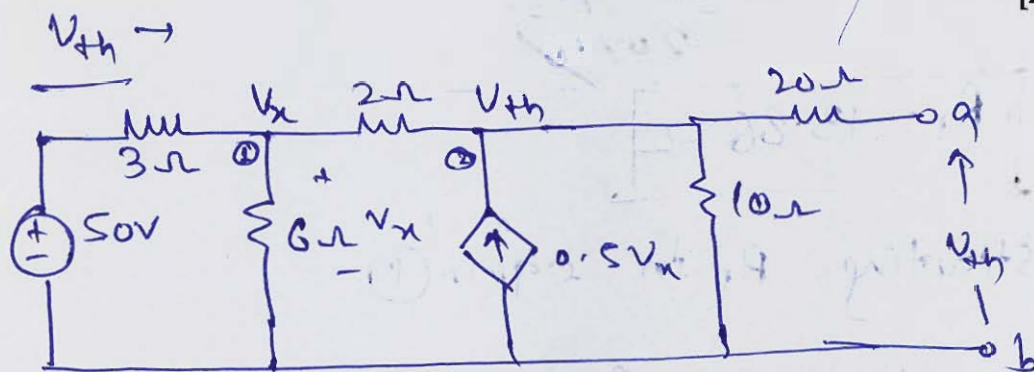

$$\frac{50 - v_x}{3} = \frac{v_x}{6} + \frac{v_x - V_{th}}{2} \rightarrow \text{KCL at ①}$$

$$100 - 2v_x = v_x + 3v_x - 3V_{th}$$

$$100 = 6v_x - 3V_{th} \quad \text{--- (1)}$$

$$\frac{v_x - V_{th}}{2} + 0.5v_x = \frac{V_{th}}{10} \rightarrow \text{KCL at ②}$$


$$v_x - V_{th} + v_x = \frac{V_{th}}{5}$$

$$5v_x - 5V_{th} + 5v_x = V_{th}$$

$$10v_x - 6V_{th} = 0 \quad \text{--- (2)}$$

Solving eqn (1) & (2)

$$v_x = 100V, \quad V_{th} = 166.67V$$

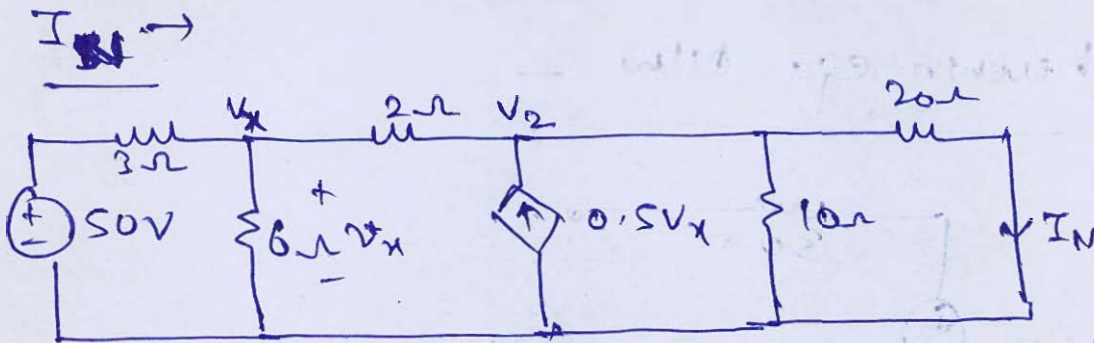

$$\frac{50 - V_x}{3} = \frac{V_x}{6} + \frac{V_x - V_2}{2}$$

$$100 - 2V_x = V_x + 3V_x - 3V_2$$

$$100 = 6V_x - 3V_2 \quad \text{--- (1)}$$

$$\frac{V_x - V_2}{2} + 0.5V_x = \frac{V_2}{10} + \frac{V_2}{20} = \frac{2V_2 + V_2}{20}$$

$$10V_x - 10V_2 + 10V_x = 3V_2$$

$$20V_x - 13V_2 = 0 \quad \text{--- (2)}$$

on solving -

$$V_x = \frac{650}{9} \text{ V}, \quad V_2 = \frac{1000}{9} \text{ V}$$

$$I_N = \frac{V_2}{20} = \frac{50}{9} = 5.55 \text{ Amp}$$


$R_{th} \rightarrow$

$$R_{th} = \frac{V_{th}}{I_N} = \frac{166.67}{5.55} = 30 \Omega$$


18

Good
Approach


Thevenin eq. N/w —

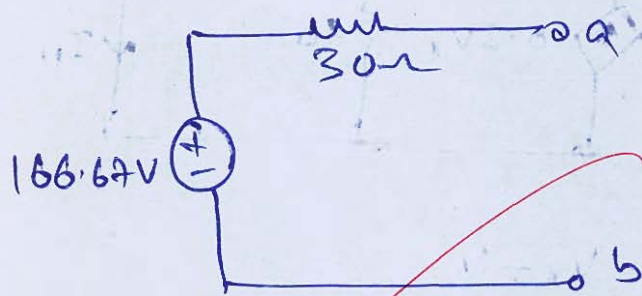

Norton eq. N/w —

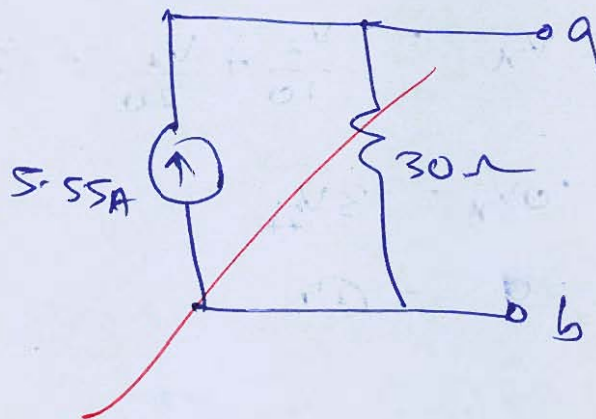

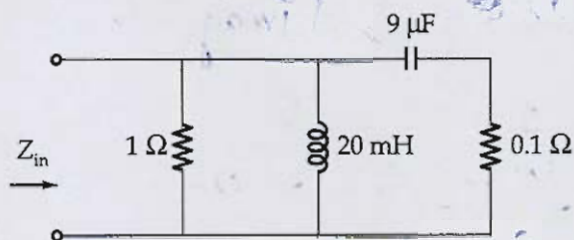
2.4 (c) (i) For the circuit shown in the figure below:



Determine:

1. The resonant frequency, ω_0 .
2. Input impedance at resonant frequency, $Z_{in}(\omega_0)$.


(ii) For the graph shown below:

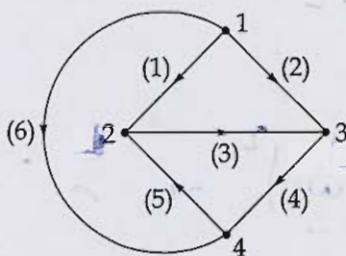

Find the number of possible trees.

[15 + 5 marks]

Solⁿ (i)

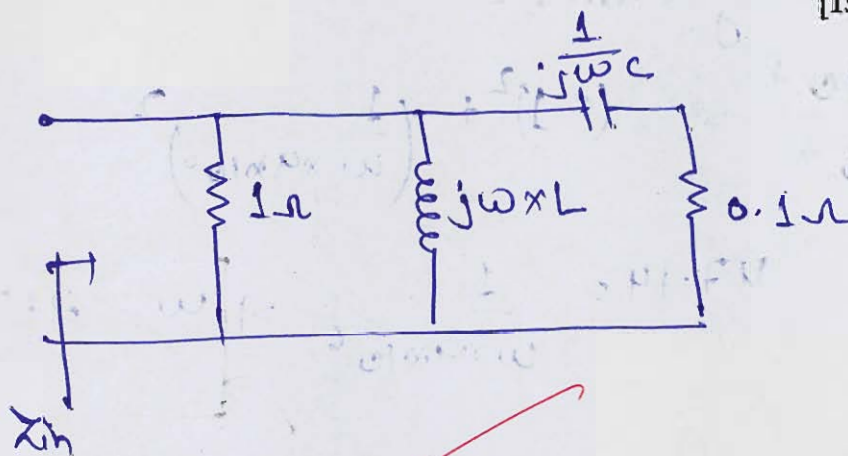

$$Z_{in} = (1\Omega) \parallel (j\omega L) \parallel \left(0.1 + \frac{1}{j\omega C}\right)$$

$$Y_{in} = \frac{1}{1} + \frac{1}{j\omega L} + \frac{1}{0.1 + \frac{1}{j\omega C}} = 1 + \frac{1}{j\omega L} + \frac{1}{0.1 - j\frac{1}{\omega C}}$$

$$= 1 - \frac{j}{\omega L} + \frac{0.1 + j\frac{1}{\omega C}}{(0.1)^2 + \left(\frac{1}{\omega C}\right)^2}$$

for resonance, $Y_{\text{imag}} = 0$

$$-\frac{1}{\omega L} + \frac{1}{\omega C} = 0$$

$$(0.1)^2 + \left(\frac{1}{\omega C}\right)^2$$

$$\frac{1}{\omega C} = \frac{1}{\omega L}$$

$$(0.1)^2 + \left(\frac{1}{\omega C}\right)^2 = \frac{1}{\omega L}$$

$$\frac{1}{C} = \frac{(0.1)^2 + \left(\frac{1}{\omega C}\right)^2}{L} \Rightarrow \frac{L}{C} = (0.1)^2 + \left(\frac{1}{\omega C}\right)^2$$

Substituting values -

$$\frac{40 \times 10^{-3}}{9 \times 10^{-6}} = (0.1)^2 + \left(\frac{1}{\omega \times 9 \times 10^{-6}}\right)^2$$

$$47.14 = \frac{1}{\omega \times 9 \times 10^{-6}} \Rightarrow \omega = 2357.02 \text{ rad/sec}$$


Resonant frequency (ω)

Y_{in} at resonance

$$= 1 + \frac{0.1}{(0.1)^2 + \left(\frac{1}{2357.02 \times 9 \times 10^{-6}}\right)^2}$$

$$\approx 1 \Omega$$
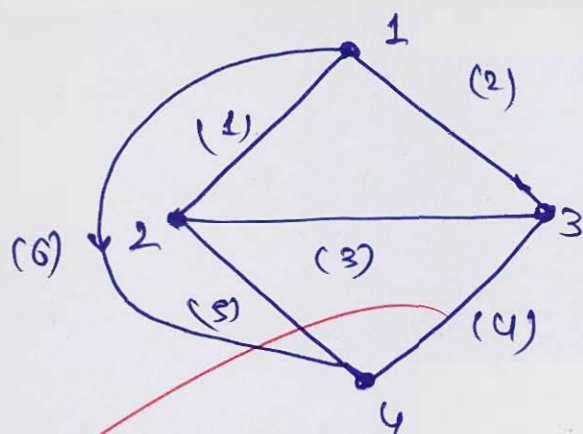
$$Y_{\text{in}} \text{ at resonance} = 1 \Omega$$



No. of nodes = 4

No. of possible trees = n^{n-2}

$$= (4)^{4-2} = 4^2 = 16$$

No. of possible trees = 16

19

Good
Approach

Section B : Engineering Mathematics

Q.5 (a) Find the solution of the differential equation $(y - x + 1)dy - (y + x + 2)dx = 0$.

[12 marks]

$$\text{Sol: } (y - x + 1)dy = (y + x + 2)dx$$

$$\frac{dy}{dx} = \frac{y + x + 2}{y - x + 1}$$

$$\text{Let } y = vx \Rightarrow \frac{dy}{dx} = v + x \frac{dv}{dx}$$

$$\begin{aligned} v + x \frac{dv}{dx} &= \frac{x + vx + 2}{vx - x + 1} \\ &= \frac{x(1+v) + 2}{x(v-1) + 1} \end{aligned}$$

$$(y - x + 1)dy - (y + x + 2)dx = 0$$

Above, equation is of the form $Mdx + Ndy = 0$

$$\text{where } M = -(y + x + 2)$$

$$N = y - x + 1$$

$$\frac{\partial M}{\partial y} = -1$$

$$\frac{\partial N}{\partial x} = -1$$

(2)

Since $\frac{\partial M}{\partial y} = \frac{\partial N}{\partial x}$, so solution of

the differential equation can be written

in the form.

$$y = \int M \cdot dx + \int (\text{terms of } x \text{ not containing } x) dy + C$$

$$y = \int -(x+y+2) dx + \int (y+1) dy + C$$

$$= -\frac{x^2}{2} - xy - 2x + \frac{y^2}{2} + y + C$$

$$= -\frac{x^2}{2} - xy - 2x + \frac{y^2}{2} + y + C$$

Ans.

Q.5 (b) Find the value of $\int_{-\infty}^{\infty} \frac{x^2 - x + 2}{x^4 + 10x^2 + 9} dx$.

[12 marks]



- 5 (c) (i) The vector field $\vec{F} = x^2\hat{i} + z\hat{j} + yz\hat{k}$ is defined over the volume of the cuboid given by $0 \leq x \leq a$, $0 \leq y \leq b$, $0 \leq z \leq c$. Evaluate the surface integral $\iint_S \vec{F} \cdot \vec{ds}$, where S is the surface of the cuboid.

[6 marks]

Soln:- Given $\vec{F} = x^2\hat{i} + z\hat{j} + yz\hat{k}$
We know that, according to Gauss divergence theorem.

$$\iint_S \vec{F} \cdot \vec{ds} = \iiint_V (\nabla \cdot \vec{F}) \cdot dV$$

$$\nabla \cdot \vec{F} = \left(\hat{i} \frac{\partial}{\partial x} + \hat{j} \frac{\partial}{\partial y} + \hat{k} \frac{\partial}{\partial z} \right) (x^2\hat{i} + z\hat{j} + yz\hat{k})$$

$$= 2x + 0 + y = 2x + y$$

$$\iiint_V (\nabla \cdot \vec{F}) \cdot dV = \int_0^a \int_0^b \int_0^c (2x + y) dz dy dx$$

$x=0 \quad y=0 \quad z=0$

$$= \int_0^a \int_0^b [2xz + yz]_0^c dy dx$$

$$= \int_0^a \int_0^b [2xc + yc] dy dx$$

$$= \int_0^a \left[2xyc + \frac{y^2}{2} c \right]_0^b dx$$

$$= \int_0^a \left[2xbc + \frac{b^2}{2} c \right] dx$$

3

$$= \left[\frac{2x^2}{2} bc + \frac{b^2 c}{2} x \right]_0^a$$

$$\int_S \vec{F} \cdot d\vec{l} = a^2 bc + b^2 ac$$

$$\int_S \vec{F} \cdot d\vec{l} = abc [a+b]$$

Ans

5 (c) (ii) Find the absolute maxima and minima of

1. $f(x) = 2x^3 - 9x^2 + 12x - 5$ in $[0, 3]$

2. $f(x) = 12x^{4/3} - 6x^{1/3}$, $x \in [-1, 1]$

Also, find points of maxima and minima.

[6 marks]

(1)

$$f(x) = 2x^3 - 9x^2 + 12x - 5$$

$$f'(x) = 6x^2 - 18x + 12 = 0$$

$$x = 2, 1 \in [0, 3]$$

$$f(0) = 2 \times 0^3 - 9 \times 0^2 + 12 \times 0 - 5 = -5$$

$$f(3) = 2 \times 3^3 - 9 \times 3^2 + 12 \times 3 - 5 = 4$$

$$f(2) = 2 \times 2^3 - 9 \times 4 + 12 \times 2 - 5 = -1$$

$$f(1) = 2 \times 1^3 - 9 \times 1^2 + 12 \times 1 - 5 = 0$$

$$f''(x) = 12x - 18$$

$$\text{at } x = 2 \quad f''(x) = 6 > 0$$

$$\text{at } x = 1 \quad f''(x) = -6 < 0$$

$f(x)$ has absolute maxima at $x = 3$

" " absolute minima at $x = 0$

$$f(x)_{\max} = 4$$

$$f(x)_{\min} = -5$$

(2)

$$f(x) = 12x^{4/3} - 6x^{1/3}$$

$$f'(x) = 12 \times \frac{4}{3} x^{1/3} - 6 \times \frac{1}{3} x^{-2/3}$$

$$f'(x) = 0$$

$$16x^{1/3} - 2x^{-2/3} = 0$$

$$8x^{1/3} - x^{-2/3} = 0$$

$$8x^{1/3} = x^{-2/3}$$

$$x^{1/3 + 2/3} = \frac{1}{8}$$

$$x = \frac{1}{8} \in [-1, 1]$$

$$f''(x) =$$

$$16x^{1/3} - 2x^{-2/3} = 0$$

$$f''\left(\frac{1}{8}\right) > 0$$

$$f(1) = 12 \times (1)^{4/3} - 6(1)^{1/3}$$

$$= 12 - 6 = 6$$

$$f(-1) = 12 \times (-1)^{4/3} - 6(-1)^{1/3}$$

$$= 12 + 6 = 18$$

$$f\left(\frac{1}{8}\right) = 12 \times \left(\frac{1}{8}\right)^{4/3} - 6\left(\frac{1}{8}\right)^{1/3}$$

$$= 12 \times \frac{1}{16} - 6 \times \frac{1}{2} = -\frac{9}{4}$$

$f(x)$ $\xrightarrow{\text{absolute}}$ maxima at $x = -1$, $f_{\max} = 18$

$f(x)$ $\xrightarrow{\text{absolute}}$ minima at $x = \frac{1}{8}$, $f_{\min} = -\frac{9}{4}$

Good
Approach

- 5 (d) Determine the values of x for which the following function fails to be continuous or differentiable.

$$f(x) = \begin{cases} 1-x & , x < 1 \\ (1-x)(2-x), & 1 \leq x \leq 2 \\ 3-x & , x > 2 \end{cases}$$

[12 marks]

At $x=1$

$$f(1^-) = 1-1 = 0$$

$$f(1^+) = (1-1)(2-1) = 0$$

$$f(1) = 0$$

Since $f(1^-) = f(1) = f(1^+)$ at $x=1$, so
 $f(x)$ is continuous as well as differentiable
 at $x=1$

At $x=2$

$$f(2^-) = (1-2)(2-2) = 0$$

$$f(2^+) = (3-2) = 1$$

$$f(2^-) \neq f(2^+)$$

So, $f(x)$ is not continuous at $x=2$

Since, it is not continuous at $x=2$, hence
 it will not be differentiable at $x=2$.

At $x=1 \rightarrow$ continuous as well as
 differentiable

$x=2 \rightarrow$ Neither continuous nor
 differentiable.

Ans

11

Good
Approach

- 5 (e) X is a continuous random variable with probability density function given by

$$f(x) = kx \quad (0 \leq x \leq 2)$$

$$= 2k \quad (2 \leq x < 4)$$

$$= -kx + 6k \quad (4 \leq x < 6)$$

Find k and mean value of X .

[12 marks]

Soln:- For continuous random variable

$$\int_{-\infty}^{\infty} f(x) dx = 1$$

$$\Rightarrow \int_0^2 kx dx + \int_2^4 2k dx + \int_4^6 (-kx + 6k) dx = 1$$

$$k \left[\frac{x^2}{2} \right]_0^2 + 2k \left[x \right]_2^4 + \left[-\frac{kx^2}{2} + 6kx \right]_4^6 = 1$$

$$k \left[\frac{4^2}{2} \right] + 2k \times 2 + \left[-\frac{k}{2} \times 36 + 36k + \frac{k}{2} \times 16 - 24k \right] = 1$$

$$2k + 4k - 18k + 36k + 8k - 24k = 1$$

$$8k = 1 \Rightarrow$$

$$k = \frac{1}{8}$$

Mean value of $f(x)$

$$= \int_{-\infty}^{\infty} xf(x) dx$$

$$= \int_0^2 kx^2 dx + \int_2^4 2kx dx + \int_4^6 (-kx^2 + 6kx) dx$$

$$\begin{aligned}
 &= K \left[\frac{x^3}{3} \right]_0^2 + 2K \left[\frac{x^2}{2} \right]_2^4 + \left[-\frac{Kx^3}{3} + \frac{3}{2}Kx^2 \right]_4^2 \\
 &= K \left[\frac{8}{3} \right] + 2K \left[\frac{16}{2} - \frac{4}{2} \right] + \left[-\frac{K}{3} \times 216 + 108K \right. \\
 &\quad \left. + \frac{1}{3} \times 64 - 48K \right] \\
 &= K \left[\frac{8}{3} \right] + 12K - 72K + 108K + \frac{64}{3}K - 48K \\
 &= 24K + 12K - 72K + 108K - 48K \\
 &= 24K = \frac{24 \times 1}{8} = 3
 \end{aligned}$$

Mean value of $x = 3$

11


Good Approach

- 6 (a) (i) State Lagrange's mean value theorem and explain the theorem in reference to it's geometrical significance.
- (ii) Find the complete solution of $y'' - 2y' + 2y = x + e^x \cos x$.

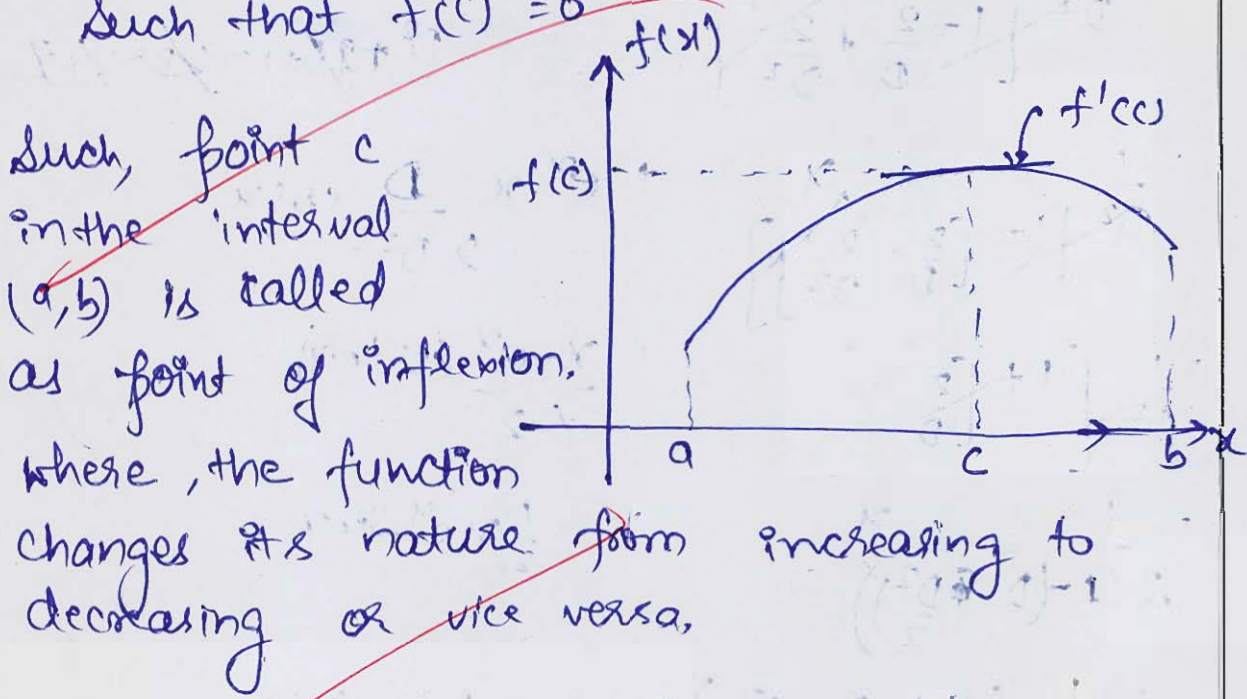(iii) Prove that the matrix, $A = \begin{bmatrix} \frac{1}{2}(1+i) & \frac{1}{2}(-1+i) \\ \frac{1}{2}(1+i) & \frac{1}{2}(1-i) \end{bmatrix}$ is unitary and find A^{-1} .

Lagrange's MVT:- [6 + 6 + 8 marks]

Soln:- (i) If $f(x)$ is continuous in $x \in [a, b]$ and differentiable in $x \in (a, b)$, then there exist a point $c \in (a, b)$ such that $f'(c) = 0$.



(ii) $y'' - 2y' + 2y = x + e^x \cos x$

C.F.:-
 $D^2 - 2D + 2 = 0$

~~$m_1 = 1+i$~~
 ~~$m_2 = 1-i$~~

C.F. = $e^x [C_1 \cos x + C_2 \sin x]$

P-I

$$\frac{1}{(D^2 - 2D + 2)} [x + e^x \cos x]$$

$$= \frac{1}{D^2 - 2D + 2} x + \frac{1}{(D^2 - 2D + 2)} e^x \cos x$$

$$= \frac{1}{D^2} \left[1 - \frac{2}{D} + \frac{1}{D^2} \right] x + e^x \cdot \frac{1}{D^2 - 2D + 2} \cos x$$

$$= \frac{1}{D^2} \left[1 - \frac{2}{D} + \frac{2}{D^2} \right] x + e^x \cdot \frac{1}{D^2 + 2D + 1 - 2D - 2 + 2} \cos x$$

$$= \frac{1}{D^2} \left[1 - \left[\frac{2}{D} - \frac{2}{D^2} \right] \right] x + e^x \cdot x \cdot \frac{D}{2D^2} \cos x$$

$$= \frac{1}{D^2} \left[1 + \frac{2}{D} \right] x + \frac{x \cdot e^x (\sin x)}{+2}$$

$$= \frac{1}{2(1 - (D + \frac{D^2}{2}))} x + \frac{1}{2} x e^x \sin x$$

$$= \frac{1}{2} \left(1 + D - \frac{D^2}{2} \right) x + \frac{1}{2} x \cdot e^x \sin x$$

$$= \frac{1}{2} [x + 1] + \frac{1}{2} x \cdot e^x \sin x$$

$$y = e^x [C_1 \cos x + C_2 \sin x] + \frac{1}{2} [x + 1] + \frac{1}{2} x \cdot e^x \sin x$$

$$(ii) A = \begin{bmatrix} \frac{1}{2}(1+i) & \frac{1}{2}(-1+i) \\ \frac{1}{2}(1+i) & \frac{1}{2}(1-i) \end{bmatrix}$$

For unitary matrix $A \cdot A^0 = I$

$$A^0 = (\bar{A})^T$$

$$\bar{A} = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(-1-i) \\ \frac{1}{2}(1-i) & \frac{1}{2}(1+i) \end{bmatrix}$$

$$(\bar{A})^T = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ \frac{1}{2}(-1-i) & \frac{1}{2}(1+i) \end{bmatrix}$$

$$A \cdot A^0 = \begin{bmatrix} \frac{1}{2}(1+i) & \frac{1}{2}(-1+i) \\ \frac{1}{2}(1+i) & \frac{1}{2}(1-i) \end{bmatrix} \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ \frac{1}{2}(-1-i) & \frac{1}{2}(1+i) \end{bmatrix}$$

$$= \begin{bmatrix} \frac{1}{4}(1-i^2 + (-1)^2 - i^2) & \frac{1}{4}(1-i^2 + i^2 - 1) \\ \frac{1}{4}(1-i^2 + (-i)^2 - 1) & \frac{1}{4}(1-i^2 + 1-i^2) \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 0 \\ 0 & 1 \end{bmatrix} = I$$

So, since $A \cdot A^0 = I$, the given matrix is unitary

$$A^0 = A^{-1}$$

$$\text{So, } A^{-1} = \begin{bmatrix} \frac{1}{2}(1-i) & \frac{1}{2}(1-i) \\ \frac{1}{2}(-1-i) & \frac{1}{2}(1+i) \end{bmatrix}$$

Ans

Good
Approach

18

- 6 (b) (i) If $A = \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix}$ show that $A^2 - 4A - 5I = 0$ where $I, 0$ are the identity matrix and the

null matrix of order 3 respectively. Use this result to find A^{-1} .

[10 marks]

Soln:- $A = \begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix}$

Cayley-Hamilton theorem -

$$|A - \lambda I| = 0$$

$$\begin{vmatrix} (1-\lambda) & 2 & 2 \\ 2 & (1-\lambda) & 2 \\ 2 & 2 & (1-\lambda) \end{vmatrix} = 0$$

$$(1-\lambda) [(1-\lambda)^2 - 4] - 2[2(1-\lambda) - 4] + 2[4 - 2(1-\lambda)] = 0$$

On simplifying we get

$$\lambda^2 - 4\lambda - 5 = 0$$

Since, each eigen value satisfies its eqn.

So, $\boxed{A^2 - 4A - 5I = 0}$

Ans

Given, $A^2 - 4A - 5I = 0$
 multiplying both side by A^{-1}

$$A - 4I - 5A^{-1} = 0$$

$$A^{-1} = \frac{1}{5} (A - 4I)$$

$$= \frac{1}{5} \left[\begin{bmatrix} 1 & 2 & 2 \\ 2 & 1 & 2 \\ 2 & 2 & 1 \end{bmatrix} - \begin{bmatrix} 4 & 0 & 0 \\ 0 & 4 & 0 \\ 0 & 0 & 4 \end{bmatrix} \right]$$

$$A^{-1} = \frac{1}{5} \begin{bmatrix} -3 & 2 & 2 \\ 2 & -3 & 2 \\ 2 & 2 & -3 \end{bmatrix}$$

Ans.

Good
Approach.

9

- 6 (b) (ii) Examine the following vectors for linear dependence and find the relation if it exists.
 $X_1 = (1, 2, 4)$, $X_2 = (2, -1, 3)$, $X_3 = (0, 1, 2)$ and $X_4 = (-3, 7, 2)$.

[10 marks]

sol:- for linear dependence, determinant of the matrix $= 0$

Given $X_1 = (1, 2, 4)$

$X_2 = (2, -1, 3)$

$X_3 = (0, 1, 2)$

$X_4 = (-3, 7, 2)$

①

Incomplete
solution

$(1, 0, 0)$ is a vector
 $(0, 1, 0)$ is a vector
 $(0, 0, 1)$ is a vector
 $(1, 1, 1)$ is a vector
 $(1, 0, 1)$ is a vector
 $(1, 1, 0)$ is a vector
 $(0, 1, 1)$ is a vector

6 (c) (i) Solve: $(D^2 - 4D + 4)y = 8x^2 e^{2x} \sin 2x$.

(ii) Find the regression line of y on x for the following data and estimate the value of y , when $x = 10$. (Use the least square approximation method)

x	1	3	4	6	8	9	11	14
y	1	2	4	4	5	7	8	9

[12 + 8 marks]

(1)

$$D^2 - 4D + 4 = 0$$

$$(D-2)^2 = 0$$

$$m = 2, 2 \Rightarrow \text{C.F.} = (C_1 + C_2 x) e^{2x}$$

P.I.

$$\frac{1}{D^2 - 4D + 4} 8x^2 e^{2x} \sin 2x$$

$$= 8x^2 e^{2x} \cdot \frac{1}{(D+2)^2 - 4(D+2) + 4} \sin 2x$$

$$= 8x^2 e^{2x} \cdot \frac{1}{D^2 + 4D + 4 - 4D - 8 + 4} \sin 2x$$

$$= 8x^2 e^{2x} \cdot \frac{1}{(-2)^2} \sin 2x$$

$$= -2x^2 \cdot e^{2x} \cdot 8 \sin 2x$$

$$y = \text{C.F.} + \text{P.I.}$$

$$= (C_1 + C_2 x) e^{2x} - 2x^2 \cdot e^{2x} \cdot 8 \sin 2x$$

Ans.

3

(ii)

x	y	y^2	xy
1	1	1	1
3	2	4	6
4	4	16	16
6	4	16	24
8	5	25	40
9	7	49	63
11	8	64	88
14	9	81	126
56	40	256	364

$$\sum y = na + b \sum x$$

$$\sum y^2 = a \sum y + b \sum xy$$

$$40 = 8a + 56b$$

$$256 = 40a + 364b$$

$$a = \frac{1}{3}, b = \frac{2}{3}$$

~~Q2~~

3

- 7 (a) If the area of the region bounded by the curve $y = x - x^2$ and the line $y = mx$ equals $\frac{9}{2}$, then find all possible value of m .

[20 marks]



Q.7 (b) (i) If $u = \log(x^3 + y^3 + z^3 - 3xyz)$, show that $\left(\frac{\partial}{\partial x} + \frac{\partial}{\partial y} + \frac{\partial}{\partial z}\right)^2 u = \frac{-9}{(x + y + z)^2}$.

(ii) Find the real root of the following equation, correct to three decimal places.

(Using Newton-Raphson method)

$$x^3 - 2x - 5 = 0$$

[12 + 8 marks]

- Q.7 (c) Show that the vector field $\vec{F} = \frac{\vec{r}}{|\vec{r}|^3}$ is irrotational as well as solenoidal. Find the scalar potential.

[20 marks]



- (a) Sixteen players S_1, S_2, \dots, S_{16} play in a tournament. They are divided into eight pairs at random, from each pair a winner is decided on the basis of a game played between the two players of the pair. Assume that all the players are of equal strength.

Find:

- (i) The probability that the player S_1 is among the eight winners.
- (ii) The probability that exactly one of the two players S_1 and S_2 is among the eight winners.

[20 marks]

- Q.8 (b)
- (i) Assuming that the diameters of 1000 brass plugs taken consecutively from a machine from a normal distribution with mean 0.7515 cm and standard deviation 0.0020 cm, how many number of brass plugs are likely to be rejected if the approved diameter is 0.752 ± 0.004 cm? (Given, $\text{Area}[Z = -1.75] = 0.4599$ and $\text{Area}[Z = 2.25] = 0.4878$).
- (ii) A periodic function of time period 4 is defined as $f(x) = |x|$, $-2 < x < 2$. Find its Fourier series expansion.

[8 + 12 marks]

Q.8 (c) Apply Runge-Kutta 4th order method to find an approximate value of y when $x = 0.2$.

Given that $\frac{dy}{dx} = x + y$, $y = 1$ when $x = 0$. (Take step size of 0.1)

[20 marks]

Space for Rough Work

Alt - 288

Space for Rough Work