



**MADE EASY**

Leading Institute for ESE, GATE & PSUs

# ESE 2025 : Mains Test Series

UPSC ENGINEERING SERVICES EXAMINATION

## Electronics & Telecommunication Engineering

Test-1 : Network Theory + Electronic Devices and Circuits [All topics]

Name : .....

Roll No : .....

### Test Centres

Delhi ☒

Bhopal ☐

Jaipur ☐

Pune ☐

Kolkata ☐

Hyderabad ☐

Ident's signature

### Instructions for Candidates

1. Do furnish the appropriate details in the answer sheet (viz. Name & Roll No).
2. There are Eight questions divided in TWO sections.
3. Candidate has to attempt FIVE questions in all in English only.
4. Question no. 1 and 5 are compulsory and out of the remaining THREE are to be attempted choosing at least ONE question from each section.
5. Use only black/blue pen.
6. The space limit for every part of the question is specified in this Question Cum Answer Booklet. Candidate should write the answer in the space provided.
7. Any page or portion of the page left blank in the Question Cum Answer Booklet must be clearly struck off.
8. There are few rough work sheets at the end of this booklet. Strike off these pages after completion of the examination.

### FOR OFFICE USE

Question No.	Marks Obtained
Section-A	
Q.1	28
Q.2	28
Q.3	—
Q.4	52
Section-B	
Q.5	22
Q.6	/
Q.7	/
Q.8	35
<b>Total Marks Obtained</b>	<b>165</b>

Signature of Evaluator

Cross Checked by

*Ch. K. Singh*

- Good attempt.
- Avoid small mistakes.

• Improve writing skills.

## IMPORTANT INSTRUCTIONS

CANDIDATES SHOULD READ THE UNDERMENTIONED INSTRUCTIONS CAREFULLY. VIOLATION OF ANY OF THE INSTRUCTIONS MAY LEAD TO PENALTY.

### DONT'S


1. Do not write your name or registration number anywhere inside this Question-cum-Answer Booklet (QCAB).
2. Do not write anything other than the actual answers to the questions anywhere inside your QCAB.
3. Do not tear off any leaves from your QCAB, if you find any page missing do not fail to notify the supervisor/invigilator.
4. Do not leave behind your QCAB on your table unattended, it should be handed over to the invigilator after conclusion of the exam.

### DO'S

1. Read the Instructions on the cover page and strictly follow them.
2. Write your registration number and other particulars, in the space provided on the cover of QCAB.
3. Write legibly and neatly.
4. For rough notes or calculation, the last two blank pages of this booklet should be used. The rough notes should be crossed through afterwards.
5. If you wish to cancel any work, draw your pen through it or write "Cancelled" across it, otherwise it may be evaluated.
6. Handover your QCAB personally to the invigilator before leaving the examination hall.

## Section A : Network Theory + Electronic Devices and Circuits

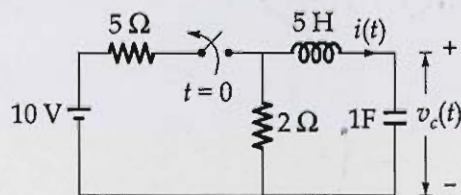Q.1 (a) Consider the circuit shown below:




If the equation of current,  $i(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$  for  $t \geq 0$ .

Then calculate the value of

- (i)  $\alpha$                       (ii)  $B_1$   
 (iii)  $B_2$                     (iv)  $\omega_d$

[12 Marks]

Ans. Laplace eq. equivalent

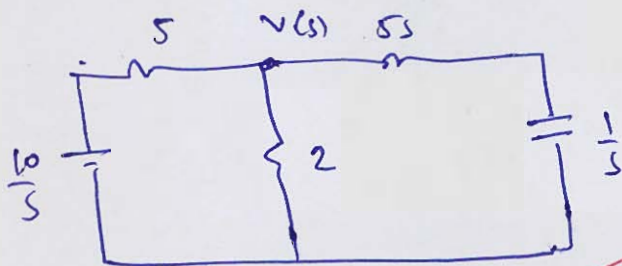

$$\frac{V(s) - \frac{10}{s}}{5} + \frac{V(s)}{2} + \frac{V(s)}{5s + \frac{1}{s}} = 0$$

$$V(s) \left[ \frac{1}{5} + \frac{1}{2} + \frac{s}{5s^2 + 1} \right] = \frac{10}{5s}$$

$$V(s) \left[ \frac{7}{10} + \frac{s}{5s^2 + 1} \right] = \frac{10}{5s}$$

$$V(s) \left[ \frac{35s^2 + 7 + 10s}{10(5s^2 + 1)} \right] = \frac{10}{5s}$$

$$V(s) = \frac{100(5s^2 + 1)}{5s(35s^2 + 10s + 7)}$$

$$I(s) = \frac{V(s)}{5s + \frac{1}{s}} = \frac{V(s)s}{5s^2 + 1}$$


$$= \frac{100 (s^2 + 1)}{s^2 (35s^2 + 10s + 7) (s^2 + 1)} \times s$$

$$I(s) = \frac{20}{35s^2 + 10s + 7}$$

$\downarrow$   
 $14s$



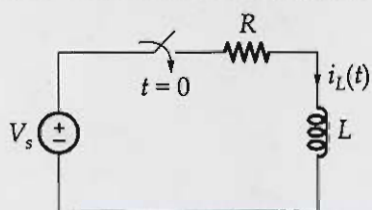Q.1 (b) Prove that the efficiency of DC excited R-L series circuit is zero.



[12 Marks]

Ans  $I(s) = \frac{V_s}{s} \cdot \frac{1}{R + sL}$

$$I(s) = \frac{\frac{V_s}{s}}{R + sL}$$

$$= \frac{V}{s(R + sL)} = \frac{V/R}{s(s + \frac{L}{R})}$$


$$= \frac{A}{s} + \frac{B}{s + \frac{L}{R}}$$

$$I(t) = \frac{V}{R} (1 - e^{-\frac{L}{R}t}) u(t)$$

4



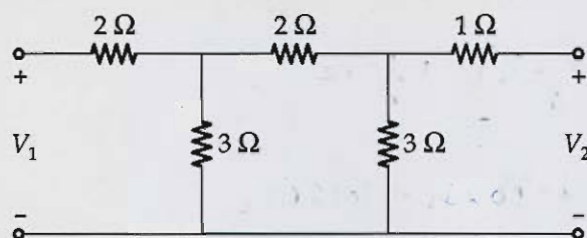Q.1 (c) Obtain ABCD parameters for the network shown in figure.




[12 marks]

ABCD parameters are

$$V_1 = AV_2 - BI_2 \quad \text{--- (i)}$$

$$I_1 = CV_2 - DI_2 \quad \text{--- (ii)}$$

Ans.

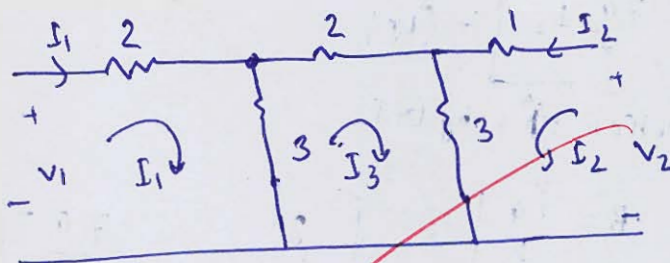

Apply KVL in loop 1

$$V_1 = 5I_1 - 3I_3 \quad \text{--- (a)}$$

Apply KVL in loop 2

$$8I_3 - 3I_1 + 3I_2 = 0$$

$$8I_3 = 3I_1 - 3I_2$$

$$I_3 = \frac{3}{8}I_1 - \frac{3}{8}I_2 \quad \text{--- (b)}$$

Apply KVL in loop 3

$$V_2 = 4I_2 + 3I_3 \quad \text{--- (c)}$$

put equation (b) in (c)

$$V_2 = 4I_2 + 3\left[\frac{3}{8}I_1 - \frac{3}{8}I_2\right] = 4I_2 + \frac{9}{8}I_1 - \frac{9}{8}I_2$$

$$V_2 = 2.875I_2 + \frac{9}{8}I_1$$

$$I_1 = \frac{8}{9}V_2 - \frac{23}{9}I_2 \quad \text{--- (d)}$$

compare --- (ii) and (d)

$$\boxed{C = \frac{8}{9} \quad \text{and} \quad D = \frac{23}{9}}$$

put equation (d) in eqn (a)

$$V_1 = 5I_1 - 3\left(\frac{3}{8}I_1 - \frac{3}{8}I_2\right)$$

$$V_1 = 5I_1 - \frac{9}{8}I_1 + \frac{9}{8}I_2$$

$$V_1 = \frac{31}{8}I_1 + \frac{9}{8}I_2 \quad \text{--- (e)}$$

Substitute equation (2) in equation (1)

$$V_1 = \frac{31}{8} \left[ \frac{8}{9} V_2 - \frac{23}{9} I_2 \right] + \frac{9}{8} I_2$$

$$= \frac{31}{9} V_2 - 9.402 I_2 + 1.125 I_2$$

$$V_1 = \frac{31}{9} V_2 - \frac{79}{2} I_2 \quad \text{--- (4)}$$

Compare equation (1) by (4)

$$A = \frac{31}{9} \quad B = \frac{79}{2}$$

[A B C D]

$$= \begin{bmatrix} \frac{31}{9} & \frac{79}{2} \\ \frac{8}{9} & \frac{23}{9} \end{bmatrix}$$

- Q.1(d) Consider an  $n$ -channel MOSFET with source and drain doping concentrations of  $N_d = 10^{19} \text{ cm}^{-3}$  and a channel region doping of  $N_a = 10^{16} \text{ cm}^{-3}$ . Assume a channel length of  $L = 1.2 \mu\text{m}$ , and assume the source and body are at ground potential (i.e.,  $|V_{SB}| = 0$ ). Calculate the theoretical punch-through voltage assuming the abrupt junction approximation.

(Assume,  $V_T = 0.0259 \text{ V}$ ;  $\epsilon_s = 11.7\epsilon_0$ ;  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$  for Si)

[12 Marks]

Ans. Punch Through voltage.  $(V_{pt}) = \frac{W^2 q N_a}{2 \epsilon}$

$$W = \sqrt{\frac{2 \epsilon}{q} \left( \frac{1}{N_a} + \frac{1}{N_d} \right) V_0}$$

Given  $N_A = 10^{16}$

$N_D = 10^{19}$

$n_i = 1.5 \times 10^{10}$

$$V_0 = W \ln \frac{N_A N_D}{n_i^2}$$

$$V_0 = 0.0259 \ln \left( \frac{10^{16} \times 10^{19}}{2.25 \times 10^{20}} \right)$$

$$V_0 = 0.874 \text{ volt}$$

width

$$W = \sqrt{\frac{2\epsilon}{q} \left( \frac{1}{N_a} + \frac{1}{N_d} \right) V_0}$$

$$= \sqrt{\frac{2 \times 11.7 \times 8.85 \times 10^{-14}}{1.6 \times 10^{-19}} \left( \frac{1}{10^{16}} + \frac{1}{10^{16}} \right) 0.874}$$


$$W = 1.132 \times 10^{-9} \text{ m}$$

punch through voltage  $V_{ix} = \frac{W^2 q N_a}{2\epsilon}$

$$= \frac{(1.132 \times 10^{-9})^2 \times 1.6 \times 10^{-19} \times 10^{16}}{2 \times 11.7 \times 8.85 \times 10^{-14}}$$

$$V_0 = 4.406 \times 10^{-10} \text{ volt}$$

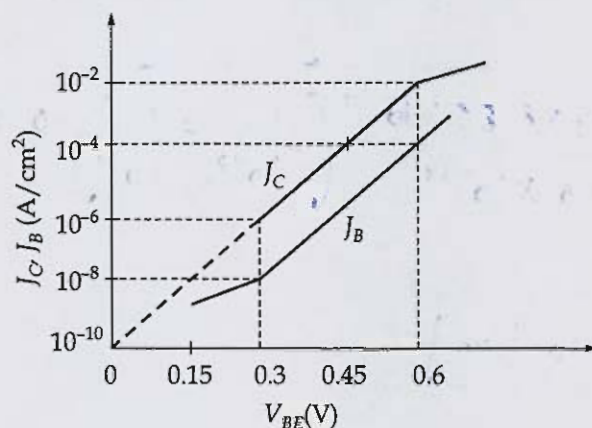- Q.1 (e) Consider an NPN transistor with Emitter, Base and Collector region width as  $W_E = 0.5 \mu\text{m}$ ,  $W_B = 0.2 \mu\text{m}$  and  $W_C = 2 \mu\text{m}$  respectively. Diffusion coefficient of carriers in base region,  $D_B = 10 \text{ cm}^2/\text{s}$ .



Calculate:

- Common Emitter Current gain,  $\beta$ .
- Base doping concentration,  $N_B$ .
- Base transit time,  $\tau_B$ .

(Assume,  $W_B \ll L_B$ ,  $n_i = 10^{10} \text{ cm}^{-3}$ ,  $\frac{kT}{q} = 0.026 \text{ V}$ )

[12 Marks]

Ans. (iii) Base transit time  $\tau_B$

$$\tau_B = \frac{W_B^2}{2D_B}$$

$$W_B = 0.2 \times 10^{-4} \text{ cm}$$

$$D_B = 10$$


$$\tau_B = \frac{0.2 \times 0.2 \times 10^{-8}}{2 \times 10}$$

$$\tau_B = 2 \times 10^{-11} \text{ sec}$$

4

*[Faint, illegible handwritten text and diagrams are visible in the main body of the page. Some faint sketches of lines and points are present.]*

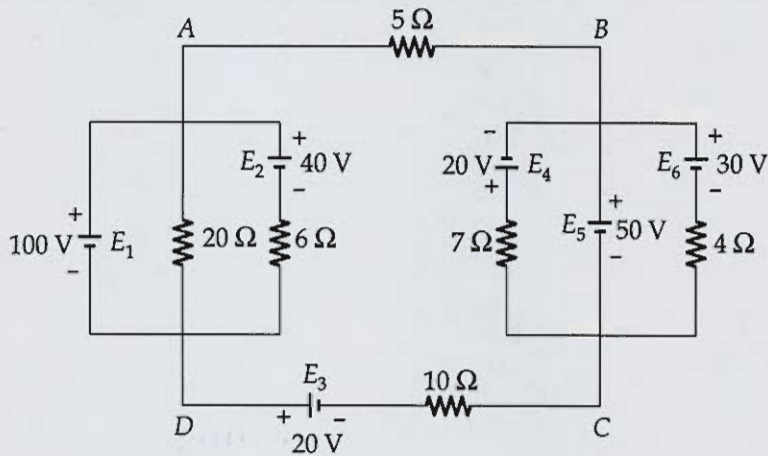
- Q.2 (a) For the circuit shown in figure, find the current through  $5\Omega$  resistor by using Thevenin's theorem and verify the same by using superposition theorem.



[20 marks]

Ans. Thevenin's theorem.

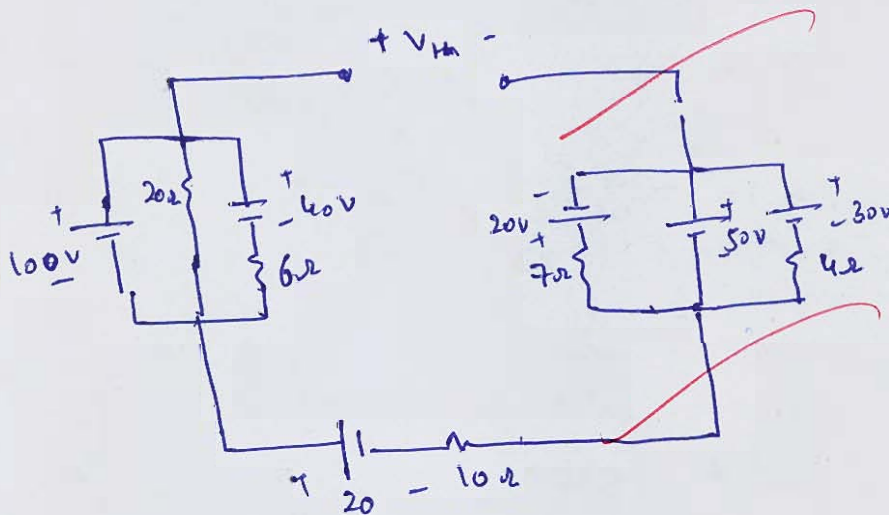Open circuit load terminal  $5\Omega$   
Thevenin equivalent voltage - Redrawn circuit




Apply KVL  $-100 + V_{th} + 50 + (10 \times 10) - 20 = 0$

$-100 + V_{th} + 50 - 20 = 0$


$V_{th} = 70V$

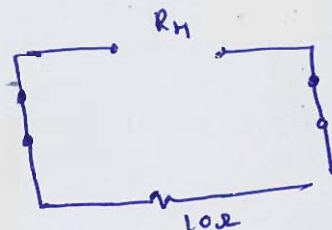Equivalent resistance  $\rightarrow$  voltage source act as short circuit  
Redrawn circuit



$R_{th} = 10\Omega$

thevenin equivalent circuit

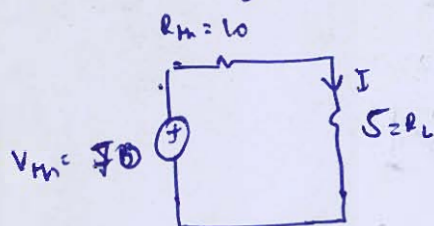


by apply KVL

$$I = \frac{10}{15} = 4.67 \text{ Amp}$$

-a

By using Superposition theorem

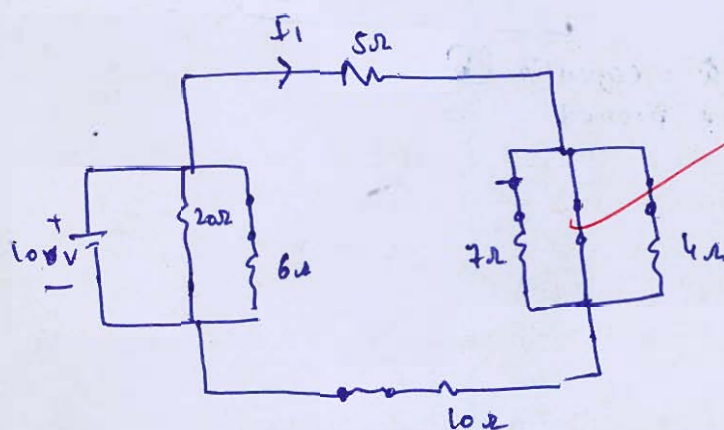For 100V  $\rightarrow$  other voltage source act as short circuit




by apply KVL

$$-100 + 5I_1 + 10I_1 = 0$$


$$I_1 = \frac{100}{15} \text{ Amp}$$

For  $\pm 40V$

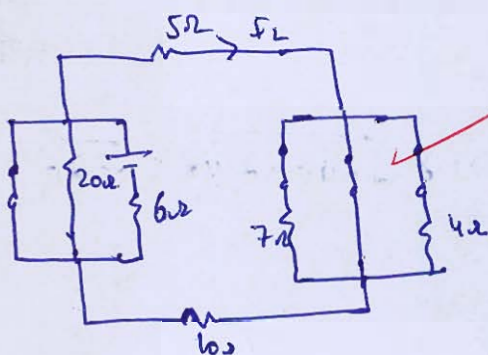

$$I_2 = 20$$

For  $\pm 50V$

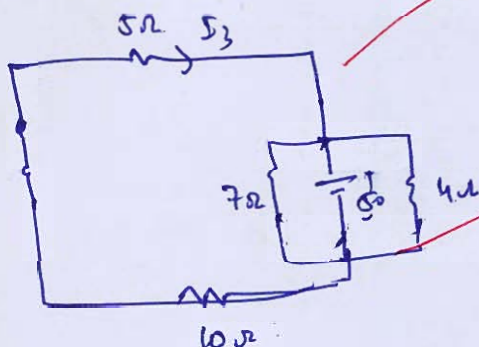


$$15I_3 + 50 = 0$$

$$I_3 = -\frac{50}{15}$$

For  $\pm 20V$   
For  $\pm 30V$   $\rightarrow$  No current flow

For = 20 V

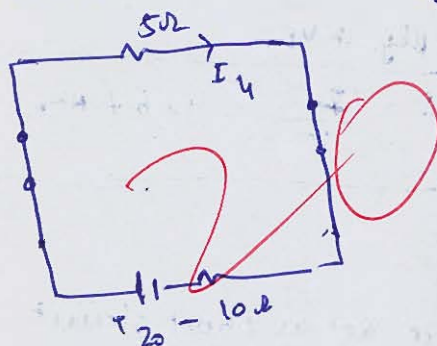

by apply KVL

$$15 I_4 - 20 = 0$$

$$I_4 = \frac{20}{15}$$

By addy  $I_1, I_3$  and  $I_4$ 

$$= \frac{100}{15} + \frac{20}{15} - \frac{50}{15} = \frac{70}{15}$$

$$I = 4.67 \text{ Amp} \quad \text{--- (b)}$$

Equation (a) = equation (b)  
hence proved.

$$\cos \approx \frac{\cos}{\cos}$$

Q.2 (b) Consider an  $n$ -channel MOSFET with a doping of  $N_a = 10^{15} \text{ cm}^{-3}$ , an oxide thickness of  $t_{ox} = 750 \text{ \AA}$  and an initial flat-band voltage of  $V_{FB} = -1.5 \text{ V}$ .

Calculate:

- Threshold voltage,  $V_T$ .
- The ion implant density ' $D_I$ ' required to achieve a threshold voltage of  $V_T = +0.9 \text{ V}$  with  $V_{SB} = 0$ .
- Using the result obtained in part (ii), determine the threshold voltage if source to body voltage,  $V_{SB} = 2 \text{ V}$  is applied.

(Assume,  $V_t = 0.026 \text{ V}$ ,  $\epsilon_s = 11.7 \epsilon_0$ ,  $\epsilon_{ox} = 3.9 \epsilon_0$ ,  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ )


[8 + 4 + 8 marks]

Ans (b) as threshold voltage

$$V_t = V_{t0} + \gamma \sqrt{2qF + 2V_{SB}} - \sqrt{2qF}$$



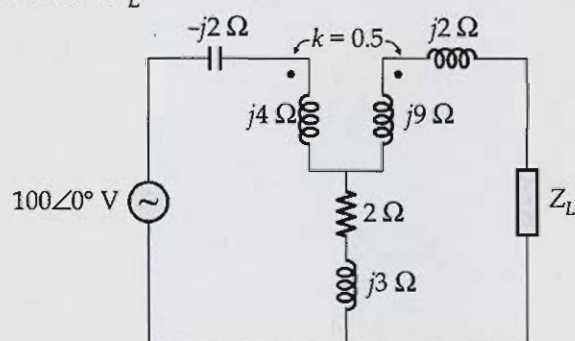
- Q.2 (c) (i) Find the Thevenin's equivalent of the circuit shown in figure below as seen from the load impedance  $Z_L$ .
- (ii) Find the value of  $Z_L$  for maximum power transfer and also the maximum power transfer to the load  $Z_L$ .



[12 + 8 marks]

Ans. i) Thevenin's equivalent circuit 'Z<sub>L</sub>' is open circuit

Redraw circuit

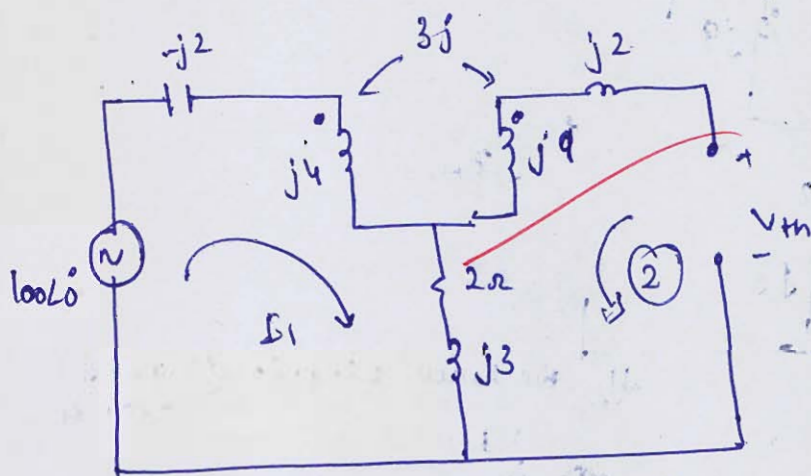

$$M = k \sqrt{L_1 L_2}$$

$$= 0.5 \sqrt{j4 \times j9}$$

$$= 0.5 \times j6 =$$

$$M = 3j$$

By apply KVL in loop 1

$$I_2 = 0$$

$$100 \angle 0^\circ = [(-j2 + j4 + j3) + 2] I_1$$

$$100 \angle 0^\circ = (j5 + 2) I_1$$

$$I_1 = \left( \frac{100 \angle 0^\circ}{2 + j5} \right)$$

Thevenin voltage  $\rightarrow$  apply KVL in loop 2

value  $I_1$

$$V_{th} = 0(j9 + j2) - 3j I_1 + (2 + j3) I_1$$

$$V_{th} = 2 I_1$$


put value  $I_1$

$$V_{th} = \frac{200 \angle 0^\circ}{2 + j5} \text{ volt}$$


$$37.12 \angle -68.2^\circ \text{ Volt}$$

Find equivalent resistance  $R_{th}$  voltage

Source act short circuit redraw circuit

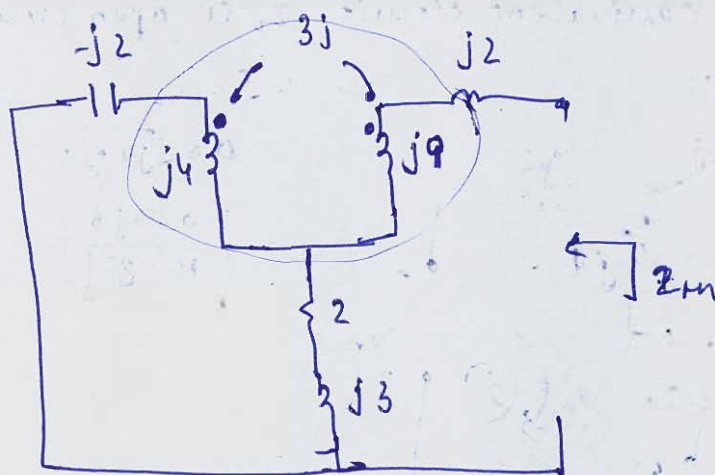

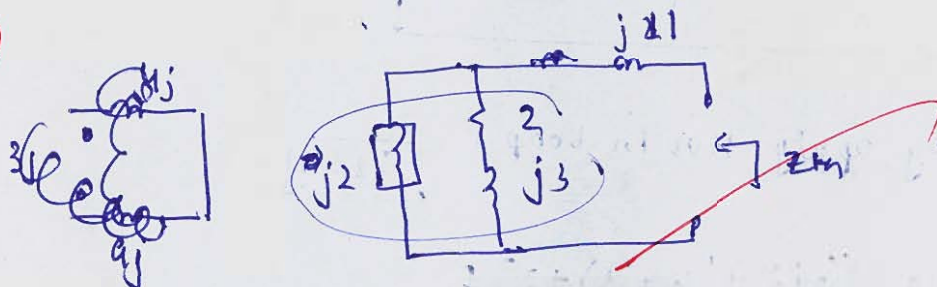Redraw circuit  $j2$  and  $j9$  in series




$2j$  and  $(2 + j3)$  in parallel and series with  $j11$

$$Z_{th} = \frac{(2j)(2 + j3)}{2j + 2 + j3} + j11$$

$$= \frac{4j - 6}{2 + j5} + j11$$

$$Z_{th} = 12.313 \angle 88.71^\circ = 0.275 + j12.31 \Omega$$

thevenin equivalent circuit

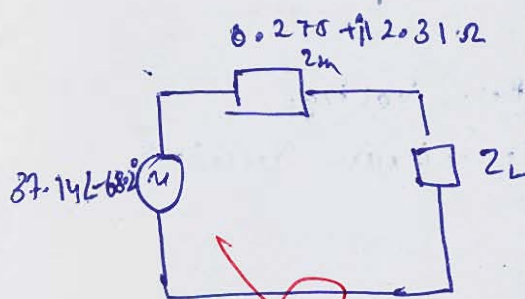


(i) For maximum power transfer theorem

$$Z_L = Z_{th}^*$$

$Z_L$

$$0.275 + j 12.312$$

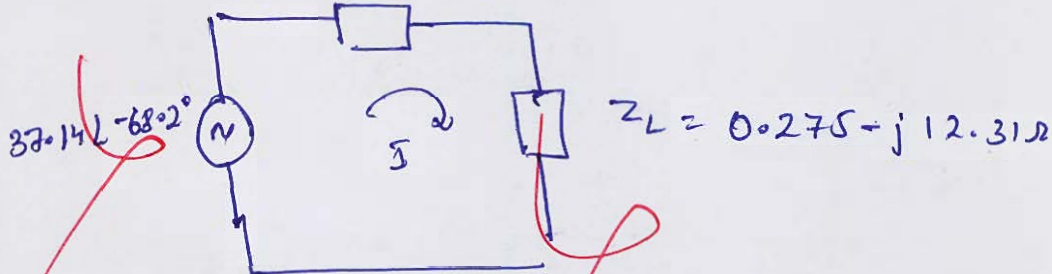

by apply KVL


$$I = \frac{37.14 \angle -68.2^\circ}{(0.275) \times 2} = 67.52 \angle -68.2^\circ$$

$$R_L = 0.275$$

$$P_{max} = I^2 R_L = (67.52)^2 \times 0.275$$

$$\text{Maximum Power} = 1.253 \text{ kWatt}$$

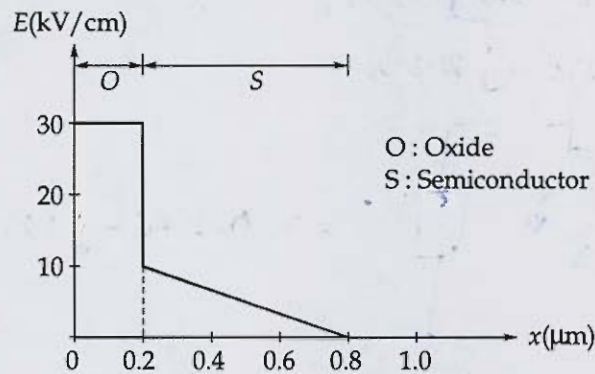- Q.3 (a) The figure shows the electric field distribution within a MOS structure (P-substrate) for a given potential  $V_G$  applied to the gate. Assume the flat band potential  $V_{FB} = 0$ .



Find:

- (i) The potential in the bulk of the semiconductor  $\psi_B$ .
- (ii) The potential at the surface of semi conductor,  $\psi_s$ .
- (iii) The threshold voltage,  $V_T$ .
- (iv) The value of the applied potential at Gate,  $V_G$ .


(Assume,  $\epsilon_{si} = 10^{-12}$  F/cm;  $\epsilon_{ox} = 3 \times 10^{-13}$  F/cm,  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ ,  $C_{ox} = 15 \text{ nF/cm}^2$ ,  $V_T = 26 \text{ mV}$ )

[20 marks]






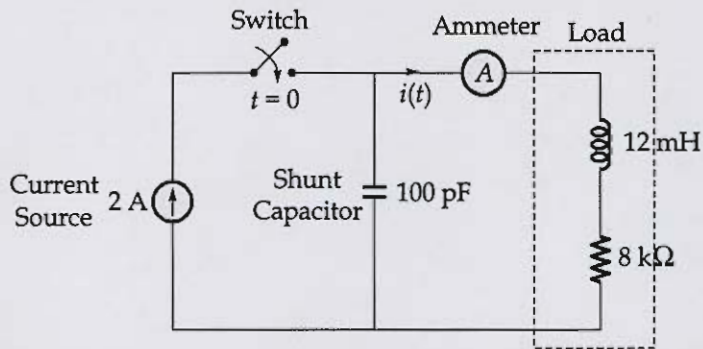- Q.3 (b) (i) The circuit in the figure contains a current source driving a load having an inductor and a resistor in series, with a shunt capacitor across the load. The ammeter is assumed to have zero resistance. The switch is closed at time  $t = 0$ .



Initially, when the switch is open, the capacitor is discharged and the ammeter reads zero ampere. After the switch is closed, the ammeter reading keep fluctuating for some time till it settle to a final steady value. Calculate the maximum ammeter reading that one will observe after the switch is closed.

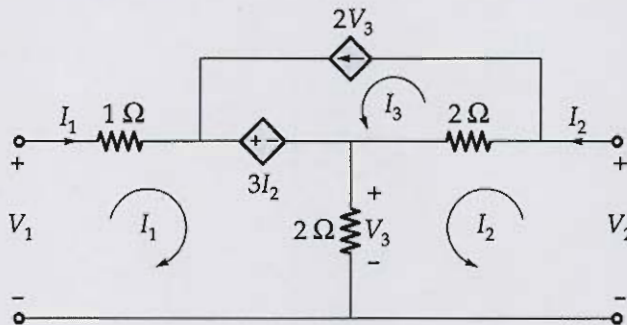- (ii) Determine Z and Y-parameters of the network shown in figure.



[10 + 10 marks]








- Q.3 (c) (i) Explain the working principle of a  $pn$ -junction solar cell.
- (ii) Consider an ideal silicon  $pn$ -junction diode with the following parameters:
- $$\tau_{n_0} = \tau_{p_0} = 0.1 \times 10^{-6} \text{ s}$$
- $$D_n = 25 \text{ cm}^2/\text{s}$$
- $$D_p = 10 \text{ cm}^2/\text{s}$$
- If  $N_d$  represents donor concentration and  $N_a$  represents acceptor concentration, what must be the ratio of  $\frac{N_a}{N_d}$  so that 95 percent of the current in the depletion region is carried by electrons?

[10 + 10 marks]




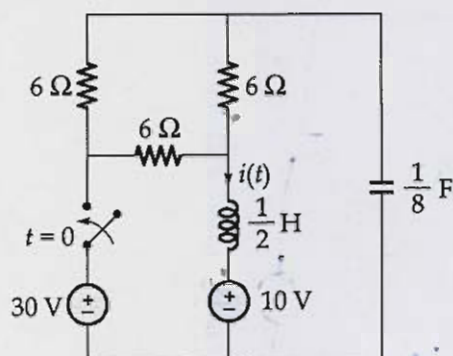Q.4 (a) For the network shown in figure, solve for  $i(t)$  for  $t > 0$ .



[20 marks]

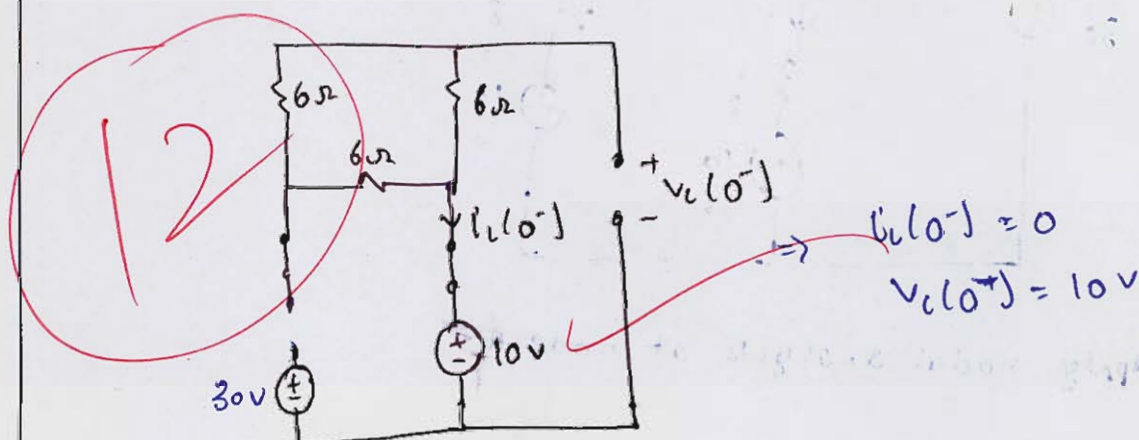as  $t=0^-$  switch is ~~closed~~ open  
at steady state inductor act as short circuit and  
Capacitor act as open circuit. Redraw the circuit




at  $t=0^+$ , switch closed.


inductor doesn't allowed sudden change  
current

$$i_L(0^-) = i_L(0^+) = 0$$


• Capacitor doesn't allowed sudden change  
of voltage  $v_C(0^-) = v_C(0^+) = 10$ .

• Redraw network in Laplace equivalent:

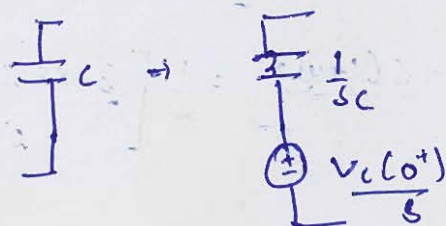

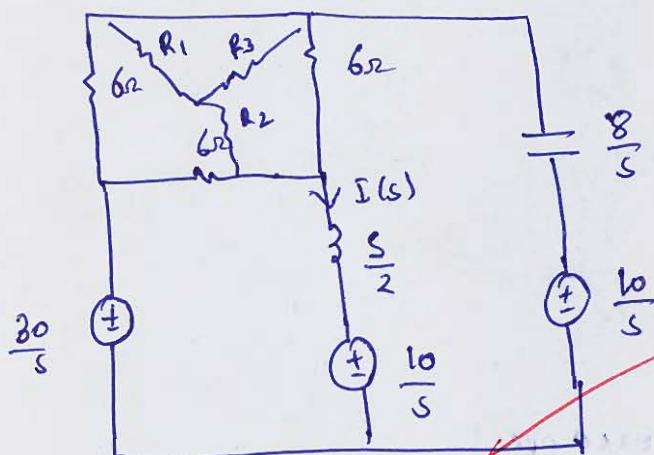

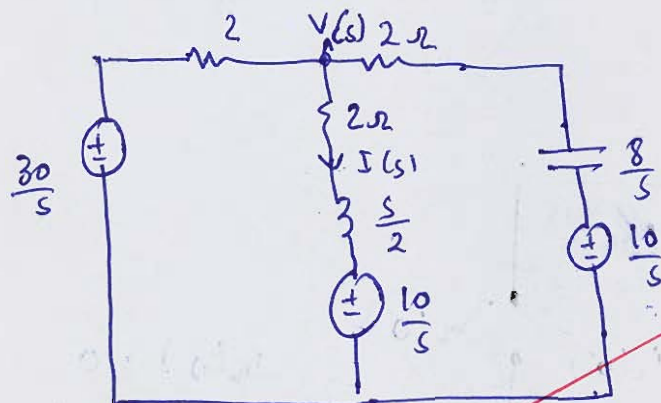Make star connection  $R_1, R_2, R_3 = 2\Omega$



Apply nodal analysis at node A

$$\frac{V(s) - \frac{30}{s}}{2} + \frac{V(s) - \frac{10}{s}}{2 + \frac{s}{2}} + \frac{V(s) - \frac{10}{s}}{\frac{8}{s}} = 0$$

$$V(s) \left[ \frac{1}{2} + \frac{1}{2 + \frac{s}{2}} + \frac{1}{8/s} \right] = \frac{30}{2s} + \frac{\frac{10}{s}}{2 + \frac{s}{2}} + \frac{\frac{10}{s}}{8/s}$$

$$V(s) \left[ \frac{1}{2} + \frac{2}{4+s} + \frac{s}{8} \right] = \frac{1}{s} \left[ \frac{30}{2} + \frac{10 \times 2}{4+s} + \frac{10s}{8} \right]$$

$$V(s) \left[ \frac{8(s+4) + 4 \times 8 + s(s+4) \cdot 2}{2(4+s) \cdot 8} \right] = \frac{1}{s} \left[ \frac{30 \times 8(s+4) + 20 \times 16 + 20s(s+4)}{2(4+s) \cdot 8} \right]$$

$$V(s) [2s^2 + 64 + 16s] = \frac{1}{s} [20s^2 + 320s + 1280]$$


$$V(s) = \frac{[20s^2 + 320s + 1280]}{s [2s^2 + 64 + 16s]} = \frac{[10s^2 + 160s + 640]}{s [s^2 + 8s + 32]}$$

$$I(s) = V(s) - \frac{10}{s} = \frac{V(s) - \frac{10}{s}}{2 + \frac{s}{2}} = \frac{V(s) - \frac{10}{s}}{\frac{4+s}{2}} = \frac{2V(s) - \frac{5}{s}}{(s+4)}$$

$$= \frac{2 \left[ \frac{10s^2 + 160s + 640}{s(s^2 + 8s + 32)} \right] - \frac{5}{s}}{(s+4)}$$


$$= \frac{20s^2 + 320s + 1280 - 5}{s(s+4)(s^2 + 8s + 32)} = \frac{20s^2 + 320s + 1275}{s(s+4)(s^2 + 8s + 32)}$$

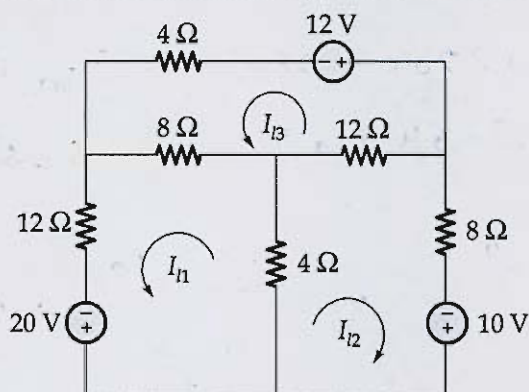- Q.4 (b) For the network shown in figure, write down the tie set matrix, obtain the network equilibrium equations in matrix form using the tie-set matrix and calculate loop currents.




[20 marks]

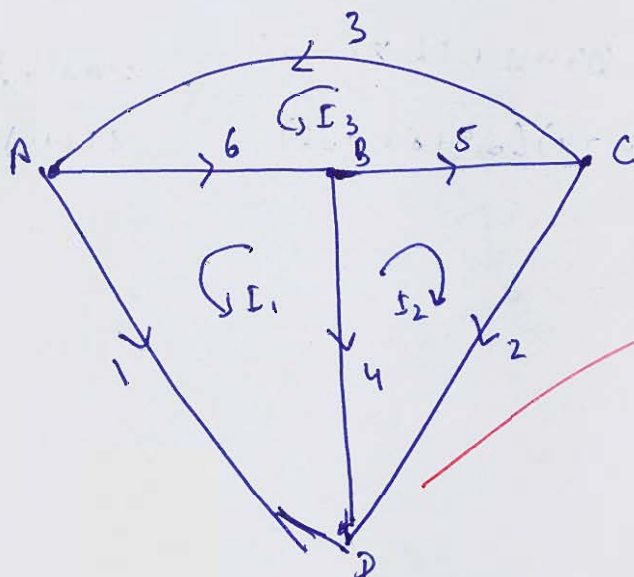Ans. Draw Graph & voltage source replace by short circuit & find



No. Number of fundamental loops are  $= b - (N - 1)$   
 $= 6 - (4 - 1) = 3$

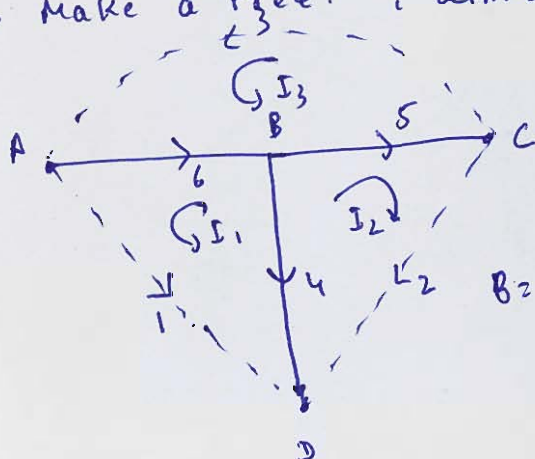• Make a tree. Links  $= b - (N - 1) = 3$



Tie set matrix is

	1	2	3	4	5	6
$I_1$	1	0	0	-1	0	-1
$I_2$	0	1	0	-1	1	0
$I_3$	0	0	1	0	1	1

Cte-set matrix

$$B = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix}$$

$$[Z_L] = [B][Z_B][B^T]$$

$Z_B$  = Impedance matrix

$$= [Z_B][B^T]$$

$$Z = \begin{bmatrix} 12 & 0 & 0 & 0 & 0 & 0 \\ 0 & 8 & 0 & 0 & 0 & 0 \\ 0 & 0 & 4 & 0 & 0 & 0 \\ 0 & 0 & 0 & 4 & 0 & 0 \\ 0 & 0 & 0 & 0 & 12 & 0 \\ 0 & 0 & 0 & 0 & 0 & 8 \end{bmatrix} \begin{bmatrix} 1 & 0 & 0 \\ 0 & 1 & 0 \\ 0 & 0 & 1 \\ -1 & -1 & 0 \\ 0 & 1 & 1 \\ -1 & 0 & 1 \end{bmatrix}$$

$$Z_L = [B][Z_B][B^T]$$

$$Z_L = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 12 & 0 & 0 \\ 0 & 8 & 0 \\ 0 & 0 & 4 \\ -4 & -4 & 0 \\ 0 & 12 & 12 \\ -8 & 0 & 8 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} 24 & +4 & -8 \\ +4 & 24 & 12 \\ -8 & 12 & 24 \end{bmatrix}$$

$[I_s] \rightarrow$  current source

as the

$$[Z_L][I_s] = [B][V_s] - [B][Z_B][I_s]$$

$$\begin{bmatrix} 24 & +4 & -8 \\ +4 & 24 & 12 \\ -8 & 12 & 24 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 1 & 0 & 0 & -1 & 0 & -1 \\ 0 & 1 & 0 & -1 & 1 & 0 \\ 0 & 0 & 1 & 0 & 1 & 1 \end{bmatrix} \begin{bmatrix} 20 & 10 & 0 \\ 0 & 10 & 0 \\ 0 & 0 & -12 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \\ 0 & 0 & 0 \end{bmatrix}$$

$$\begin{bmatrix} 24 & 4 & -8 \\ 4 & 24 & 12 \\ -8 & 12 & 24 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \\ I_3 \end{bmatrix} = \begin{bmatrix} 20 \\ 10 \\ -12 \end{bmatrix}$$

$$24I_1 + 4I_2 - 8I_3 = 20$$

$$4I_1 + 24I_2 + 12I_3 = 10$$

$$-8I_1 + 12I_2 + 24I_3 = -12$$

$$I_1 = 0.5 \text{ Ampere}$$

$$I_2 = \frac{2}{3} \text{ Ampere}$$

$$I_3 = -\frac{2}{3} \text{ Ampere}$$

Ans.

20


- Q.4 (c) (i) Consider a semiconductor in thermal equilibrium (no current). Assume that the donor concentration varies exponentially as,

$$N_d(x) = N_{d_0} e^{-\alpha x}$$

over the range  $0 \leq x \leq \frac{1}{\alpha}$  where  $N_{d_0}$  is a constant.

1. Calculate the electric field as a function of 'x' for  $0 \leq x \leq \frac{1}{\alpha}$ .
2. Calculate the potential difference between  $x = 0$  and  $x = \frac{1}{\alpha}$ .

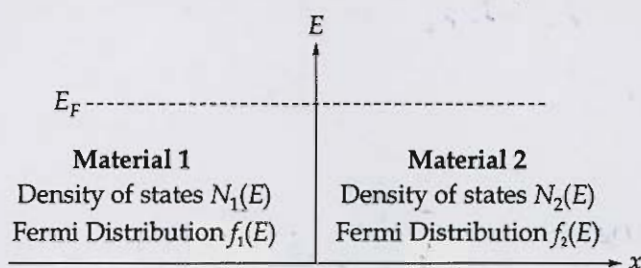- (ii) Consider two materials in intimate contact at equilibrium as shown below.



Assume the net motion of electrons is zero, show that the equilibrium Fermi level must be constant throughout, that is,  $E_{F_1} = E_{F_2}$  (or) show that no gradient exists in

the Fermi level at equilibrium,  $\frac{dE_F}{dx} = 0$

[10 + 10 marks]

Ans. ii) Given

material = 1

Density of states =  $N_1(E)$

$$\text{Fermi Distribution } f_1(E) = \frac{1}{1 + e^{(E - E_F)/kT}}$$

material = 2

Density of states =  $N_2(E)$

$$\text{Fermi Distribution } f_2(E) = \frac{1}{1 + e^{(E - E_F)/kT}}$$

$$N_x = \text{Electron concentration of material 1} = N_1 f_1 \Rightarrow N_x$$

$$P_x = \text{hole concentration of material 1} = N_1 (1 - f_1)$$

$$\text{Electron concentration of material 2} = N_2 f_2$$

$$\text{Hole concentration of material 2} = N_2 (1 - f_2)$$

At under steady state :  
equilibrium. Net electron concentration

$$N_A P_Y = N_Y P_X$$

$$(N_1 f_1) [N_2 (1 - f_2)] = (N_2 f_2) [N_1 (1 - f_1)]$$


$$f_1 (1 - f_2) = f_2 (1 - f_1)$$

$$f_1 - f_1 f_2 = f_2 - f_1 f_2$$

$$\boxed{f_1 = f_2}$$

$$\frac{1}{1 + e^{(E - E_F)/kT}} = \frac{1}{1 + e^{(E - E_F)/kT}}$$

$$\therefore \boxed{E_{F1} = E_{F2}}$$

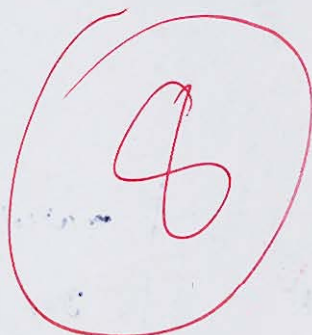

Ans. i) Given  $N_d(x) = N_{d0} e^{-\alpha x}$

i) at equilibrium no current  
 $0 = neq \ln E + e D_n \frac{dn}{dx}$

$$E = -\frac{V_T}{n} \frac{dn}{dx}$$

Given  $\Rightarrow n = N_{d0} e^{-\alpha x}$

$$E = -\frac{V_T}{N_{d0} e^{-\alpha x}} \frac{d(N_{d0} e^{-\alpha x})}{dx}$$

$$= -\frac{V_T}{N_{d0} e^{-\alpha x}} N_{d0} (e^{-\alpha x}) (-\alpha)$$

$$E = \alpha V_T \quad V/m$$

ii. e

$$E = -\frac{d\phi}{dx}$$

$$\int_0^x d\phi = -\int_0^x E \cdot dx$$

Put value of E

$$= -\int_0^x \alpha V_T dx$$

$$\phi = -\alpha V_T [x]_0^x$$

$$\phi = -V_T$$

$$\phi = -V_T$$

10

## Section B : Network Theory + Electronic Devices and Circuits

- Q.5 (a) Consider a sample of silicon at  $T = 300$  K. A hall effect device is fabricated with the following geometry:

$$d = 5 \times 10^{-3} \text{ cm}$$

$$W = 5 \times 10^{-2} \text{ cm}$$

$$L = 0.50 \text{ cm}$$

The electrical parameters measured are:

$$I_x = 0.50 \text{ mA}$$

$$V_x = 1.25 \text{ V}$$

$$B_z = 650 \text{ gauss} = 6.5 \times 10^{-2} \text{ tesla}$$

The Hall field is  $E_H = -16.5 \text{ mV/cm}$

Determine:

- the Hall voltage,
- the conductivity type,
- the majority carrier concentration,
- the majority carrier mobility.

[12 marks]

Ans. i) Hall voltage

$$V_H = \frac{BI}{\rho W}$$

$$E = +16.5 \text{ mV/cm}$$

$$E_H = \frac{V_H}{L}$$

$$V_H = \frac{-16.5 \times 10^{-3} \times 0.50}{0.50}$$

$$V_H = -33 \text{ mV}$$

$$\text{ii) } V_H = \frac{BI}{\rho W}$$

$$\sigma = ne\mu$$

$$\frac{1}{ne} = \rho$$

$$\rho = \frac{-33 \times 5 \times 10^{-2}}{6.5 \times 10^{-2} \times 0.50}$$

$$\rho = -500.76$$



Q.5 (b) Consider a long silicon  $pn$ -junction photodiode at  $T = 300$  K with the following parameters:

$$N_a = 2 \times 10^{16} \text{ cm}^{-3} \quad N_d = 10^{18} \text{ cm}^{-3}$$

$$D_n = 25 \text{ cm}^2/\text{s} \quad D_p = 10 \text{ cm}^2/\text{s}$$

$$\tau_{n_0} = 2 \times 10^{-7} \text{ s} \quad \tau_{p_0} = 10^{-7} \text{ s}$$

Assume a reverse-bias voltage of  $V_R = 5$  volts is applied and assume a uniform generation rate of  $G_L = 10^{21} \text{ cm}^{-3} \text{ s}^{-1}$  exists throughout the entire photodiode.

Calculate:

- The prompt photocurrent density and
- The total steady-state photocurrent density.

Given:  $n_i$  for Si =  $1.5 \times 10^{10} \text{ cm}^{-3}$

$$\epsilon_{r_{Si}} = 11.7$$

[12 marks]

Ans. (i)  $G_L = 10^{21}$

at steady state

$$\Delta p = 10^{21} \times 2 \times 10^{-7} \\ = 2 \times 10^{14}$$

$$\Delta n = 10^{21} \times 10^{-7} \\ \Delta n = 10^{14}$$

$$N_a = 2 \times 10^{16} + 2 \times 10^{14}$$

$$N_a \approx 2.02 \times 10^{16}$$

$$N_D = 10^{18} + 10^{14}$$

$$N_D \approx 10^{18}$$

$$J = q n_i^2 \left[ \frac{1}{N_D} \sqrt{\frac{D_p}{\tau_p}} + \frac{1}{N_A} \sqrt{\frac{D_n}{\tau_n}} \right] \left( e^{\frac{qV}{kT}} - 1 \right)$$

$$J_s =$$



- 5 (c) (i) Calculate the temperature at which there is a  $10^{-6}$  probability that an energy state 0.55 eV above the Fermi energy level is occupied by an electron.
- (ii) A silicon  $n^+p$  junction is biased at  $V_R = 10$  V.  
Determine the  $\Delta V_{bi}$  (Change in built-in potential), if the doping in the  $p$ -region increases by a factor of 2.

[6 + 6 marks]

Ans. i) Fermi  $f(E) = \frac{1}{1 + e^{(E-E_F)/kT}}$

acc to  
Boltzman  
approximation

$f(E) \approx e^{-(E-E_F)/kT}$

$10^{-6} \approx e^{-(0.55)/kT}$

$\ln(10^{-6}) \approx -\frac{0.55}{kT}$

$13.81 \approx \frac{0.55}{kT}$


$kT = \frac{0.55}{13.81}$

$\frac{1}{11600} = \frac{0.55}{13.81}$


$T_{\text{temp}} = 461.74 \text{ K}$



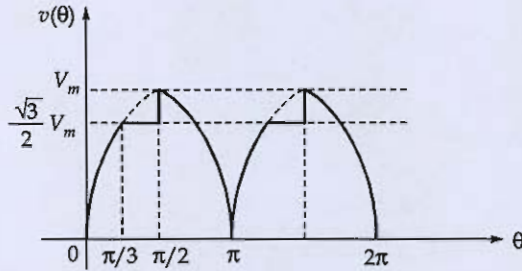- 5 (d) (i) The periodic function  $v(\theta)$  given below is applied to a resistor of  $1\ \Omega$ . Calculate the power dissipated in the resistor.  
[Given,  $V_m = 1\text{ V}$ ]



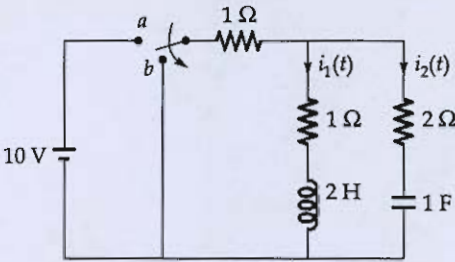
- (ii) In the circuit shown below, at  $t = 0$ , the switch is moved from position 'a' to 'b'.



Determine the value of  $\frac{di_1(0^+)}{dt}$ .


[6 + 6 Marks]

Ans. ii) at  $t=0^-$  switch at 'a'

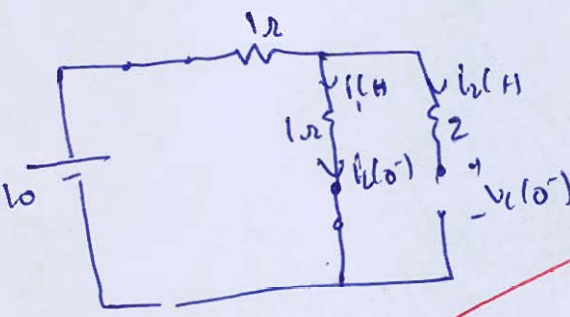


$i_L(0^-) = 5\text{ A}$   
 $v_L(0^-) = 5\text{ V}$

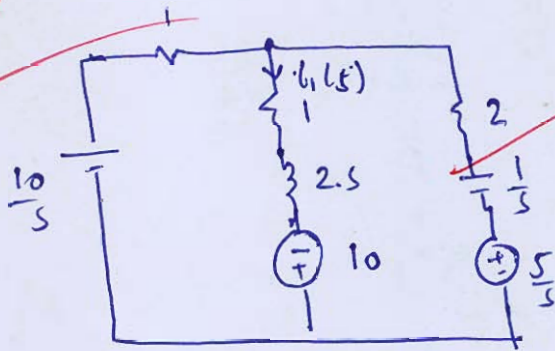at  $t=0^+$  switch at 'b'  $v_L(0^-) = v_L(0^+) = 5\text{ V}$   
 $i_L(0^-) = i_L(0^+) = 5\text{ A}$






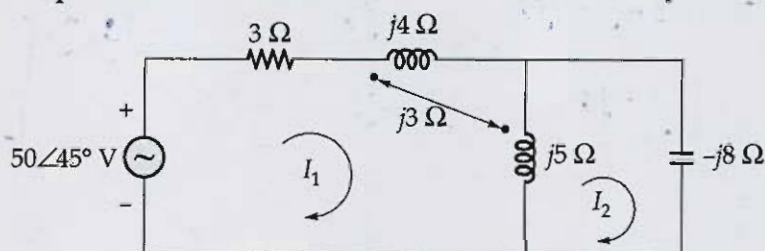- 5 (e) For the network shown in figure, write down the tie set matrix and obtain network equilibrium equations in matrix form.



[12 marks]

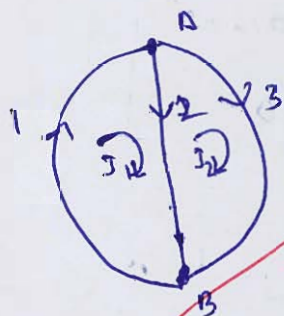Ans. Draw Graph ... Voltage source replace by short circuit



Fundamental tie-set loop  

$$= L = b - (N - 1)$$

$$= 3 - (2 - 1)$$

$$= 2$$

• Draw a tree.



Tie-set matrix

$$B = \begin{bmatrix} 1 & 2 & 3 \\ I_1 & 1 & 1 & 0 \\ I_2 & 0 & -1 & 1 \end{bmatrix}$$

$$B = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix}$$

Impedance  
matrix

$$Z_B = \begin{bmatrix} 3+j4 & j3 & 0 \\ j3 & j5 & 0 \\ 0 & 0 & -j8 \end{bmatrix}$$

$$Z_L = [B][Z_B][B^T]$$

$$= \begin{bmatrix} 1 & 0 \\ 1 & -1 \end{bmatrix} \begin{bmatrix} 3+j4 & j3 & 0 \\ j3 & j5 & 0 \\ 0 & 0 & -j8 \end{bmatrix} \begin{bmatrix} 1 & 0 \\ 1 & -1 \\ 0 & 1 \end{bmatrix} = \begin{bmatrix} 3+j2 & -j3 \\ j8 & -j8 \\ 0 & -j8 \end{bmatrix}$$

$$Z_L = \begin{bmatrix} 1 & 1 & 0 \\ 0 & -1 & 1 \end{bmatrix} \begin{bmatrix} 3+j2 & -j3 \\ j8 & -j8 \\ 0 & -j8 \end{bmatrix} =$$

$$= \begin{bmatrix} 3+j7+j8 & -j8 \\ -j8 & -j3 \end{bmatrix}$$

$$[I_S] = \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

equation

$$[Z_L][I_S] = [B][Z_B][I_S] + [B][Z_B][I_S]$$

$$\begin{bmatrix} 3+j15 & -j8 \\ -j8 & -j3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 50 \angle 45^\circ \\ 0 \end{bmatrix}$$

$$(3+j15)I_1 - j8I_2 = 50 \angle 45^\circ$$

$$-j8I_1 - j3I_2 = 0$$

Ans.

- 6 (a) (i) A series resonant circuit has its impedance,

$$Z(s) = \frac{20(s+1+j10)(s+1-j10)}{s}$$

Find:


- Resonant frequency
  - Q-factor
  - Bandwidth
  - Impedance of the circuit under resonance condition
- (ii) Draw a parallel RLC circuit using the elements of  $Z(s)$ . And also calculate the extra capacitance ( $C_{\text{ext}}$ ) that must be added in series with capacitor  $C$  so that the resonant frequency of parallel RLC circuit is increased by factor of 5.

[10 + 10 marks]





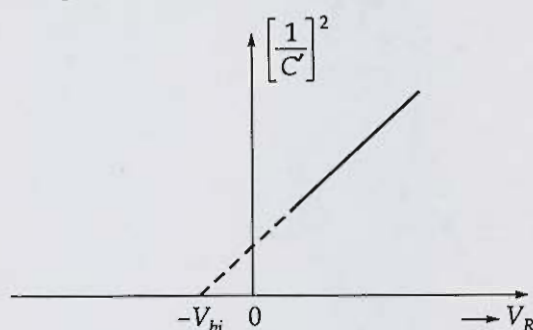- Q.6 (b) (i) A silicon device with n-type material is to be operated at  $T = 550$  K. At this temperature, the intrinsic carrier concentration must contribute no more than 5 percent of the total electron concentration. Determine the minimum donor concentration to meet this specification.  
(Given :  $n_i = 3.20 \times 10^{14} \text{ cm}^{-3}$  at  $T = 550$  K)
- (ii) Assume a silicon  $p^+n$  junction at  $T = 300$  K with  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ . The inverse depletion layer capacitance per unit area squared is a linear function of applied reverse-bias voltage as shown below.



Assume that the intercept of the curve on the voltage axis in above figure gives  $-0.855$  V and that the slope is  $1.32 \times 10^{15} (\text{F/cm}^2)^{-2} \text{V}^{-1}$ .

Determine the impurity doping concentrations ' $N_d$ ' and ' $N_a$ '.


[Given : Relative permittivity of Si = 11.7]

[8 + 12 marks]





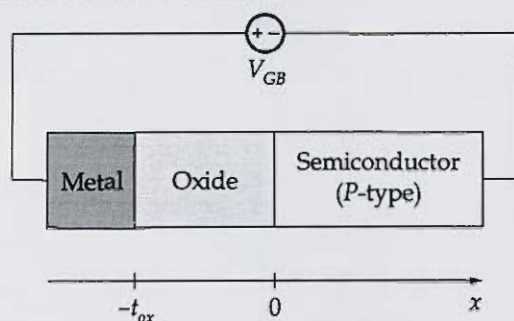5 (c) Consider a MOS structure shown below:



The oxide thickness,  $t_{ox} = 50$  nm and the doping level in the  $p$ -type substrate is  $N_a = 10^{16} \text{ cm}^{-3}$ . Assume, intrinsic carrier concentration of semiconductor,  $n_i = 10^{10} / \text{cm}^3$ , thermal voltage,  $V_T = 26$  mV,  $\epsilon_{\text{oxide}} = 3.45 \times 10^{-13} \text{ F/cm}$ ,  $\epsilon_{si} = 1.05 \times 10^{-12} \text{ F/cm}$ .

Calculate the hole concentration,  $p$  at the oxide-semiconductor interface (i.e.,  $x = 0$ ) under the following conditions:

- (i) At flatband.
- (ii) At threshold.
- (iii) At a condition in which the potential build up from the quasi-neutral body of semiconductor to  $x = 0$  is 0.5 V.
- (iv) At a condition when the capacitance per unit area of the MOS structure is  $50 \text{ nF/cm}^2$ .

[20 marks]






- Q.7 (a) Show that the ratio of hole diffusion current to electron diffusion current crossing a  $p$ - $n$  junction is given by,  $\frac{I_{pn}(0)}{I_{np}(0)} = \left( \frac{\sigma_p}{\sigma_n} \right) \times \left( \frac{L_n}{L_p} \right)$  where  $\sigma_p, \sigma_n$  are the conductivities and  $L_n, L_p$  are diffusion lengths of ' $p$ ' and ' $n$ ' regions respectively. Assume the junction is located at  $x = 0$  and neglect the depletion layer width.

[20 marks]



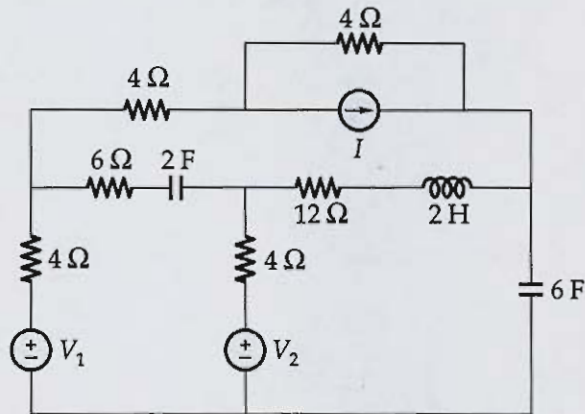**Q.7(b)** For the network shown in figure, draw the oriented graph and compute.



- (i) Complete incidence matrix and reduced incidence matrix.
- (ii) Tie set matrix.
- (iii) f-cut set matrix.

**[20 marks]**







- (c) (i) In a certain application, the circuit shown below must be designed to meet these two criteria:

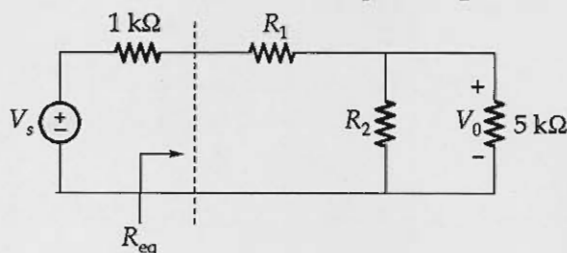1.  $\frac{V_0}{V_s} = 0.05$       2.  $R_{eq} = 39 \text{ k}\Omega$

If the load resistor  $5 \text{ k}\Omega$  is fixed, find  $R_1$  and  $R_2$  to meet the criteria.



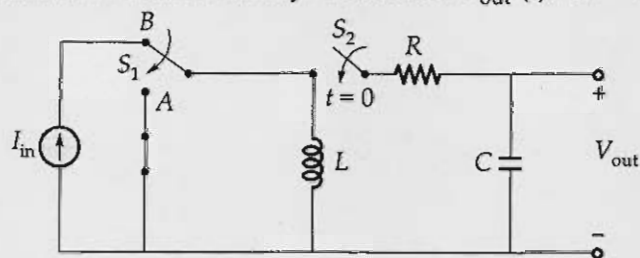- (ii) In the circuit shown below,  $L = 0.5 \text{ H}$ ,  $C = 0.75 \text{ F}$ ,  $R = 3 \Omega$  and  $I_{in}(t) = 12 \text{ A (DC)}$  for all time. Suppose that switch  $S_1$  has been in position  $B$  for a very long time and switch  $S_2$  has been open for all time. At time  $t = 0$  switch  $S_1$  moves to position  $A$  and switch  $S_2$  closes instantaneously. Calculate  $V_{out}(t)$  at  $t = 1.5$  seconds if  $V_{out}(0^-) = 0$



[10 + 10 marks]





- Q.8 (a) (i) In a very long  $p$ -type Si bar with cross-sectional area  $= 1 \text{ cm}^2$  and  $N_A = 10^{17} \text{ cm}^{-3}$ , we inject holes such that the steady state excess hole concentration is  $3 \times 10^{16} \text{ cm}^{-3}$  at  $x = 0$ . What is the steady state separation between  $E_i$  and  $E_{Fp}$  at  $x = 500 \text{ \AA}$ ?  
[Assume that  $\mu_p = 500 \text{ cm}^2/\text{V-s}$  and  $\tau_p = 10^{-10} \text{ s}$ ,  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ ]
- (ii) Assume that an  $n$ -type semiconductor is uniformly illuminated, producing a uniform excess generation rate  $g'$ .  
Show that in steady state the change in the semiconductor conductivity is given by,  
 $\Delta\sigma = q(\mu_n + \mu_p) \tau_{p0} g'$

[12 + 8 marks]

Ans. i) Given  $p$ -type Si bar. Area  $A = 1 \text{ cm}^2$

$$p_0 = N_A = 10^{17} \text{ cm}^{-3}$$

$$\Delta p = 3 \times 10^{16} \text{ cm}^{-3} \rightarrow x = 0$$

steady state separation  $E_i - E_{Fp} = kT \ln \left( \frac{N_A}{n_i} \right)$  at  $x = 500 \text{ \AA}$

$$p(x) = p_0 + \Delta p e^{-x/L_p}$$

$$x = 500 \text{ \AA}$$

$$L_p = \sqrt{D_p \tau_p} = \sqrt{\mu_p V_T \tau_p}$$

$$L_p = \sqrt{500 \times 0.0259 \times 10^{-10}}$$

$$L_p = 3.64 \times 10^{-5} = 3.6 \times 10^{-5} \text{ cm}$$

$$= 10^{17} + 3 \times 10^{16} e^{-\frac{500 \times 10^{-8}}{3.6 \times 10^{-5}}}$$

$$= 10^{17} + 2.61 \times 10^{16}$$

$$p(500 \text{ \AA}) = 12.61 \times 10^{16} \text{ cm}^{-3}$$

$$E_i - E_{Fp} = kT \ln \left( \frac{12.61 \times 10^{16}}{1.5 \times 10^{10}} \right)$$

$$E_i - E_{Fp} = 1.6057 \text{ eV}$$

Ques. ii) n-type semiconductor

$$\text{Generation Rate} = g' = \frac{\text{excess electron}}{\text{minority carrier}} = \frac{\Delta n}{\tau_n} = \frac{\Delta p}{\tau_p}$$

$$p = p_0 + \Delta p$$

$$n = n_0 + \Delta n$$

$$\Delta p = g' \tau_{p0}$$

$$\therefore p \approx \Delta p$$

$$\Delta n = g' \tau_{n0}$$

$$n \approx \Delta n$$

at steady state  $\Rightarrow \frac{\text{excess } e^-}{e^- \text{ minority carrier}} = \frac{\text{excess hole}}{\text{hole minority carrier}}$

$$\Rightarrow \frac{\Delta n}{\tau_{n0}} = \frac{\Delta p}{\tau_{p0}}$$

As conductivity of semiconductor

$$\sigma = ne\mu_n + pe\mu_p$$

$\therefore$  change in conductivity

$$\Delta \sigma = q\mu_n(\Delta n) + q\mu_p(\Delta p)$$


$$= q\mu_n(g'\tau_{n0}) + q\mu_p(g'\tau_{p0})$$

as at steady state  $\Delta n = \Delta p$


$$\Delta \sigma = q(\mu_n + \mu_p)\tau_{p0}g' \quad \text{Ans.}$$

8

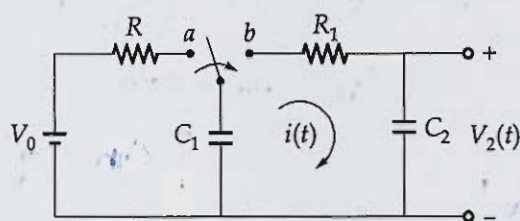- Q.8 (b) (i) The switch is moved from the position  $a$  to  $b$  at  $t = 0$ , having been in the position  $a$  for a long time before  $t = 0$ . The capacitor  $C_2$  is uncharged at  $t = 0$ . Find  $i(t)$  and  $V_2(t)$  for  $t > 0$ .




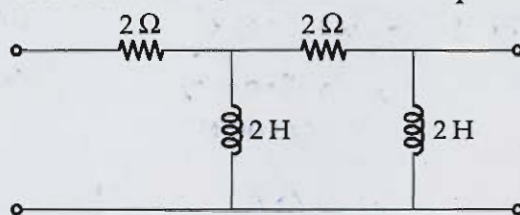- (ii) For the ladder network below, determine the  $h$  parameters in the  $s$  domain.




[10 + 10 marks]

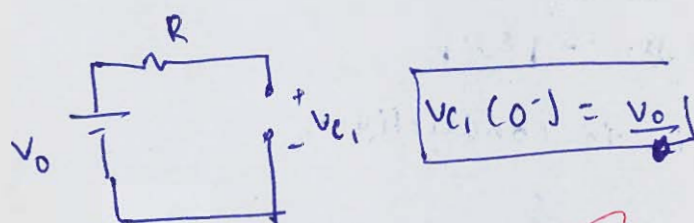Ans: i) at  $t = 0^-$  switch position (a)



at  $t = 0^+$  switch position (b)  $V_{C_1}(0^-) = V_{C_1}(0^+) = \frac{V_0}{R}$

Redraw circuit in Laplace

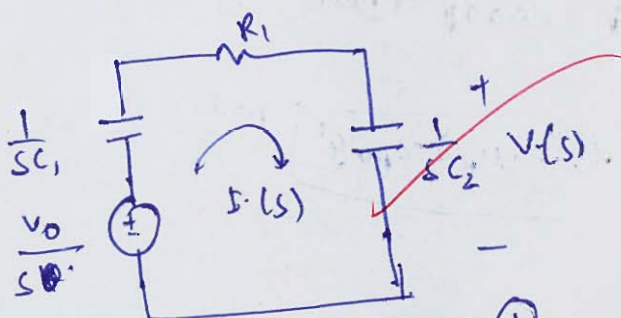

apply KVL in loop (1)

$$I(s) = \frac{\frac{V_0}{s}}{\left(R_1 + \frac{1}{sC_1} + \frac{1}{sC_2}\right)} = \frac{V_0}{s \left( sR_1C_1C_2 + C_2 + C_1 \right)}$$

$$= \frac{V_0 (C_1 C_2)}{R_1 C_1 C_2 \left[ s + \frac{(C_1 + C_2)}{R_1 C_1 C_2} \right]}$$

$$I(s) = \frac{V_0/R_1}{s + \left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right)} \Rightarrow \text{Apply Inverse Laplace transform}$$

$$i(t) = \frac{V_0}{R_1} e^{-\left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right) t} \text{ Amp}$$

Now  $V(s)$  by ohm's law

$$V(s) = I(s) \times \frac{1}{sC_2}$$

$$\Rightarrow \left[ \frac{V_0/R_1}{s + \left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right)} \right] \frac{1}{sC_2} = \frac{V_0/R_1 C_2}{s \left( s + \frac{C_1 + C_2}{R_1 C_1 C_2} \right)}$$

partial fraction


$$\frac{V_0}{R_1 C_2} = \frac{A}{s} + \frac{B}{s + \left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right)}$$

$$V(s) = \frac{V_0 C_1}{\frac{C_1 + C_2}{s}} - \frac{V_0 C_1}{\frac{C_1 + C_2}{s + \left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right)}}$$

inverse Laplace

$$v(t) = \frac{V_0 C_1}{C_1 + C_2} \left[ 1 - e^{-\left( \frac{C_1 + C_2}{R_1 C_1 C_2} \right) t} \right] u(t) \text{ Volt}$$

Ans. (ii)

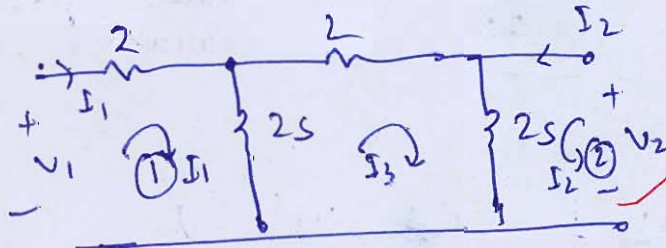

as h-parameter as

$$V_1 = h_{11} I_1 + h_{12} I_2 \quad \text{--- a}$$

$$I_2 = h_{21} I_1 + h_{22} V_2 \quad \text{--- b}$$

a.

apply KVL in  
loop-1

$$V_1 = (2 + 2s)I_1 - 2sI_3$$

$$V_1 = 2(s+1)I_1 - 2sI_3 \quad \text{--- (3)}$$

apply KVL in  
loop 2

$$(2 + 2s)I_3 + 2sI_2 - 2sI_1 = 0$$

$$I_3 = \frac{sI_1}{(2s+1)} - \frac{sI_2}{(2s+1)} \quad \text{--- (1)}$$

apply KVL  
in loop 3

$$V_2 = 2sI_2 + 2sI_3 \quad \text{--- (2)}$$

substitute equation (1) in equation (2)

$$V_2 = 2sI_2 + 2s \left[ \frac{sI_1}{(2s+1)} - \frac{sI_2}{(2s+1)} \right]$$

$$V_2 = \frac{2s(s+1)I_2 + 2s^2I_1}{(2s+1)}$$

$$I_2 = \left( \frac{-2s^2}{2s+1} \right) \frac{V_2}{2s(s+1)} + \frac{(2s+1)}{2s(s+1)} I_1$$

$$I_2 = \frac{-s}{s+1} I_1 + \frac{(2s+1)}{2s(s+1)} V_2 \quad \text{--- (c)}$$

compare equation b and c

$$h_{11} = \frac{-s}{s+1} \quad \left| \quad h_{22} = \frac{2s+1}{2s(s+1)} \right|$$

substitute equation (c) in equation (3)

$$V_1 = 2(s+1)I_1 - 2s \left[ \frac{sI_1}{(2s+1)} - \frac{sI_2}{(2s+1)} \right]$$

$$V_1 = \left( \frac{2s^2 + 6s + 1}{2s+1} \right) I_1 + \frac{2s^2}{2s+1} I_2$$

substitute  
value  $I_2$  from  
equation c

$$V_1 = \left( \frac{8s^2 + 7s + 1}{(2s+1)(s+1)} I_1 + \frac{s}{s+1} V_2 \right) \quad \text{--- d}$$

compare equation (d) & d

$$h_{11} = \frac{8s^2 + 7s + 1}{(2s+1)(s+1)} \quad \left| \quad h_{12} = \frac{s}{s+1} \right|$$

- c) (i) Assume the base transit time of a BJT is 100 ps and carriers cross the  $1.2 \mu\text{m}$  base-collector space charge region at a speed of  $10^7 \text{ cm/s}$ . The emitter-base junction charging time is 25 ps and the collector capacitance and resistance are 0.1 pF and  $10 \Omega$  respectively. Determine the cut-off frequency of the BJT.
- (ii) An npn silicon transistor is biased in the inverse active mode with  $V_{BE} = -3 \text{ V}$  and  $V_{BC} = 0.6 \text{ V}$ . The doping concentrations are  $N_E = 10^{18} \text{ cm}^{-3}$ ;  $N_B = 10^{17} \text{ cm}^{-3}$ , and  $N_C = 10^{16} \text{ cm}^{-3}$ . Other parameters are  $x_B = 1 \mu\text{m}$ ,  $\tau_{E0} = \tau_{B0} = \tau_{C0} = 2 \times 10^{-7} \text{ s}$ ,  $D_E = 10 \text{ cm}^2/\text{s}$ ,  $D_B = 20 \text{ cm}^2/\text{s}$ ,  $D_C = 15 \text{ cm}^2/\text{s}$  and area  $A = 10^{-3} \text{ cm}^2$ . Calculate the collector and emitter currents (Neglect geometry factors and assume the recombination factor is unity) (Assume,  $n_i = 1.5 \times 10^{10} \text{ cm}^{-3}$ ,  $V_t = 0.0259 \text{ V}$ ,  $\tau$  = carrier life time and  $D$  = diffusion coefficient.)

[10 + 10 marks]





**Space for Rough Work**

---

**Space for Rough Work**

---

## Space for Rough Work

---

## Space for Rough Work

---

## Space for Rough Work

---

