

NAME —


Roll No —

TEST NO — 1

SUBJECT NAME — Digital Electronics + Control Systems

Ans 1 @

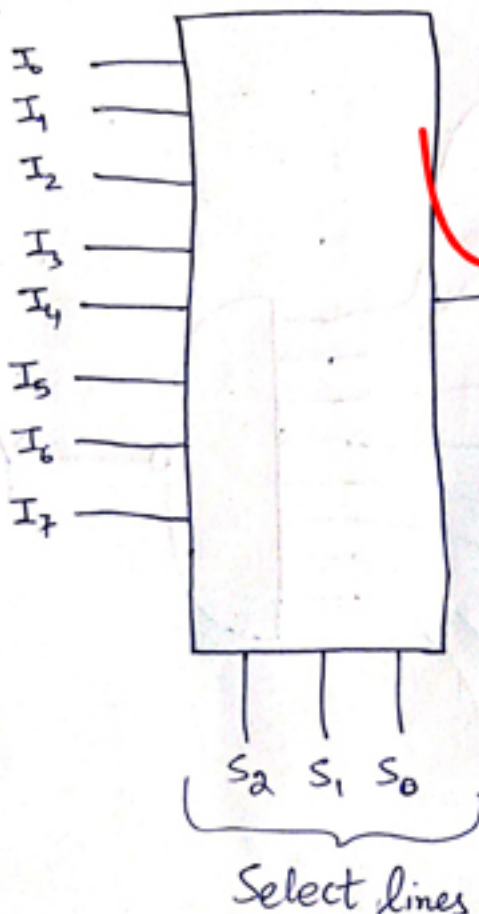Design the 8x1 multiplexer using NAND gates only.




$$Y = \bar{S}_2 \bar{S}_1 \bar{S}_0 I_0 + \bar{S}_2 \bar{S}_1 S_0 I_1 + \bar{S}_2 S_1 \bar{S}_0 I_2 + \bar{S}_2 S_1 S_0 I_3 + S_2 \bar{S}_1 \bar{S}_0 I_4 + S_2 \bar{S}_1 S_0 I_5 + S_2 S_1 \bar{S}_0 I_6 + S_2 S_1 S_0 I_7$$

$$\overline{Y} = \overline{S_2 S_1 S_0 I_0} + \overline{S_2 S_1 S_0 I_1} + \overline{S_2 S_1 S_0 I_2} + \overline{S_2 S_1 S_0 I_3} + \overline{S_2 S_1 S_0 I_4} + \overline{S_2 S_1 S_0 I_5} + \overline{S_2 S_1 S_0 I_6} + \overline{S_2 S_1 S_0 I_7}$$

Applying De-morgan's law

$$Y = \left(\overline{S_2 S_1 S_0 I_0} \cdot \overline{S_2 S_1 S_0 I_1} \cdot \overline{S_2 S_1 S_0 I_2} \cdot \overline{S_2 S_1 S_0 I_3} \cdot \overline{S_2 S_1 S_0 I_4} \cdot \overline{S_2 S_1 S_0 I_5} \cdot \overline{S_2 S_1 S_0 I_6} \cdot \overline{S_2 S_1 S_0 I_7} \right)'$$

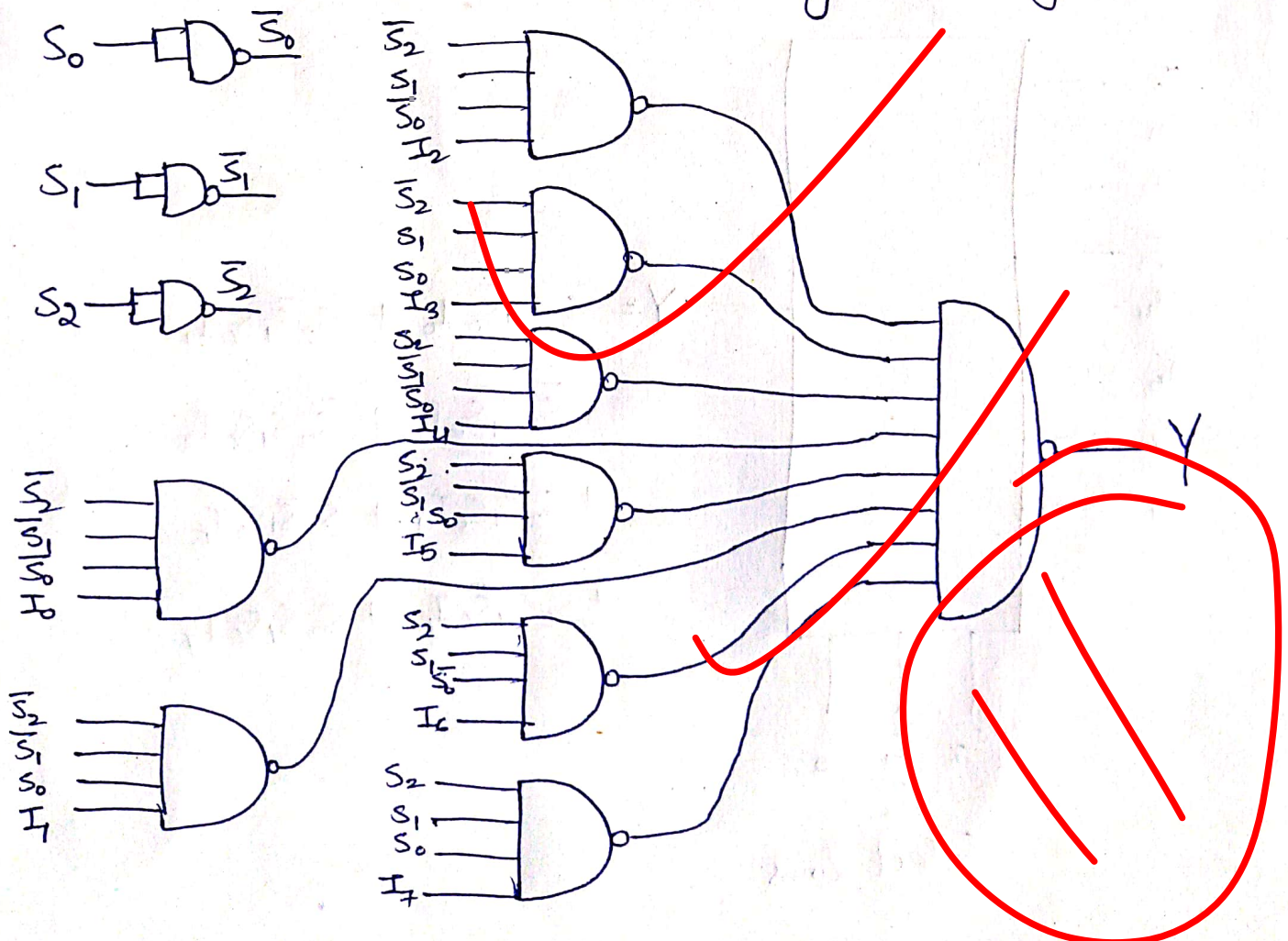Implementing the Output Y using NAND gates.



Ans 1 b) For a 8-bit counter type analog to digital converter using a 2 MHz clock.

Determine:

i) Maximum conversion rate

As frequency given = $2 \times 10^6 \text{ Hz}$

$$\text{Time period } T = \frac{1}{2 \times 10^6} = 0.5 \mu\text{sec.}$$

$$\text{Max}^m \text{ conversion rate} = \frac{1}{T} = \frac{1}{0.5} = 2 \times 10^6 \text{ persec}$$

ii) Maximum conversion time = $(2^n - 1)T$

$$= (2^8 - 1)0.5 \mu\text{sec}$$

$$= 127.5 \mu\text{sec}$$

iii) Average conversion time = ~~Minimum~~

$$\text{Avg. conversion time} = \frac{\text{Min}^m \text{ con. time} + \text{Max}^m \text{ con. time}}{2}$$

$$= \frac{T + (2^n - 1)T}{2}$$

$$= \frac{(0.5 + 127.5) \mu\text{sec}}{2}$$

$$= 64 \mu\text{sec}$$

Ans 1 c) Convert a D-flip flop to function as a SR flip-flop
Draw circuit.

→


Characteristic table of SR			Excitation table of D flip flop		
S	R	Q_{n+1}	Q_n	Q_{n+1}	D
0	0	Q_n	0	0	0
0	1	0	0	1	0
1	0	1	1	0	1
1	1	X	1	1	1

Now to convert D flip flop to SR flip flop—

S	R	Q_n	Q_{n+1}	D
0	0	0	0	0
0	0	1	1	1
0	1	0	0	0
0	1	1	0	0
1	0	0	1	1
1	0	1	1	1
1	1	0	X	X
1	1	1	X	X

S	RQ_n			
	00	01	10	11
\bar{S}	0	1	0	0
S	1	1	X	X

$$D = S + R\bar{Q}_n$$

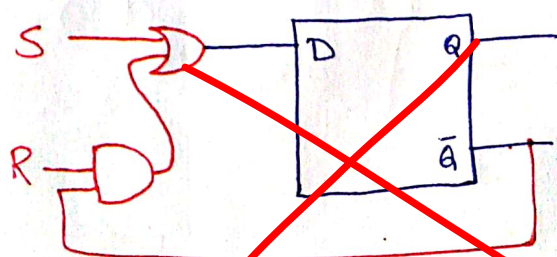

Ans 1 d) Reduce the expression $f(A,B,C,D) = \Pi M(2,8,9,10,11,12,14)$ and implement the same using NOR gates.


Q →

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	CD	$C\bar{D}$
$\bar{A}\bar{B}$	1	1	1	
$\bar{A}B$	1	1	1	1
AB		1	1	
$A\bar{B}$				

$$\Pi(M)(2,8,9,10,11,12,14)$$

$$= \sum m(0,1,3,4,5,6,7,13,15)$$
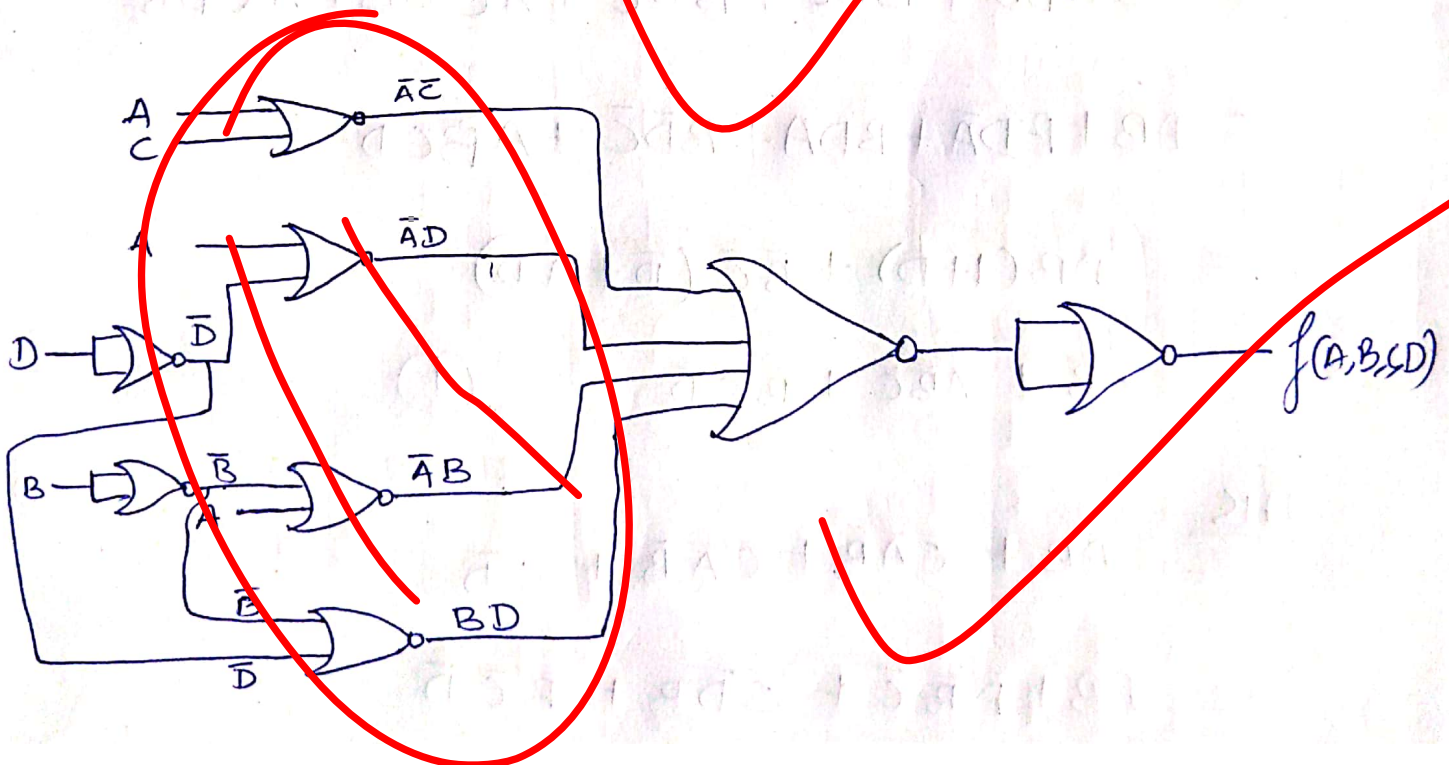
$$f(A,B,C,D) = \bar{A}\bar{C} + \bar{A}D + \bar{A}B + BD = \bar{A}(B+C+D) + BD$$



Ans 1 e) If $\bar{A}B + C\bar{D} = 0$, then prove that

$$AB + \bar{C}(\bar{A} + \bar{D}) = AB + BD + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$

$$\bar{A}B + C\bar{D} = 0 \quad \text{means} \quad \bar{A}B = 0$$

$$C\bar{D} = 0$$

taking LHS

$$AB + \bar{C}\bar{A} + \bar{C}\bar{D}$$

RHS

$$AB + BD + \bar{B}\bar{D} + \bar{A}\bar{C}\bar{D}$$

$$= AB + BD + \bar{B}\bar{D}C + \bar{B}\bar{D}\bar{C} + \bar{A}\bar{C}\bar{D}B + \bar{A}\bar{C}\bar{D}\bar{B}$$

$$= AB + B\bar{D}\bar{A} + B\bar{D}A + \bar{B}\bar{D}\bar{C} + \bar{A}\bar{B}\bar{C}\bar{D}$$

$$= AB(1 + \bar{D}) + \bar{B}\bar{C}(\bar{D} + \bar{A}\bar{D})$$

$$= AB + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}\bar{D} \quad \text{--- (1)}$$

$$\text{LHS} = AB + \bar{C}\bar{A}B + \bar{C}\bar{A}\bar{B} + \bar{C}\bar{D}$$

$$= AB + \bar{A}\bar{B}\bar{C} + \bar{C}\bar{D}B + \bar{B}\bar{C}\bar{D}$$

$$= AB + \bar{A}\bar{B}\bar{C} + \bar{B}\bar{C}\bar{D} \quad \text{--- (2)}$$

eqⁿ (1) = (2) Hence proved.

Ans 4 a) What is Gray code? Give applications of Gray code?

→ It is a binary code. It is a way of generating binary numbers such that every step has a change of single bit only. i.e. Hamming distance of this code is 1.

Applications

- Karnaugh Map
- Rotary encoders

(As there is only one digit change from one step to next step. It's easy to find the next location).

Ans 4 b) Obtain minimal SOP expression for outputs of combinational circuit that produce the 2's complement of a 4 bit binary number?

Let the 4 bit binary nos are ABCD.


and the corresponding 2's complement = PQRS

So

A	B	C	D	P	Q	R	S
0	0	0	0	0	0	0	0
0	0	0	1	1	1	1	1
0	0	1	0	1	1	1	0
0	0	1	1	1	1	0	1
0	1	0	0	1	1	0	0
0	1	0	1	1	0	0	1
0	1	1	0	1	0	1	0
0	1	1	1	1	0	1	1
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	0	1	1	1
1	0	1	1	0	1	0	0
1	1	0	0	0	1	0	1
1	1	0	1	0	0	1	1
1	1	1	0	0	0	1	0
1	1	1	1	0	0	0	1

Now we find the expression for P, Q, R, S using K-map.


(For P)

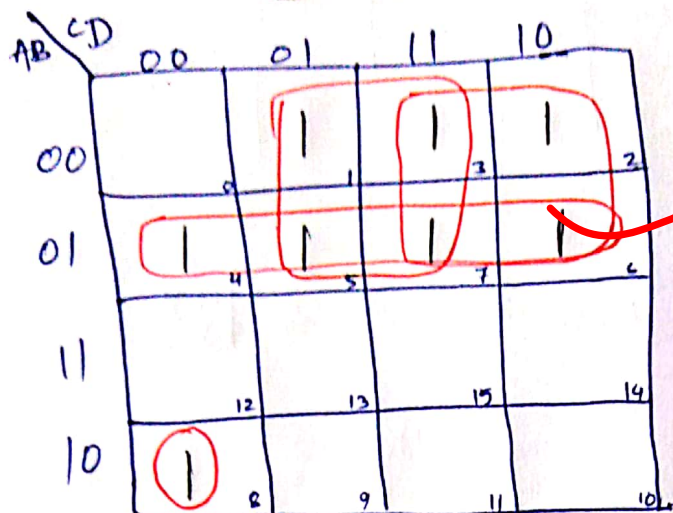

$$P = \bar{A}B + \bar{A}D + \bar{A}C + A\bar{B}\bar{C}\bar{D}$$

$$P = \bar{A}(B+C+D) + A\bar{B}\bar{C}\bar{D}$$


(For Q)

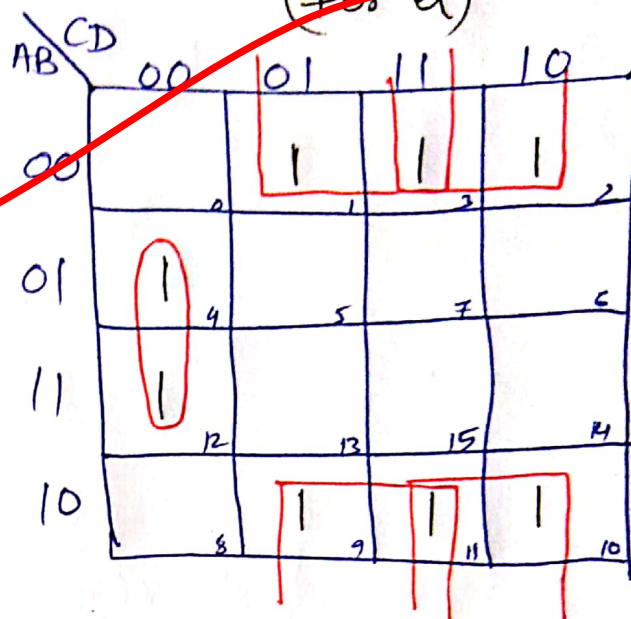

$$Q = \bar{B}C + \bar{B}D + B\bar{C}\bar{D}$$


$$Q = \bar{B}(C+D) + B(\bar{C}\bar{D})$$

(For R)

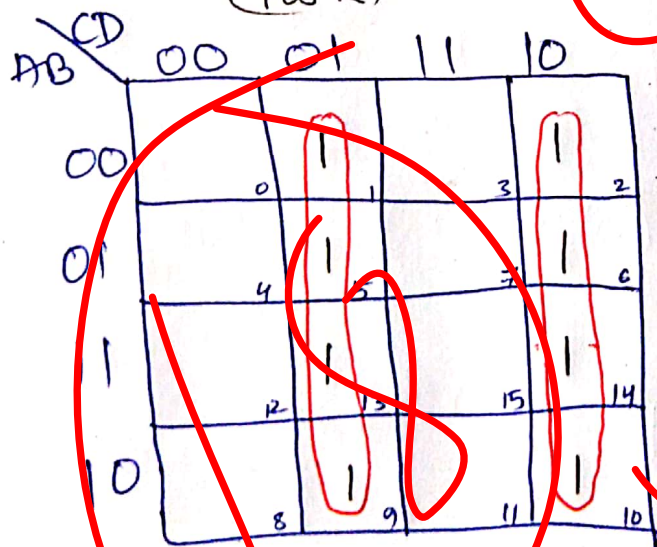

$$R = \bar{C}D + C\bar{D} = C \oplus D$$



(For S)

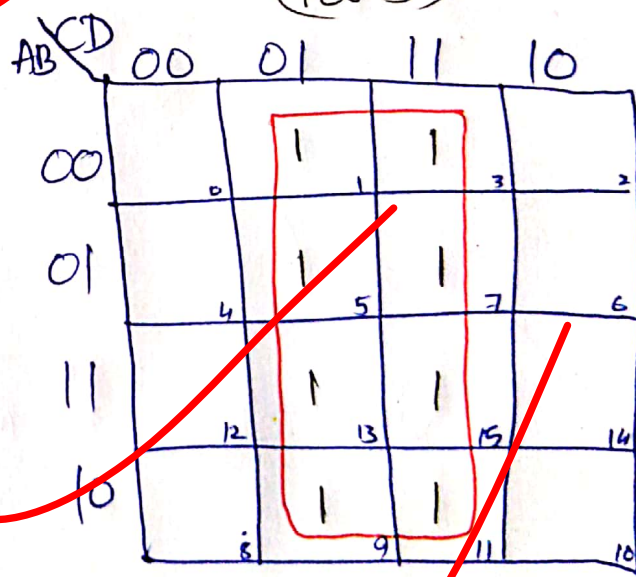

$$S = D$$

Ans 4 c)

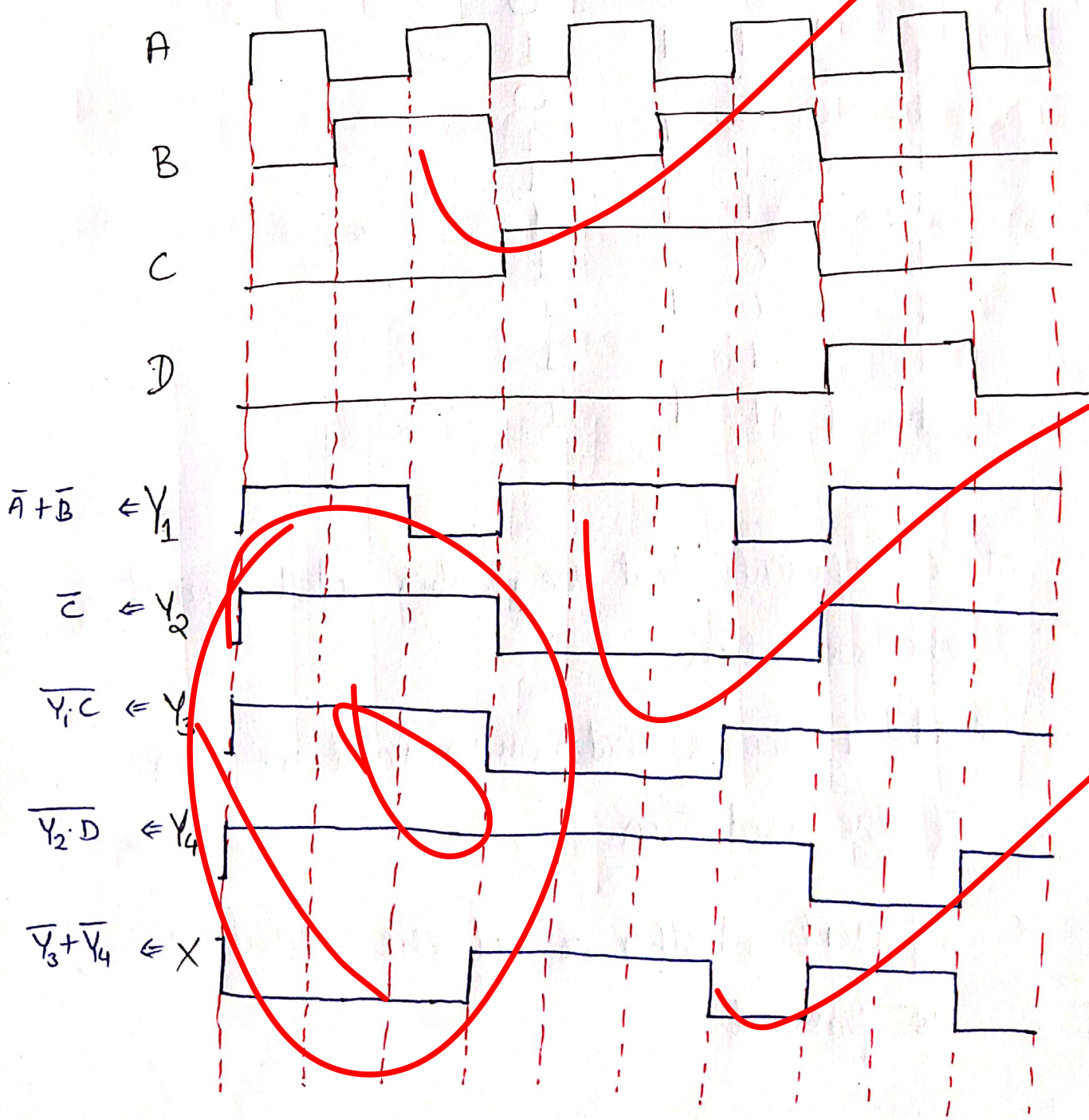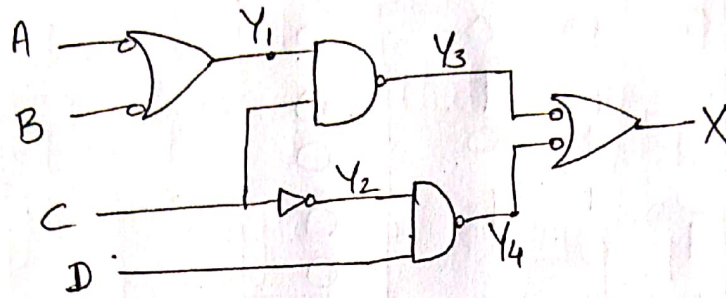Consider the logic circuit shown below. Waveforms of A, B, C, D are shown below.



Ans 4 d) The possible no. of cases are given in Truth table form.

P (30)	Q (25)	R (23)	S (22)	X
0	0	0	0	0
0	0	0	1	0
0	0	1	0	0
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	1
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	1
1	1	0	1	1
1	1	1	0	1
1	1	1	1	1

Let '0' represents that the member voted against the resolution.

and '1' denotes that member voted in favor of the resolution.


X represent wheather or not the resolution is passed.

when sum of the votes are greater than ^{or equal to} 50%
in favor of resolution then we take $X=1$.

PQ \ RS	$\bar{R}\bar{S}$	$\bar{R}S$	RS	$R\bar{S}$
$\bar{P}\bar{Q}$	0	1	3	2
$\bar{P}Q$	4	5	1	7
$P\bar{Q}$	1	1	1	1
PQ	1	1	1	1


$$X = PQ + PS + PR + QRS$$

$$X = P(Q+R+S) + QRS$$

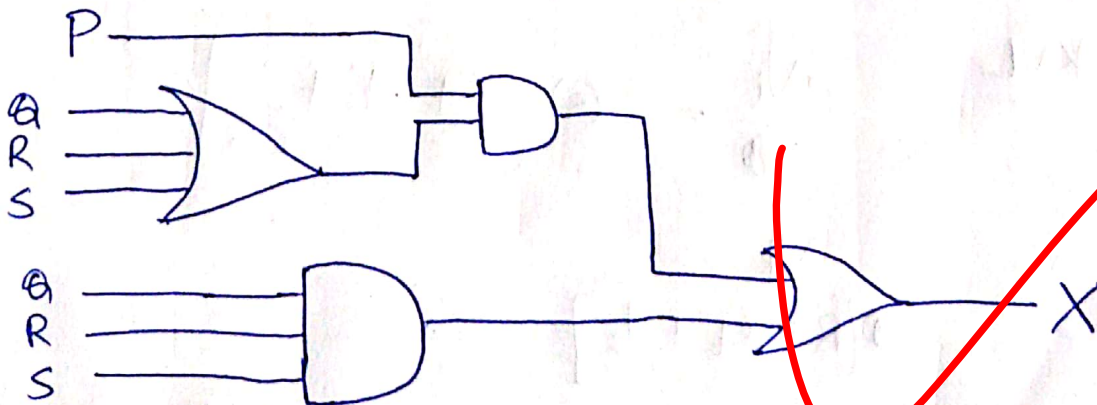


Ans 5 a)

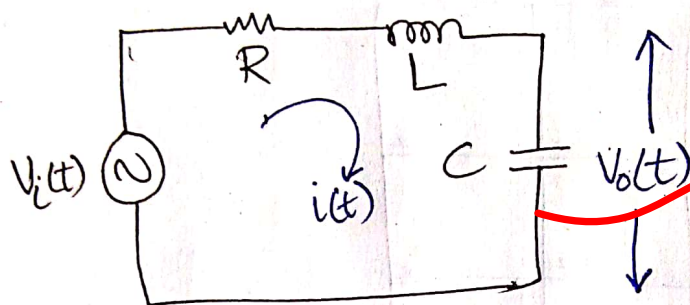If $V_i(t)$ is a step voltage in the network shown in figure, find the value of resistor such that a 20% overshoot in voltage will be seen across the capacitor if $C = 10^{-6} \text{ F}$ and $L = 0.5 \text{ H}$.



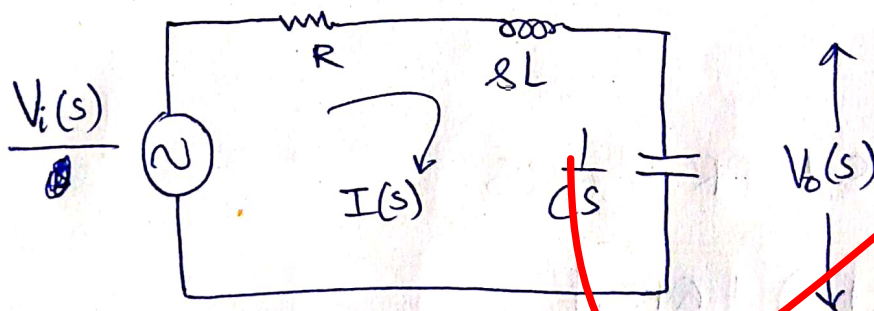Applying Laplace to circuit and redrawing—



By KVL.

$$\frac{V_i}{\text{circle}} = I(s) \left[R + sL + \frac{1}{Cs} \right]$$

$$I(s) = \frac{V_i}{\text{circle} \left[R + sL + \frac{1}{Cs} \right]}$$

$$\text{Also, } V_o(s) = I(s) \cdot \frac{1}{Cs} = \frac{1}{\text{circle} C} \left[\frac{V_i}{sR + s^2 L + \frac{1}{C}} \right]$$

$$V_o(s) = \frac{V_i(s)}{s^2 LC + sRC + 1}$$

$$\text{Transfer function} = \frac{V_o}{V_i} = \frac{1/LC}{s^2 + s\frac{R}{L} + \frac{1}{LC}}$$

Comparing with $s^2 + 2\xi\omega_n s + \omega_n^2$

$$\frac{R}{L} = 2\xi\omega_n$$

$$\omega_n^2 = \frac{1}{LC} = \frac{1}{0.5 \times 10^{-6}}$$

$$\omega_n = \sqrt{2 \times 10^6} = 1.414 \text{ Krad/s}$$

given: $M_p = 20\%$

$$M_p = e^{-\frac{\xi\pi}{\sqrt{1-\xi^2}}}$$

$$0.2 = e^{-\pi/\tan\theta}$$

$$\ln(0.2) = -\pi/\tan\theta$$

$$\tan\theta = 1.952$$

$$\theta = 62.874^\circ$$

$$\cos\theta = \xi = 0.456$$

$$2\xi\omega_n = \frac{R}{L}$$


$$R = L \cdot 2\xi\omega_n$$

$$R = 0.5 \times 2 \times 0.456 \times 1.414 \times 10^3$$

$$R = 644.81 \text{ } \Omega$$

Ans 5. b)

Determine the Transfer Function.

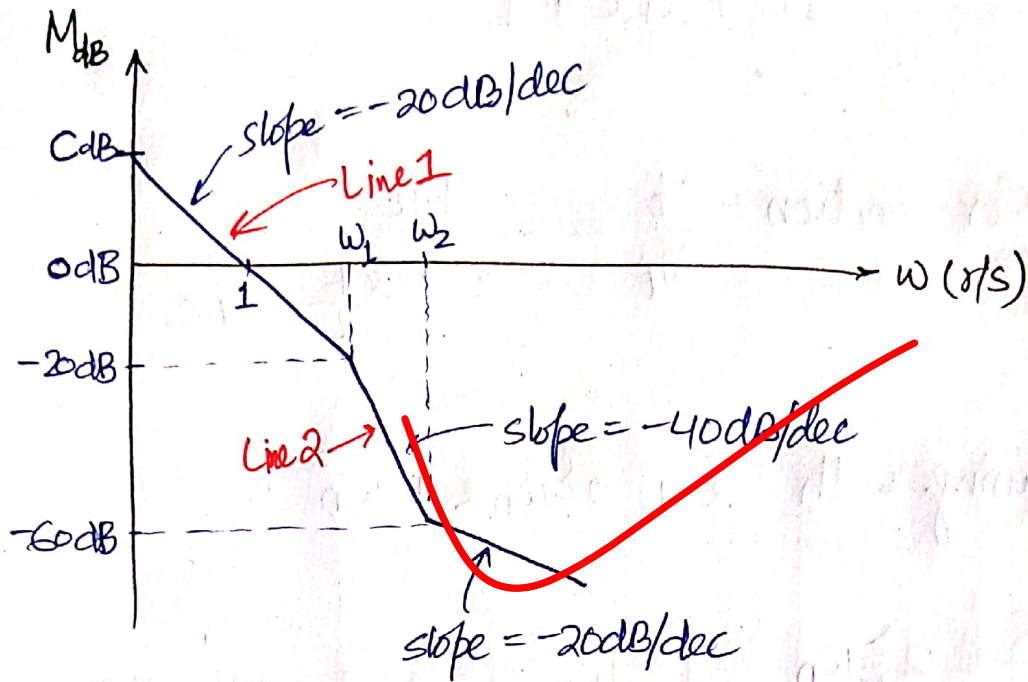

From the Bode plot it is clear that we have a pole at origin, then another pole at $\omega=\omega_1$ and a zero at $\omega=\omega_2$.

So the transfer function would be -

$$T(s) = \frac{K (1 + s/\omega_2)}{s (1 + s/\omega_1)}$$

$$T(j\omega) = \frac{K (1 + j\omega/\omega_2)}{j\omega (1 + j\omega/\omega_1)}$$

$$\text{Slope of line 2} = \frac{-20 - (-60)}{\log \omega_1 - \log \omega_2} = -40 \text{ dB/dec}$$

$$\frac{40}{\log \omega_2 - \log \omega_1} = 40$$

$$\log \omega_2 = \log \omega_1 + 1$$

$$\log \omega_2 = \log \omega_1 + \log 10$$

$$\omega_2 = 10\omega_1 \quad \text{--- ①}$$

$$\text{Slope of Line 1} = \frac{-20}{\log \omega_1 - \log 1} = -20$$

$$\log \omega_1 = \log 1 + 1$$

$$\omega_1 = 10 \text{ rad/s}$$

from eqⁿ ①

$$\omega_2 = 100 \text{ rad/s}$$

Eqⁿ of line 1 can be written as

$$-20 = -20 \log \omega_1 + C$$

$$C = 0$$


$$C = 20 \log K$$

$$K = 1$$

$$\text{Transfer Function } \Rightarrow T(s) = \frac{(1 + \frac{s}{100})}{s(1 + \frac{s}{10})}$$

Ans 5 c)

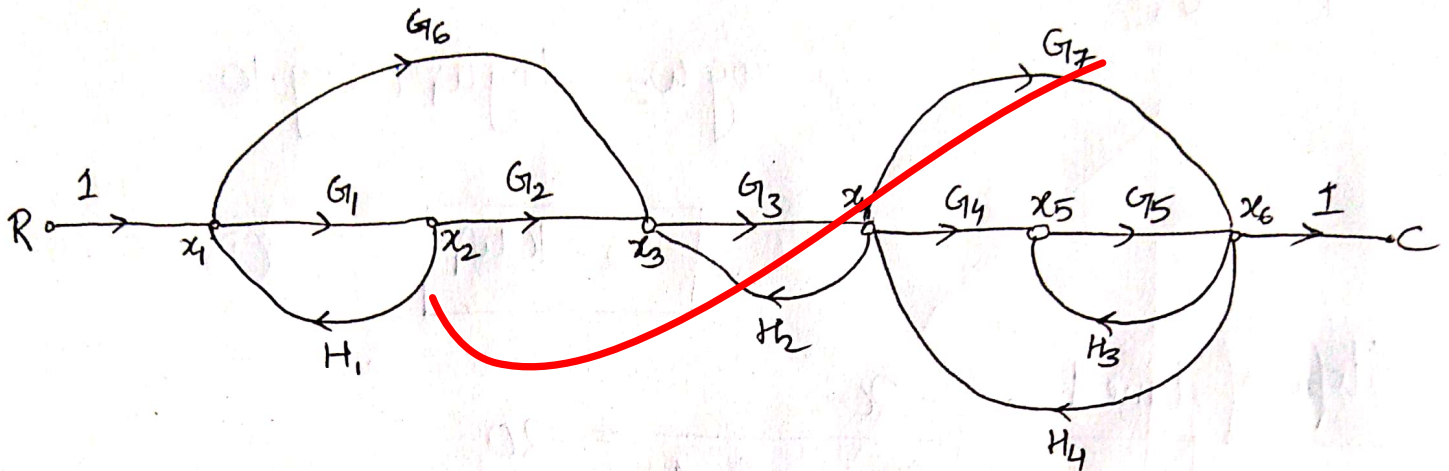By Mason's gain formula, Determine $\frac{C}{R}$



Mason's Gain Formula : $\frac{C}{R} = \frac{\sum_{i=1}^n P_i \Delta_i}{\Delta}$

P_i = Forward path

Δ_i = Δ corresponding to P_i

$$\Delta = 1 - \left(\text{Sum of total loops} \right) + \left(\text{Sum of Two non-touching loops} \right) - \left(\text{Sum of Three non-touching loops} \right) + \dots$$

Total loops :

$$L_1 = G_1 H_1$$

$$L_2 = G_3 H_2$$

$$L_3 = G_5 H_3$$

$$L_4 = G_4 G_5 H_4$$

$$L_5 = G_7 H_4$$

Forward paths: $P_1 = G_1 G_2 G_3 G_4 G_5$

$\Delta_1 = 1$ - loops not touching P_1

$$\Delta_1 = 1$$

$$P_2 = G_6 G_3 G_4 G_5 \quad \Delta_2 = 1$$

$$P_3 = G_1 G_2 G_3 G_7 \quad \Delta_3 = 1$$

$$P_4 = G_6 G_3 G_7 \quad \Delta_4 = 1$$

Two Non-touching loops: $L_1 L_3 = G_1 H_1 G_5 H_3$

$$L_1 L_4 = G_1 H_1 G_4 G_5 H_4$$

$$L_1 L_2 = G_1 H_1 G_3 H_2$$

$$L_1 L_5 = G_1 H_1 G_7 H_4$$

$$L_2 L_3 = G_3 H_2 G_5 H_3$$

Three non-touching loops:

$$L_1 L_2 L_3 = G_1 H_1 G_3 H_2 G_5 H_3$$

Now the transfer function $\frac{C}{R}$ using Mason's Gain formula is —

$$\frac{C}{R} = \frac{P_1 + P_2 + P_3 + P_4}{1 - L_1 - L_2 - L_3 - L_4 - L_5 + L_1 L_2 + L_2 L_3 + L_1 L_4 + L_1 L_5 - L_1 L_2 L_3}$$

$$\frac{C}{R} = \frac{G_1 G_2 G_3 G_4 G_5 + G_3 G_4 G_5 G_6 + G_1 G_2 G_3 G_7 + G_3 G_6 G_7}{1 - G_1 H_1 - G_3 H_2 - G_5 H_3 - G_4 G_5 H_4 - G_7 H_4 + G_1 H_4 [G_3 H_2 + G_5 H_3 + G_4 G_5 H_4 + G_7 H_4] - G_1 H_4 G_3 H_2 G_5 H_3}$$

Ans 5 d)

Given: 2% tolerance

~~Settling time~~

$$R(s) = \frac{1}{s} \longrightarrow \boxed{\frac{15}{s+15}} \longrightarrow C(s)$$

$$C(s) = \frac{15}{s^2 + 15s} = \frac{A}{s} + \frac{B}{s+15}$$

Using partial fraction $A=1, B=-1$

$$C(s) = \frac{1}{s} - \frac{1}{s+15}$$

Taking Laplace inverse

$$C(t) = u(t) [1 - e^{-15t}]$$

so,

$$\text{Time Constant} = \frac{1}{15} \text{ sec}$$

$$\text{Rise time} \Rightarrow 1 - e^{-15t} = 0.9$$

$$e^{-15t} = 0.1$$

$$-15t = \ln(0.1)$$

$$\text{Rise time} = \boxed{t_r = 0.1535 \text{ sec}}$$

$$\text{Settling time} \Rightarrow 1 - e^{-15t} = 0.98$$

$$-15t = \ln(0.02)$$

$$\boxed{t_s = 0.26 \text{ sec}}$$

Ans 5 e)


$$\left. \frac{C(s)}{R(s)} \right|_{D(s)=0}$$

and

$$\left. \frac{C(s)}{D(s)} \right|_{R(s)=0}$$


Considering $D(s)=0$

Signal flow graph

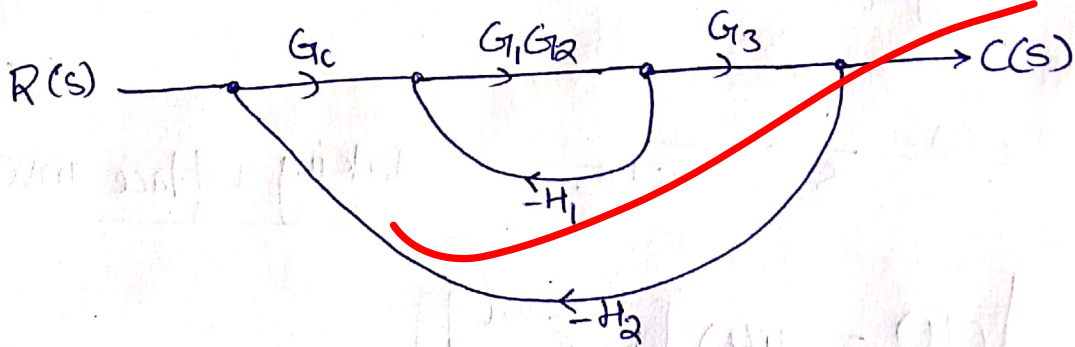

$$\left. \frac{C(s)}{R(s)} \right|_{D(s)=0} = \frac{G_c G_1 G_2 G_3}{1 + G_1 G_2 H_1 + G_c G_1 G_2 G_3 H_2}$$

Now taking $R(s)=0$

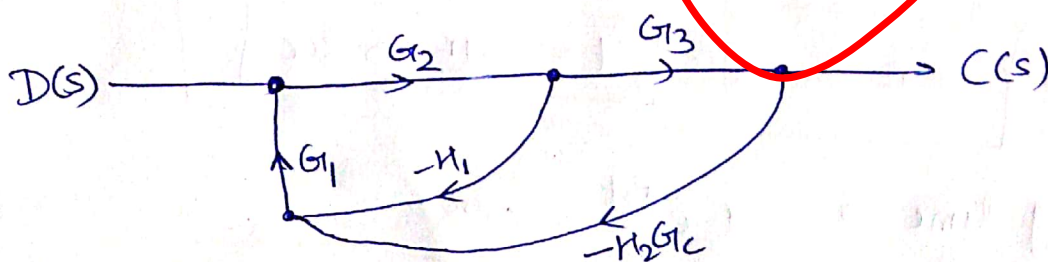

$$\left. \frac{C(s)}{D(s)} \right|_{R(s)=0} = \frac{G_2 G_3}{1 + G_1 G_2 H_1 + G_1 G_2 G_3 G_c H_2}$$

Here Transfer functions are calculated by using Mason's Gain formula.

$$\frac{C}{R} = \frac{\sum_{k=1}^n P_k \Delta_k}{\Delta}$$

P_k = Forward path Gain

Δ_k = Δ corresponding to P_k

$$\Delta = 1 - \left(\text{Sum of total loops} \right) + \left(\text{Sum of two non-touching loops} \right) - \left(\text{Sum of three non-touching loops} \right) + \dots$$

Ans 6 a)

$$T(s) = \frac{73.626}{(s+3)(s^2+4s+24.542)}$$

Unit step response C(s)

$$C(s) = \frac{73.626}{s(s+3)(s^2+4s+24.542)}$$

$$C(s) = \frac{A}{s} + \frac{B}{s+3} + \frac{Cs+D}{(s+2)^2+20.542}$$

Using partial fraction, & solving

$$A=1 \quad B=-1.14 \quad C=0.14 \quad D=-2.856$$

$$C(s) = \frac{1}{s} - \frac{1.14}{s+3} + \frac{0.14s - 2.856}{(s+2)^2 + 20.542}$$

$$= \frac{1}{s} - \frac{1.14}{s+3} + 0.14 \left[\frac{s-20.4}{(s+2)^2 + 20.542} \right]$$


$$C(s) = \frac{1}{s} - \frac{1.14}{s+3} + 0.14 \left[\frac{s+2}{(s+2)^2 + 20.542} - (4.94) \frac{4.532}{(s+2)^2 + 20.542} \right]$$

Taking Laplace inverse of the $C(s)$.

$$C(t) = u(t) \left[1 - 1.14e^{-3t} + 0.14 \left(e^{-2t} \cos(4.53t) - 4.94e^{-2t} \sin(4.53t) \right) \right]$$

$$C(t) = \left[1 - 1.14e^{-3t} + e^{-2t} (0.14 \cos(4.53t) - 0.692 \sin(4.53t)) \right]$$

Ans 6 b)

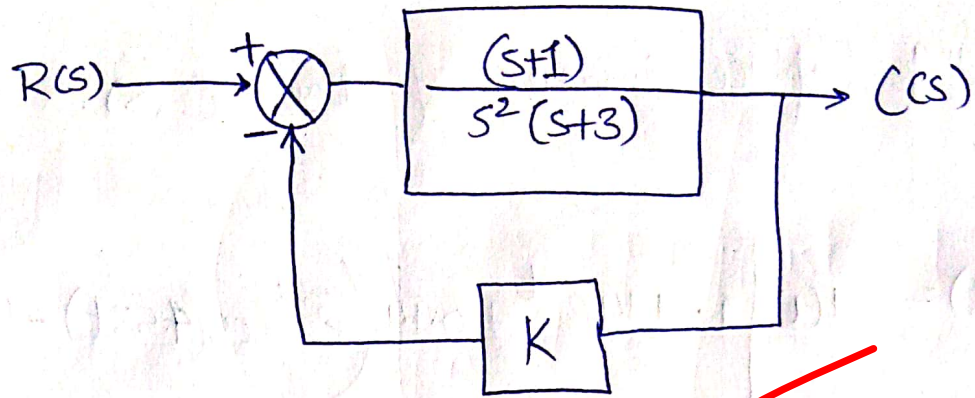

To find the type of the system, we need to convert it into a ~~unity~~ unity feedback system.

$$G(s) = \frac{s+1}{s^2(s+3)} \quad H(s) = K$$

$$\text{Open Loop TF} = \frac{G(s)}{1+GH - G(s)}$$

$$= \frac{s+1/s^2(s+3)}{1 + \frac{K(s+1)}{s^2(s+3)} - \frac{s+1}{s^2(s+3)}}$$

$$= \frac{s+1}{s^2(s+3) + K(s+1) - (s+1)}$$

$$G'(s) = \frac{s+1}{s^2(s+3) + (s+1)(K-1)}$$

i) From $G(s)$ Type of System = 0

ii) For $e_{ss} = 0.001$ when $R(s) = \frac{1}{s}$ $K = ?$

$$e_{ss} = \lim_{s \rightarrow 0} \frac{s R(s)}{1 + G(s)H(s)} \quad [H(s) = 1]$$

$$= \lim_{s \rightarrow 0} \frac{s \cdot \frac{1}{s}}{1 + \frac{s+1}{s^2(s+3) + (s+1)(K-1)}}$$

$$= \lim_{s \rightarrow 0} \frac{1}{1 + \frac{1}{K-1}}$$

$$e_{ss} = \frac{K-1}{K} = 0.001$$

$$0.001K = K-1$$

$$0.999K = 1$$

$$K = \frac{1.001}{0.999} = \frac{1000}{999}$$

Ans 6 c)

A/c to Nyquist criteria, $N = P - Z$

N = no. of encirclements by Nyquist plot of ~~open~~ $(-1, 0)$ point.

P = RHS poles of open loop Transfer func.

Z = RHS zeros of characteristic eqn


$$|G(j\omega)| = \frac{K}{\omega \sqrt{\omega^2 + 9} \cdot \sqrt{\omega^2 + 25}}$$

$$\angle G(j\omega) = -90^\circ - \tan^{-1}(\omega/3) - \tan^{-1}(\omega/5)$$

ω	0	1	3.875	10	∞
$ G(j\omega) $	∞	0.062	0.0083K	0.00085K	0
$\angle G(j\omega)$	-90°	-120°	-180°	-226.7°	$+90^\circ$

$P = 0$ For stability $Z = 0$

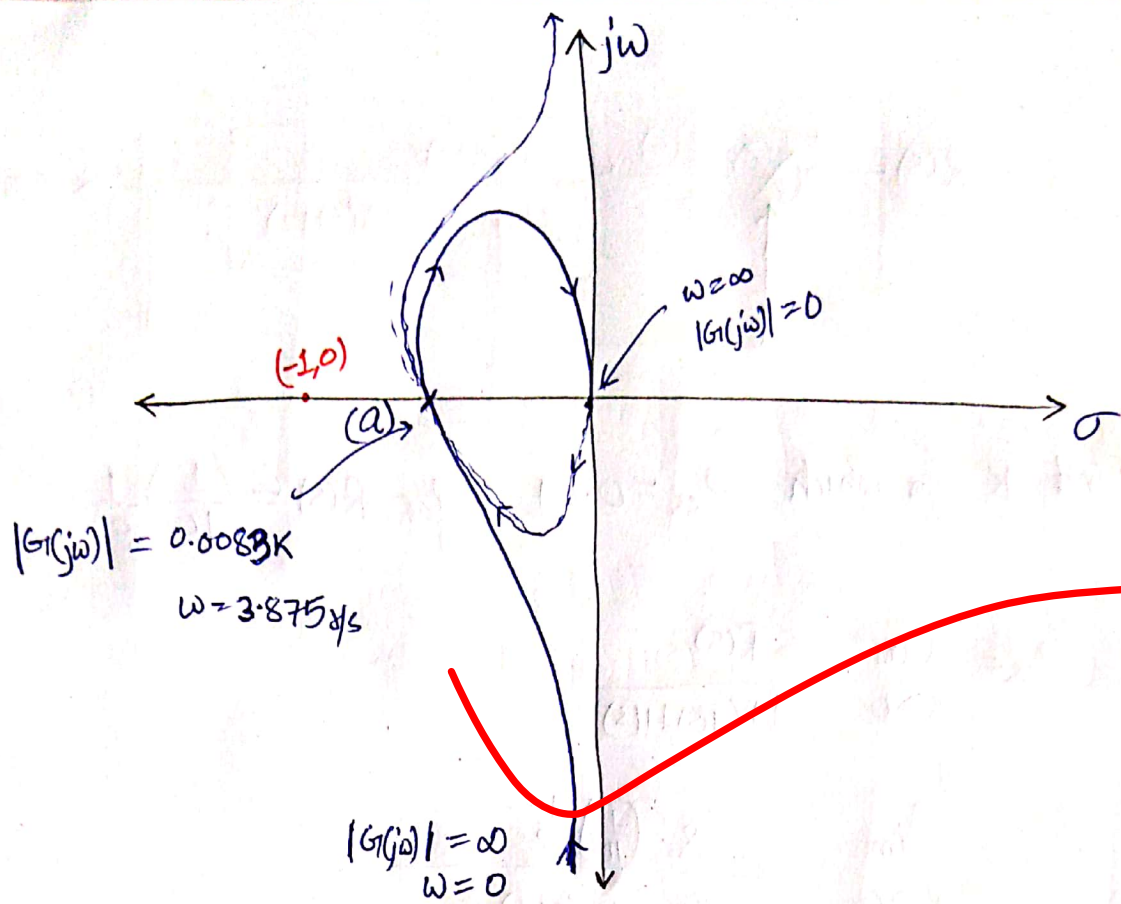means $N = 0$ there should be no encirclements of $(-1, 0)$ pt.



For stability pt (a) should be on ~~left~~ ^{Right} side of point $(-1,0)$ on real axis

means

$$0.0083K < 1$$

$$K < \frac{1}{0.0083} = 120.482$$

Also $K > 0$

Range of K


$$= 0 < K < 120.482$$

$$K_{\text{marginal}} = 120.482$$

$$\omega_{\text{oscillation}} = 3.875 \text{ rad/sec}$$

[from table]

Ans 7 a)

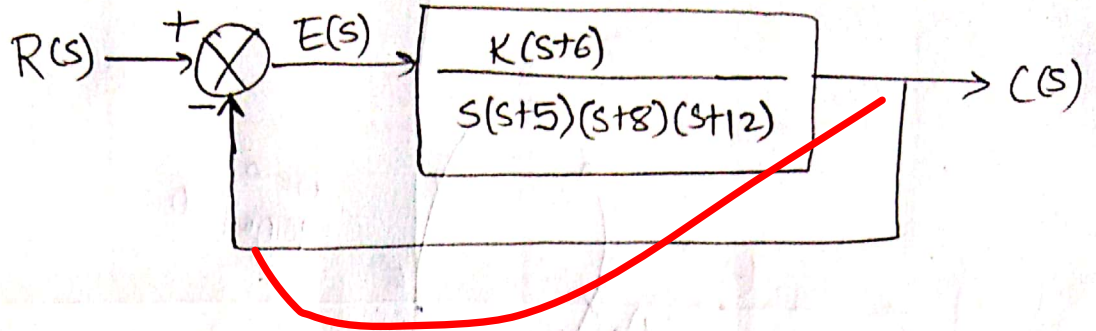

i> Find K for which $e_{ss} = 0.01$ for $R(s) = \left(\frac{1}{10}\right) \frac{1}{s^2}$

$$e_{ss} = \lim_{s \rightarrow 0} \frac{s R(s)}{1 + G(s)H(s)}$$

$$= \lim_{s \rightarrow 0} \frac{s \cdot \left(\frac{1}{10}\right) \frac{1}{s^2}}{1 + \frac{K(s+6)}{s(s+5)(s+8)(s+12)}}$$

$$= \lim_{s \rightarrow 0} \frac{\left(\frac{1}{10}\right)}{s + \frac{K(s+6)}{(s+5)(s+8)(s+12)}}$$

$$e_{ss} = \frac{\left(\frac{1}{10}\right)}{0 + \frac{K \cdot 6}{5 \times 8 \times 12}} = \frac{8}{K} = 0.01$$

$$K = \frac{8}{0.01} = 800$$

Ans 7 a) ii)

$$e_{ss} = \frac{8}{K}$$

e_{ss} will be minimum
for maximum value of K .

To find maximum possible value of K we use
Routh Hurwitz criteria.

$$\begin{aligned}\text{Characteristic eq}^n &= s(s+5)(s+8)(s+12) + K(s+6) \\ &= s^4 + 25s^3 + 196s^2 + (480+K)s + 6K\end{aligned}$$

s^4	1	196	6K
s^3	25	(480+K)	0
s^2	$\frac{196 \times 25 - (480+K)}{25}$	6K	
s^1	$\frac{\left(\frac{4420-K}{25}\right) \times (480+K) - 150K}{\left(\frac{4420-K}{25}\right)}$	0	
s^0	6K		

$$6K > 0 \Rightarrow \boxed{K > 0} \text{ --- Condition ①}$$

$$4420 - K > 0 \Rightarrow \boxed{K < 4420} \text{ --- Condition ②}$$

$$\left(\frac{4420 - K}{25} \right) \cdot (480 + K) > 150K$$

$$2121600 + 4420K - 480K - K^2 > 3750K$$

$$-K^2 + 190K + 212160 > 0$$

$$-375.3 < K < 565.3$$

$$\boxed{K < 565.3} \text{ --- Condition ③}$$

from combining condition ①, ② and ③

$$\boxed{0 < K < 565.3}$$

$$\underline{K_{\max} = 565.3}$$

So,

$$l_{ss(\text{minimum})} = \frac{8}{565.3} = 0.01415$$

Ans 7 b)

Bandwidth is that frequency at which Magnitude becomes $\frac{1}{\sqrt{2}}$ of its ~~peak~~ _{DC} value.

$$\text{Let } \frac{C(s)}{R(s)} = T(s) = \frac{\omega_n^2}{s^2 + 2\xi\omega_n s + \omega_n^2}$$

$$|T(s)| = \frac{\omega_n^2}{-\omega^2 + j2\xi\omega_n\omega + \omega_n^2}$$

$$|T(j\omega)| = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + (2\xi\omega_n\omega)^2}} = \frac{1}{\sqrt{2}} \left(\text{DC value of } T(s) \right)$$

$$\frac{1}{\sqrt{2}} = \frac{\omega_n^2}{\sqrt{(\omega_n^2 - \omega^2)^2 + (2\xi\omega_n\omega)^2}} \quad \left[\begin{array}{l} \text{DC value} \\ \text{of } |T(j\omega)| = 1 \end{array} \right]$$

$$(\omega_n^2 - \omega^2)^2 + 4\xi^2\omega_n^2\omega^2 = 2\omega_n^4$$

$$\omega_n^4 + \omega^4 - 2\omega_n^2\omega^2 + 4\xi^2\omega_n^2\omega^2 = 2\omega_n^4$$

$$\omega^4 - 2\omega_n^2\omega^2(1 - 2\xi^2) - \omega_n^4 = 0$$

$$\text{Let } \begin{array}{l} \omega^4 = x^2 \\ \omega^2 = x \end{array} \quad \left| \quad x^2 - x(2\omega_n^2(1 - 2\xi^2)) - \omega_n^4 = 0 \right.$$

$$\text{sol}^n \text{ of } x = \frac{+2\omega_n^2(1-2\xi^2) \pm \sqrt{4\omega_n^4(1+4\xi^4-4\xi^2)+4\omega_n^4}}{2}$$

$$= \omega_n^2(1-2\xi^2) \pm \sqrt{\omega_n^4(4\xi^4-4\xi^2+1)+\omega_n^4}$$

$$= \omega_n^2(1-2\xi^2) \pm \sqrt{\omega_n^4(4\xi^4-4\xi^2+2)}$$

$$x = \omega_n^2 \left[1-2\xi^2 \pm \sqrt{4\xi^4-4\xi^2+2} \right]$$

$$\omega_b = x^{1/2} = \omega_n \left(1-2\xi^2 + \sqrt{4\xi^4-4\xi^2+2} \right)^{1/2} \quad \text{--- ①}$$

$$\text{As } t_p = \frac{\pi}{\omega_d} = \frac{\pi}{\omega_n \sqrt{1-\xi^2}}$$

$$\omega_b = \frac{\pi}{t_p \sqrt{1-\xi^2}} \left(1-2\xi^2 + \sqrt{4\xi^4-4\xi^2+2} \right)^{1/2}$$

Hence
proved.

From eqⁿ ①


$$\frac{\omega_b}{\omega_n} = \left[1-2\xi^2 + \sqrt{4\xi^4-4\xi^2+2} \right]^{1/2}$$

y

taking $\xi = x$

Now plotting x vs y graph

$\frac{\omega_b}{\omega_n}$	1.5537	1.272	1.01	0.6435	0.2665	0.05
ξ	0	0.5	0.7	1	2	10

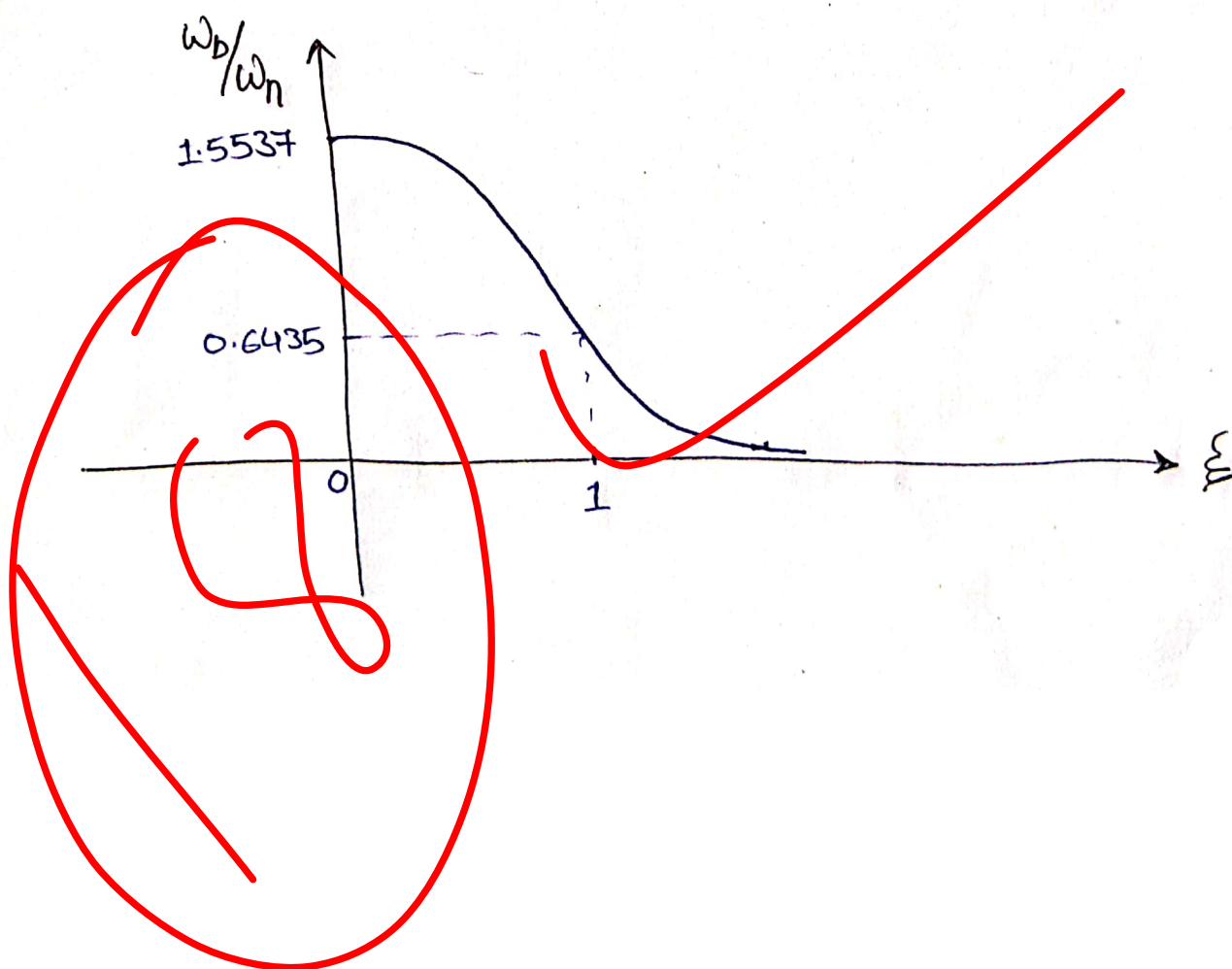

Ans 7 c)

$$A = \begin{bmatrix} -1 & -2 & -2 \\ 0 & -1 & 1 \\ 1 & 0 & -1 \end{bmatrix} \quad B = \begin{bmatrix} 2 \\ 0 \\ 1 \end{bmatrix}$$

$$C = [1 \ 1 \ 0]$$

For controllability, we find $|Q_c|$.

$$Q_c = [B \ AB \ A^2B]$$

$$= \begin{bmatrix} 2 & -4 & 0 \\ 0 & 1 & 0 \\ 1 & 1 & -5 \end{bmatrix}$$

$$|Q_c| = 2(-5) + 4(0) + 0 = -10 \neq 0$$

As $|Q_c| \neq 0$ System is controllable

Now for Observability we find $|Q_o|$.

$$Q_o = [C^T \ A^T C^T \ (A^T)^2 C^T]$$

$$Q_o = \begin{bmatrix} 1 & -1 & 0 \\ 1 & -3 & 5 \\ 0 & -1 & 0 \end{bmatrix}$$

$$|Q_o| = 1(0+5) + 1(0) + 0 = 5 \neq 0$$

As $|Q_o| \neq 0$ System is Observable

Hence,

System is both Controllable and Observable