

1. (a)
(i)

$$x_a(t) = 3 \cos(100\pi t)$$

$$\omega_m = 100\pi \Rightarrow f_m = \frac{\omega_m}{2\pi} = 50 \text{ Hz}$$

for avoiding aliasing effecting

$$\text{Sampling rate } f_s \geq 2f_m$$

$$\therefore f_{s \text{ min}} = 2f_m \Rightarrow \boxed{f_{s \text{ min}} = 2 \times 50 = 100 \text{ Hz}}$$

(ii)

$$f_s = 200 \text{ Hz}$$


$$x_a(t) = 3 \cos(100\pi t)$$

$$x_a(nT) = 3 \cos(100\pi nT) = 3 \cos\left(\frac{4n\pi}{2}\right)$$

} No aliasing effect

now sampling at $f_s = 200 \text{ Hz}$

as $f_s > f_{s \text{ min}}$.

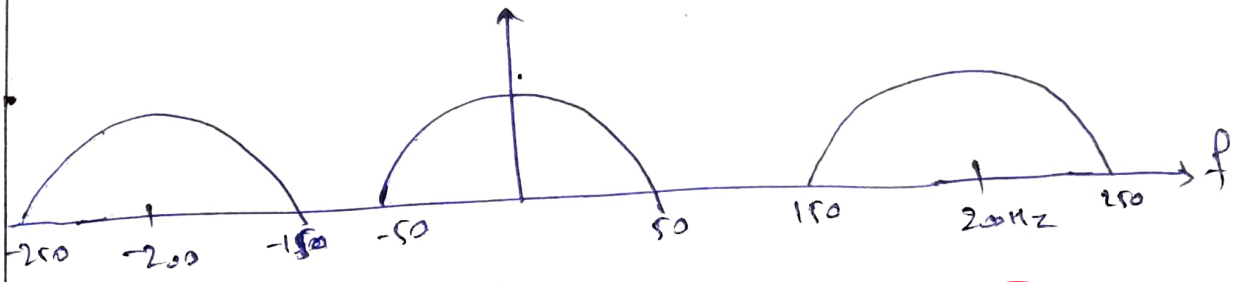


(iii)

Now at $f_s = 75 \text{ Hz}$

$$x_a(nT) = 3 \cos(100\pi nT) = 3 \cos\left(\frac{4n\pi}{3}\right)$$

overlapping (aliasing effect)

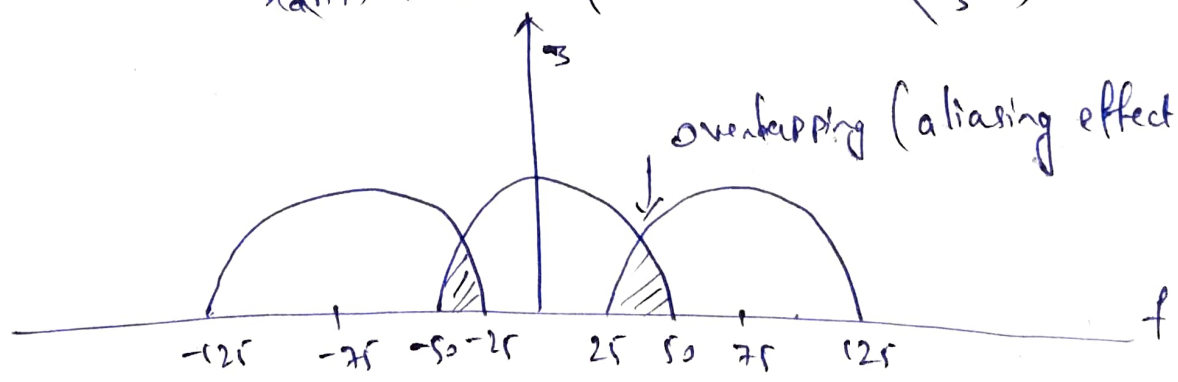

as $f_s < f_{s \text{ min}}$.

$$x_a(nT) = 3 \cos\left(2\pi - \frac{2\pi}{3}\right)n = \left[3 \cos\left(\frac{2\pi}{3}n\right)\right]$$


1. (a)

To get the samples as in Part (iii), there should be again aliasing effect

$$\text{then fore, } F = f F_s = f \cdot 75$$

$$f = \frac{1}{3} \text{ in Part (iii)}$$
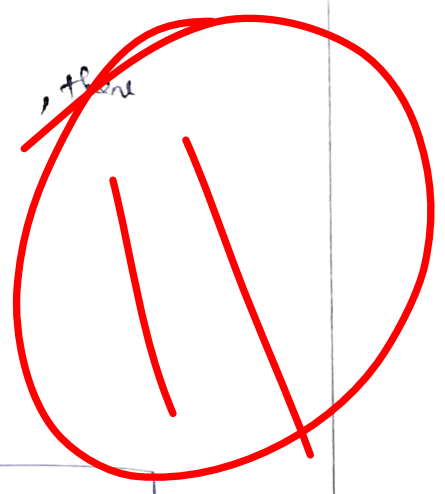
$$\Rightarrow \therefore F = \frac{75}{3} \Rightarrow \boxed{F = 25 \text{ Hz}}$$



1. (b)

$$x(n) = \{0, 1, 2, 3\}$$

$$X(K) = [W_N^K] [x(n)]$$

$$\begin{bmatrix} X(0) \\ X(1) \\ X(2) \\ X(3) \end{bmatrix} = \begin{bmatrix} 1 \\ W_4 \\ W_4^2 \\ W_4^3 \end{bmatrix} \begin{bmatrix} x(0) \\ x(1) \\ x(2) \\ x(3) \end{bmatrix}$$

$$= \begin{bmatrix} 1 & 1 & 1 & 1 \\ 1 & -j & -1 & j \\ 1 & -1 & 1 & -1 \\ 1 & j & -1 & -j \end{bmatrix} \begin{bmatrix} 0 \\ 1 \\ 2 \\ 3 \end{bmatrix}$$

$$= \begin{bmatrix} 0+1+2+3 \\ 0-j-2+j^3 \\ 0-1+2-3 \\ 0+j-2-j^3 \end{bmatrix}$$

$$\begin{bmatrix} X(0) \\ X(1) \\ X(2) \\ X(3) \end{bmatrix} = \begin{bmatrix} 6 \\ -2+j^2 \\ -2 \\ -2-j^2 \end{bmatrix}$$

$$\boxed{X(K) = [6, -2+j^2, -2, -2-j^2]}$$

1(c)

$$T = \frac{1}{2} I^2 \frac{dL}{d\theta} = K\theta$$

for $I = 1.5 \text{ A}$, $\theta = 90^\circ = \frac{\pi}{2}$

$$\frac{1}{2} \times (1.5)^2 \times \frac{d}{d\theta} [200 + 40\theta + 4\theta^2 - \theta^3] \times 10^{-6} = K\theta$$

$$\frac{1}{2} \times 2.25 \times [40 + 8\theta - 3\theta^2] \times 10^{-6} = K\theta$$

$$\frac{1}{2} \times 2.25 \times \left[40 - 8 \times \frac{\pi}{2} - 3 \times \left(\frac{\pi}{2}\right)^2 \right] \times 10^{-6} = K \times \frac{\pi}{2}$$

$$K = 14.346 \times 10^{-6} \text{ Nm/rad.}$$

Now for $I = 1 \text{ A}$,

$$\frac{1}{2} \times 1^2 \times \frac{d}{d\theta} [200 + 40\theta - 4\theta^2 - \theta^3] \times 10^{-6} = 14.346 \times 10^{-6} \theta$$

$$\frac{1}{2} \times [40 - 8\theta - 3\theta^2] = 14.346 \theta$$


$$\Rightarrow 3\theta^2 + [8 + 28.6929] \theta - 40 = 0$$

$$\theta = 1.007 \text{ radian} \quad [\text{ignoring negative value}]$$

$$\theta = 57.697^\circ$$




(6)

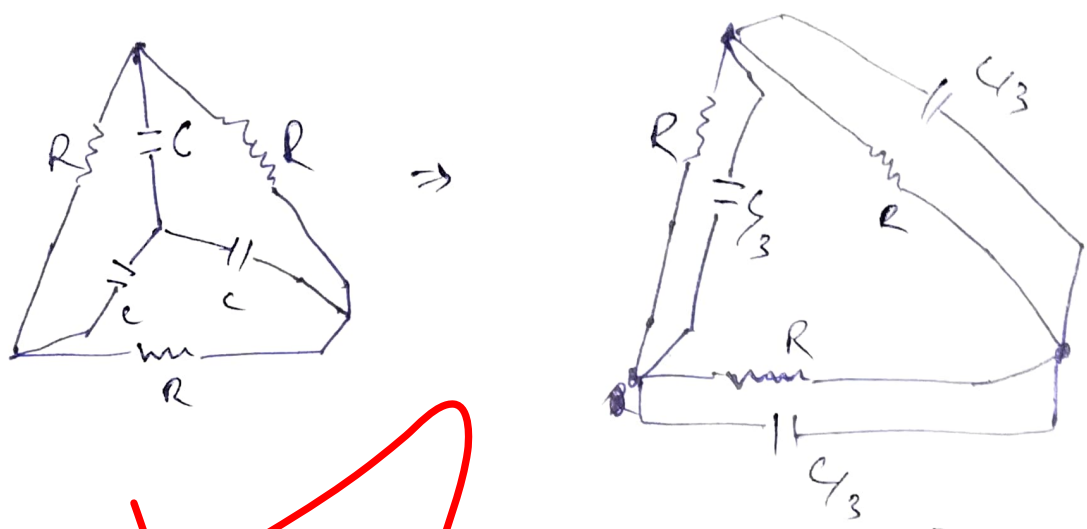

$$Z = \left[R \parallel \frac{1}{j\omega C/3} \right] = \left[1000 \parallel \frac{3}{j1000 \times 156} \right]$$

$$= (900 - j300) \Omega$$

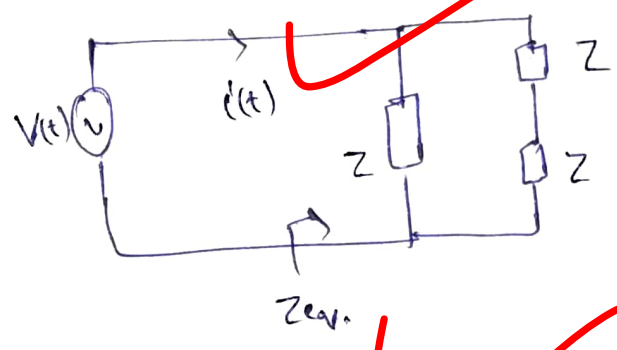

$$Z_{eq} = 2Z \parallel Z$$

$$= 2(900 - j300) \parallel (900 - j300)$$

$$= 600 - j200$$


$$i(t) = \frac{V(t)}{Z_{eq}} = \frac{2 \sin 1000t}{600 - j200}$$

$$i(t) = 3.162 \sin[1000t + 18.435^\circ] \text{ mA}$$



1(e)

Schenky bridge.

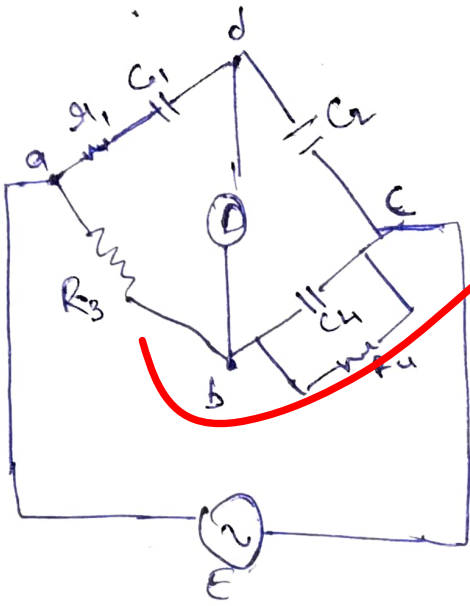

To obtain ~~the~~ balance

$$\left[R_3 + \frac{1}{j\omega C_1} \right] \times \left[\frac{R_4 \times \frac{1}{j\omega C_4}}{R_4 + \frac{1}{j\omega C_4}} \right] = \left[\frac{1}{j\omega C_2} \times R_3 \right]$$

$$\left[R_3 + \frac{1}{j\omega C_1} \right] \frac{R_4}{C_4} = \frac{R_3}{C_2} \left(R_4 + \frac{1}{j\omega C_4} \right)$$

Comparing Real and imaginary parts.

$$1. \frac{R_4}{C_4} = \frac{R_3 R_4}{C_2}$$

$$\frac{R_4}{C_1 C_4} = \frac{R_3}{C_2 C_4}$$

$$\Rightarrow \boxed{R_1 = R_3 \frac{C_4}{C_2}}$$

$$\boxed{C_1 = \frac{R_4 C_2}{R_3}}$$

$$C_1 = \frac{1000}{\pi \times 260} \times 106 \text{ PF}$$

$$\boxed{C_1 = 129.77 \text{ PF}}$$

$$\text{Dissipation factor (tan } \delta) = \omega R_1 C_1 = 2\pi f \times \frac{R_3 C_4}{C_2} \times \frac{R_4 C_2}{R_3}$$

$$= 2\pi f \times R_4 C_4$$


$$= 2 \times \pi \times 50 \times \frac{1000}{\pi} \times 0.5 \times 10^{-6}$$

$$\boxed{D = \tan \delta = 0.05}$$

$$C_1 = \frac{q_0 q_1 A}{t} = \frac{8.854 \times 10^{-12} \times 0.1 \times \pi \times 0.01^2}{4.5 \times 10^{-3} \times 4} = 121.77 \times 10^{-12}$$

$$\epsilon_1 = 5.83$$

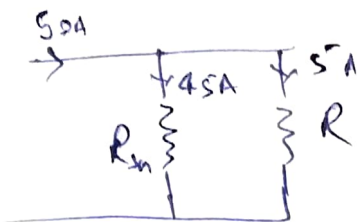3(a) (i) ON DC, Inductor behaves as short circuit so, L can be neglected on dc




$$45 \times R_{sh} = 5 \times R$$

$$R_{sh} = \frac{5 \times 0.09}{45}$$

$$R_{sh} = 0.01 \Omega \rightarrow \text{shunt resistance to extend the range,}$$

Now on AC, $f = 50 \text{ Hz}$

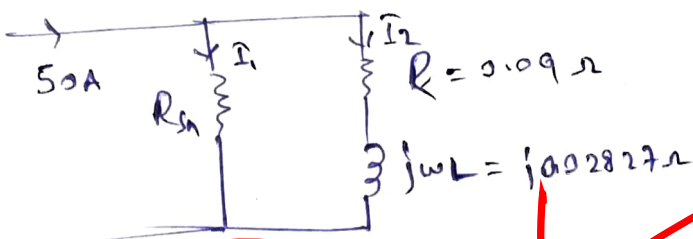

Using Current division Rule,


$$I_2 = 50 \times \frac{R_{sh}}{R_{sh} + R + j\omega L} = 50 \times \frac{0.01}{0.01 + 0.09 + j0.02827}$$

$$= 4.811 \angle -15.78^\circ$$

$$\% \text{ Error} = \frac{I_{\text{measured}} - I_{\text{true}}}{I_{\text{true}}} \times 100 = \frac{4.811 - 5}{5} \times 100$$

$$\% \text{ Error} = -3.78 \%$$

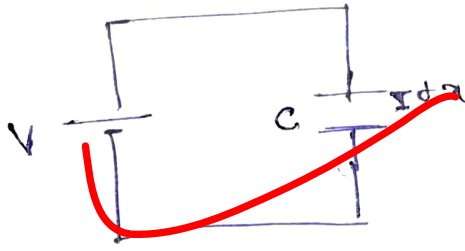(ii) Considering an Electrostatic Instrument



In this capacitor one plate can be moved to change the capacitance, and for that some force will be applied by

So, here capacitance is variable with respect to distance between plates 'x'.

Let Energy stored by capacitor = $\frac{1}{2} C V^2$

As we know

$$F = \frac{dW}{dx}$$

$$F = \frac{d}{dx} \left(\frac{1}{2} C V^2 \right)$$

$$F = \frac{1}{2} V^2 \frac{dC}{dx}$$

→ expression of force developed by an electrostatic instrument.

3. (b)

$$x(t) = a_0 + \sum_{n=1}^{\infty} a_n \cos n\omega_0 t + \sum_{n=1}^{\infty} b_n \sin n\omega_0 t \quad \text{--- (1)}$$

$$a_0 = \frac{1}{T_0} \int_{T_0} x(t) \cdot dt$$

Here, $T_0 = 2\pi$, $\omega_0 = \frac{2\pi}{T_0} = \frac{2\pi}{2\pi} = 1$

$$a_0 = \frac{1}{2\pi} \int_0^{2\pi} x(t) dt = \frac{1}{2\pi} \int_0^{\pi} A \sin \omega_0 t dt$$

$$a_0 = \frac{A}{2\pi} \int_0^{\pi} \sin t dt = \frac{2A}{2\pi} = \frac{A}{\pi}$$

$$a_0 = \frac{A}{\pi}$$

$$a_n = \frac{2}{T_0} \int_{T_0} x(t) \cdot \cos n\omega_0 t dt$$

$$= \frac{2}{2\pi} \int_0^{2\pi} x(t) \cos nt dt = \frac{2}{\pi} \int_0^{\pi} A \sin t \cdot \cos nt dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \sin t \cos nt dt$$

$$= \frac{A}{2\pi} \int_0^{\pi} [\sin(1+n)t + \sin(1-n)t] dt$$

$$= \frac{A}{2\pi} \left[-\frac{\cos(1+n)t}{(1+n)} - \frac{\cos(1-n)t}{(1-n)} \right]_0^{\pi}$$

$$= -\frac{A}{2\pi} \left[\frac{\cos((1+n)\pi)}{(1+n)} + \frac{\cos(1-n)\pi}{1-n} - \frac{1}{1+n} - \frac{1}{1-n} \right]$$

$$= -\frac{A}{2\pi} \frac{(1-n) \times (-1)^{1+n} + (-1)^{1-n} (1+n) - 1 - 1}{1-n^2}$$

$$= -\frac{A}{2\pi} \left[\frac{(-1)^n [-1+n-1-n] - 2}{1-n^2} \right]$$

$$= \frac{2A}{2\pi} \left[\frac{1 + (-1)^n}{1-n^2} \right] = \frac{A}{\pi} \left[\frac{1 + (-1)^n}{1-n^2} \right]$$

now for $n=1$, $\frac{0}{0}$ form occurs,

$$\therefore a_n = \frac{2}{2\pi} \int_0^{2\pi} x(t) \cos \omega_n t \, dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \sin t \cdot \cos t \, dt = 0$$

Now

$$a_n = \begin{cases} \frac{2A}{\pi} \times \frac{1}{n^2-1} & n = \text{even} \\ 0 & n = \text{odd} \end{cases}$$

$$\text{Now, } b_n = \frac{2}{T_0} \int_{T_0} x(t) \sin n \omega t \, dt = \frac{2}{2\pi} \int_0^{2\pi} x(t) \sin n t \, dt$$

$$= \frac{A}{\pi} \int_0^{\pi} \sin t \cdot \sin n t \, dt = \frac{A}{2\pi} \int_0^{\pi} (\cos(1+n)t - \cos(1-n)t) \, dt$$

$$= \frac{A}{2\pi} \left[\frac{\sin(1-n)t}{1-n} - \frac{\sin(1+n)t}{1+n} \right]_0^{\pi}$$

$$= \left[\frac{\sin(1-n)\pi}{1-n} - \frac{\sin(n\pi)}{1+n} \right] \times \frac{A}{2\pi}$$

$$= \frac{A}{2\pi} \left[\frac{\sin(\pi - n\pi)}{1-n} - \frac{\sin(\pi + n\pi)}{1+n} \right]$$

$$= \frac{A}{2\pi} \left[\frac{\sin\pi \cdot \cos n\pi - \cos\pi \cdot \sin n\pi}{1-n} - \frac{\sin\pi \cdot \cos n\pi + \cos\pi \cdot \sin n\pi}{1+n} \right]$$

$$= \frac{A}{2\pi} \left[\frac{A}{2\pi} \left(\frac{\sin n\pi}{1-n} + \frac{\sin n\pi}{1+n} \right) \right] = \frac{A}{2\pi} \left(\frac{\sin n\pi \times 2}{1-n^2} \right)$$

At $n=1$, $\frac{0}{0}$ form

by L'Hospital rule,


$$b_1 = \frac{A}{\pi} \cdot \frac{\cos\pi \times \pi}{-2} = \frac{A}{2}$$

$$b_n = \begin{cases} \frac{A}{2} & , n=1 \\ 0 & \text{for } 1 < n < \infty \end{cases}$$

Using ①

~~$x(t) =$~~
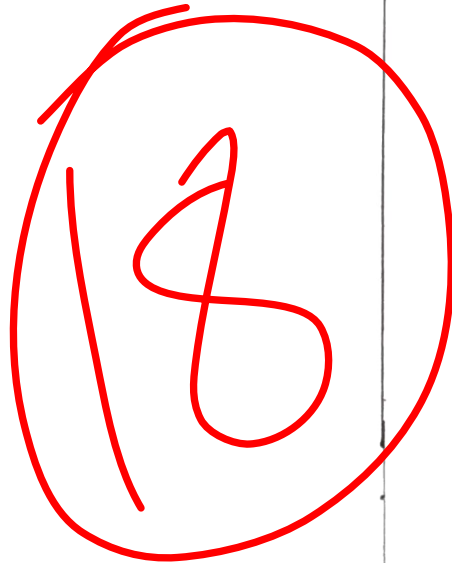
$$x(t) = \frac{A}{\pi} + \sum_{n=2,4,6,\dots}^{\infty} \frac{-2A}{\pi} \times \frac{1}{n^2-1} \cos nt + \frac{A}{2}$$



30(ii)


$$R = n + \frac{I_0 \sin(\alpha + \delta)}{I_s} = n + \frac{I_w \cos \delta + I_u \sin \delta}{I_s} \quad \text{--- (1)}$$

$$K = n = \frac{1000}{5} \approx 200 \quad I_s = 5A$$

$I_u = 0$
 ↓
 No leakage reactance.

$$\delta = 0^\circ$$

↓
 Purely resistive burden.

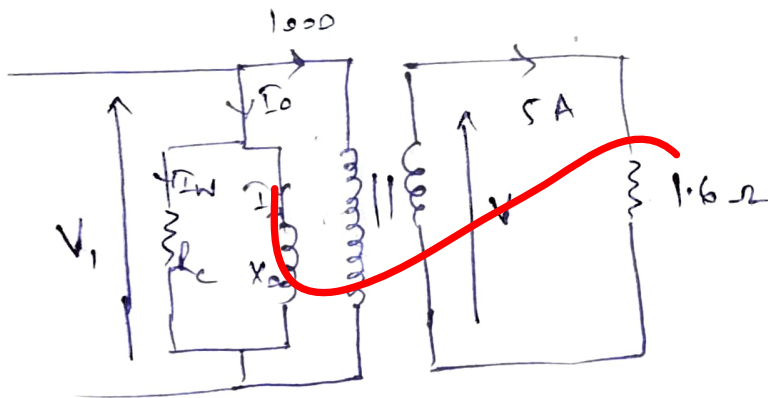

$$V = 1.6 \times 5 = 8V$$

$$V_1 = \frac{8}{1000} \times 5 = 0.04V$$

$$\frac{V_1^2}{R_c} = 1.5W \Rightarrow R_c = \frac{(0.04)^2}{1.5} = 1.0667 \times 10^{-3} \Omega$$

$$I_w = \frac{V_1}{R_c} = \frac{0.04}{1.0667 \times 10^{-3}} = 37.5A$$

$$R = 200 + \frac{37.5 \times \cos 0}{5} = 207.5$$

$$\text{Regulation } (\%) = \frac{K - R}{R} = \frac{200 - 207.5}{207.5} = -0.0361$$


$$\boxed{\begin{aligned} \sigma &= -0.0361 \\ &= -3.61\% \end{aligned}}$$

Now by using emf equat

$$e = \sqrt{2\pi f} N_{pr} \phi$$

$$8 = \sqrt{2 \times \pi \times 50 \times 200 \times \phi}$$

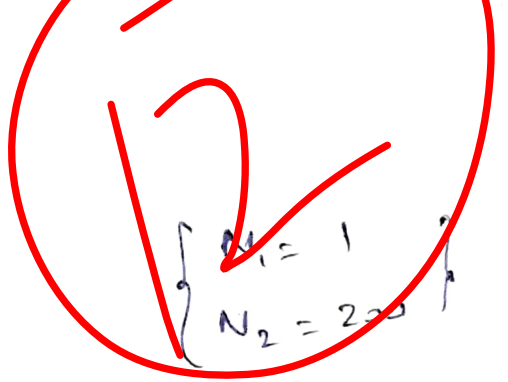
$$\phi = 1.8 \times 10^{-4} \text{ wb} \rightarrow \text{Flux in the core.}$$



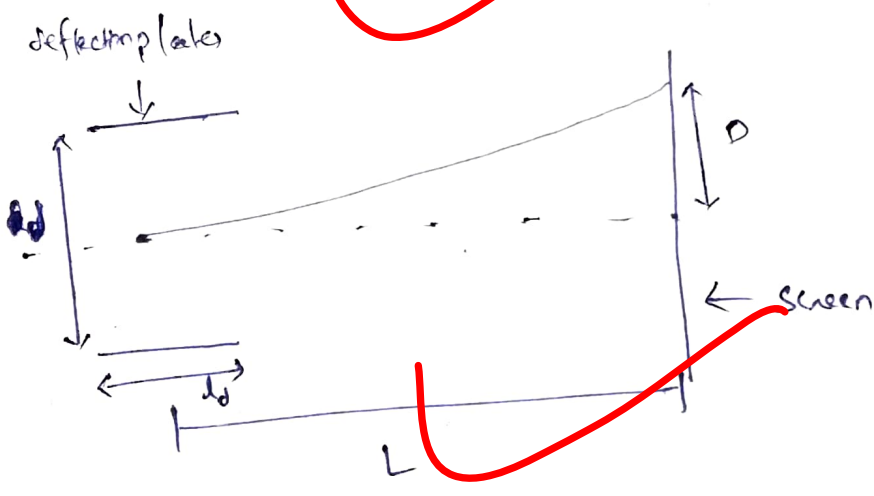3. (ii)

$$D = \frac{L d V_y}{2d V_A}$$

expression for deflection
of electron beam on
screen in Electrostatic
deflection arrangement



- $D \rightarrow$ deflection on electron beam
- $L \rightarrow$ distance from centre of plate to the screen
- $L_d \rightarrow$ length of deflection plates
- $d \rightarrow$ distance between deflection plates
- $V_y \rightarrow$ voltage at deflecting plates.
- $V_A \rightarrow$ Anode voltage

Given, $V_A = 2000 \text{ V}$, $l_d = 2 \times 10^{-2} \text{ m}$
 $d = 5 \times 10^{-3} \text{ m}$, $L = 30 \times 10^{-2} \text{ m}$
 $D = 3 \times 10^{-2} \text{ m}$, $A = 100$

Using (1)

$$3 \times 10^{-2} = \frac{30 \times 10^{-2} \times 2 \times 10^{-2} \times V_y}{2 \times 5 \times 10^{-3} \times 2000}$$

$$V_y = 100 \text{ V}$$


$$V_y = A V_{in}$$

[A = gain]

$$100 = 100 \times V_{in}$$

$$\boxed{V_{in} = 1 \text{ V}}$$

input voltage.

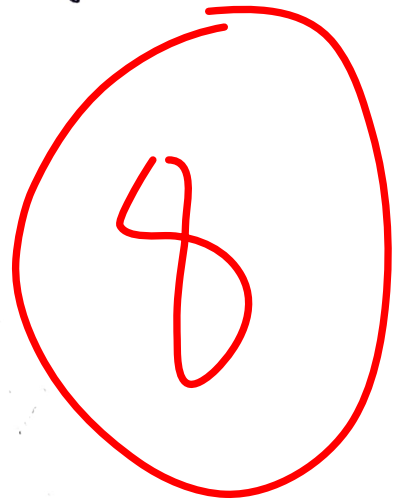

5(a)

number of atoms in a unit cell = 4

(∵ fcc structure)

$$r = 0.15 \times 10^{-9} \text{ m}$$

$$m = 65.5 \text{ gm mol}^{-1}$$

(i)

$$\text{atomic concentration} = \frac{\text{no. of atoms in unit cell}}{\text{Volume of unit cell}}$$

In fcc,

$$16r^2 = 2a^2 \Rightarrow a = 2\sqrt{2}r$$

$$\text{atomic concentration} = \frac{4}{[2\sqrt{2} \times 0.15 \times 10^{-9}]^3}$$

$$n_{\text{at}} = 5.238 \times 10^{28} \text{ m}^{-3}$$

(ii)

$$\text{Density } (\rho) = \frac{n m}{N_A \times V} = \frac{4 \times 65.5}{6.023 \times 10^{23} \times [2\sqrt{2} \times 0.15 \times 10^{-9}]^3}$$

$$\rho = 5.696 \text{ gm cm}^{-3}$$

5(b)

Glass Ceramic combines the property of glass with benefits of ceramics.

Properties!

→ Glass Ceramics can range from highly crystalline to containing a more substantial glassy phase. So it can range from transparent to opaque.

→ In general they exhibit almost zero thermal expansion and high toughness.

→ They are resistant to thermal shock and high impact resistance.

Application:

→ Household appliances including toasters and clothes irons

→ Smartphone Screens

→ Infrared heating elements

→ In high temperature ~~not~~ furnaces as an insulation material, due to their high thermal robustness.

→ Bio medical engineering

→ Optoelectronic applications

→ Dental applications.

5(e) (i) current gain (A_I) = $\frac{I_L}{I_{in}}$

$$I_L = \frac{V_L}{R_L} = \frac{9}{1k\Omega} = 9mA$$

$$A_I = \frac{9}{0.1} \Rightarrow \boxed{A_I = 90}$$

(ii) Power gain $\Rightarrow A_P = \frac{V_L I_L}{V_{in} I_{in}} = \frac{9}{1} \times \frac{9}{0.1}$

$$\boxed{A_P = 810}$$

5001

(iii) Power drawn from DC supplies.

$$P = (10 \times 9.5) \times 2 \text{ mW}$$

$$P = 190 \text{ mW}$$

(iv) Power dissipated in amplifier

$$P_{out} = \frac{V_{out}^2}{R_L} = \frac{9 \times 9}{2 \times 1 \text{ k}\Omega} = \frac{81 \text{ mW}}{2}$$

$$P_{out} = 40.5 \text{ mW}$$

$$(P_{in})_{ac\text{-side}} = \frac{1}{2} \times 1 \times 0.1 = 0.05 \text{ mW}$$

Power dissipated = $P - P_{out} + P_{in}$


$$P_d = 190 - 40.5 + 0.05$$

$$P_d = 149.55 \text{ mW}$$

$$\eta_{\text{amplifier}} = \frac{P_{out}}{P + P_{in}} = \frac{40.5}{190 + 0.05} = 0.2131$$

$$\eta = 21.31\%$$

5.(d)

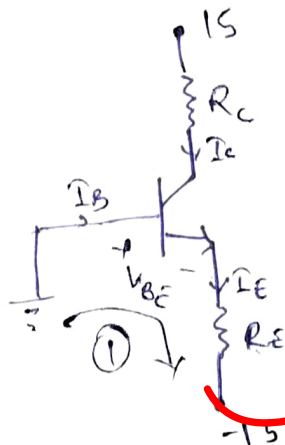

$I_{C1} = 1 \text{ mA} \Rightarrow V_{BE1} = 0.7 \text{ V}$

$I_{C2} = 2 \text{ mA} \Rightarrow V_{BE2} = ?$

$I_C = I_0 e^{V_{BE}/V_T} \quad \text{--- (1)}$

\Rightarrow Using the (1) equation

$$\frac{I_{C2}}{I_{C1}} = \frac{e^{V_{BE2}/V_T}}{e^{V_{BE1}/V_T}} = e^{\frac{V_{BE2} - V_{BE1}}{V_T}}$$

$\Rightarrow \frac{2}{1} = e^{\frac{V_{BE2} - 0.7}{25 \text{ mV}}}$

$\Rightarrow V_{BE2} = 0.7173 \text{ V}$

Now applying KVL in loop (1)

$0 = V_{BE} + I_E R_E - 15$

$0 = 0.7173 + 2 \times \left(\frac{1+100}{100} \right) R_E - 15$

$\left[I_E = \frac{1+\beta}{\beta} I_C \right]$

$\Rightarrow R_E = 7.07 \text{ k}\Omega$

Now, $I_C = \frac{15 - V_C}{R_C} \Rightarrow 2 \text{ mA} = \frac{15 - 5}{R_C}$

$R_C = 5 \text{ k}\Omega$

5(c)

$$S_{in} = S_1 + S_2 + S_3$$

$$S_1 = \frac{100}{0.78} \angle \cos^{-1} 0.78 = 128.209 \angle 38.74 \text{ KVA}$$

$$S_2 = \frac{200}{0.8} \angle \cos^{-1} 0.8 = 250 \angle 36.87 \text{ KVA}$$

$$S_3 = \frac{150}{0.9} \angle -\cos^{-1} 0.9 = 166.667 \angle -25.842 \text{ KVA}$$

$$S_{in} = 128.209 \angle 38.74 + 250 \angle 36.87 + 166.667 \angle -25.842$$

$$= 476.792 \angle 19.3 \text{ KVA}$$

$$S_{in} = \sqrt{3} V_L I_L^* \quad \left[\text{Assuming the System is 3 phase} \right]$$


$$\sqrt{3} \times 480 I_L^* = 476.792 \angle 19.3 \text{ KVA}$$

$$I_L = 573.492 \angle 19.3 \text{ A}$$

Transmission line Current


$$\text{System Power factor} = \cos(19.3)$$

$$= 0.9438 \text{ lagging}$$

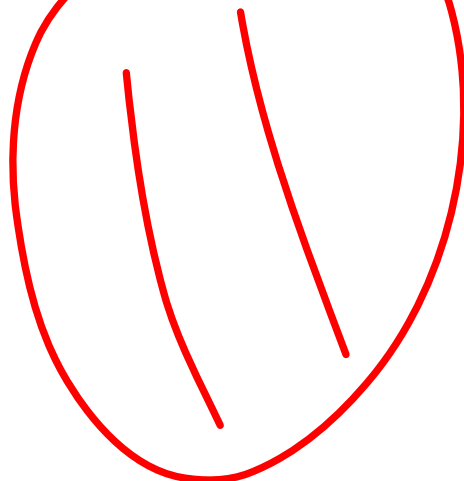


7a) DC Analysis

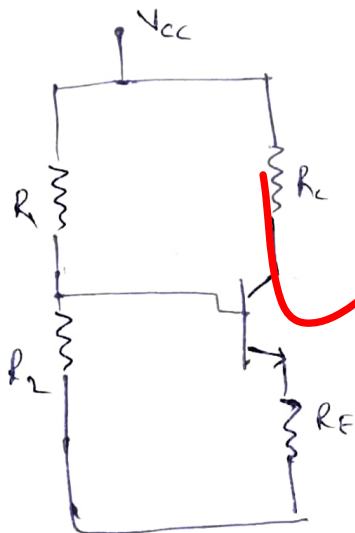(1) All AC supplies will be shorted and, all capacitors will be open circuited.



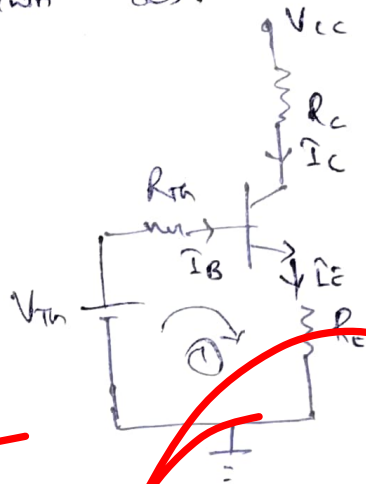By using thevenin theorem, circuit can be redrawn as.



$$V_{th} = \frac{V_{cc} \times R_2}{R_1 + R_2} = \frac{10 \times 15}{27 + 15} = 3.5714 \text{ V}$$

$$R_{th} = \frac{R_1 \cdot R_2}{R_1 + R_2} = \frac{27 \times 15}{27 + 15} = 9.643 \text{ K}\Omega$$

KVL in loop ①

$$V_{th} = I_B R_{th} + V_{BE} + I_E R_E$$

$$3.5714 = I_B \times 9.643 + 0.7 + (1 + 100) \times 1.2 I_B \quad [I_E = (1 + \beta) I_B]$$

$$I_B = 21.945 \mu\text{A}$$

$$I_C = \beta I_B = 100 \times 21.945 = 2.1945 \text{ mA}$$


$$I_E = 2.2165 \text{ mA}$$

(ii)
$$g_m = \frac{I_C}{V_T} = \frac{2.1945}{25} = 0.08778 \text{ S}$$

$$g_{\pi} = \beta / g_m = \frac{100}{0.08778} = 1.14 \text{ K}\Omega$$

$$r_o = \frac{V_A}{I_C} = \frac{100}{2.1945 \text{ mA}} = 45.57 \text{ k}\Omega$$

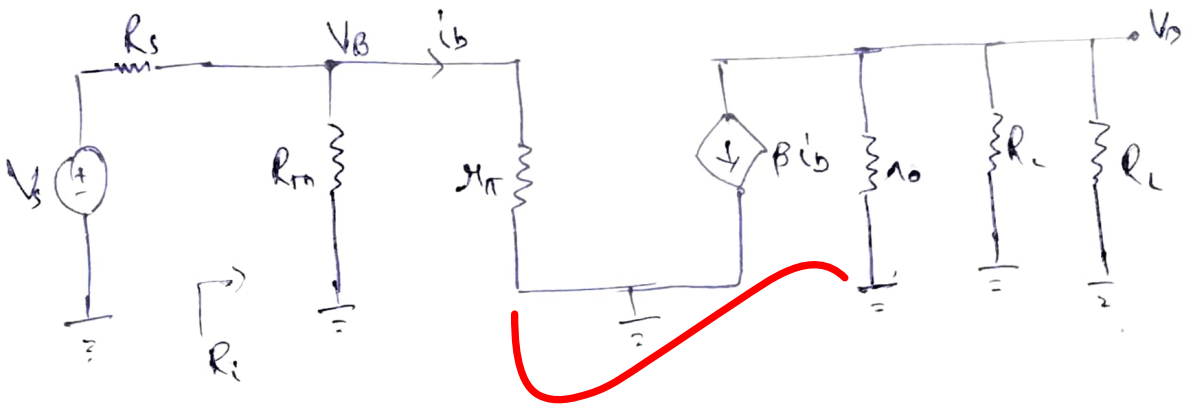AC equivalent circuit \rightarrow (T-model)



from the circuit

$$R_i = R_B \parallel r_{\pi} = [9.643^{-1} + 1.14^{-1}]^{-1} \text{ k}\Omega$$

$$R_i = 1.019 \text{ k}\Omega$$

Now for voltage gain (V_o/V_s)

$$V_B = r_{\pi} i_b = 1.14 i_b \times 10^3$$

$$V_o = -\beta i_b \times [r_o \parallel R_C \parallel R_L]$$

$$= -100 i_b [45.57 \parallel 2.2 \parallel 2.5] \times 10^3$$

$$V_o = -114.09 i_b \times 10^3$$

$$A_v = \frac{V_o}{V_B} = \frac{-114.09 i_b \times 10^3}{1.14 i_b \times 10^3}$$

$$\Rightarrow A_v = 100.08$$

$$A_v \approx 100$$

$$N_s = \frac{120 \times f}{P} = \frac{120 \times 50}{6} = 1000 \text{ rpm}$$

$$\omega_s = \frac{2\pi N_s}{60} = \frac{2\pi \times 1000}{60}$$

$$\omega_s = 104.72 \text{ rad s}^{-1}$$

$$|E_f| = 480 \text{ V}$$

$$E_f = V + jI_a X_s \quad \text{--- (1)}$$

$$\frac{480}{\sqrt{3}} \angle \delta = V \angle 0^\circ + j1 \times 60 \angle -\cos^{-1} 0.8$$

(leading power factor)

Equating the magnitudes.

$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V - 36)^2 + (48)^2$$

$$V - 36 = 272.94$$

$$V = 308.94 \text{ V (phase value)}$$

$$V_L = \sqrt{3} \times 308.94$$

Terminal voltage at leading Power factor of 0.8

$$V_L = 535. \text{ Volts.}$$

Now at rated current 0.8 p.f lag.
using (1)

$$\frac{480}{\sqrt{3}} \angle \delta = V \angle 0^\circ + j1 \times 60 \angle -\cos^{-1} 0.8$$

Equating magnitudes

$$\left(\frac{480}{\sqrt{3}}\right)^2 = (V+36)^2 + (48)^2$$

$$V = 236.94 \text{ Volts (phase)}$$

$$V_L = \sqrt{3} \times 236.94$$

$$V_L = 410.4 \text{ Volts. } \rightarrow \text{Terminal voltage.}$$

(ii)

$$P_{out} = \sqrt{3} \times V_L \times I \times \cos \phi$$

$$= \sqrt{3} \times 410.4 \times 60 \times 0.8 = 34120 \text{ Watts}$$

$$P_{in} \times \eta = \frac{P_{out} \times 100}{P_{out} + \text{Losses}}$$

$$\eta = \frac{34120}{34.12 + 1.94} \times 100$$

$$\eta = 93.17 \%$$


19

(iv) Voltage Regulation at O.P.f leading

$$\%VR = \frac{V_{NL} - V_{FL}}{V_{FL}} \times 100 = \frac{480 - 535.1}{535.1} \times 100$$

$$\%VR = -10.29 \%$$

7(c) (i) DC Analysis

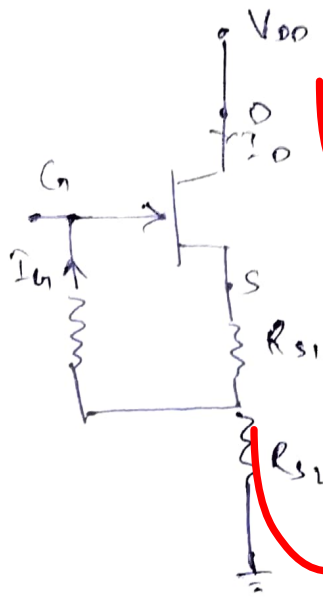

$I_D = 10 \mu A$
 $V_S = I_D (R_{S1} + R_{S2})$
 $V_{GS} = I_D R_{S2}$ — (1)

$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$ — (2)

$I_D = 12 \left(1 - \left(\frac{-2}{-5} \right) \right)^2 = 4.32 \text{ mA}$

from the circuit

$V_{DD} = V_{DS} + V_S$
 $15 = 10 + V_S \Rightarrow V_S = 5V$

$V_{GS} = -2 \Rightarrow V_{GS} - V_S = -2$

$V_{GS} - 5 = -2 \Rightarrow V_{GS} = 3 \text{ Volts.}$

using (1)


$3 = 4.32 \times R_{S2} \Rightarrow R_{S2} = 0.6944 \text{ K}\Omega$

also, $V_S = I_D (R_{S1} + R_{S2})$

$5 = 4.32 (R_{S1} + 0.6944)$

$R_{S1} = 0.463 \text{ K}\Omega$

7(c)(ii)

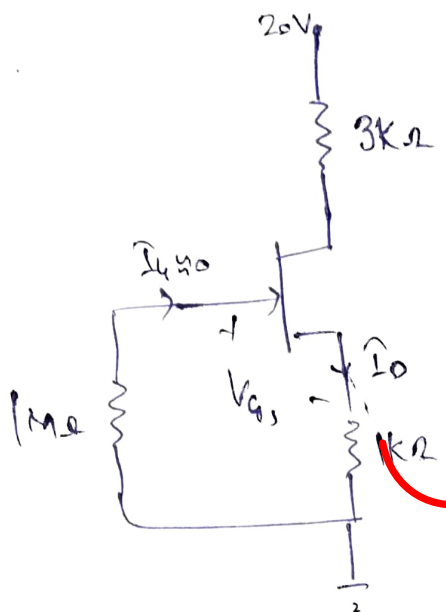

$\therefore V_G = 0$

$V_S = I_D \times 1K = I_D$

[Assuming I_D in mA]

$V_{DS} = -I_D$

As, $I_D = I_{DSS} \left[1 - \frac{V_{DS}}{V_P} \right]^2$

$I_D = 10 \left[1 - \frac{+I_D}{+4} \right]^2$

$I_D = 10 \left[1 + \frac{I_D^2}{16} - \frac{I_D}{2} \right]$

$\frac{10}{16} I_D^2 - 6 I_D + 10 = 0$

Solving above equation.

$I_D = 7.453 \text{ mA}$

$I_D = 2.146 \text{ mA}$

↓

↓

$V_{DS} = -7.453 \text{ V}$

$V_{DS} = -2.146 \text{ V}$

As, I_D to flow, $V_{DS} > V_P$

So, $I_D = 2.146 \text{ mA}$

$V_{DSQ} = -2.146 \text{ V}$

from the circuit,

$$20 = 3\hat{I}_0 + V_{os} + \hat{I}_0$$

$$20 = 3 \times 2.146 + V_{os} + 2.146$$

$$V_{os} = 11.416 \text{ V}$$

8(a) (i)

Generator 1

250 kW

$$\hat{I}_{FL} = \frac{250 \times 10^3}{400} = 625 \text{ A}$$

Drop in voltage at fullload

$$= 0.03 \times 400$$

$$= 12 \text{ V}$$

Generator 2


150 kW

$$\hat{I}_{FL} = \frac{150 \times 10^3}{400} = 375 \text{ A}$$

Drop in voltage at fullload

$$= 0.06 \times 400$$

$$= 24 \text{ V}$$

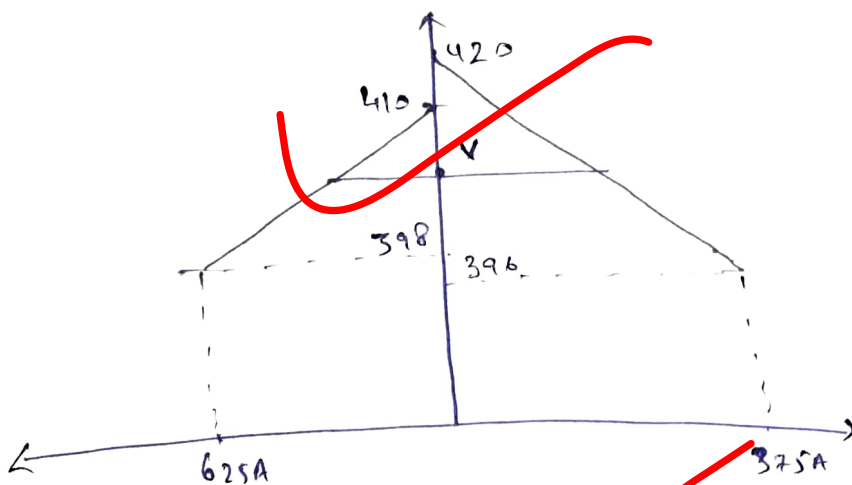

$$\Rightarrow \hat{I}_1 + \hat{I}_2 = 1000 \text{ A}$$

using slopes

$$\frac{410 - 398}{625} = \frac{410 - V}{\hat{I}_1} \Rightarrow$$

$$12 \hat{I}_1 = 256250 - 625V$$

$$625V + 12V_1 = 256250 \quad \text{--- (1)}$$

$$\frac{420 - 396}{375} = \frac{420 - V}{1000 - I_1} \Rightarrow \frac{8}{125} = \frac{420 - V}{1000 - I_1}$$

$$8000 - 8I_1 = 52500 - 125V$$

$$125V + 8I_1 = 44500 \quad \text{--- (2)}$$

Solving (1) & (2)

$$V = 397.54 \text{ Volts.} \rightarrow \text{bus voltage.}$$

$$I_1 = 649.04 \text{ A}$$

$$I_2 = 350.96 \text{ A}$$

(ii)

Assuming Let $\% \text{ drop}$ for Generator 2 (150 kW)
and No load voltage 'V'

for Proportional load sharing.

$$\frac{0.03V}{250} = \frac{V - V'}{I_1} \quad \text{--- (1)}$$

$$\frac{\% V}{150} = \frac{V - V'}{\frac{3}{5} I_1} \quad \text{--- (2)}$$

↑
for Generator 1

from (1) & (2)

$$\frac{0.03V}{250} = \frac{\% V}{150} \times \frac{3}{5}$$

$$\Rightarrow \boxed{\% = 0.03} = \underline{\underline{3\%}}$$

∴ for Proportional load sharing


these $\% \text{ drops}$ ~~are~~ should be same.

for load current of 1000 A

$$\hat{I}_2 = 375 \text{ A}$$

$$V_{NL} = V_t + \alpha V_t \\ = 400 + 0.03 \times 400$$

$$V_{NL} = 412 \text{ V}$$

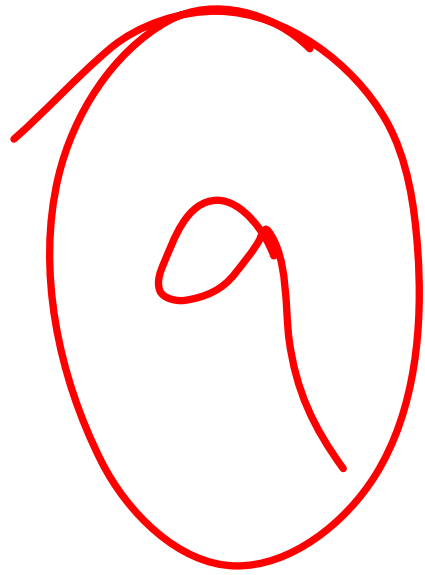

$$P = \frac{V E_f}{X_s} \sin \delta + \frac{1}{2} V^2 \left[\frac{1}{X_q} - \frac{1}{X_d} \right] \sin 2\delta$$

When $E_f = 0$, $P_{max} = 540 \text{ kW}$

$$540 \times 10^3 = \frac{1}{2} V^2 \left[\frac{1}{15.4} - \frac{1}{25.4} \right] \sin 90^\circ$$

$$V = 6499.637 \text{ Volts.}$$

$$V \approx 6.5 \text{ KV}$$

Now when excited with minimal field.


$$P = \omega T = \frac{2\pi \times 1000}{60} \times 3.5 \times 10^3$$

$$P = 366.52 \text{ KW}$$

$$P = \sqrt{3} \times V \times I_a \times \cos \phi$$

$$366.52 \times 10^3 = \sqrt{3} \times 6.5 \times I_a \times 0.8$$

$$I_a = 40.69 \text{ A}$$

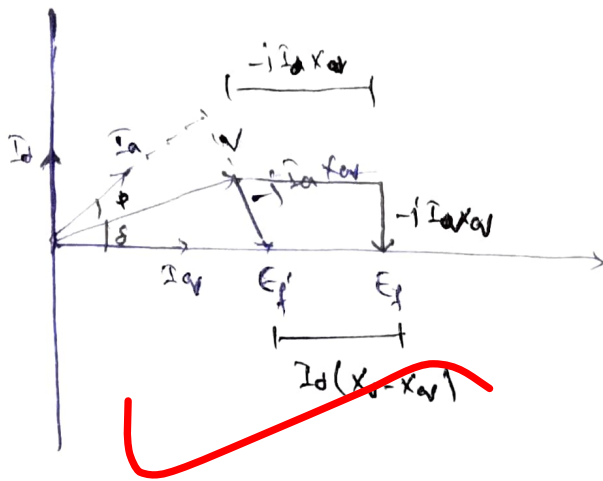

$$\psi = \phi + \delta$$

$$E_f' = V - j \hat{I}_d X_{dV}$$

$$= \frac{6.5}{\sqrt{3}} \angle 0^\circ \times 10^3 - j 1544 \times 40.69 \angle (\cos 0.8)$$

$$E_f' = 4.159 \angle -6.922 \text{ KV}$$

$$\text{Power angle } \delta = 6.922$$

$$I_d = I_a \sin \psi = 40.69 \sin (6.922 + 36.87)$$

$$= 28.159 \text{ A}$$


$$|E_f| = 4.159 + I_d (X_d - X_q)$$

$$= 4.159 + 28.159 (25.4 - 10.4) \times 10^{-3}$$

$$= 4.44 \text{ KV}$$

$$E_{f \text{ L-L}} = \sqrt{3} \times 4.44 = 7.69 \text{ KV}$$

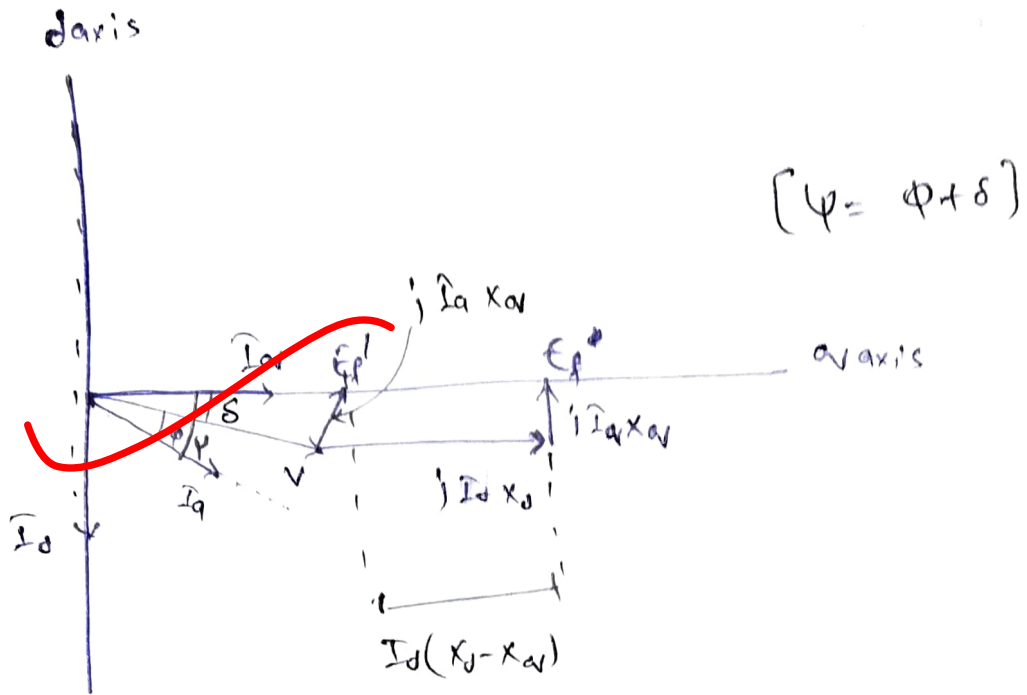(ii) Taking a synchronous machine working at lagging pf
(Alternator)



from phasor diagram.

$$I_a X_a = V \sin \delta$$

$$E_f = V \cos \delta + I_d X_d$$

$$I_d = I_a \sin \psi, \quad I_a \cos \psi = I_a \cos \phi$$

$$I_d = I_a \sin [\phi + \delta]$$

$$= I_a \sin \phi \cdot \cos \delta + I_a \cos \phi \cdot \sin \delta$$

$$I_a \cos \psi = I_a \cos \phi \cdot \cos \delta - I_a \sin \phi \cdot \sin \delta$$

$$\text{Now, } P = V I_a \cos \phi = V I_a \cos (\psi - \delta)$$

$$P = V I_a [\cos \psi \cdot \cos \delta + \sin \psi \cdot \sin \delta]$$

$$P = V I_a \cos \delta + V I_d \sin \delta$$


$$P = \frac{V \cos \delta}{X_a} I_a X_a + \frac{V I_d \sin \delta}{X_d} X_d$$

$$P = \frac{V \cos \delta}{X_d} V \sin \delta + \frac{V \sin \delta}{X_d} (E_f - V \cos \delta) \quad (\text{from phasor diagram})$$


$$P = \frac{V^2}{2 X_d} \sin 2\delta + \frac{E_f V}{X_d} \sin \delta - \frac{V^2 \cos \delta \sin 2\delta}{2 X_d}$$

$$P = \frac{E_f V}{X_d} \sin \delta + \frac{V^2}{2} \left[\frac{1}{X_d} - \frac{1}{X_d} \right] \sin 2\delta$$

Power angle Characteristics

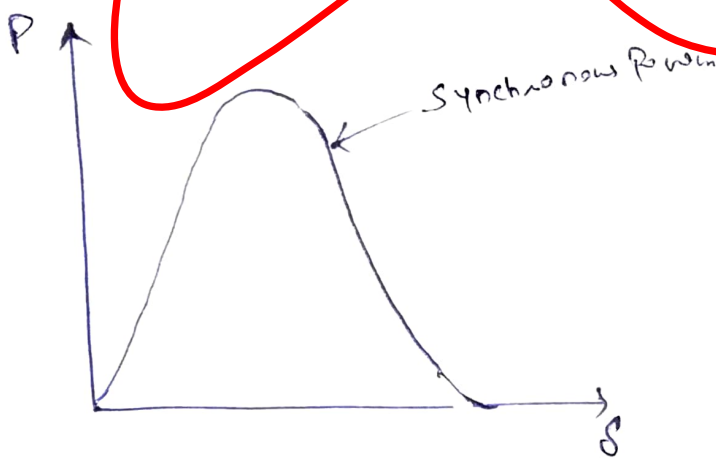

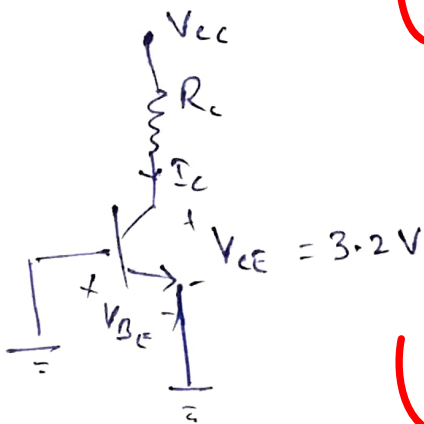8(c) (i) As $I_c = I_s e^{V_{BE}/V_T}$ (1)



$$I_c = \frac{V_{CC} - V_{CE}}{R_C} = \frac{10 - 3.2}{6.8} = 1mA$$

$$I_c = 1mA$$

using (1)


$$1 \times 10^{-3} = 10^{-15} \cdot e^{V_{BE}/25mV}$$

$$V_{BE} = 690.77 mV \approx 0.69V$$

(ii)

$$g_m = \frac{I_c}{V_T} = \frac{1}{25} \text{ S}$$

$$r_{\pi} = \beta / g_m$$

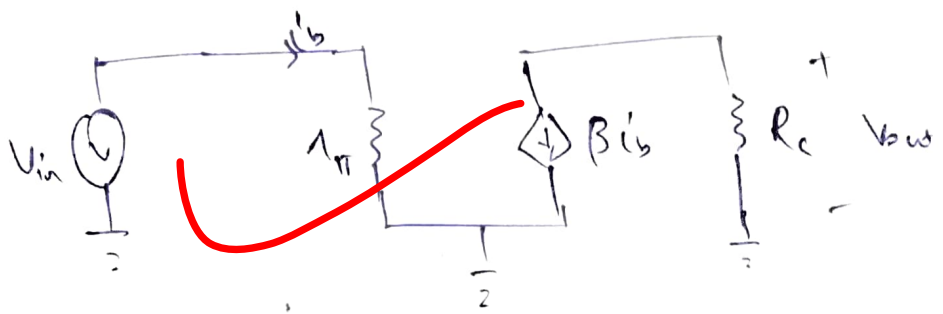

$$V_{out} = -\beta i_b R_c$$

$$V_{in} = r_{\pi} i_b$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{-\beta R_c i_b}{r_{\pi} i_b} = \frac{-\beta R_c g_m}{\beta} = -g_m R_c$$

$$= -\frac{1}{25} \times 6.8 \times 10^3$$

$A_v = -272$

$$[V_{out \text{ peak}}] = \cancel{272} \times A_v \times V_{in} = 272 \times 5 \times 10^{-3}$$

$V_{out \text{ peak}} = 1.36 \text{ Volts.}$

(iii)

$$V_{CE} = 0.3$$

$$I_c = \frac{V_{CC} - V_{CE}}{R_c} = \frac{1 - 0.3}{6.8} = 1.426 \text{ mA}$$

Using ①

$$1.426 \times 10^{-3} = 10^{-15} \times e^{V_{BE}/25\text{mV}}$$

$$V_{BE} = 699.64 \text{ mV}$$

$$\Delta V_{BE} = 699.64 - 690.77$$

$$\Delta V_{BE} = 8.877 \text{ mV}$$

19