

Name -

Roll No -

Test No -

Full Syllabus (Paper-1)

Section-A

Qus - (1) (a)

Solution → In a Semiconductor Sample,

Concentration of electron

$$n = N_c e^{-(E_c - E_F)/KT}$$

Conc. of hole, $(P) = N_v e^{-(E_F - E_v)/KT}$

from the law of mass action,

$$np = n_i^2 \quad \text{where } n_i \text{ is intrinsic}$$

$$\therefore N_c N_v e^{-(E_c - E_F + E_F - E_v)/KT} = n_i^2$$

$$n_i^2 = N_c N_v e^{-E_g/KT}$$

$$\text{where } N_c = 2 \left(\frac{2\pi m_n \bar{K}T}{h^2} \right)^{3/2}$$

$$N_v = 2 \left(\frac{2\pi m_p \bar{K}T}{h^2} \right)^{3/2}$$

$$\therefore n_i^2 = \sqrt{A_0} T^3 e^{-E_g/KT}$$

where A_0 is material constant.

$$\therefore n_i = \sqrt{A_0} T^{3/2} e^{-E_g/2KT}$$

Take log on both sides,

$$\log n_i = \log \sqrt{A_0} + \log T^{3/2} + \log e^{-E_g/2KT}$$

Differentiating with respect to T (Temperature)

$$\frac{1}{n_i} \frac{dn_i}{dT} = 0 + \frac{3}{2T} - \frac{E_{g0}}{2k} \left(\frac{-1}{T^2} \right)$$

$$\frac{1}{n_i} \frac{dn_i}{dT} = \frac{3}{2T} + \frac{E_{g0}}{2kT^2}$$

$$\left(\frac{dn_i}{n_i} \right) \frac{1}{dT} = \frac{3}{2T} + \frac{E_{g0}}{2kT^2}$$

for every 1°c rise in temperature,
% rise in intrinsic carrier conc. is given by.

$$\left(\frac{dn_i}{n_i} \right) \times 100 = \left(\frac{3}{2 \times 300} + \frac{1.2}{2 \times 8.6 \times 10^{-5} \times (300)^2} \right) \times 100\%$$

$$\therefore \frac{dn_i}{n_i} \times 100 = 0.0825 \times 100$$

\therefore % Increase in Intrinsic carrier Conc. /°c rise = 8.25% * Ans.

Qus - (1) d.

Solution -

Critical magnetic field
for a superconductor

$$H_c \text{ at } 4\text{K} \quad H_c(4\text{K}) = 0.02 \text{ T.}$$

$$\& \quad H_c \text{ at } 3\text{K}, \quad H_c(3\text{K}) = 0.03 \text{ T.}$$

We have to calculate

$$H_c \text{ at } 2\text{K} \quad \text{i.e. } H_c(2\text{K}) = ?$$

for Superconductors, critical magnetic field & Temperature
are related as

$$H_c = H_0 \left[1 - \left(\frac{T}{T_c} \right)^2 \right]$$

$$0.02 = H_0 \left(1 - \left(\frac{4}{T_c} \right)^2 \right) \quad \text{--- (1) Given}$$

$$\text{or } 0.03 = H_0 \left(1 - \left(\frac{3}{T_c} \right)^2 \right) \quad \text{--- (2) Given}$$

Put $\frac{1}{T_c} = x$ we have,

$$H_0 [1 - 16x^2] = 0.02 \quad \text{--- (1.1)}$$

$$\text{or } H_0 [1 - 9x^2] = 0.03 \quad \text{--- (2.1)}$$

Dividing, $\frac{1 - 16x^2}{1 - 9x^2} = \frac{2}{3}$

$$3 - 48x^2 = 2 - 18x^2$$

$$1 = 30x^2$$

$$\therefore \boxed{x^2 = \frac{1}{30}}$$

$$\text{ie } \boxed{\frac{1}{T_c^2} = \frac{1}{30}}$$

from (1.1), $H_0 = \frac{0.02}{1 - 16x^2}$

Put in (2.1)

$$\frac{0.02 (1 - 9x^2)}{(1 - 16x^2)} = 0.03$$

Put $x^2 = \frac{1}{30}$ in eqn (1.1) to get H_0

$$\therefore H_0 \left[1 - \frac{16}{30} \right] = 0.02$$

$$\therefore H_0 = \frac{0.02}{\left(1 - \frac{16}{30} \right)} = 0.04286 \text{ T}$$

\therefore Critical magnetic field at Temp 2 K


$$H_c(2) = 0.04286 \left[1 - 2^2 \times \frac{1}{30} \right]$$

$$\boxed{H_c(2) = 0.03714 \text{ Tesla}}$$

Ans.

Ques - 1(e)

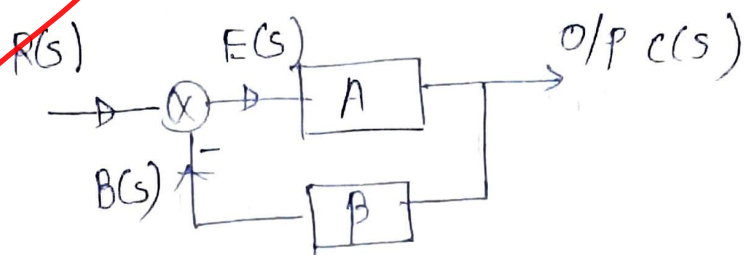Solution - Consider a block Diagram of feedback amplifier with open loop gain A & feedback factor β as shown



$$\frac{C(s)}{E(s)} = A$$

$$\frac{B(s)}{E(s)} = A\beta$$

$$E(s) = R(s) - B(s)$$

$$E(s) + B(s) = R(s)$$

$$E(s) + A\beta E(s) = R(s)$$

$$E(s) [1 + A\beta] = R(s)$$

from (1) Put $E(s) = \frac{C(s)}{A}$

$$\therefore \frac{C(s)}{A} [1 + A\beta] = R(s)$$

$$\therefore \boxed{\frac{C(s)}{R(s)} = A_f = \frac{A}{1 + A\beta}} \quad \text{--- (A)}$$

Sensitivity of feedback amplifier is defined as Quantitative measure of change in gain of f/b amplifier due to internal parameter variation either due to temperature or due to component ageing. Mathematically

$$S_{A_f}^A = \frac{dA_f/A_f}{dA/A} = \frac{dA_f}{dA} \cdot \frac{A}{A_f}$$

from eqn (A) Differentiate (A) w.r.t A.

$$\frac{dA_f}{dA} = \frac{(1 + A\beta) - A\beta}{(1 + A\beta)^2} = \frac{1}{(1 + A\beta)^2}$$

$$\therefore \frac{A}{A_f} = (1 + A\beta)$$

$$\therefore \frac{dA_f/A_f}{dA/A} = \frac{1}{(1+A\beta)^2} \times (1+A\beta) = \frac{1}{(1+A\beta)}$$

$$\therefore \boxed{\frac{dA_f}{A_f} = \left(\frac{1}{1+A\beta} \right) \frac{dA}{A}}$$

Proved

where A is gain of feedback amplifier
 β is feedback gain,

Given $A = 1000 \pm 100$

$$\therefore \frac{dA_f}{A_f} = \pm \frac{0.1}{100}$$

$$\frac{dA}{A} = \frac{100}{1000} = \frac{1}{10}$$

\therefore Put in derived eqⁿ we have,

$$\frac{0.1}{100} = \frac{1}{1+1000\beta} \times \frac{1}{10}$$

$$1+1000\beta = 100$$

$$\therefore \beta = \frac{100-1}{1000} = \frac{99}{1000}$$

$$\boxed{\beta = 0.099}$$

ie 9.9% feedback required.

Ans.



Ques-1(b)
Solution-

$$V_{rms} = 8$$

$$\frac{V_m}{\sqrt{2}} = 8V$$

$$\therefore V_m = 8\sqrt{2} \text{ volt}$$

O/P of HWR is

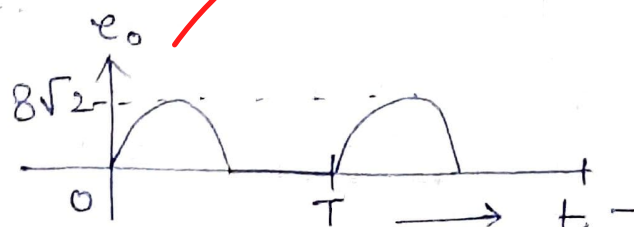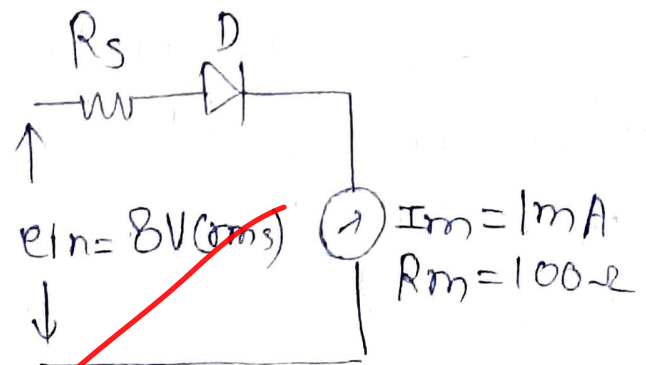

Since voltmeter is PMMC Type Instrument that measures avg. value.

Therefore, average value of waveform,

$$V_{avg} = \frac{V_m}{\pi} = \frac{8\sqrt{2}}{\pi}$$

Value of multiplier (m) given by


$$m = \frac{V_{avg}}{V_m} = \frac{8\sqrt{2}/\pi}{100 \times \frac{1}{1000}}$$

$$\therefore m = \frac{8\sqrt{2}}{\pi} \times 10 = 36$$

$$\boxed{m = 36}$$

$$\therefore R_s (\text{multiplier Resistance}) = R_m (m-1) = 100 (36-1) = 3.5 \text{ k}\Omega$$
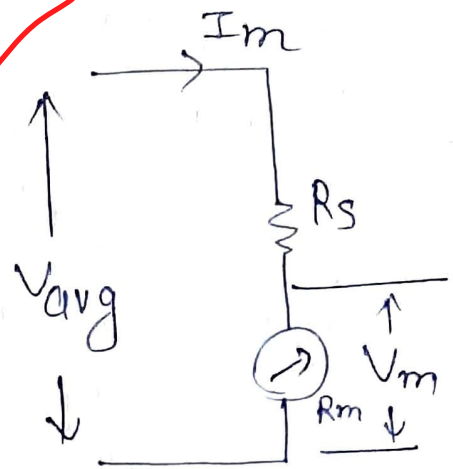
$$\boxed{R_s = 3.5 \text{ k}\Omega} \quad \leftarrow \text{Ans.}$$



Qus-1(c)


Solution-

Consider a PN junction

Under Forward bias condition,

Emitter injection efficiency is defined as Ratio of electron current crossing the junction to total current, i.e.
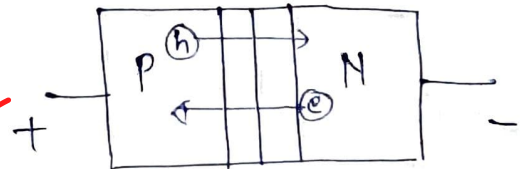
$$\gamma = \frac{I_{NE}}{I_{NE} + I_{PE}} = \frac{1}{1 + \frac{I_{PE}}{I_{NE}}}$$



where, I_{pE} denotes hole current crossing the JE from P to N side, which is diffusion current.

$$I_{pE} = -A \cdot e D_p \frac{d p(x)}{dx}$$

where, $p_n(x) = p_{n0} + \Delta p e^{-x/L_p}$.

$$\frac{d p_n(x)}{dx} = 0 + \frac{\Delta p}{L_p} e^{-x/L_p}$$

$$\text{at } x=0 \quad \frac{d p_n(0)}{dx} = \frac{-\Delta p}{L_p}$$

$$\text{where } \Delta p = p_n(0) e^{V_D/V_T} = \frac{n_i^2}{N_D} e^{V_D/V_T}$$

similarly, $\frac{d n_p(0)}{dx} = \frac{n_i^2}{N_A} e^{V_D/V_T}$

$$\therefore \frac{I_{pE}}{I_{nE}} = \frac{A e D_p n_i^2 e^{V_D/V_T} \times N_A \cdot L_N}{A e D_n N_D \cdot n_i^2 e^{V_D/V_T} \times L_p}$$

where L_N & L_p are diffusion length,

$$\therefore \frac{I_{pE}}{I_{nE}} = \frac{D_p N_A L_N}{D_n N_D L_p} \frac{\omega_p \times N_A \times \sqrt{\frac{\tau_n}{\epsilon_p}} \times \sqrt{\frac{\omega_n}{\epsilon_p}}}{\omega_n \times N_D}$$

$$\frac{I_{pE}}{I_{nE}} = \frac{N_A}{N_D} \times \sqrt{\frac{\tau_n}{\epsilon_p}} \times \sqrt{\frac{\omega_p}{\epsilon_n}}$$

$$\therefore \gamma = \frac{1}{1 + \frac{N_A}{N_D} \times \sqrt{\frac{\tau_n}{\epsilon_p}} \times \sqrt{\frac{\omega_p}{\epsilon_n}}} = \frac{1}{1 + \frac{N_A}{N_D} \sqrt{10} \times \frac{1}{\sqrt{2.4}}}$$

$$\gamma = \frac{1}{1 + \frac{N_A}{N_D} \times \sqrt{\frac{10}{2.4}}} = \frac{1}{\left(1 + 2.04 \frac{N_A}{N_D}\right)}$$

$$\boxed{\gamma = \frac{1}{1 + 2.04 \frac{N_A}{N_D}}}$$

← Ans.

Ques-4(a)(1)


Solution- Given,

Identical Diodes D_1 & D_2

$\eta = 1$ $V_\gamma = 0.6$ V, $V_T = 26$ mV.

$I_0 = 2 \times 10^{-13}$ A. at 300K

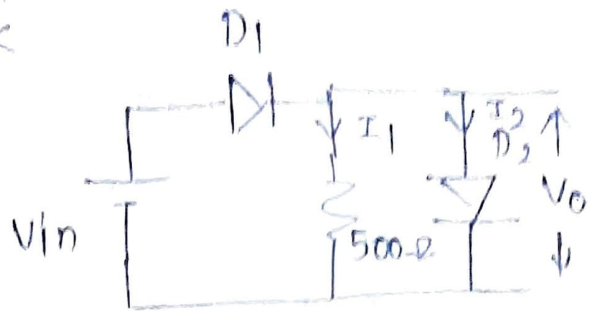We have to calculate V_{in}
when $V_0 = 600$ mV.




$I_2 = I_0 e^{V_{D2}/V_T}$

$\therefore D_2$ will conduct as $V_0 = V_\gamma = 0.6$ volt.

$\therefore I_2 = I_0 e^{V_{D2}/V_T}$

$I_2 = 2 \times 10^{-13} e^{0.6/26 \times 10^{-3}}$

$I_{D2} = 2.105$ mA.

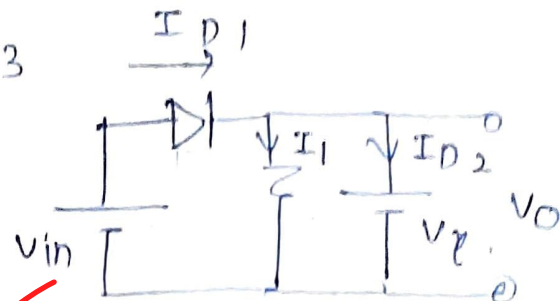

$I_1 = \frac{V_0}{500} = \frac{0.6}{500} = 1.2$ mA.

$\therefore I_{D1} = I_1 + I_{D2} = 1.2 + 2.105 = 3.305$ mA.

$I_{D1} = 3.305$ mA

Now, $V_{D1} = V_{in} - 0.6$

$I_{D1} = I_0 e^{V_{D1}/V_T}$

$3.3 \times 10^{-3} = 2 \times 10^{-13} e^{V_{D1}/26 \times 10^{-3}}$

$\therefore V_{D1} = \frac{23.528 \times 26}{1000} = 0.612$ volt

i.e. $V_{in} - 0.6 = 0.612$

$\therefore V_{in} = 1.212$ V

Ans.

Qus-4(a)(ii)

Solution -

Given,

$$f_0 = 50 \text{ Hz}$$

$$V_{\text{rms}} = 100 \text{ V}$$

$$\text{Capacitor (C)} = 50 \mu\text{F}$$

$$I_{\text{DC}} = 50 \text{ mA}$$

Ripple factor of Full wave Rectifier is given by,

$$\alpha = \frac{V'_{\text{rms}}}{V_{\text{avg}}}$$

$$V'_{\text{rms}} = \frac{V_{\text{mrr}}}{2\sqrt{3}} \quad \text{where } V_{\text{mrr}} \text{ is peak to peak o/p Ripple}$$

$$V_r = \frac{I_{\text{DC}}}{f_0 C}$$

$$\frac{I_{\text{DC}} T_0}{2} = C V_r$$

$$\therefore V_r = \frac{I_{\text{DC}}}{2 f_0 C}$$

$$\therefore \alpha = \frac{1}{4\sqrt{3} f_0 C R_L}$$

where $R_L = \frac{V_{\text{DC}}}{I_{\text{DC}}}$

$$V_{\text{DC}} = V_m - \frac{I_{\text{DC}}}{2 f_0 C} = 100\sqrt{2} - \frac{50 \times 10^{-3}}{4 \times 50 \times 10^{-6} \times 50}$$
$$= 100\sqrt{2} - 5 = 136.42 \text{ VOLT}$$

$$\therefore R_L = \frac{V_{\text{DC}}}{I_{\text{DC}}} = \frac{136.42}{50 \times 10^{-3}} = 2.728 \text{ K}\Omega$$

Now, ripple factor,

$$\alpha = \frac{1}{4\sqrt{3} f_0 C R_L} = \frac{10^6}{4\sqrt{3} \times 50 \times 50 \times 2.728 \times 10^3}$$

$$\alpha = 0.0212$$

$$\text{or } \underline{\underline{2.12\%}}$$

Ques-4 (b)

Solution-

accuracy of voltmeter = $\pm 1\%$ of FSD

$$\text{i.e. } \frac{\Delta V}{V} \times 100 = 1$$

$$\therefore \frac{\Delta V}{V} = \frac{1}{100}$$

Since, voltmeter reads 100V on its 150V Range.

$$\text{i.e. } V_{\text{FSD}} = 150\text{V}$$

$$\therefore \frac{\Delta V}{150} = \frac{1}{100}$$

$$\therefore \Delta V = \frac{150}{100} = 1.5$$

\therefore Limiting error in measuring 100V.

$$\frac{\Delta V}{V_m} = \frac{1.5}{100} = 0.015$$

Similarly accuracy of ammeter = $\pm 1\%$ FSD

$$\text{i.e. } \frac{\Delta I}{I} = \frac{1}{100}$$

$$\therefore \Delta I = \frac{100}{100} = 1\text{mA}$$

Since, ammeter reads 50mA on its 100mA Range

Limiting error in measuring 50mA.

$$\frac{\Delta I}{I_m} = \frac{1}{50} = 0.02$$

Calculation of Power, $P = VI$.

Take log on both sides

$$\log P = \log V + \log I$$

Differentiating,

$$\frac{1}{P} dP = \frac{dV}{V} + \frac{dI}{I}$$

$$\text{or } \left| \frac{\Delta P}{P} = \frac{\Delta V}{V} + \frac{\Delta I}{I} \right|$$

∴ limiting error in Power Calculation,

$$\frac{\Delta P}{P} = \frac{\Delta V}{V} + \frac{\Delta I}{I} = 0.015 + 0.02$$

$$\frac{\Delta P}{P} = 0.035$$

Absol. Relative limiting error

$$\therefore \Delta P = 0.035 \times P$$

where $P = VI = \frac{100 \times 50}{1000} = 5 \text{ watt}$

$$\therefore P = P_0 \pm \Delta P$$

$$P = (5 \pm 0.175) \text{ watt}$$

∴ Relative limiting error = $\frac{\Delta P}{P} \times 100 = 3.5\%$

Ans.:

Ques-4 (c)

$$N_D = 10^{19} / \text{cm}^3$$


$$N_A = 10^{16} / \text{cm}^3$$

$$\tau_n = \tau_p = 10^{-6} \text{ sec}$$

$$L_n = L_p = 500 \mu\text{m}$$


$$L \gg x_n, x_p$$
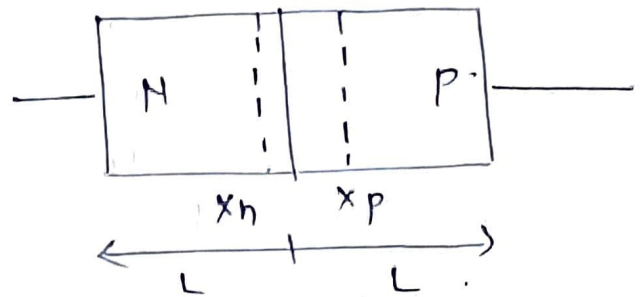
$$T = 300 \text{ K}, \quad \mu_n = 1248 \text{ cm}^2/\text{V}\cdot\text{s}, \quad n_i = 10^{10} / \text{cm}^3$$



Current density at $x=0$

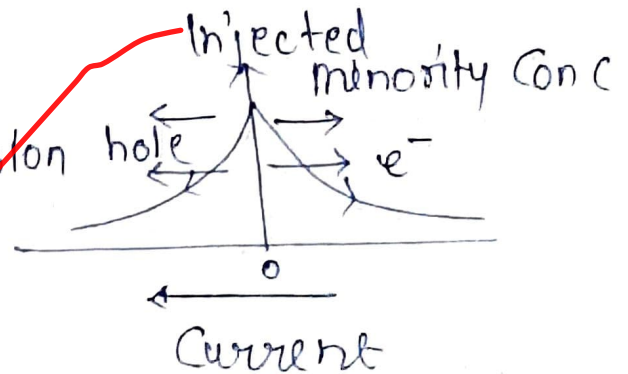is sum of hole & e^- diffusion current densities.



$$P_n(x) = P_{n0} + \Delta P e^{-x/L_p}$$

$$\frac{dP_n(x)}{dx} \Big|_{x=0} = 0 + \left(\frac{-\Delta P}{L_p} \right) = -\frac{n_i^2}{L_p \times N_D} e^{V_0/V_T}$$

∴ forward current density

$$J_F = q n i^2 \left[\frac{D_p}{L_p N_D} + \frac{D_n}{L_n N_A} \right] (e^{V_D/V_T} - 1)$$

$$L_p = \sqrt{D_p \tau_p} = \sqrt{\mu_p V_T \tau_p}$$

$$L_n = \sqrt{D_n \tau_n} = \sqrt{\mu_n V_T \tau_n} = \sqrt{1248 \times 0.026 \times 10^{-6}}$$

$$= 5.696 \times 10^{-3} \text{ cm}$$

$$\therefore 1.5 \times 10^{-6} = 1.6 \times 10^{-19} \times 10^{20} (e^{V_D/0.026}) \left[\frac{1248 \times 0.026}{5.696 \times 10^{-3} \times 10^6} \right]$$

neglecting $\frac{D_p}{L_p N_A}$ term as $N_A \gg N_D$

$$1.5 \times 10^{-6} = 1.6 \times 10^{-19} \times 10^{20} \times 5.6966 \times 10^{-13} e^{V_D/0.026}$$

$$\therefore e^{V_D/V_T} = \frac{1.5 \times 10^{-6}}{1.6 \times 5.69663 \times 10^{-13}} = 164571.006$$

Take natural log, on both sides

$$\frac{V_D}{V_T} = 12.01 \text{ volt}$$

$$\therefore V_D = 0.3123 \text{ mV}$$

(ii) $J = J_0 e^{V_D/V_T}$

$$J = K e^{-E_g/KT} \cdot e^{V_D/V_T}$$

Take log on both sides

$$\log J = \log K - \frac{E_g}{KT} + \frac{V_D}{V_T} = \log K - \frac{E_g}{KT} + \frac{K' V_D}{T}$$

Differentiating w.r.t T


$$\frac{1}{J} \times \frac{dJ}{dT} = 0 + \frac{E_g}{KT^2} - \frac{11600 V_D}{T^2}$$

Given, T is constant
ie $\frac{\partial T}{\partial T} = 0$.

$$\text{ie } \frac{E_g}{kT^2} = \frac{11600}{T^2}$$

$$\therefore V_D = \frac{E_g}{11600 \times K} = \frac{1.12 \times 1.6 \times 10^{-19}}{11600 \times 8.6 \times 10^{-5}}$$
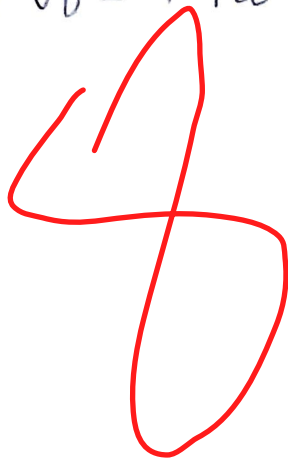
$$\therefore V_D = 1.12 \text{ volt}/^\circ\text{K} \quad \# \text{ Ans}$$



Section-B

Qus-5(a)

Solution→

Given,

No. of e^- /sec carried in a
Picture Tube = 10^{15} e^- /sec.

$$\therefore \text{Current } I = \frac{Ne}{t}$$

$$\text{i.e. } I = 10^{15} \times 1.6 \times 10^{-19}$$

$$I = 1.6 \times 10^{-4} \text{ Amp.}$$

Let Voltage Required be V_0
such that to accelerate beam to
achieve Power of 5 Watt.

$$\text{therefore, } V_0 I = P$$

$$V_0 I = 5$$

$$\therefore V_0 = \frac{5}{1.6 \times 10^{-4}} = \frac{50}{1.6} \text{ kVolt}$$

$$\boxed{V_0 = 31.25 \text{ Kv}} \quad \text{-Ans.}$$

Qus 5(c)

Solution-

Given,

Series-shunt feedback.

open loop gain = 10^5 .

close loop gain = 50.

Input Resistance of Amp^r

without feedback $R_i = 20 \text{ k}\Omega$

o/p Resistance of Amp^r

without feedback = $40 \text{ k}\Omega$.

We have to calculate Input & output Resistance of amplifier with feedback.

for Series-shunt feedback. since f/B N/w is connected in shunt with load (Voltage sampling) & f/B N/w is connected in series with signal source i.e. Voltage mixing.

$$\therefore R_{if} = R_i (1 + A\beta)$$

$$\& R_{of} = \frac{R_o}{(1 + A\beta)}$$

for feedback amplifier,

$$A_{CL} = \frac{A}{1 + A\beta}$$

$$\therefore (1 + A\beta) = \frac{A}{A_{CL}} = \frac{10^5}{50} = \frac{100 \times 10^3}{50} = 2000$$

$$1 + A\beta = 2000$$

$$\therefore R_{if} = 20 \text{ k}\Omega \times 2000$$

$$R_{if} = 40 \text{ M}\Omega \quad \leftarrow \text{Ans}$$



$$\& R_{of} = \frac{40 \times 1000}{2000} = 20 \Omega$$

$$R_{of} = 20 \Omega \quad \leftarrow \text{Ans}$$

Qus-5(b) Given Network

Solution-

from Star-delta Transformation, we have

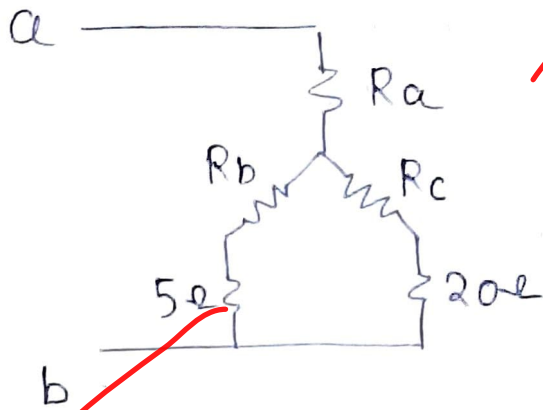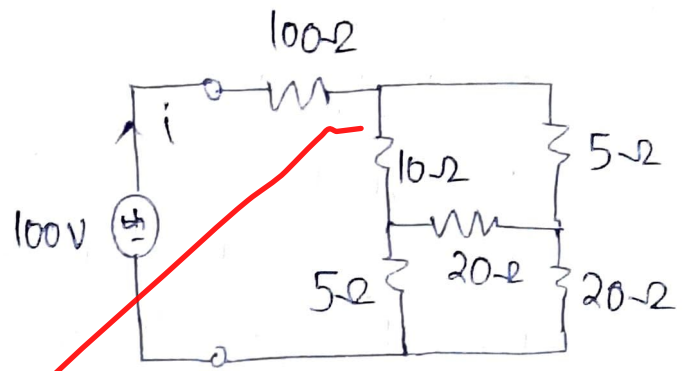

where

$$R_a = \frac{10 \times 5}{10 + 20 + 5} = \frac{50}{35} \Omega$$

$$R_b = \frac{10 \times 20}{10 + 20 + 5} = \frac{200}{35} \Omega$$

$$R_c = \frac{20 \times 5}{35} = \frac{100}{35} \Omega$$

$$R_{eq} = [(R_b + 5) \parallel (R_c + 20)] + R_a$$

$$R_b + 5 = \frac{200}{35} + 5 = \frac{375}{35} \Omega = 10.714 \Omega$$

$$(R_c + 20) = \frac{100}{35} + 20 = \frac{800}{35} \Omega = 22.857 \Omega$$

$$\therefore (R_b + 5) \parallel (R_c + 20) = \frac{1}{\left(\frac{35}{375} + \frac{35}{800}\right)} = 7.295 \Omega$$

$$\therefore R_{ab} = \frac{50}{35} + 7.295 = 8.723 \Omega$$

$$R_{ab} = 8.723 \Omega$$

← Ans

$$\text{Current (i)} = \frac{V_{ab}}{R_{ab}} = \frac{100}{8.723} = 11.46 \text{ Amp}$$

$$i = 11.46 \text{ amp}$$

← Ans

Ques-5(e)

Given,

$$E_2 I_2 = E_1 I_1 = 50 \text{ kVA}$$

$$E_1 / E_2 = 2000 / 200$$

$f = 50 \text{ Hz}$ Transformer

$$\text{Iron loss } (W_I) = 400 \text{ W}$$

$$\text{Primary winding Resistance} = 0.6 \Omega (R_1)$$

$$\text{Secondary winding Resistance} = 0.006 \Omega (R_2)$$

Total equivalent Resistance w.r.t 2^ory side

$$R_{02} = R_2 + R_1'$$

$$R_{02} = R_2 + \left(\frac{I_1}{I_2}\right)^2 R_1 = R_2 + \left(\frac{N_2}{N_1}\right)^2 R_1$$

$$\frac{N_2}{N_1} = \frac{200}{2000} = \frac{E_2}{E_1} = \frac{1}{10}$$

$$\therefore R_{02} = 0.006 + \frac{0.6}{100} = 0.012 \Omega$$

$$\boxed{R_{02} = 0.012 \Omega}$$

$$I_2 = \frac{50 \times 10^3}{200} = 250 \text{ amp}$$

$$\therefore \text{Total FL Cu loss} = I_2^2 R_{02} = 250^2 \times 0.012$$

$$\boxed{W_{FL \text{ cu}} = 750 \text{ watt}}$$

Transformer efficiency,

$$\eta \% = \frac{x E_2 I_2 \cos \theta_2}{(x E_2 I_2 \cos \theta_2 + x^2 W_{FL \text{ cu}} + W_I)} \times 100 \%$$

$$\eta \% = \frac{0.5 \times 50 \times 10^3 \times 0.8}{0.5 \times 50 \times 10^3 \times 0.8 + 0.5^2 \times 750 + 400} = \frac{20,000}{20587.5}$$

$$\boxed{\eta \% = 97.146 \%}$$

← Ans.


Qus-5(d)

Solution-


Design of SR-Flif-flop using NMOS-

Gate Level Designing - (SR f/f)


using NAND Latch-

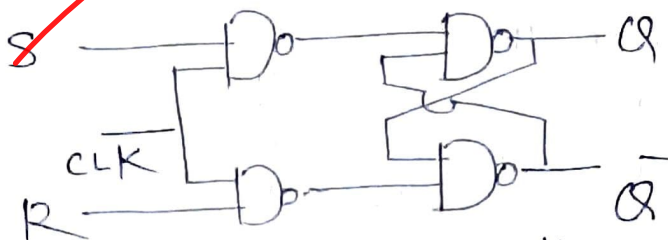

Implementation of NAND Gate using NMOS-

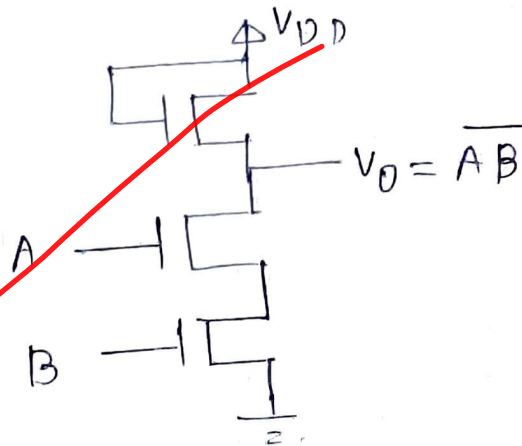

Therefore Implementing SR f/f using NMOS

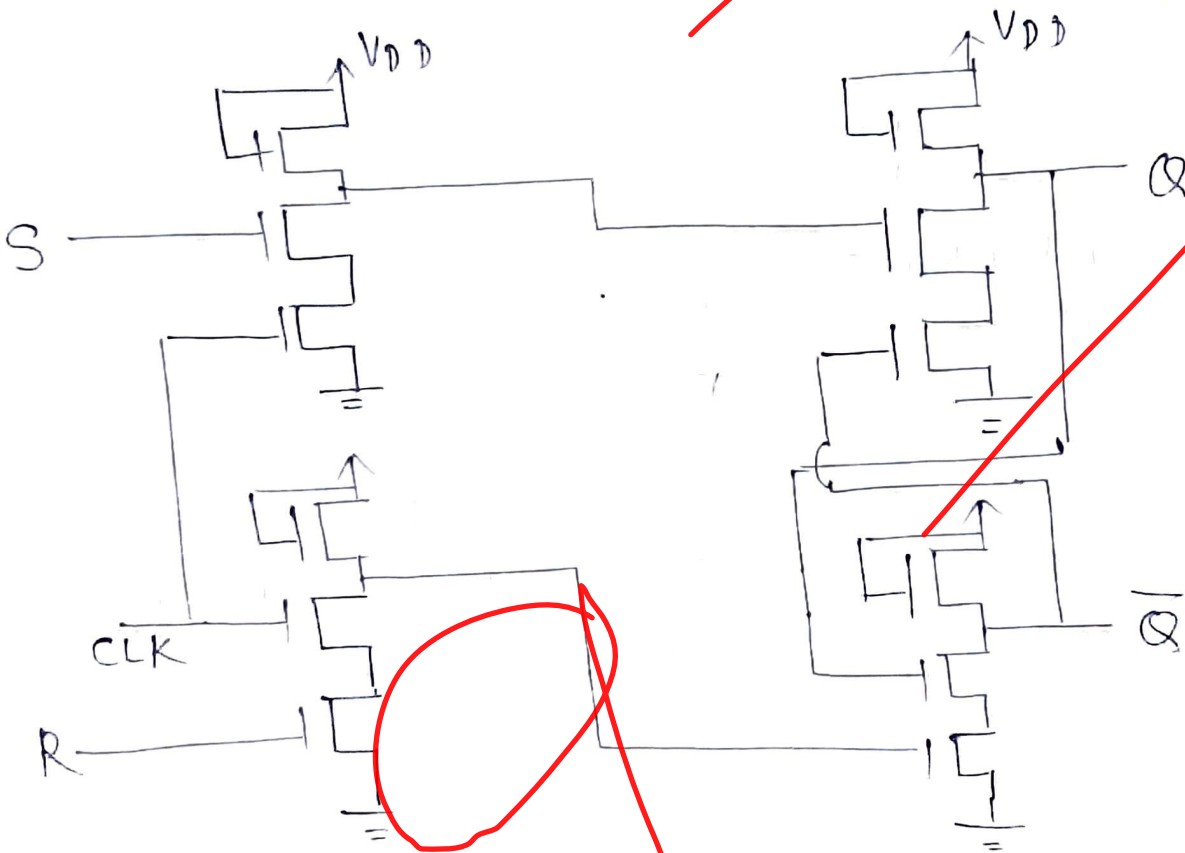

+ Ans.

Ques-6 (d)


Solution-

$F(A, B, C, D) = \sum m(0, 1, 3, 6, 8, 10, 12, 14)$
Implementing $F(A, B, C, D)$ using 8-to-1 multiplexer
needs 3 selection lines. Let A, B, C be the
selection lines,

A	B	C	D	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

	I_0	I_1	I_2	I_3	I_4	I_5	I_6	I_7
\bar{D}	0	2	4	6	8	10	12	14
D	1	3	5	7	9	11	13	15
	1	\bar{D}	0	\bar{D}	\bar{D}	\bar{D}	\bar{D}	\bar{D}

Implementation using mux-

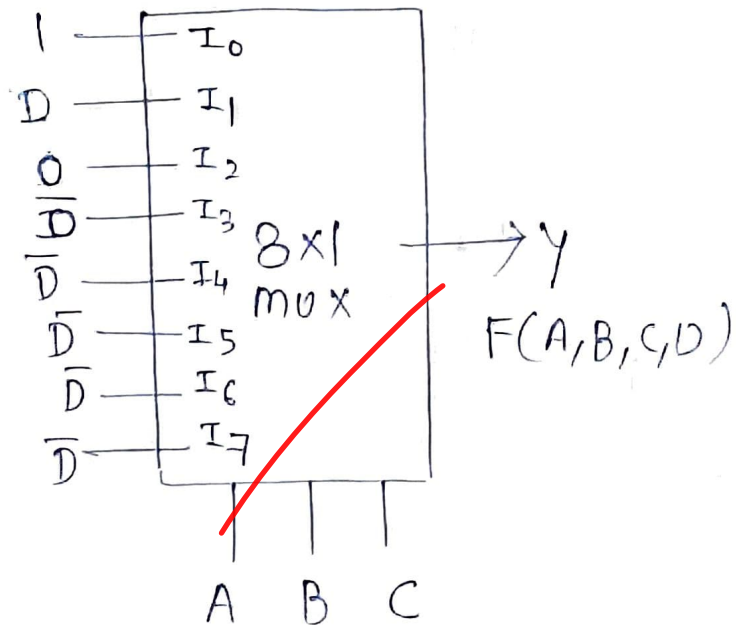


Ans-

Qus-6 (b)

Solution →

h-parameter equations,

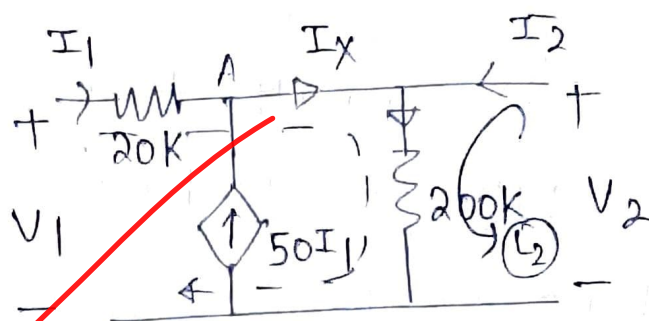

$$\begin{aligned} V_1 &= h_{11} I_1 + h_{12} V_2 \\ I_2 &= h_{21} I_1 + h_{22} V_2 \end{aligned}$$

apply KCL at Node A.

$$I_1 + 50I_1 = I_x$$

$$I_{200K} = I_x + I_2$$

$$\therefore I_x = 51I_1$$

apply KVL in Loop shown

$$V_1 = 20 \times 10^3 I_1 + 200 \times 10^3 (51I_1 + I_2)$$

$$V_1 = 20 \times 10^3 I_1 + 10,200 \times 10^3 I_1 + 200 \times 10^3 I_2$$

$$V_1 = 10,220 \times 10^3 I_1 + 200 \times 10^3 I_2 \quad \text{--- (1)}$$

8 KVL in Outer Loop (2)

$$V_2 = 200 \times 10^3 (51I_1 + I_2)$$

$$V_2 = 10,200 \times 10^3 I_1 + 200 \times 10^3 I_2 \quad \text{--- (2)}$$

from (2)

$$200 \times 10^3 I_2 = -10,200 \times 10^3 I_1 + V_2$$

$$\therefore I_2 = -51I_1 + (0.005 \times 10^{-3}) V_2 \quad \text{--- (3)}$$

Put I_2 in eqn (1).

$$V_1 = 10,220 \times 10^3 I_1 + 200 \times 10^3 (-51I_1 + 0.005 \times 10^{-3}) V_2$$

$$V_1 = (10,220 - 10,200) \times 10^3 I_1 + V_2$$

$$V_1 = 20 \times 10^3 I_1 + V_2 \quad \text{--- (4)}$$

from eqn (3) & (4)

Comparing with standard h-parameter equation, we have


$$\begin{bmatrix} h_{11} = 20 \times 10^3 \Omega \\ h_{21} = -51 \end{bmatrix}$$

$$h_{12} = 1$$

$$h_{22} = 0.005 \times 10^{-3} \Omega$$

← Ans.

Ques-6(a)
Solution:-

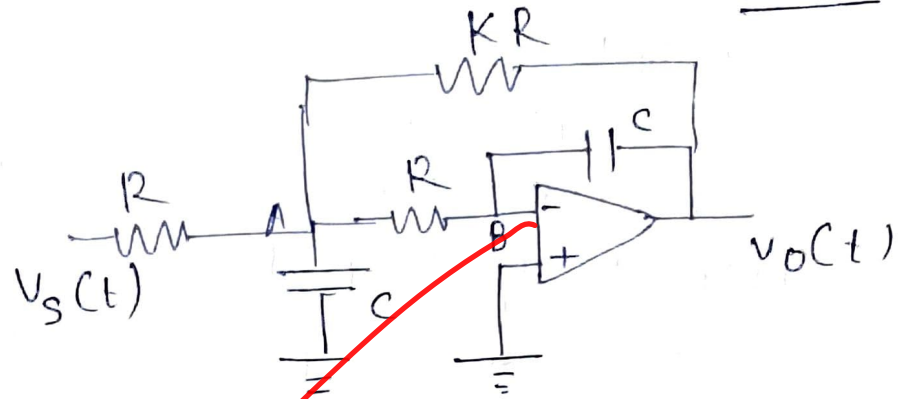

from virtual Ground Concept

$$V_B = 0$$

apply KCL at B

$$\frac{V_B - V_A}{R} = \frac{V_B - V_O(s)}{1/Cs}$$

$$\therefore V_A = RCs V_O(s) \quad \text{--- (1)}$$

apply KCL at Node A,

$$\frac{V_A}{R} + \frac{V_A - V_S}{R} + \frac{V_A}{1/Cs} + \frac{V_A - V_O}{KR} = 0$$

$$\frac{2V_A}{R} + V_A(Cs) + \frac{V_A}{KR} - \frac{V_O}{KR} = \frac{V_S}{R} \quad \text{--- (2)}$$

Put $V_A = RCs V_O(s)$ in eqn (2)

$$\frac{2RCs V_O(s)}{R} + RC^2s^2 V_O(s) + \frac{RCs V_O(s)}{KR} - \frac{V_O}{KR} = \frac{V_S}{R}$$

$$V_o(s) \left[2sC + R(cs)^2 + \frac{cs}{k} - \frac{1}{kR} \right] = \frac{V_s}{R}$$

$$V_o(s) \left[\frac{(2kRC)s + k(RC)^2 s^2 + (RCs) - 1}{kR} \right] = \frac{V_s}{R}$$

$$\frac{V_o(s)}{V_i(s)} = \frac{k}{s^2(kR^2C^2) + s(RC - 2kRC) - 1}$$

when frequency is high.

i.e. $\omega \rightarrow \infty$

$\frac{1}{sC} = \frac{1}{j\omega C}$ will be shortcircuited

\therefore ckt will have o/p zero.

i.e. they are blocking Highfreq.

when freq is Low.

then $\frac{1}{sC} \rightarrow \infty$ i.e. (o/c)

then ckt will act as.

Inverting amplifier.

So they allow lower frequency.

\therefore ckt will be passing lower freq. & blocking higher freq.

Hence, it acts as Low Pass filter.



(ii) $R = 10k\Omega,$

$C = 1\mu F$

$V_s(t) = 10 \sin(t)$

$k = 1$

We have to find $V_o(t)$.

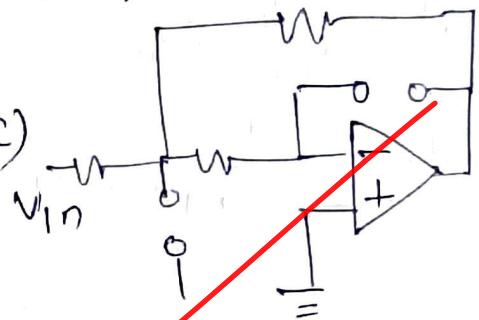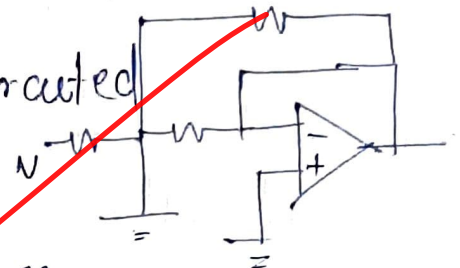

$$V_1(s) = L[V_1(t)] \\ = L[10\delta(t)] = 10$$

$$V_0(s) = \frac{10 \times 1}{s^2(1 \times 10^{-4}) + s \times 10^{-2}(1-2) - 1}$$

$$V_0(s) = \frac{10}{s^2 \times 10^{-4} - s \times 10^{-2} - 1}$$

$$V_0(s) = \frac{10^5}{(s^2 - 100s - 10^4)} = \frac{10^5}{(s - 161.8)(s + 61.8)}$$

$$\frac{10^5}{(s - 161.8)(s + 61.8)} = \frac{A}{(s - 161.8)} + \frac{B}{(s + 61.8)}$$

$$A = \frac{10^5}{161.8 + 61.8} = 447.227$$


$$B = \frac{10^5}{-(61.8 + 161.8)} = -447.227$$

$$\therefore V_0(t) = 447.227 [e^{161.8t} - e^{-61.8t}] u(t)$$

Ans

Ques-7(b)

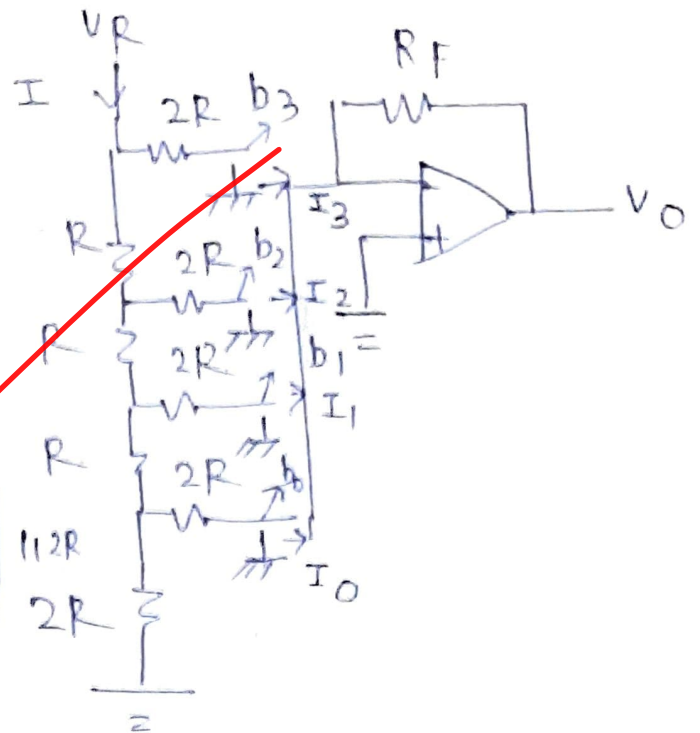4 bit Inverted R-2R
ladder type Digital to analog
Converter →



Total Current:

$$I = \frac{V_R}{R_{eq}}$$

$$R_{eq} = \left[\left[\left[\left(2R \parallel 2R \right) + R \right] \parallel 2R \right] + R \right] \parallel 2R$$

ie $R_{eq} = R$

$$\therefore I = \frac{V_R}{R}$$

$$I_3 = \frac{I}{2} \times b_3 \quad I_2 = \frac{I}{4} b_2 \quad I_1 = \frac{I}{8} b_1 \quad I_0 = \frac{I}{16} b_0$$

$$\therefore I_f = I_0 + I_1 + I_2 + I_3$$

$$I_f = \frac{V_R}{2R} b_3 + \frac{V_R}{4R} b_2 + \frac{V_R}{8R} b_1 + \frac{V_R}{16R} b_0$$

$$I_f = \frac{V_R}{16R} [8b_3 + 4b_2 + 2b_1 + b_0]$$

$$I_f = \frac{V_R}{2^n R} \times \sum_{i=0}^n 2^i b_i$$

$$\therefore V_0 = -I_f \cdot R_f = \frac{-V_R \cdot R_f}{2^n R} \cdot \sum_{i=0}^n 2^i b_i \quad \leftarrow \text{Proved}$$

Given, $V_0 = 10V$

for Digital input $(1000)_2$

$$\therefore V_R = -5 \text{ volt}$$

i.e $10 = \frac{5 R_f \times 8}{2^4 R}$

$10 = \frac{5 \times 8 \times R_f}{16^2 R}$

$\therefore \frac{R_f}{R} = 4$

$\therefore \boxed{R_f = 4R}$

Put $R = 5K\Omega$
then $R_f = 20K\Omega$


for the designed ckt,
analog o/p voltage for digital input (1100)

$V_0 = \frac{5}{2^4} \times 4 [8 + 4 + 0 + 0]$

$V_0 = \frac{5}{16} \times 4 \times 12^3$

$\boxed{V_0 = 15V}$

← Ans.

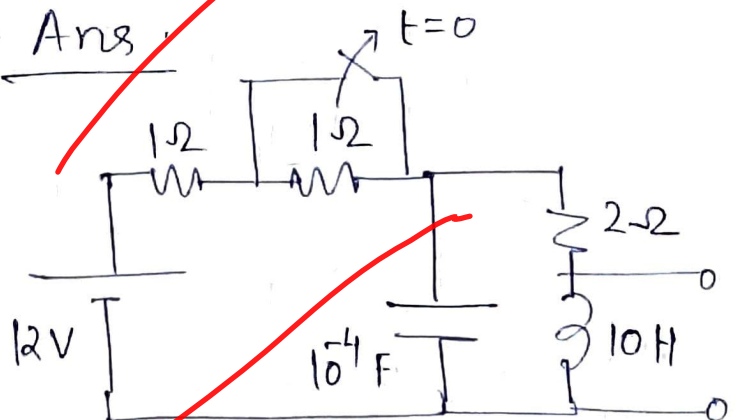

Ques-7(c) Given ckt,

ckt was in steady state when switch was closed

\therefore eq. ckt diagram under steady state at $t=0^-$ just before opening switch,

$$i_L(0^-) = \frac{12}{1+2} = 4 \text{ amp}$$

cap. will be open

Inductor will be short in steady state condition

$$v_C(0^-) = 8 \text{ volt}$$

for $t > 0$, Transforming ckt in S-domain,

$$v_C(0^+) = v_C(0^-) = 8 \text{ V}$$

$$i_L(0^+) = i_L(0^-) = 4 \text{ A}$$

Using mesh analysis,
KVL in mesh (1)

$$-\frac{12}{s} + 2I_1(s) + \frac{10^4}{s}[I_1(s) - I_2(s)] + \frac{8}{s} = 0$$

$$\text{i.e. } \left(2 + \frac{10^4}{s}\right) I_1(s) - \frac{10^4}{s} I_2(s) = \frac{4}{s} \quad \text{--- (1)}$$

KVL in mesh (2)



$$I_2(s) \left[2 + 10s + \frac{10^4}{s}\right] - \frac{10^4}{s} I_1(s) - 40 - \frac{8}{s} = 0$$

$$I_2(s) \left[2 + 10s + \frac{10^4}{s}\right] - \frac{10^4}{s} I_1(s) = 40 + \frac{8}{s} \quad \text{--- (2)}$$

from (1) $\frac{10^4}{s} I_2(s) = \left(2 + \frac{10^4}{s}\right) I_1(s) - \frac{4}{s}$

$$\therefore I_2(s) = \frac{\left(2 + \frac{10^4}{s}\right) I_1(s) - \frac{4}{s}}{\left(\frac{10^4}{s}\right)}$$

substitute $I_2(s)$ in eqn (2)

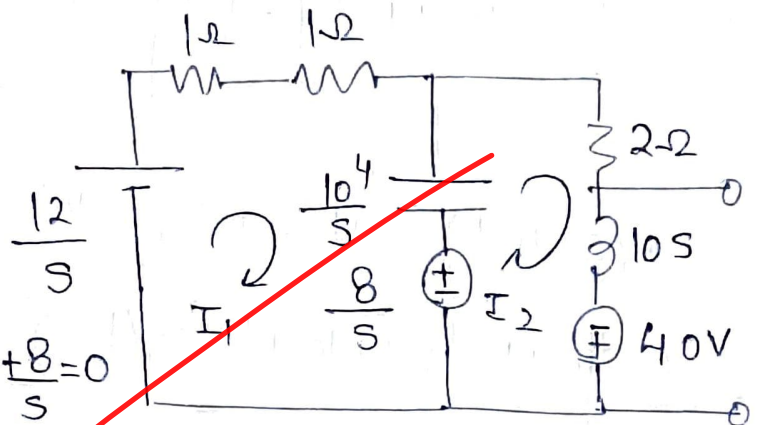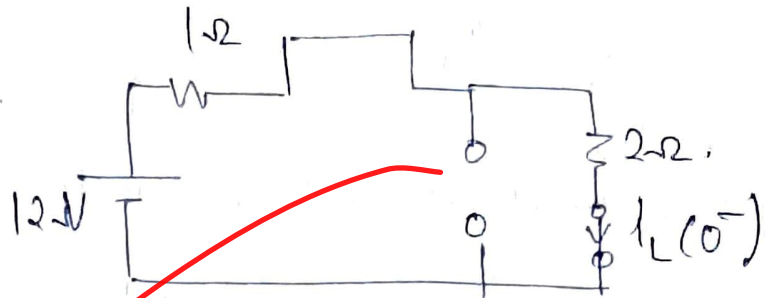

$$\left(2 + 10s + \frac{10^4}{s}\right) \left(2 + \frac{10^4}{s}\right) I$$

from eqⁿ (1) get $I_1(s)$ in terms of $I_2(s)$ & Put in eqⁿ (2)

$$I_1(s) = \frac{\frac{4}{s} + \frac{10^4}{s} I_2(s)}{\left(2 + \frac{10^4}{s}\right)}$$

substitute in eqⁿ (2)

$$I_2(s) \left[2 + 10s + \frac{10^4}{s}\right] - \frac{10^4}{s} \left[\frac{\frac{4}{s} + \frac{10^4}{s} I_2(s)}{\left(2 + \frac{10^4}{s}\right)} \right] = \left(40 + \frac{8}{s}\right)$$

$$I_2(s) \left(2 + \frac{10^4}{s}\right) \left(2 + 10s + \frac{10^4}{s}\right) - \frac{10^4}{s} \left(\frac{4}{s}\right) - \frac{10^4}{s} \cdot \frac{10^4}{s} I_2(s) = \left(40 + \frac{8}{s}\right) \left(2 + \frac{10^4}{s}\right)$$

$$I_2(s) \left[\left(2 + \frac{10^4}{s}\right) \left(2 + 10s + \frac{10^4}{s}\right) - \left(\frac{10^4}{s}\right)^2 \right] = \left(40 + \frac{8}{s}\right) \left(2 + \frac{10^4}{s}\right) + \frac{4}{s} \times \frac{10^4}{s}$$

$$I_2(s) \left[\left(2 + \frac{10^4}{s}\right)^2 + \left(2 + \frac{10^4}{s}\right) 10s - \left(\frac{10^4}{s}\right)^2 \right] = 80 + \frac{40 \times 10^4}{s} + \frac{16}{s} + \frac{8 \times 10^4}{s^2} + \frac{4 \times 10^4}{s^2}$$

$$I_2(s) \left[4 + \frac{(10^4)^2}{s^2} + \frac{4 \times 10^4}{s} + 20s + 10^5 - \left(\frac{10^4}{s}\right)^2 \right] = 80 + \frac{16}{s} + \frac{40 \times 10^4}{s} + \frac{12 \times 10^4}{s^2}$$

$$I_2(s) \left[\frac{4s + 4 \times 10^4 + 20s^2 + 10^5 s}{s} \right] = \left[\frac{80s^2 + 16s + 40 \times 10^4 s + 12 \times 10^4}{s^2} \right]$$

$$\therefore I_2(s) = \frac{80s^2 + (16 + 40 \times 10^4)s + 12 \times 10^4}{s [20s^2 + (4 + 10^5)s + 4 \times 10^4]}$$

$$V_L(s) = (10s) I_2(s) - 40$$

$$\text{ie, } V_L(s) = 10 \times \left[\frac{80s^2 + (16 + 40 \times 10^4)s + 12 \times 10^4}{20s^2 + (4 + 10^5)s + 4 \times 10^4} \right] - 40$$

$$V_L(s) = \frac{80s^2 + (16 + 40 \times 10^4)s + 12 \times 10^4}{2s^2 + (0.4 + 10^4)s + 0.4 \times 10^4} - 40$$

$$V_L(s) = \frac{80s^2 + (16 + 40 \times 10^4)s + 12 \times 10^4 - 80s^2 + (16 + 40 \times 10^4)s + 6 \times 10^4}{2s^2 + (0.4 + 10^4)s + 0.4 \times 10^4}$$

$$V_L(s) = \frac{-4 \times 10^4}{2s^2 + 10^4s + 0.4 \times 10^4} = \frac{-2 \times 10^4}{s^2 + 5000s + 2000}$$

$$V_L(s) = \frac{-2 \times 10^4}{(s + 0.4)(s + 4999.6)} = \frac{A}{s + 0.4} + \frac{B}{s + 4999.6}$$

$$\therefore A = \frac{-2 \times 10^4}{(-0.4 + 4999.6)} = -4.00064$$

$$B = \frac{-2 \times 10^4}{(-4999.6 + 0.4)} = 4.00064$$

$$\therefore V_L(t) = 4.00064 \left[e^{-4999.6t} - e^{-0.4t} \right] u(t)$$

← Ans.

Qus-7(a)

Solution-

Given:

15 KVA, 2400/240, 60 Hz Transformer

Circuit Parameter

$$R_1 = 2.5 \Omega$$

$$X_1 = 7 \Omega$$

$$R_c = 32 \text{ K}\Omega$$

$$R_2 = 0.025 \Omega$$

$$X_2 = 0.07 \Omega$$

$$X_m = 11.5 \text{ K}\Omega$$

If T/F is supplying a 10 kW, 0.8 pf lagging at Rated voltage.


We have to draw eq. ckt referred to H.V side

$$\frac{E_1}{E_2} = \frac{N_1}{N_2} = \frac{2400}{240} = 10 = \frac{I_2}{I_1}$$

$$I_2 = \frac{E_2 I_2}{E_2} = \frac{15 \text{ KVA}}{240} = 62.5 \text{ Amp}$$

$$\therefore I_1 = 6.25 \text{ A}$$

eq. ckt -

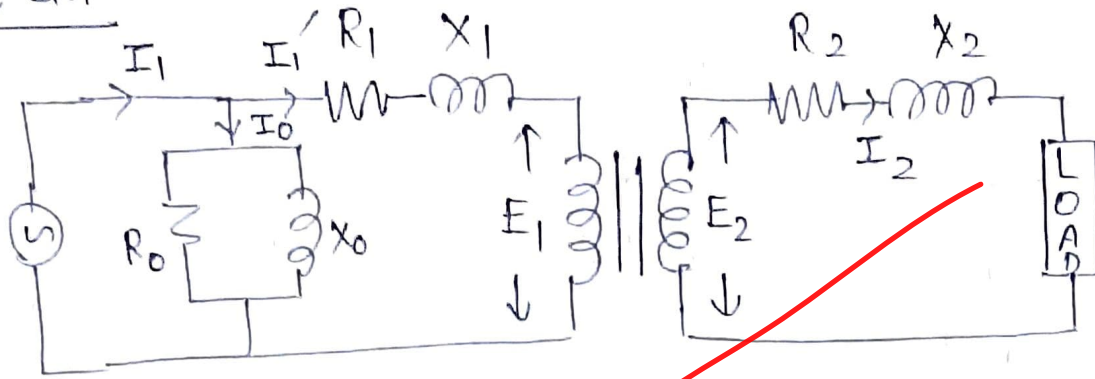

Transforming Resistance from 2^ory to Primary sides,

$$I_1^2 R_2' = I_2^2 R_2$$

$$\therefore R_2' = \left(\frac{I_2}{I_1}\right)^2 R_2 = 10^2 \times 0.025$$

$$R_2' = 2.5 \Omega$$

\therefore Total eq Resistance Referred to Primary (HV)

$$R_{01} = R_1 + R_2' = 2.5 + 2.5 = 5 \Omega$$

Transforming Reactance from 2^ory to 1^ory side


$$I_1^2 X_2' = I_2^2 X_2$$

$$\therefore X_2' = \left(\frac{I_2}{I_1}\right)^2 X_2 = 10^2 \times 0.07 = 7 \Omega$$

\therefore Total eq. Reactance referred to Primary (HV)


$$X_{02} = X_1 + X_2' = 7 + 7 = 14 \Omega$$

eq. ckt referred to HV side.

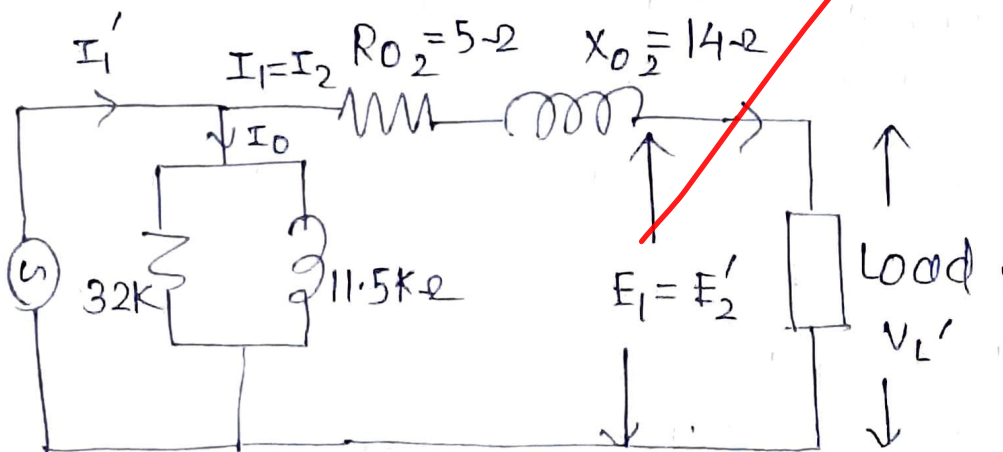

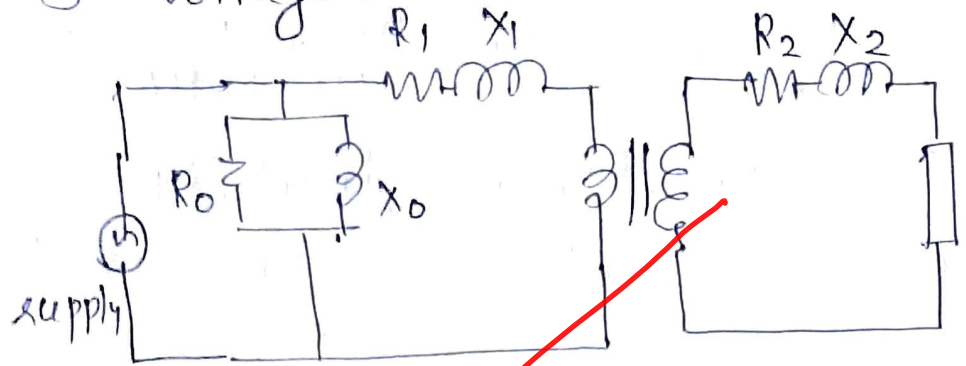(i) Input Current -

T/F is supplying 10 kW, 0.8 pf lag load at Rated Voltage.



$$I_1 = I_2'$$

$$\therefore I_2' = \frac{E_2' I_2'}{E_2'} = \frac{10 \times 10^3}{2400} = 4.167 \text{ Amp}$$

$$\therefore \text{Input Current } I_1 = 4.167 \text{ amp}$$