



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRICAL ENGINEERING

Date of Test : 27/05/2024


ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (d) | 13. (b) | 19. (b) | 25. (c) |
| 2. (d) | 8. (c) | 14. (d) | 20. (d) | 26. (b) |
| 3. (b) | 9. (c) | 15. (c) | 21. (d) | 27. (d) |
| 4. (d) | 10. (b) | 16. (a) | 22. (d) | 28. (c) |
| 5. (a) | 11. (b) | 17. (a) | 23. (b) | 29. (a) |
| 6. (d) | 12. (b) | 18. (c) | 24. (a) | 30. (b) |

DETAILED EXPLANATIONS

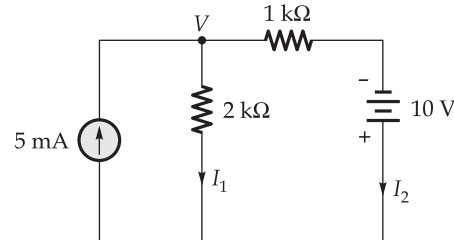1. (a)

On applying short circuit test, D_1 and D_2 are replaced by short circuit



On applying Nodal analysis

$$\frac{V}{2} + \frac{V + 10}{1} = 5$$

$$3V = -10$$

$$V = \frac{-10}{3}$$

$$\therefore I_1 = \frac{V}{2} = \frac{-10}{6} \text{ mA} < 0$$

So, D_1 off,

$$I_1 = 0 \text{ mA}$$

$$I_2 = 5 \text{ mA}$$

2. (d)

Relationship between reverse saturation current and temperature can be given as

$$I \propto 2^{(T/10)}$$

$$\frac{I_2}{I_1} = \frac{2^{\left(\frac{T_2}{10}\right)}}{2^{\left(\frac{T_1}{10}\right)}} = 2^{\left(\frac{T_2 - T_1}{10}\right)}$$

$$\frac{I_2}{I_1} = 2^{\left(\frac{T_2 - T_1}{10}\right)}$$

$$T_2 - T_1 = 3^\circ \text{ C}$$

$$I_2 = I_1 \times 2^{(3/10)} = 1.23 I_1$$

$$I_2 = I_1 \times 123\%$$

So, % increased in $I_2 = 23\%$

3. (b)

From the diode circuit,

$$I_D = \frac{V_i - V_{DO}}{r_d} = \frac{V_i}{r_d} - \frac{V_{DO}}{r_d} \rightarrow \text{shows the PWL model of diode}$$

So, option (b) shows the best characteristics of above diode circuit.

4. (d)

When $V_{in} > 2.7$, $D \rightarrow ON$, $V_o = V_i - 0.7 V$ $V_{in} < 2.7 V$, $D \rightarrow OFF$, $V_o = 2 V$

5. (a)

As we know,

$$\text{Gain} \times \text{Bandwidth} = \text{Constant} \quad \dots(1)$$

Closed loop gain with -ve feedback is

$$A_{CL} = \frac{A_{OL}}{1 + A_{OL}\beta} \quad (A_{OL} = \text{Open loop gain; } \beta = \text{Feedback factor})$$

Given : $A_{OL} = 100$, $(BW)_{OL} = 100 \text{ kHz}$ From eqn. (1), $A_{OL}(BW)_{OL} = A_{CL}(BW)_{CL}$

$$100 \times 10^5 = \frac{100}{1 + 100\beta} \times 10^6$$

$$1 + 100\beta = 10$$

$$\beta = 0.09$$

6. (d)

Let

$$V_o(t) = V_m \sin \omega_m t$$

$$\text{S.R.} = \left| \frac{dV_o(t)}{dt} \right|_{\max} = V_m \omega_m \cos \omega_m t = V_m \omega_m$$

$$5 = V_m (2\pi \times 10^7)$$

$$V_m = \frac{5}{20\pi} = \frac{1}{4\pi} \text{ Volts}$$

So, the largest sine wave output possible at a frequency of 10 MHz is $\frac{1}{4\pi}$ volts.

7. (d)

As we know,

$$V_o = A_{OL}(V^+ - V^-)$$

Since, $A_{OL} = \infty$ (for ideal Op-Amp)So, $V^+ = V^- = V_{in}$

On applying KCL at inverting terminal

$$\frac{V^-}{3} + \frac{V^- - V_o}{2} = 0$$

$$2V^- + 3V^- - 3V_o = 0$$

$$5V_{in} = 3V_o$$

$$V_o = \frac{5}{3} V_{in} = A_V \cdot V_{in}$$

$$\frac{V_o}{V_{in}} = A_V = \frac{5}{3}$$

8. (c)
 It is non-inverting amplifier.

The gain,
$$K = 1 + \frac{R_F}{R_1}$$

where,
$$R_F = R_Y$$

$$R_1 = R_X$$

So,
$$\text{gain } K = 1 + \frac{R_Y}{R_X}$$

9. (c)

$$V_{GS} = 2 - 0.5$$

$$= 1.5 > V_{Th}$$

MOSFET is ON

Assume,
$$V_{DS} \geq V_{GS} - V_t \text{ (current saturation)}$$


$$2 - 0.5 \geq 2 - 0.5 - 0.4$$

$$1.5 \geq 1.1$$

MOSFET is in current saturation.

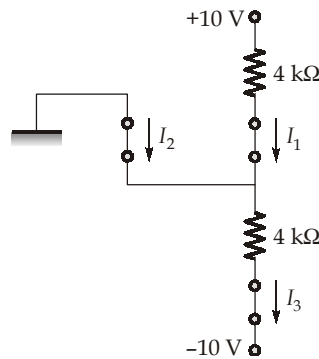10. (b)

Assuming initially all diodes are ON and can be replaced by short circuit,



Current,
$$I_1 = I_3 = \frac{10 - (-10)}{8k\Omega} = \frac{20}{8k\Omega} = 2.5 \text{ mA}$$


as no current is drawn from ground

$$I_2 = 0$$

∴ D_2 is in off state.

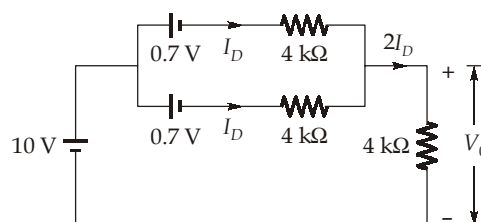11. (b)

As current flows in both diodes from anode to cathode



Voltage across each parallel branch

$$V_p = 0.7 + (4 \text{ k}) (I_D)$$

By KVL in main loop,

$$-10 + 0.7 + (4 \text{ k}) (I_D) + 4 \text{ k}(2I_D) = 0$$


$$-10 + 0.7 + 12 \text{ k } I_D = 0$$

$$12 \text{ k}(I_D) = 9.3$$

or $I_D = 0.775 \text{ mA}$


So, output voltage, $V_0 = (2I_D) \times 4 \text{ k}\Omega$
 $= 2 \times 0.775 \times 10^{-3} \times 4 \times 10^3$
 $= 6.2 \text{ V}$

Alternate Solution:

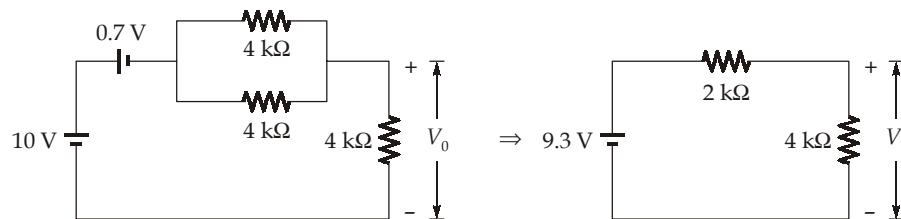

$$V_0 = \frac{9.3 \times 4 \text{ k}}{(4 + 2) \text{ k}} = 6.2 \text{ V}$$

12. (b)

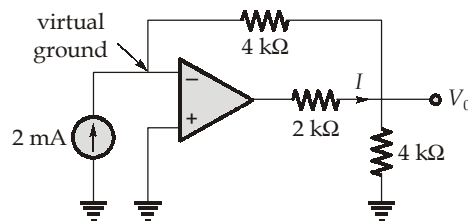

$$V_0 = 0 - (2 \times 10^{-3} \times 4 \times 10^3) = -8 \text{ V}$$

Applying KCL at output node

$$I + 2 \text{ mA} = \frac{V_0}{4 \text{ k}\Omega}$$

$$I = -2 \text{ mA} - \frac{8}{4 \text{ k}\Omega} = -4 \text{ mA}$$


13. (b)

Circuit can be redraw as

For non inverting configuration,

$$V_0 = \left(1 + \frac{R_f}{R_1} \right) V_s = (1 + 1) 5$$

$$= 10 \text{ V}$$

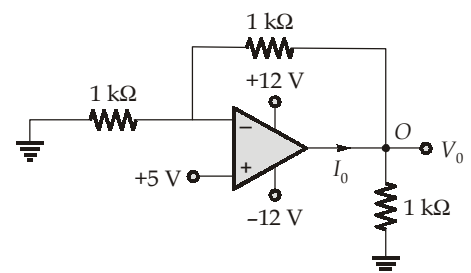

Applying KCL at node-O,

$$\frac{5-10}{1\text{k}\Omega} + I_0 + \frac{0-10}{1\text{k}\Omega} = 0$$

$$\frac{-5}{1\text{k}\Omega} + I_0 - \frac{10}{1\text{k}\Omega} = 0$$

$$I_0 = 15 \text{ mA}$$

14. (d)

Given,

$$R_1 = 14 \text{ k}\Omega,$$

$$R_2 = 6 \text{ k}\Omega,$$

$$R_S = 0.5 \text{ k}\Omega,$$

$$R_D = 1.2 \text{ k}\Omega$$

$$V_G = \frac{R_2}{R_1 + R_2} \times 10 + \frac{R_1}{R_1 + R_2} (-10)$$

$$= \frac{6 \times 10}{20} - \frac{14}{20} \times 10 = -4 \text{ V}$$

As transistor operating in saturation

$$I_D = \frac{V_S - (-10)}{R_S} = \frac{V_G - V_{GS} + 10}{R_S} = K_n (V_{GS} - V_{TN})^2$$

$$K_n = \frac{K'_n W}{2 L} = \frac{(60)(60 \times 10^{-6})}{2} = 1.8 \text{ mA/V}^2$$

$$(1.8 \times 10^{-3})(V_{GS} - 2)^2 \times 0.5 \times 10^3 = -4 - V_{GS} + 10$$

$$0.9(V_{GS}^2 + 4 - 4 V_{GS}) = 6 - V_{GS}$$

$$0.9V_{GS}^2 + 3.6 - 3.6V_{GS} = 6 - V_{GS}$$

$$0.9V_{GS}^2 - 2.6V_{GS} - 2.4 = 0$$

$$\Rightarrow V_{GS} = 3.62 \text{ V}, -0.73 \text{ V}$$


As V_{GS} is +ve so correct value $V_{GS} = 3.62 \text{ V}$

$$I_D = \frac{V_G - V_{GS} + 10}{R_S}$$

$$= \frac{-4 - 3.62 + 10}{500} = 4.76 \text{ mA}$$

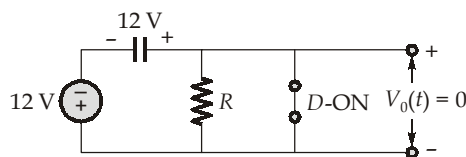
15. (c)

For given figure, when V_{in} is negative



Output is zero

When $V_i(t)$ is positive

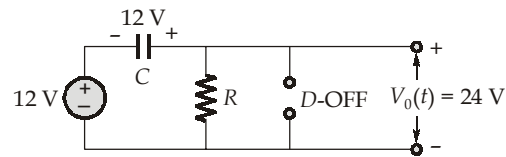


At $t = 15\text{ msec}$

The capacitor voltage and source voltage together will appear at the output :

$$12\text{ V} + 12\text{ V} = 24\text{ V}$$

16. (a)

As we know for a $n-p-n$ BJT transistor

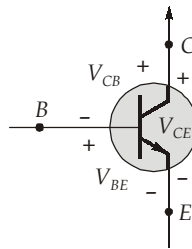

$$\begin{aligned} V_{CE} &= V_{BE} + V_{CB} \\ &= 0.7 + 0.2 = 0.9\text{ V} \end{aligned}$$

Since, $V_{CE} > 0.2$ [$V_{CE(\text{sat})} = 0.2\text{ V}$]

Therefore transistor is operating in active region.

17. (a)

As we know,

$$I_S = I_Z + I_L$$

$$I_Z = I_S - I_L$$

$$I_{Z(\text{min})} = I_{S(\text{min})} - I_{L(\text{max})}$$

$$2\text{ mA} = I_{S(\text{min})} - 4\text{ mA}$$

$$I_{S(\text{min})} = 6\text{ mA}$$

$$\frac{V_{i(\text{min})} - V_Z}{R_S} = 6\text{ mA}$$


$$V_{i(\text{min})} = 6 \times 5 + 50 = 80\text{ V}$$

and

$$I_{Z(\text{max})} = I_{S(\text{max})} - I_{L(\text{min})} \Rightarrow I_{S(\text{rms})} = 8\text{ mA}$$

$$8 = \frac{V_{i(\text{max})} - V_Z}{R_S} \Rightarrow V_{i(\text{max})} = 8 \times 5 + 50 = 90\text{ V}$$

18. (c)

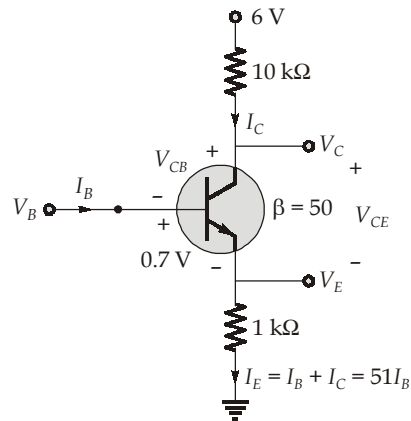

As we know, $V_{CE} = V_{BE} + V_{CB}$ [$\because V_C = V_B \Rightarrow V_{CB} = 0 \text{ V}$]

$$V_{CE} = 0.7 \text{ V}$$

$$V_B = V_{BE} + V_E$$

$$I_C = \frac{6 - V_C}{10} = \frac{6 - 0.7 - V_E}{10} = 50I_B$$

$$5.3 - 500 I_B = V_E$$

Also $V_E = 51 I_B \times 1$

Therefore, $51 I_B + 500 I_B = 5.3$

$$I_B = 9.61 \times 10^{-3} \text{ mA}$$

$$I_C = \beta I_B = 9.61 \times 10^{-3} \times 50 = 0.48 \text{ mA}$$

Hence, $V_C = 6 - I_C \times 10$

$$= 6 - 0.48 \times 10 = 1.19 \text{ V}$$

Therefore, $V_B = V_C = 1.19 \text{ V}$


19. (b)

$$g_m = \frac{\partial I_D}{\partial V_{GS}} = \frac{\partial}{\partial V_{GS}} \left[K_n (V_{GS} - V_{th})^2 \right]$$

$$= 2K_n (V_{GS} - V_{th})$$

20. (d)

Laplace equivalent circuit,

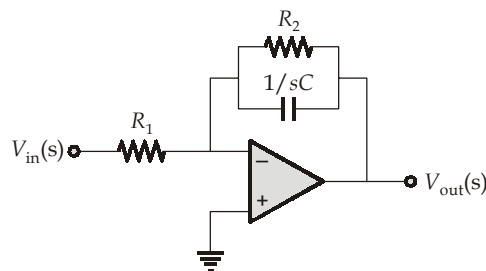

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2 \parallel \left(\frac{1}{sC} \right)}{R_1}$$

$$\frac{V_0(s)}{V_i(s)} = \frac{-R_2}{R_1} \times \frac{1}{1 + sCR_2}$$

It is low pass filter with, $\omega_c = \frac{1}{R_2C}$

So, $f_c = \frac{1}{2\pi R_2C}$

21. (d)

$$Q = 0.5 \sqrt{\frac{C_2}{C_1}} = 0.5 \sqrt{\frac{1.64 \text{ nF}}{820 \text{ pF}}} = 0.707$$

The pole frequency, $f_p = \frac{1}{2\pi R \sqrt{C_1 C_2}} = \frac{1}{2\pi(30) \times 10^3 \sqrt{820 \times 1.64 \times 10^{-21}}}$
 $= 4.58 \text{ kHz}$

Here $Q = 0.707$ tells us that this is a butterworth response, so cutoff frequency is the same as the pole frequency,

$$f_c = f_p = 4.58 \text{ kHz}$$

22. (d)

- In the circuit R_E provides feedback to the circuit, the feedback is directly connected to the output node. So voltage sampling.
- The feedback is not directly connected to input node, so series mixing.

So, feedback topology is voltage series feedback.

23. (b)


Applying KVL, we get

$$-V_{CC} + (I_B + I_C)R_C + I_B R_B + V_{BE} = 0$$

$$I_B = \frac{V_{CC} - I_C R_C - V_{BE}}{R_C + R_B}$$

Now, $\frac{dI_B}{dI_C} = \frac{-R_C}{R_C + R_B}$
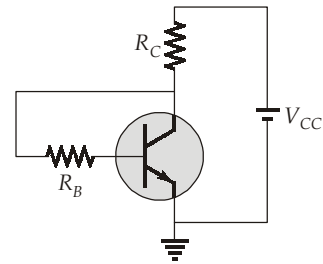
$$\therefore S = \frac{1 + \beta}{1 - \beta \left(\frac{dI_B}{dI_C} \right)} = \frac{1 + \beta}{1 + \frac{\beta R_C}{(R_C + R_B)}}$$



24. (a)

The diode current, $I_D = \frac{2.8 - 0.8}{2} = 1 \text{ mA}$

The thermal voltage, $V_T = \frac{KT}{e} = \frac{1.38 \times 10^{-23} \times 300}{1.6 \times 10^{-19}} = 25.87 \text{ mV}$


The dynamic resistance, $r_d = \frac{\eta V_T}{I_d} = \frac{2 \times 25.87}{1}$

$$r_d = 51.75 \Omega \approx 52 \Omega$$

25. (c)

By concept of virtual short,

$$V^+ = V^- = 0 \text{ V}$$

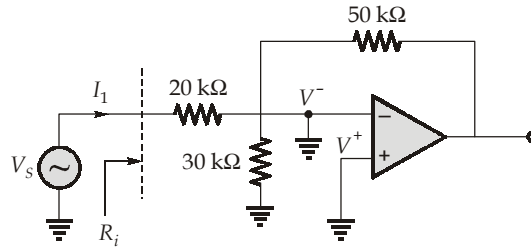

$$R_i = \frac{V_s}{I_1} = 20 \text{ k}\Omega$$

26. (b)

For Silicon diode, $\frac{dV}{dT} \approx -2.5 \text{ mV}/^\circ\text{C}$

Here, $dV = 640 - 700 = -60 \text{ mV}$

So, $dT = \frac{dV}{-2.5} = \frac{-60}{-2.5} = 24$


So, $T^\circ = T_1 + dT = 30^\circ + 24^\circ$
 $T = 54^\circ \text{ C}$

27. (d)

The Thevenin voltage, $V_{Th} = \frac{30}{30+70} \times 20 = 6 \text{ V}$


The Thevenin resistance $R_{Th} = 30 \parallel 70 = 21 \text{ k}\Omega$

The equivalent circuit

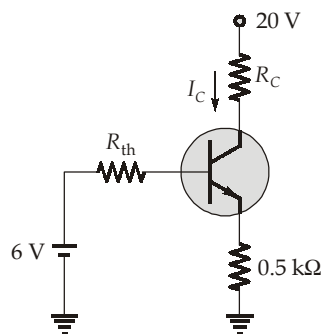

The operating state of BJT will be decided by value of R_C . According the value of R_C . BJT may be in active state or saturation state. So, I_C can not be found out.

28. (c)

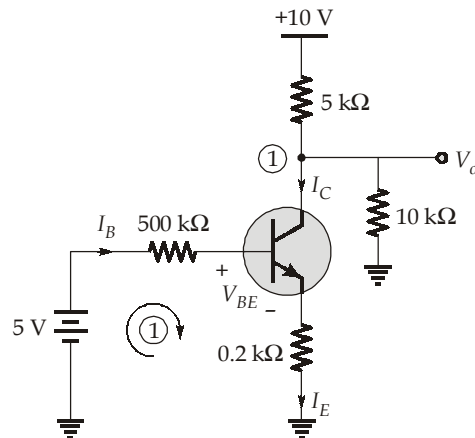

The base current,

$$I_B = \frac{V_{BB} - V_{BE}}{R_B + (1 + \beta) R_E} = \frac{5 - 0.7}{500 + (1 + 100) \times 0.2}$$

$$I_B = 8.266 \mu\text{A}$$

So, collector current,

$$I_C = \beta I_B = 0.8266 \text{ mA}$$

KCL at node (1),

$$I_C + \frac{V_o}{10} + \frac{V_o - 10}{5} = 0$$

$$0.8266 + \frac{V_o}{10} + \frac{V_o - 10}{5} = 0$$

$$V_o = \frac{2 - 0.8266}{\left(\frac{1}{10} + \frac{1}{5}\right)} = 3.911 \text{ Volt}$$

and

$$V_{CE} = V_o - V_E = 3.911 - 8.266 \times 10^{-3} \times 101 \times 0.20$$

$$V_{CE} = 3.744 \text{ V} > 0.2$$


So, BJT is in active mode.

So,

$$V_o = 3.91 \text{ Volt}$$

29. (a)

Applying KVL in the base-emitter loop

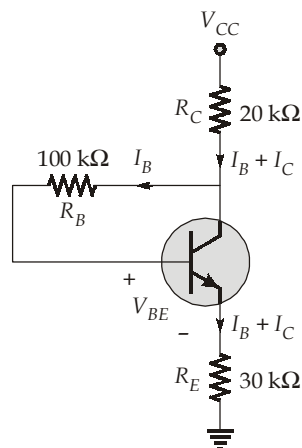

$$+V_{BE} - V_{CC} + (I_C + I_B)R_C + I_B R_B + (I_C + I_B) (R_E) = 0$$

Difference w.r.t. I_C

$$\left(1 + \frac{\partial I_B}{\partial I_C}\right) (R_C + R_E) + \frac{\partial I_B}{\partial I_C} R_B = 0$$


$$\frac{\partial I_B}{\partial I_C} = -\frac{(R_C + R_E)}{R_C + R_B + R_E}$$

$$\frac{\partial I_B}{\partial I_C} = \frac{-(20 + 30)}{100 + 20 + 30} = -\frac{1}{3}$$

So, stability factor,

$$S = \frac{1 + \beta}{1 - \beta \frac{\partial I_B}{\partial I_C}} = \frac{1 + 99}{1 - 99 \left(-\frac{1}{3}\right)} = 2.94$$

30. (b)

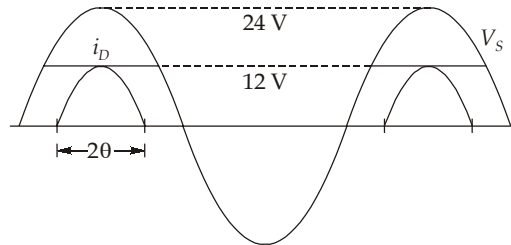

The diode conducts when V_s exceeds 12 V, as shown above,

The conduction angle is 2θ , where θ is given by

$$24 \cos \theta = 12$$

$$\theta = 60^\circ$$

and the conduction angle is 120°

That is $\frac{1}{3}$ of a cycle.

