



MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ANALOG ELECTRONICS

ELECTRONICS ENGINEERING

Date of Test : 11/07/2024

ANSWER KEY >

1. (b)	7. (b)	13. (d)	19. (c)	25. (c)
2. (a)	8. (a)	14. (b)	20. (a)	26. (b)
3. (a)	9. (c)	15. (c)	21. (c)	27. (b)
4. (c)	10. (c)	16. (d)	22. (c)	28. (c)
5. (d)	11. (a)	17. (b)	23. (a)	29. (d)
6. (d)	12. (d)	18. (a)	24. (b)	30. (b)

Detailed Explanations

1. (b)

Case-I

For positive input voltage when $V_i > 5.7$ V, the diode D_1 will turn ON, thus voltage at the output = $5 + 0.7 = 5.7$ V.

Case-II

For negative input voltage when $V_i < -0.7$ V, then diode D_2 will enter into forward region and thus will start conducting with a drop of 0.7 V on it.

Thus, $V_0 = V_{in}$ for -0.7 V $< V_i < 0$ and $V_0 = 0.7$ V for $V_i < -0.7$ V.

2. (a)

\therefore The feedback is series-series feedback, so the amplifier will be a voltage amplifier.

3. (a)

The above circuit is a positive half-wave precision rectifier.

Case 1: If $V_{in} > 0$, then diode will conduct thus, $V_{out} = V_{in}$ (\therefore the op-amp will work as a buffer.)

Case 2: If $V_{in} < 0$, then diode will be OFF hence $V_{out} = 0$.

4. (c)

For a fixed biased circuit,


$$I_C = \beta I_B + (\beta + 1)I_{CO}$$

$$\therefore \frac{\partial I_C}{\partial I_{CO}} = (\beta + 1) \quad \left[\because I_B = \frac{V_{CC} - V_{BE}}{R_B} = \text{constant} \right]$$

$$\therefore S = \frac{\partial I_C}{\partial I_{CO}} = 100 + 1 = 101$$

5. (d)

The circuit can be redrawn as,

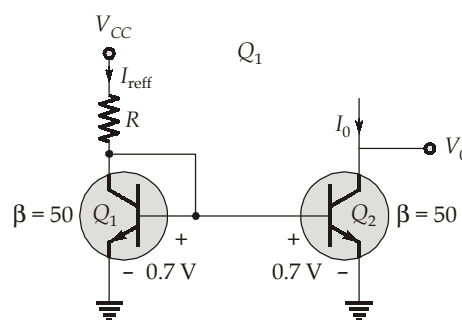

For current mirror circuit,


$$I_{\text{reff}} = \frac{V_{CC} - V_{BE}}{R} = \frac{10 - 0.7}{37 \times 10^3} = 0.251 \text{ mA}$$

now,

$$I_0 = \frac{I_{\text{reff}}}{\left(1 + \frac{2}{\beta}\right)} = \frac{0.251}{\left(1 + \frac{2}{50}\right)} = 0.241 \text{ mA}$$

6. (d)

The circuit can be redrawn as,

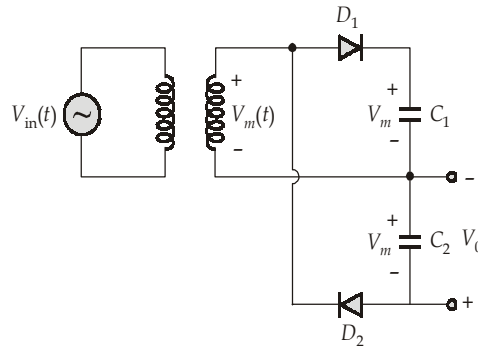

The circuit represents a voltage doubler circuit, if the voltage was taken by adding voltages of both the capacitors, but to calculate V_0 we have to find the voltage stored on a single capacitor. Thus, comparing from the above figure,

$$V_0 = -V_m$$

7. (b)

The early voltage V_A can be calculated as

$$V_A = r_0 I_C$$

where $r_0 = \text{output resistance} = \frac{1}{\text{slope of } I_C - V_{CB} \text{ curve}}$

$$r_0 = \frac{1}{3 \times 10^{-5}}$$


thus,
$$V_A = \frac{1}{3 \times 10^{-5}} \times 3 \times 10^{-3} = 100 \text{ V} \quad (\because I_C = 3 \times 10^{-3} \text{ A})$$

8. (a)

Since, the op-amp represents a closed loop unity gain amplifier.

$$\begin{aligned} \text{Thus, } A_{CL} &= \frac{A_{OL}}{1 + A_{OL}} \\ &= \frac{999}{1 + 999} = 0.999 \end{aligned}$$

9. (c)

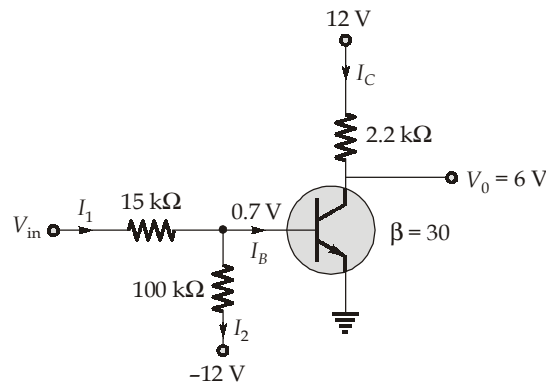

$$\text{Now, } I_C = \frac{12 - 6}{2.2} \times 10^{-3} = 2.727 \text{ mA}$$

$$\therefore I_B = \frac{I_C}{\beta} = \frac{2.727}{30} = \frac{1}{11} \text{ mA}$$


Now,
$$I_2 = \frac{0.7 - (-12)}{100 \text{ k}\Omega} = 0.127 \text{ mA}$$

$$\therefore I_1 = I_2 + I_B = 0.218 \text{ mA}$$

thus,
$$V_{in} = I_1 \times 15 \times 10^3 \Omega + 0.7$$

$$V_{in} = 3.968 \text{ V} \approx 3.97 \text{ V}$$

10. (c)

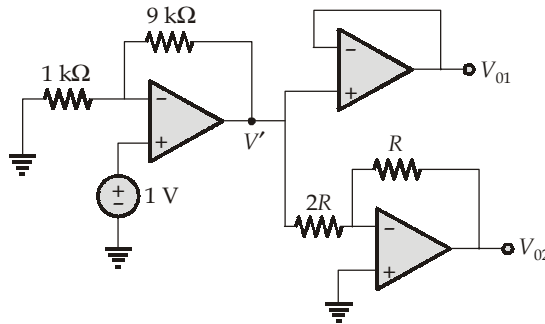

$$V' = \left(1 + \frac{9 \text{ k}\Omega}{1 \text{ k}\Omega} \right) \times 1 \text{ V} \quad (\because \text{non-inverting amplifier})$$

$$V' = 10 \text{ V}$$

now,
$$V_{01} = V' = 10 \text{ V} \quad (\because \text{it is a voltage buffer})$$


and
$$V_{02} = -\frac{R}{2R} V' \quad (\because \text{inverting amplifier})$$

$$V_{02} = -\frac{1}{2} V' = -\frac{10 \text{ V}}{2} = -5 \text{ V}$$

$$\therefore V_{02} - V_{01} = -5 \text{ V} - 10 \text{ V} = -15 \text{ V}$$

11. (a)

Assume both the diode to be ON.

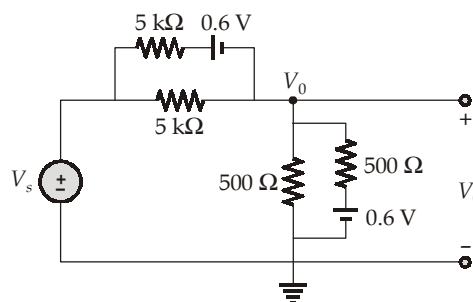

Applying the KCL at node V_0 , we get,

$$\frac{V_0 + 0.6 - V_s}{5 \text{ k}} + \frac{V_0 - V_s}{5 \text{ k}} + \frac{V_0}{500} + \frac{V_0 - 0.6}{500} = 0$$

$$\therefore V_0 = \frac{2}{22} V_s + \frac{5.4}{22}$$

$$V_0 = \frac{1}{11}V_s + \frac{54}{220}$$

For diode D_1 to be ON.


$$\begin{aligned} \therefore V_{D1} &= \frac{5 \text{ k}\Omega}{5 \text{ k}\Omega + 0.5 \text{ k}\Omega} \times V_s \\ &= \frac{5}{5.5} \times V_s > 0.6 \text{ V} \end{aligned}$$

For diode D_2 to be ON.

$$\begin{aligned} V_0 &> 0.6 \text{ V} \\ \frac{2V_s + 5.4}{22} &> 0.6 \\ V_s &> 3.9 \text{ V} \end{aligned}$$

12. (d)

The above circuit can be redrawn as

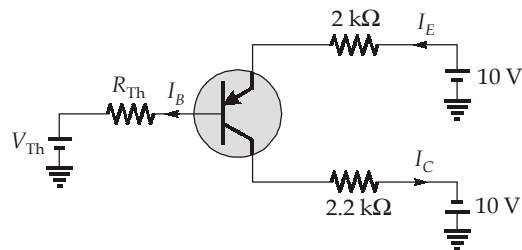

$$\begin{aligned} V_{Th} &= 6.67 \text{ V} \\ R_{Th} &= 10 \text{ k}\Omega \parallel 20 \text{ k}\Omega = 6.67 \text{ k}\Omega \end{aligned}$$

Applying KVL in the emitter base loop.

$$10 - (1 + \beta) I_{BQ}(2 \text{ k}\Omega) - V_{EB} - I_{BQ}(6.67 \text{ k}\Omega) - V_{Th} = 0$$

$$I_{BQ} = \frac{10 - 6.67 - 0.7}{6.67 + 122} \times 10^{-3} = 20.44 \mu\text{A}$$


$$\begin{aligned} \therefore I_{CQ} &= \beta I_{BQ} = 1.226 \text{ mA} \\ I_{EQ} &= (\beta + 1) I_{BQ} = 1.247 \text{ mA} \end{aligned}$$

Applying KVL in emitter-collector loop, we get,


$$\begin{aligned} 10 - I_E \times (2 \text{ k}\Omega) - V_{ECQ} - (2.2 \text{ k}\Omega) I_C + 10 &= 0 \\ V_{ECQ} &= 20 - 1.247 \times 2 - 2.2 \times 1.226 = 14.81 \text{ V} \end{aligned}$$

$$\therefore V_{CEQ} = -14.81 \text{ V}$$


13. (d)

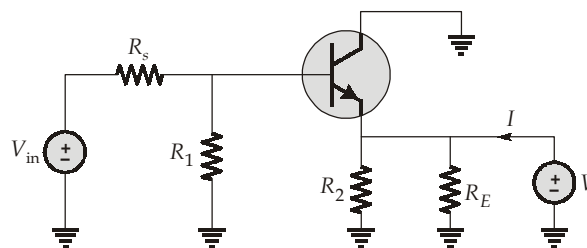

Drawing small signal equivalent circuit,

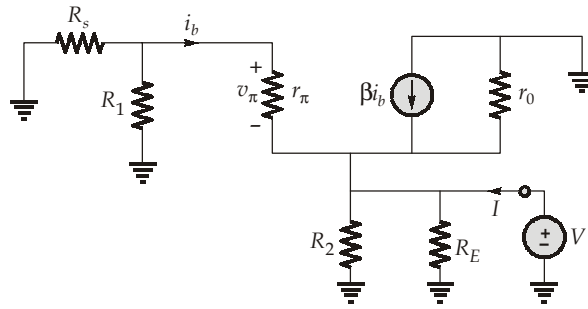

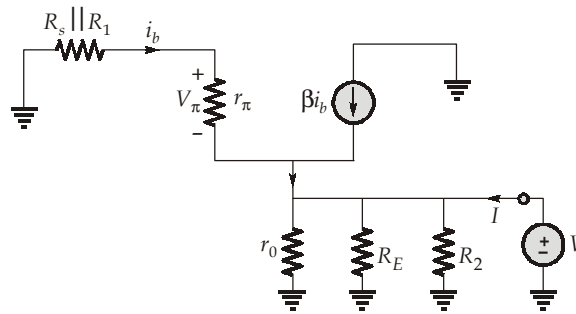thus, the circuit can be further reduced to



$$\therefore I = \frac{V}{R_2} + \frac{V}{R_E} + \frac{V}{r_0} - (\beta + 1)i_b$$

now,

$$i_b = \frac{V}{r_\pi + R_s \parallel R_1}$$

\therefore

$$I = V \left[\frac{1}{R_2} + \frac{1}{R_E} + \frac{1}{r_0} \right] + \frac{V}{\frac{r_\pi + R_s \parallel R_1}{\beta + 1}}$$


\therefore

$$\frac{V}{I} = (R_2 \parallel r_0 \parallel R_E) \parallel \left[\frac{1}{g_m} + \frac{R_s \parallel R_1}{\beta + 1} \right]$$

\therefore

$$g_m r_\pi = (\beta + 1)$$

14. (b)

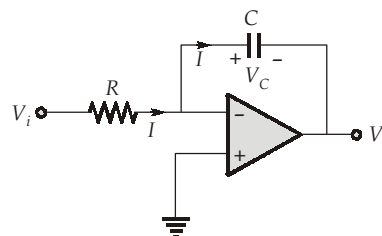

$$I = \frac{V_i}{R}$$

Thus,

$$V_c(t) = \frac{1}{C} \int_0^t I dt = \frac{1}{C} \int_0^t \frac{V_i}{R} dt$$

$$= \frac{V_i}{CR} \cdot t$$

($\because V_i$ is constant)


$$\therefore V_o(t) = -\frac{1\text{ V} \times (nT_p)}{10^3 \times 10^{-5}} = -1\text{ V}$$

$$nT_p = 10^{-2} \text{ and } T_p = 10\ \mu\text{sec}$$

$$n = \frac{10^{-2}}{10^{-5}} = 1000$$

Thus, minimum number of pulses required to reach the value of $|V_o| = 1\text{ V}$ is 1000.

15. (c)
 Redrawing the circuit

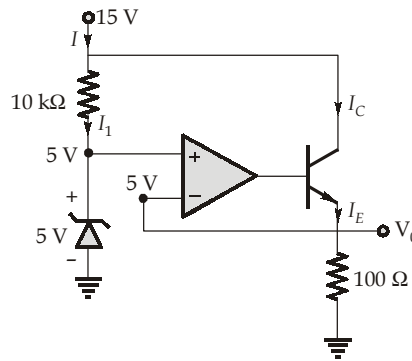


$$I_1 = \frac{15 - 5}{10\text{ k}\Omega} = 1\text{ mA}$$

$$I_E = \frac{5 - 0}{100} = 50\text{ mA}$$

$$I_E \approx I_C$$

$$I = I_1 + I_C = (50 + 1)\text{ mA} = 51\text{ mA}$$

16. (d)

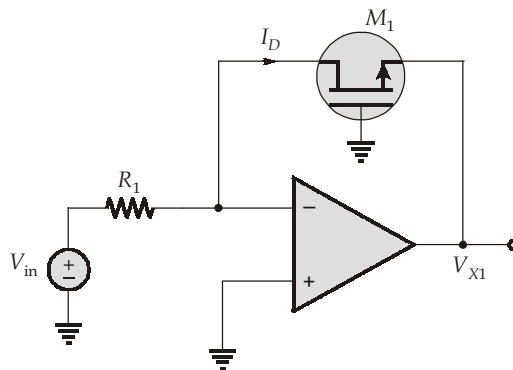

For the circuit in fig. 1 the value of output voltage.

V_{out} can be given as $V_{\text{out}} = V_{X1} + V_{Th}$
 and $V_{X1} = -V_{GS}$
 where $I_D = K_n(V_{GS} - V_{Th})^2$


$$\sqrt{\frac{I_D}{K_n}} = V_{GS} - V_{Th}$$

$$-V_{GS} = -\sqrt{\frac{I_D}{K_n}} - V_{Th}$$

$$-V_{GS} + V_{Th} = -\sqrt{\frac{I_D}{K_n}}$$

$$V_{out1} = V_{X1} + V_{Th} = -\sqrt{\frac{I_D}{K_n}} = -\sqrt{\frac{I_{in}}{K_n}}$$

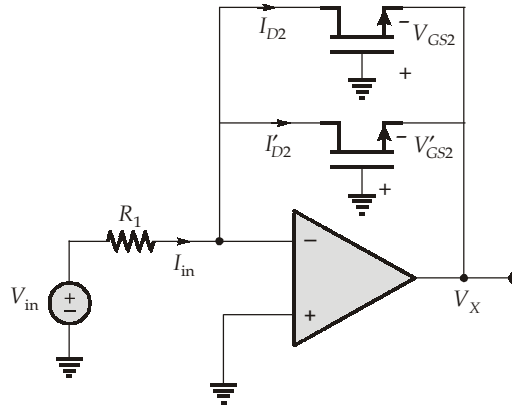now, for figure 2, since the two MOS circuit are in parallel thus,



$$I'_{D2} = I_{D2} = \frac{I_{in}}{2}$$

and


$$V_{out2} = -\sqrt{\frac{I_{D2}}{K_n}} = -\sqrt{\frac{I_{in}}{2K_n}}$$

now for both transistors

$$I_{in} = \frac{V_{in}}{R_1}$$

$$\therefore \frac{V_{out2}}{V_{out1}} = \frac{1}{\sqrt{2}} = 0.707$$

17. (b)

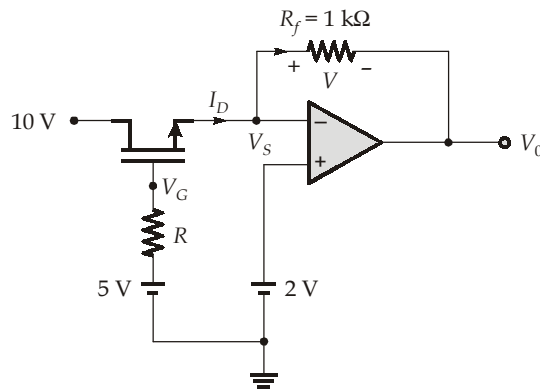

$$I_D = K_n(V_{GS} - V_T)^2$$

$$V_{GS} = V_G - V_S = 5\text{ V} - 2\text{ V} = 3\text{ V} \quad (\because V_S = 2\text{ V due to virtual ground})$$

Now,

$$I_D = 10^{-3}(3 - 1)^2$$

$$I_D = 4\text{ mA}$$

\therefore


$$V_0 = V_S - I_D R_f = 2 - I_D R_f$$

$$= 2 - 4 \times 10^{-3} \times 1 \times 10^3$$

$$= -2\text{ V}$$

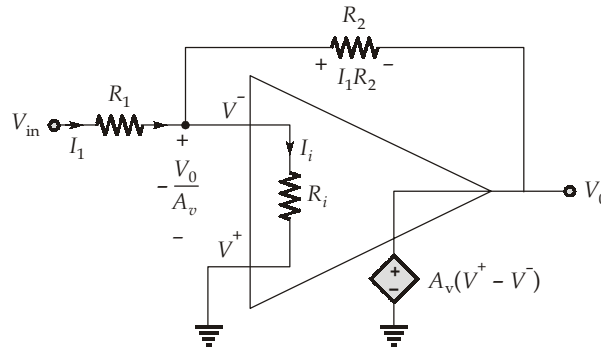18. (a)

$\because R_i \neq \infty$ thus concept of virtual ground is not applicable for this circuit.



$$V_0 = -\frac{R_2}{R_1} \left[V_{in} + \frac{V_0}{A_v} \right] - \frac{V_0}{A_v}$$


$$V_0 = -\frac{R_2}{R_1} V_{in} - \frac{1}{A_v} \left[1 + \frac{R_2}{R_1} \right] V_0$$

$$\therefore \frac{V_0}{V_{in}} = \frac{-\frac{R_2}{R_1}}{1 + \frac{1}{A_v} \left(1 + \frac{R_2}{R_1} \right)}$$

Thus,
$$\frac{V_0}{V_{in}} = \frac{-100/1}{1 + \frac{1}{10^3} \left(1 + \frac{100}{1} \right)} = \frac{-100}{1.1} = -90.83 \text{ V/V}$$

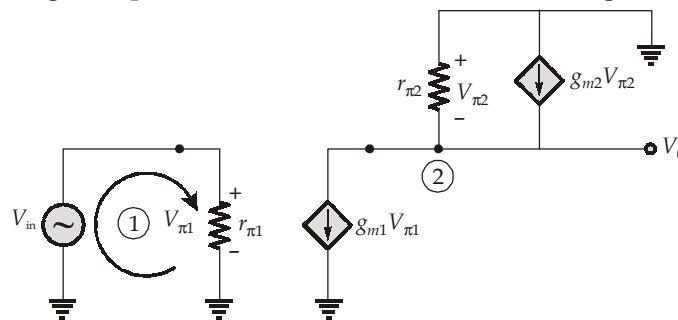19. (c)

Drawing the small signal equivalent model of the transistor, we get,



Now,

$$V_{in} = V_{\pi 1}$$

and

$$V_0 = -V_{\pi 2}$$

Applying KCL at node-2 we get

$$g_{m1} V_{\pi 1} + \frac{V_0}{r_{\pi 2}} = g_{m2} V_{\pi 2}$$

$$\Rightarrow g_{m1} V_{in} + \frac{V_0}{r_{\pi 2}} = -g_{m2} V_0$$

$$V_0 \left[\frac{1}{r_{\pi 2}} + g_{m2} \right] = -g_{m1} V_{in}$$

$$|A_v| = \left| \frac{V_0}{V_{in}} \right| = \frac{g_{m1}r_{\pi2}}{1 + g_{m2}r_{\pi2}}$$

Since $\beta \gg 1$ for both the transistors.

Thus, the above expression can be approximated as

$$|A_v| \approx \frac{g_{m1}}{g_{m2}}$$

20. (a)


In the circuit, the capacitor starts charging from 0 V (as the switch was initially closed) towards the steady state value of 20 V.

Now, when the switch is flipped open, the capacitor will charge upto 20 V.

$$\begin{aligned} \therefore V_c(t) &= V_c(\infty) - [V_c(0) - V_c(\infty)]e^{-t/RC} \\ RC &= 1 \times 10^3 \times 0.01 \times 10^{-6} = 10 \mu\text{sec} \end{aligned}$$

$$\therefore V_c(t) = 20(1 - e^{-t/RC})$$

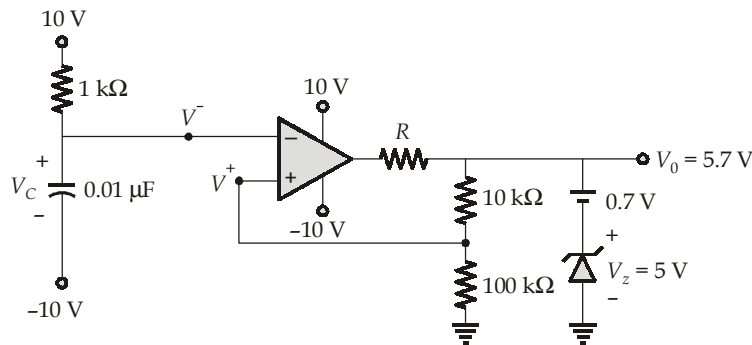Voltage at non-inverting amplifier is obtained as



$$V^+ = V_0 \times \frac{100 \text{ k}\Omega}{(10 + 100) \text{ k}\Omega}$$

$$V^+ = V_0 \times \frac{100}{110} = \frac{V_0 \times 10}{11}$$

\therefore Initially V^- was equal to -10 V, thus $V_0 = +5.7$ V.

Thus, now capacitor will start charging as soon as the switch is opened.

Thus, $V^- = V_C - 10$ V

or, $V_C = V^- + 10$ V

now, $V^- = V^+ = \frac{5.7 \text{ V} \times 10}{11}$ [\therefore the op-amp will switch]

thus, $V_C = \frac{10 \times 5.7}{11} + 10$

now, $V_C = 20(1 - e^{-t/RC})$

$$\therefore 20(1 - e^{-t/RC}) = 10 + \frac{57}{11}$$


$$1 - e^{-t/RC} = \frac{1}{2} + \frac{57}{220}$$

$$1 - e^{-t/RC} = 0.7590$$

$$e^{-t/RC} = 0.2409$$

$$T = 14.23 \mu\text{sec}$$

Hence, the output voltage wave will be,

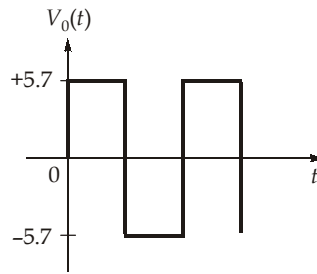


21. (c)

Now,
$$g_{m1} = 2\sqrt{k_{n1}I_{D1}} = 2\sqrt{0.5 \times 0.2 \times 10^{-6}} = 0.632 \text{ mA/V}$$

and
$$g_{m2} = 2\sqrt{k_{n2}I_{D2}} = 2\sqrt{(0.2)(0.5) \times 10^{-6}} = 0.632 \text{ mA/V}$$

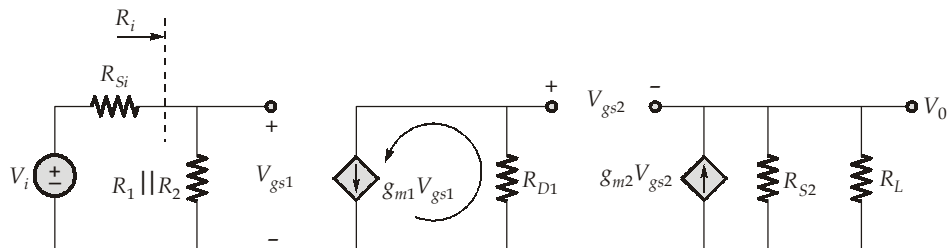Now, drawing the small signal equivalent circuit, we get,



Now,
$$V_0 = g_{m2}(R_{S2} \parallel R_L) \cdot V_{gs2} \quad \dots (i)$$

Also,
$$V_{gs2} + V_0 = -g_{m1} V_{gs1} R_{D1} \quad \dots (ii)$$

and
$$V_{gs1} = \frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \times V_i \quad \dots (iii)$$

Putting values of V_{gs1} and V_{gs2} from equation (i) and (iii) in equation (ii), we get

$$\frac{V_0}{g_{m2}(R_{S2} \parallel R_L)} + V_0 = -g_{m1} R_{D1} \left[\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \right] \cdot V_i$$

$$\therefore A_V = \frac{V_0}{V_i} = \frac{-g_{m1} g_{m2} R_{D1} (R_{S2} \parallel R_L)}{1 + g_{m2} (R_{S2} \parallel R_L)} \times \left[\frac{R_1 \parallel R_2}{R_1 \parallel R_2 + R_{Si}} \right]$$

Now,
$$R_{S2} \parallel R_L = \frac{8}{3} \text{ k}\Omega$$

$$R_1 \parallel R_2 = 99.8 \text{ k}\Omega \approx 100 \text{ k}\Omega$$

$$\therefore A_v = \frac{V_0}{V_i} = \frac{-(0.632)(0.632)(16.1)(8/3)}{1 + (0.632)(8/3)} \times \left[\frac{100}{104} \right] \approx -6.14$$

22. (c)

Assuming all the diodes are forward biased,

$$V_B = -0.7 \text{ V}$$

$$V_A = 0 \text{ V}$$

$$\therefore I_2 = \frac{10 - 0}{10 \text{ k}} = 1 \text{ mA}$$

and
$$I_1 = \frac{-0.7 - (-10)}{10 \text{ k}} = 0.93 \text{ mA}$$

$$\therefore I_2 = I_{D1} + I_{D2}$$

and
$$I_1 = I_{D2} + I_{D3}$$

applying KVL in the outer loop, we get,

$$10 \text{ k} I_2 + 0.7 + 10 \text{ k} I_{D1} - 20 = 10$$

$$10 \text{ k} (I_{D1} + I_{D2}) + 10 \text{ k} I_{D1} = 30 - 0.7 = 29.3$$

$$20 \text{ k} I_{D1} + 10 \text{ k} I_{D2} = 29.3$$

$$2I_{D1} + I_{D2} = 2.93 \text{ mA} \tag{... (i)}$$

also,
$$I_{D1} + I_{D2} = I_2 = 1 \text{ mA} \tag{... (ii)}$$

from (i) and (ii)

$$I_{D1} = 1.93 \text{ mA} \text{ and } I_{D2} = -0.93 \text{ mA}$$

$$\therefore I_{D2} + I_{D3} = 0.93 \text{ mA}$$


$$\Rightarrow I_{D3} = -I_{D2} + 0.93 \text{ mA} = 1.86 \text{ mA}$$

Here I_{D2} is negative, Hence, our assumption is incorrect.


Therefore, D_2 is reverse biased

and $\therefore I_{D1}$ and I_{D3} are positive,

D_1, D_3 are forward biased.

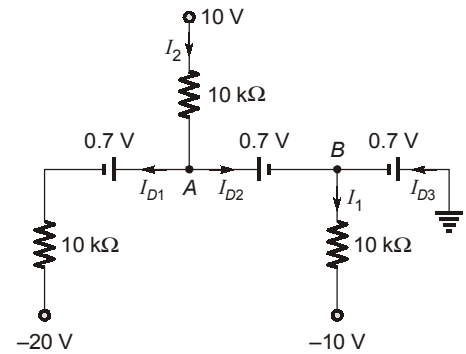

23. (a)

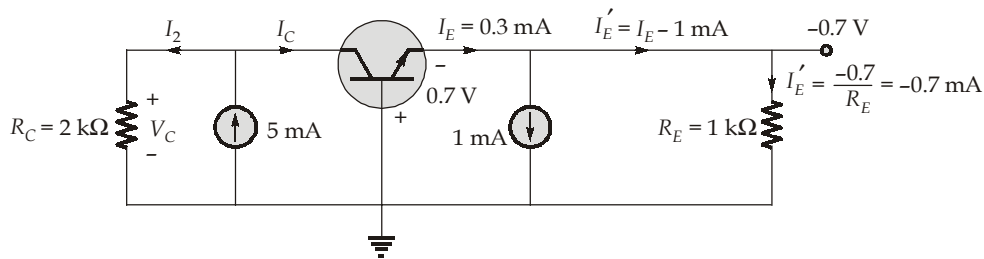

now,
$$I_E = I_E' + 1 \text{ mA}$$

$$I_E = 1 \text{ mA} - 0.7 \text{ mA} = 0.3 \text{ mA}$$

now,
$$I_C = \alpha I_E$$

$$\alpha = \frac{\beta}{1 + \beta} = \frac{99}{1 + 99} = 0.99$$

$$\therefore I_C = 0.99 \times 0.3 = 0.297 \text{ mA}$$

$$\therefore I_2 + I_C = 5 \text{ mA}$$

$$I_2 = 5 \text{ mA} - I_C = 4.703 \text{ mA}$$


$$\therefore V_C = I_2 \cdot R_C = 4.703 \times 2$$

$$V_C = 9.406$$

$$\therefore V_{CE} = 9.406 + 0.7 = 10.1 \text{ V}$$

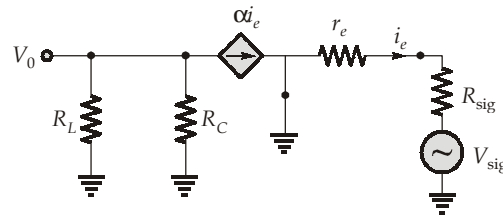24. (b)

The small signal r_e equivalent circuit can be drawn as



$$V_0 = -\alpha(R_C \parallel R_L)i_e \quad \dots(i)$$

and
$$i_e = \frac{-V_{sig}}{R_{sig} + r_e} \quad \dots(ii)$$

Combining equation (i) and (ii), we get,

$$V_0 = \frac{\alpha(R_C \parallel R_L)}{R_{sig} + r_e} \cdot V_{sig}$$


thus,
$$\frac{V_0}{V_{sig}} = \frac{\alpha(R_C \parallel R_L)}{R_{sig} + r_e}$$

25. (c)

The small signal equivalent model can be drawn as

∴ The output can be expressed as,
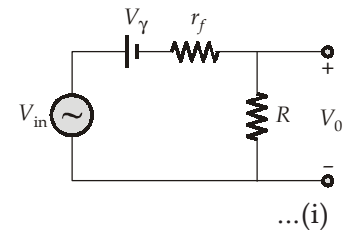
$$V_0 = \frac{R}{R + r_f} V_{in} - \frac{R}{R + r_f} V_\gamma$$




Thus, the slope of line in the graph of the input output curve can be written

$$\text{Slope} = \frac{R}{R + r_f} = \frac{1.2}{2 - 0.7} = \frac{1.2}{1.3} \quad \dots \text{from equation (i)}$$

Thus,
$$r_f = 83.33 \, \Omega$$

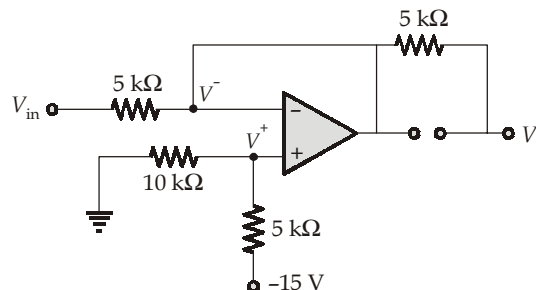26. (b)

Case -I : When $V_{in} > -10 \text{ V}$, then the voltage across diode D_1 is positive so diode D_1 is in ON state, and therefore the equivalent circuit can be drawn as



$$V^+ = -15 \times \frac{10}{15} = -10 \text{ V}$$

Due to virtual ground, $V^+ = V^- = -10 \text{ V}$


and $V_0 = V^- = -10 \text{ V}$

∴ $V_0 = -10 \text{ V}$

Case -II : When $V_{in} < -10\text{ V}$

$$V_0 = +V_{sat}$$

Thus,

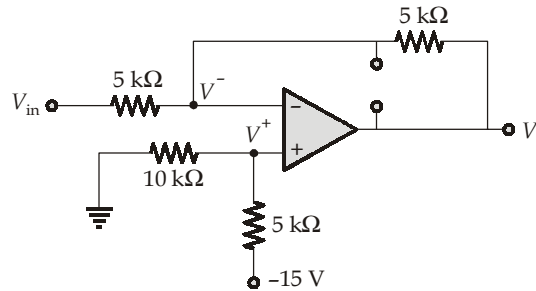

$$\therefore V_0 = -\frac{5}{5} \times V_{in} = -V_{in} \text{ (for } V_{in} < -10\text{ V)}$$


Alternately, we can write the equation of the graph by applying KCL at node V^-

$$\therefore V^- = V^+ = -10\text{ V}$$

$$\frac{-10 - V_{in}}{5\text{ k}\Omega} + \frac{-10 - V_0}{5\text{ k}\Omega} = 0$$


$$-20 - V_{in} - V_0 = 0$$

$$V_0 = -V_{in} - 20$$

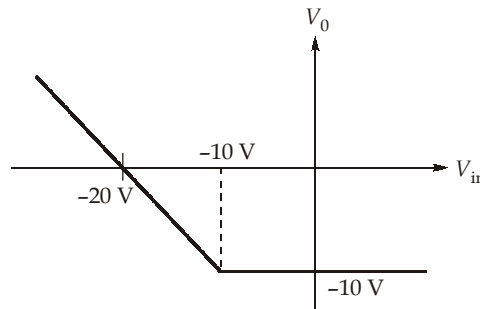

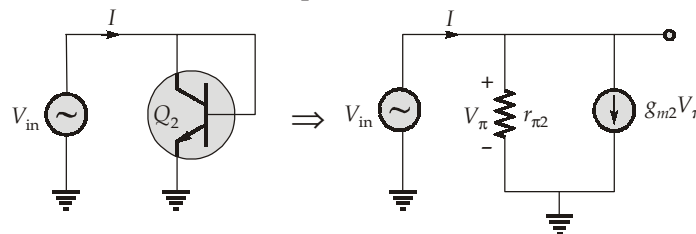27. (b)

For transistor Q_2 , we can calculate the equivalent resistance as



$$\therefore I = \frac{V_{\pi}}{r_{\pi 2}} + g_{m 2} V_{\pi}$$

Now,


$$V_{in} = V_{\pi}$$

$$\therefore \frac{I}{V_{in}} = \frac{1}{r_{\pi 2}} + g_{m 2}$$

or

$$R' = r_{\pi 2} \parallel \frac{1}{g_{m 2}}$$

Now, the circuit can be redrawn as

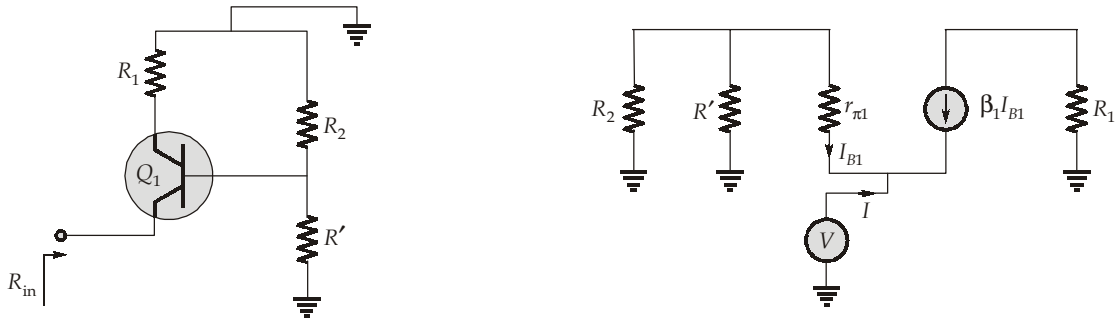

$$I = -I_{B1} - \beta_1 I_{B1}$$

$$I = -(1 + \beta_1) I_{B1}$$

Now,

$$I_{B1} = \frac{-V}{r_{\pi 1} + R' || R_2}$$

$$\therefore \frac{V}{I} = \frac{r_{\pi 1} + R' || R_2}{\beta_1 + 1}$$


$$\therefore R_{in} = \frac{1}{\beta_1 + 1} \left(r_{\pi 1} + \frac{1}{g_{m2}} || r_{\pi 2} || R_2 \right)$$

$$\therefore \text{where, } \beta_1 = 99$$

$$\therefore R_{in} = \frac{1}{100} \left(r_{\pi 1} + \frac{1}{g_{m2}} || r_{\pi 2} || R_2 \right)$$

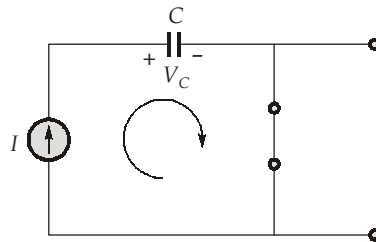28. (c)


For negative cycle $V_{in} < 3.2$ V always, thus the MOSFET M_1 will be OFF and diode D_1 will be ON



$$\therefore V_C = \frac{I}{C} \cdot t$$

$$\Rightarrow V_C = \frac{I}{C} \cdot T_{off} = \frac{I}{C} (1 - D) T$$

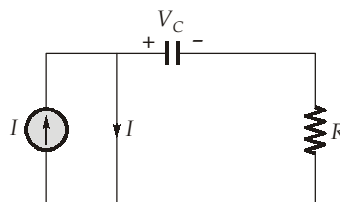Now, when $V_{in} > 3.2$ V, thus the MOSFET transistor will be switched ON and hence



Now, since R is very large, thus, V_c will not reduce substantially and thus, V_c will not change during the positive going pulse.

Hence, after 5 clock pulse value of V_c

$$V_c = \frac{5I}{C}(1-D)T$$

29. (d)

$$I_D = k_n(V_{GS} - V_{th})^2 (1 + \lambda V_{DS})$$

$$r_0 = \frac{\Delta V_{DS}}{\Delta I_D} = \frac{1}{(\partial I_D / \partial V_{DS})}$$

$$\frac{\partial I_D}{\partial V_{DS}} = k_n(V_{GS} - V_{th})^2 \lambda$$

at

$$V_{GS} = 0.5, \quad I_D = 1 \text{ mA}$$

so,

$$1 \text{ mA} = k_n(V_{GS} - V_{th})^2 (1 + 0.05)$$

$$k_n(V_{GS} - V_{th})^2 = \frac{1}{1.05} \text{ m}\mathcal{U}$$

$$r_0 = \frac{1.05}{0.1} \text{ k}\Omega = 10.5 \text{ k}\Omega$$

30. (b)

For the transistor

$$V_S = V_B = V_A$$

due to virtual ground,

thus,

$$V_S = 0 \text{ V}$$

Hence,

$$I_D = \frac{0 - (-10)}{10 \times 10^3} = 1 \text{ mA}$$

$$I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

$$\therefore V_{GS} - V_T = \sqrt{\frac{I_D}{\frac{\mu_n C_{ox} W}{2L}}}$$

$$V_{GS} - V_T = \sqrt{\frac{1 \times 10^{-3}}{\frac{0.5 \times 10^{-3}}{2}}}$$

$$V_{GS} - V_T = 2 \text{ V}$$

For the MOSFET to be in saturation region

$$V_{DS} \geq V_{GS} - V_T$$

\therefore at the edge of saturation

$$V_{DS} = V_{GS} - V_T = 2 \text{ V}$$

\therefore

$$V_S = 0$$

\therefore

$$V_D = V_G - V_T$$

\Rightarrow

$$V_{DD} = 2 \text{ V}$$

