



MADE EASY

Leading Institute for ESE, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

DC Machine

ELECTRICAL ENGINEERING

Date of Test: 24/07/2024

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (b) | 13. (c) | 19. (c) | 25. (c) |
| 2. (b) | 8. (d) | 14. (b) | 20. (b) | 26. (b) |
| 3. (a) | 9. (c) | 15. (a) | 21. (a) | 27. (d) |
| 4. (b) | 10. (a) | 16. (b) | 22. (b) | 28. (a) |
| 5. (d) | 11. (a) | 17. (a) | 23. (b) | 29. (a) |
| 6. (a) | 12. (b) | 18. (b) | 24. (d) | 30. (a) |

DETAILED EXPLANATIONS

1. (a)

For series DC motor,

$$T \propto I^2$$

as torque is constant means current also remains constant

$$T = \frac{E_b I_a}{\omega}$$

as both T and I_a as constant

$$E_b \propto \omega$$

In case of series connection $E_b \approx V/2$

for parallel connection, $E_b \approx V$

So speed becomes double


2. (b)

Back emf is given by,

$$E_b = \frac{NP\phi Z}{A \times 60}$$

$$= \frac{1000 \times 0.15 \times 100}{60} = 250 \text{ V}$$
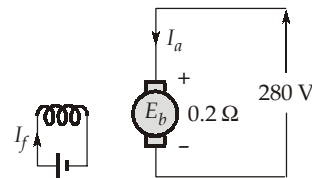
$$I_a = \frac{280 - 250}{0.2} = 150 \text{ A}$$



3. (a)

Let, induced emf = x

$$x + I_a r_a = 300 \text{ V} \quad \dots(i)$$

When load is reduced to half,

$$x + \frac{I_a r_a}{2} = 250 \text{ V} \quad \dots(ii)$$

Solving equation (i) and (ii), we get

$$\text{Induced emf, } x = 200 \text{ V}$$

4. (b)

For maximum efficiency,

Constant loss = losses proportional to square of variable

$$\text{Cu loss} = I^2 R$$

Brush loss $\propto I$ (so it is not included in constant losses)

$$\text{So, Constant loss} = 150 + 200 + P_i$$

$$150 + 200 + P_i = 400$$

$$P_i = 50 \text{ W}$$

5. (d)

For series motor, $T \rightarrow \text{Torque}$

$$T \propto I_a^2$$


or, $I_a \propto \sqrt{T} \quad \dots(i)$

and also, $E_b \propto N\phi$
 or $E_b \propto NI_a$ (as $\phi \propto I_a$)
 $N \propto \frac{E_b}{I_a}$

From equation (i),

$$N \propto \frac{E_b}{\sqrt{T}}$$

6. (a)

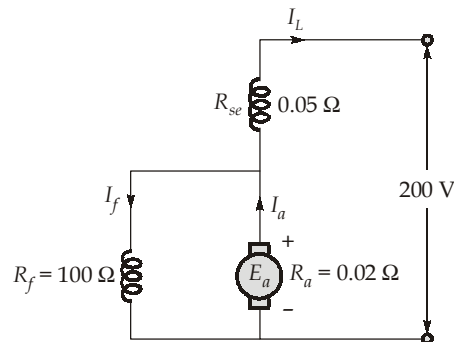

Rated load at rated terminal voltage,

$$I_L = \frac{20000}{200} = 100 \text{ A}$$

Using dc generator equation,

$$E = V + I_a R_a + I_L R_{se} + V_{BD}$$

$$E_a = I_a R_a + I_L R_{se} + V_{BD} + 200$$

...(i)

and $I_a = I_f + I_L$

...(ii)

and $I_f = \frac{200 + I_L \times R_{se}}{100}$

$$= \frac{200 + 100 \times 0.05}{100}$$

$$I_f = 2.05 \text{ A}$$

From equation (ii),

$$I_a = 2.05 + 100 = 102.05$$

From equation (i),

$$E_a = 102.05 \times 0.02 + 100 \times 0.05 + 200 + 2$$

$$= 209.041 \text{ V}$$

7. (b)

We know that,

$$E_g = K\phi \omega_m$$

$$E_g = KK_f I_f \omega_m$$

$$\frac{E_g}{I_f} = R_f = KK_f \omega_m$$

$$R_f = K' \omega_m = 1 \times \left(\frac{2\pi N}{60} \right) = 1 \times \left(\frac{2\pi \times 1450}{60} \right)$$

Critical field resistance, $R_f = 151.84 \Omega$

8. (d)

We know,

$$\text{Pole pitch} = \frac{\text{Periphery of armature}}{\text{No. of poles}} = \frac{2\pi r}{P} = \frac{\pi \times 0.4}{6}$$

$$\frac{\text{Pole arc}}{\text{Pole pitch}} = 0.8$$

$$\therefore \text{Pole arc} = \frac{0.8 \times \pi \times 0.4}{6} = 0.168 \text{ m}$$

$$\text{Area of pole face} = 0.168 \times 0.2 = 0.0336 \text{ m}^2$$

$$\text{Emf, } E_b = \frac{P\phi ZN}{60 A}$$

$$\Rightarrow 300 = \frac{600 \times 6 \times \phi \times 1000}{60 \times 2} = 0.01 \text{ Wb}$$

$$\text{Flux density} = \frac{\phi}{A} = \frac{0.01}{0.0336} = 0.2976 \text{ T}$$

9. (c)

$$\text{Torque developed in motor} = \frac{\text{Power developed in armature}}{\left(\frac{2\pi N}{60}\right)}$$

$$T = \frac{E_b \cdot I_a \times 60}{2\pi N}$$

$$= \frac{\phi z N P}{60 A} \times \frac{I_a \times 60}{2\pi N} \quad [P = A, \text{ since it is lap winding}]$$

$$T = \frac{\phi z I_a}{2\pi} = \frac{23 \times 10^{-3} \times 60 \times 20 \times 50}{2\pi} = 219.63 \text{ Nm}$$

10. (a)

In a wave winding the armature current get equally divided between two parallel paths but in lap winding there can be a problem of circulating currents between two parallel paths and hence causing unequal currents in both paths.

11. (a)

$$AT_{CW}/\text{Pole} = AT_a(\text{peak}) \times \frac{\text{Pole arc}}{\text{Pole pitch}}$$

$$= 20000 \times 0.8 = 16000$$

$$AT_a(\text{peak}) \text{ interpolar region} = 20000 - 16000 = 4000$$

$$AT_i = AT_a(\text{peak}) + \frac{B_i}{\mu_0} l_{gl}$$

$$= 4000 + \left[\frac{0.3}{4\pi \times 10^{-7}} \times 1.2 \times 10^{-2} \right] = 6865 \text{ AT/P}$$


$$N_i = \frac{6865}{1000} \approx 7 \text{ turns}$$

12. (b)

$$\text{No load loss} = 200 \times 10 = 2000 \text{ W}$$


$$I_f = \frac{200}{100} = 2 \text{ A}$$
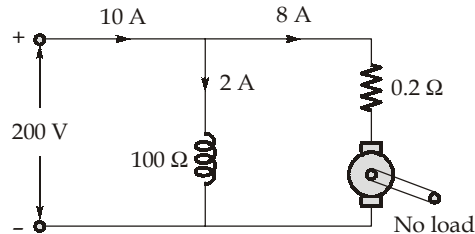
$$\begin{aligned} \text{Core loss} &= (200 \times 8) - (8^2 \times 0.2) \\ &= 1587.2 \text{ W} \end{aligned}$$



At load:
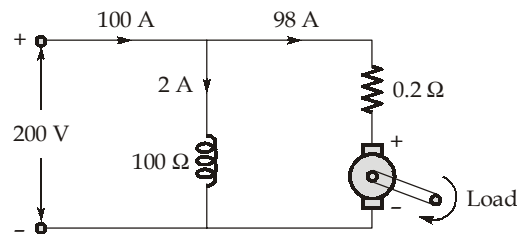
$$\text{Stray load loss} = 0.5 \times 2000 = 1000 \text{ W}$$



$$P_L = (I_a^2 R_a + V_{\text{brush}} I_a + P_{\text{stray}}) + (P_{\text{core}} + P_{\text{shunt field}})$$

$$P_L = (98^2 \times 0.2) + (2 \times 98) + 1000 + 1587.2 + (200 \times 2)$$

$$P_L = 5.104 \text{ kW}$$

13. (c)

$$\begin{aligned} \text{Compensating winding, } AT/\text{pole} &= \text{armature AT/pole} \times \frac{\text{Pole arc}}{\text{Pole pitch}} \\ &= 19000 \times 0.7 = 13300 \end{aligned}$$

$$\text{Turn/pole} = \frac{AT_{cw} / \text{pole}}{\text{Armature current}} = \frac{13300}{1000} = 13.3 \approx 14$$

No. of compensating conductor per pole,


$$14 \times 2 = 28$$

$$\text{AT for airgap under interpole} = \frac{B_g}{\mu_0} l_g = \frac{0.3}{4\pi \times 10^{-7}} \times 1 \times 10^{-2} = 2387.324 \text{ ATs}$$

$$\text{Net AT for interpole} = 19000 + 2387.324 - 14000$$

$$\text{No. of turns in interpole} = \frac{19000 + 2387.324 - 14000}{1000} \approx 8$$

14. (b)

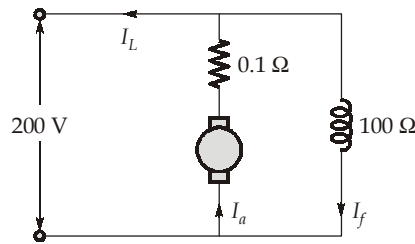

As generator:

$$\text{Load current, } I_{L1} = \frac{60 \times 1000}{200} = 300 \text{ A}$$

$$\text{Armature current, } I_{a1} = I_{L1} + I_f = 300 + \frac{200}{100} = 302 \text{ A}$$

Generator induced emf, $E_{g1} = V_t + I_{a1}R_a + \text{brush drop}$

$$E_{g1} = 200 + 2 + 302 \times 0.1 = 232.2 \text{ V}$$

When belt breaks it will behave as motor then

$$I_{L2} = \frac{5000}{200} = 25 \text{ A}$$

Now,

$$I_{a2} = I_{L2} - I_f = 25 - 2 = 23 \text{ A}$$

$$E_{b2} = 200 - 2 - 23 \times 0.1 = 195.7 \text{ V}$$

as $E \propto N\phi$ or $E \propto N$ $\phi \rightarrow \text{constant}$


$$\frac{E_{b1}}{E_{b2}} = \frac{N_1}{N_2}$$

$$\Rightarrow \frac{232.2}{195.7} = \frac{500}{N_2}$$

$$\Rightarrow \text{Speed, } N_2 = 421.4 \text{ rpm}$$

15. (a)

At full load:

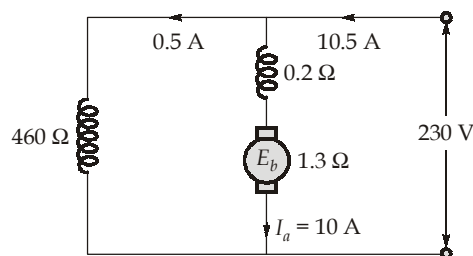

At full load,

$$\text{Armature current, } I_a = 10.5 - \frac{230}{460} = 10 \text{ A}$$

$$\begin{aligned} \text{Back emf, } E_b &= V - I_a(R_a + R_{se}) \\ &= 230 - 10(1.3 + 0.2) \end{aligned}$$

$$E_b = 215 \text{ Volt}$$

$$\begin{aligned} \therefore \text{Power developed in armature} &= E_b \cdot I_a \\ &= 215 \times 10 = 2150 \text{ Watt} \end{aligned}$$

Given that, rotational losses is 5% of power developed

$$\begin{aligned} P_{\text{output}} &= 0.95 \times P_{\text{developed}} \\ &= 0.95 \times 2150 \\ &= 2042.5 \text{ Watt} \end{aligned}$$

$$\therefore \text{Efficiency, } \eta = \frac{P_{\text{output}}}{P_{\text{input}}} = \frac{2042.5}{230 \times 10.5} = 0.8457 \text{ (or) } 84.57\%$$

16. (b)

$$\text{Time constant} = \frac{L}{r} = 0.2; \quad I^2 r = 400 \text{ W}$$

$$\begin{aligned} \text{Energy stored in Joules} &= \frac{1}{2} L I^2 = \frac{1}{2} \times I^2 r \times \frac{L}{r} \\ &= \frac{1}{2} \times 400 \times 0.2 = 40 \text{ Joules} \end{aligned}$$

17. (a)

$$\begin{aligned} V_{t1} &= 400 \text{ V}; & I_{a1} &= 150 \text{ A} \\ R_a &= 0.12 \text{ } \Omega; & N_1 &= 1500 \text{ rpm} \end{aligned}$$

The value of load resistance,

$$R_L = \frac{400}{150} = 2.67 \text{ } \Omega$$

Load current 100 A, the terminal voltage,

$$V_{t2} = 100 \times R_L = 100 \times 2.67 = 267 \text{ V}$$

$$I_{a2} = 100 \text{ A}; \quad R_a = 0.12 \text{ } \Omega$$

$$E_g = \frac{\phi N Z}{60} \times \left(\frac{P}{A} \right) \Rightarrow E_g \propto N$$

$$\frac{E_{g1}}{E_{g2}} = \frac{N_1}{N_2} = \frac{V_{t1} + I_{a1} R_a}{V_{t2} + I_{a2} R_a}$$

$$\Rightarrow \frac{400 + 150 \times 0.12}{267 + 100 \times 0.12} = \frac{1500}{N_2}$$

$$N_2 = 1001.19 \text{ rpm}$$

18. (b)

There is a change of flux/pole due to armature reaction,

$$E_G \propto \phi_1 N_1$$

$$\Rightarrow I_f = \frac{230}{200} = 1.15 \text{ A}$$

$$(V - IR) \propto \phi_1 N_1$$

$$[230 - (10 - 1.15)(0.1)] \propto 1400 \phi_1 \quad \dots(1)$$

$$[230 - (200 - 1.15)(0.1)] \propto N_2 \phi_2 \quad \dots(2)$$

Equation (2) divided by (1),

$$\frac{210.1}{229.1} = \frac{N_2}{1400} \times 0.96$$

$$\Rightarrow N_2 = 1337 \text{ rpm}$$

$$\therefore \text{Torque developed } (T_d) = \frac{210.115 \times (200 - 1.15)}{\left(\frac{2\pi \times 1337}{60}\right)} = 298.4 \text{ N-m}$$

19. (c)

$$V = 240 \text{ V}, \quad I_a = 40 \text{ A}$$

$$N_1 = 1500 \text{ rpm}, \quad R_a = 0.3 \Omega$$

$T \propto I_a^2$, since the torque is constant.

$$\therefore I_{a1}^2 = I_{a2}^2$$

$$\Rightarrow I_{a1} = I_{a2} = 40 \text{ A}$$

During starting the induced emf is zero, hence the current is limited only by the resistance in the armature circuit.

$$\therefore \text{Total resistance} = \frac{240}{40} = 6 \Omega$$

Extra resistance to be added in series with armature = $6 - 0.3 = 5.7 \Omega$

20. (b)

$$E_a = K_a \phi N \Rightarrow \phi = \frac{E_a}{K_a N}$$

$$\phi = \frac{V - I_a R_a}{K_a N}$$

$$\phi_{(\text{no-load})} = \left[\frac{250 - 1.6 \times 0.7}{K_a \times 1250} \right] = \frac{0.1991}{K_a}$$

$$\phi_{\text{load}} = \left[\frac{250 - 40 \times 0.7}{1150 \times K_a} \right] = \frac{0.193}{K_a}$$

\therefore Reduction in ϕ due to armature redrawn

$$= \left(\frac{0.1991 - 0.193}{0.1991} \right) \times 100 = 3.06\%$$

21. (a)

We know, Field current, $I_f = \frac{400}{200} = 2 \text{ A}$

At no load, $I_{a0} = 5.6 - 2 = 3.6 \text{ A}$

$$E_{a0} = 400 - (0.18 \times 3.6) - 2 = 397.35 \text{ V}$$

At full load, $I_a(fl) = 60.3 - 2 = 58.3 \text{ A}$

$$E_a(fl) = 400 - 0.18 \times 58.3 - 2 = 387.506 \text{ V}$$

Assuming initial flux be ϕ ,

New flux value due to weakening,

$$\phi' = (1 - 0.04)\phi = 0.96 \phi$$

$$\frac{n(fl)}{n(nl)} = \frac{387.506}{397.35} \times \frac{1}{0.96} = 1.016$$

22. (b)

We know, flux/pole = $\frac{\pi D l}{P} \times \text{pole pitch}$

$$= \frac{\pi \times 30 \times 10^{-2}}{4} \times 20 \times 10^{-2} \times 0.4 = 0.0188 \text{ Wb}$$

Induced emf, $E = \frac{P\phi n Z}{60 A} = \frac{0.0188 \times 1500 \times 400}{60} = 188 \text{ V}$

Gross mechanical power developed

$$= \frac{188 \times 30}{1000} = 5.64 \text{ kW}$$

Torque developed = $\frac{5.64 \times 1000}{\frac{2\pi \times 1500}{60}} = 35.905 \text{ N-m}$

23. (b)

Number of coils = 32,

Turns in each coil = 6

Total number of turn = $32 \times 6 = 192$ Total number of conductor = $192 \times 2 = 384$

In wave wound configuration,

$$A = 2$$

Induced emf, $E = \frac{P\phi N Z}{60 A} = \frac{P\phi N Z}{60 \times 2}$

$$= \frac{6 \times 0.08 \times 384 \times 360}{60 \times 2} = 552.96 \text{ V}$$

24. (d)

For dc series motor, $T \propto I_a^2$

$$\frac{T_1}{T_2} = \frac{I_{a1}^2}{I_{a2}^2}$$

When,

$$I_{a1} = 40 \text{ A}$$

$$E_b = V_t - I_{a1}(R_{se} + R_a) = 200 - 40(2)$$

$$= 200 - 80 = 120 \text{ V}$$

At field current,

$$I_f = 40 \text{ A}$$

$$E_b = 194 \text{ V}$$

$$E_b \propto \phi_N \propto NI_f$$

$$\frac{120}{194} = \frac{40 \times N}{40 \times 800}$$

$$N = 494.845 \text{ rpm}$$

25. (c)

Armature resistance is assumed negligible,

Also field current is ignored in comparison to armature current

$$I_L = I_a$$

$$200 = K_e \times 600 \quad \dots(i)$$

$$T = K_t \times 20 = K_L \times (600)^2 \quad \dots(ii)$$

When 20 Ω resistor added in armature circuit

$$(200 - 20I_a) = K_e \times n \quad \dots(iii)$$

$$K_t I_a = K_L n^2 \quad \dots(iv)$$

Dividing equation (iii) by (i) and (iv) by (ii),

$$\frac{200 - 20I_a}{200} = \frac{n}{600}$$

$$\frac{I_a}{20} = \frac{n^2}{(600)^2}$$

$$I_a = \frac{20n^2}{(600)^2}$$

$$1 - \frac{1}{10} \left[\frac{20n^2}{(600)^2} \right] = \frac{n}{600}$$

$$(600)^2 - 2n^2 = 600n$$

$$2n^2 + 600n - (600)^2 = 0$$

$$n = 300, -600$$

practical value, $n = 300$ rpm

$$\frac{I_a}{20} = \frac{n^2}{(600)^2} = \frac{(300)^2}{(600)^2} = \frac{1}{4}$$

$$I_a = \frac{20}{4} = 5 \text{ A}$$

26. (b)

- As torque remain rated at 1500 rpm and 1000 rpm, so armature current and flux will be same.
- At 1500 rpm, using motor equation

$$V = E_b + I_a R_a$$

$$240 = E_b + 50 \times 0.2$$

$$E_b = 230 \text{ V}$$

$$E_{b2} = \frac{N_2}{N_1} E_{b1} \quad (\text{as } \phi \text{ is constant})$$

$$E_{b2} = \frac{1000}{1500} \times 230 = 153.33 \text{ V}$$

At 1000 rpm, R_{ext} is introduced

Applying motor equation, $V = E_{b2} + I_a(R_a + R_{\text{ext}})$

$$240 = 153.33 + 50(0.2 + R_{\text{ext}})$$

$$240 = 153.33 + 10 + 50R_{\text{ext}}$$

$$R_{\text{ext}} = 1.5334 \text{ } \Omega$$

27. (d)

Given load:

100 lamps of rating 110 V, 55 W

$$\therefore \text{Line current, } I_L = \frac{100 \times 55}{110} = 50 \text{ A}$$


As the compound generator is connected in long shunt configuration

$$\text{Field current, } I_f = \frac{110 \text{ V}}{25} = 4.4 \text{ A}$$

$$\text{Armature current, } I_a = I_L + I_f = 50 + 4.4 = 54.4 \text{ A}$$

$$\begin{aligned} E_a &= V + I_a(R_a + R_{se}) \\ &= 110 + 54.4(0.06 + 0.04) \end{aligned}$$

With diverter

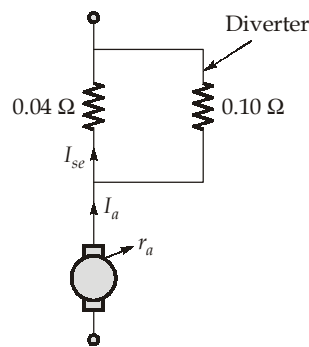

$$\text{New series field current, } I_{se}^d = 54.4 \times \frac{0.1}{0.14} = 38.857 \text{ A}$$

$$\text{Initial series field current, } I_{sc} = 54.4$$

New series field AT,

$$\frac{38.857}{54.4} \times 100 = 71.43\%$$

Then the change in ampere turn of series field = 100 - 71.43 = 28.57%

28. (a)

Given,

$$\text{Terminal voltage} = 120 \text{ V}$$

$$\text{Armature resistance, } R_a = 0.2 \text{ } \Omega$$

$$\text{shunt resistance, } R_{sh} = 60 \text{ } \Omega$$

$$I_{sh} = \frac{V}{R_{sh}} = \frac{120}{60} = 2 \text{ A,}$$

$$I_L = 50 \text{ A}$$

$$I_{a1} = I_L - I_{sh} = 50 - 2 = 48 \text{ A}$$

$$\begin{aligned} E_1 &= V - I_a R_a - \text{brush drop} = 120 - 48 \times 0.2 - 2 \\ &= 108.4 \text{ V} \end{aligned}$$

At rated speed of 1200 rpm,

$$E_1 = 108.4 \text{ V}$$

and

$$I_{a1} = 48 \text{ A (full load)}$$

$$\text{At half load, } I_{L \text{ (half)}} = \frac{50}{2} = 25 \text{ A}$$

$$I_{a2} = I_L (\text{half}) - I_{sh} = 25 - 2 = 23 \text{ A}$$

$$E_2 = V - I_a R_a - \text{brush drop} = 120 - 23 \times 0.2 - 2$$

$$= 113.4 \text{ V}$$

At half load speed, $N_2 = \frac{113.4}{108.4} \times 1200 = 1255.35 \text{ rpm}$

29. (a)

Load torque is constant,

$$T \propto \phi I_a = \text{constant}$$

Here, $\phi = \text{constant}$

So, $I_a = \text{constant}$

So, $E_{b1} = V_t - I_a R_a \quad \dots(i)$

if R_{ext} is added

$$E_{b2} = V_t - I_a (R_a + R_{ext}) \quad \dots(ii)$$

Here, $E_{b2} < E_{b1}$ so speed will decrease

(since $E_B \propto N$)

30. (a)

The back emf, $E_b = V_t - I_a R_a$
 $= 240 - 0.5 \times 25 = 227.5 \text{ Volt}$

So, Load torque, $T = \frac{E_b I_a}{N \times \frac{2\pi}{60}} = \frac{227.5 \times 25}{1200 \times \frac{2\pi}{60}} = 45.26 \text{ N-m}$

Load torque = 45.26 N-m

