



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: [www.madeeasy.in](http://www.madeeasy.in) | E-mail: [info@madeeasy.in](mailto:info@madeeasy.in) | Ph: 011-45124612

# DIGITAL LOGIC

## COMPUTER SCIENCE & IT


Date of Test : 16/09/2024

### ANSWER KEY >


- |        |         |         |         |         |
|--------|---------|---------|---------|---------|
| 1. (c) | 7. (c)  | 13. (a) | 19. (b) | 25. (d) |
| 2. (a) | 8. (a)  | 14. (b) | 20. (a) | 26. (b) |
| 3. (b) | 9. (a)  | 15. (d) | 21. (d) | 27. (d) |
| 4. (b) | 10. (d) | 16. (d) | 22. (a) | 28. (a) |
| 5. (c) | 11. (c) | 17. (d) | 23. (b) | 29. (c) |
| 6. (c) | 12. (c) | 18. (a) | 24. (b) | 30. (a) |

**DETAILED EXPLANATIONS**


1. (c)
2. (a)

 

 3. (b)  
Example:  $F(A, B, C) = \sum m(0, 2, 3, 4, 5, 7)$


 
$$F(A, B, C) = \bar{A}\bar{C} + BC + \bar{A}B$$



$$F(A, B, C) = \bar{B}\bar{C} + \bar{A}B + AC$$


$F(A, B, C)$  is having cyclic PI K-map and it is having '2' minimal forms.

In general, based on above example when the Boolean function is having cyclic prime implicants K-map it will be having 2 minimal forms.

4. (b)  
The truth table for the circuit is obtained below:

Present state		FF input		Next state	
$Q_A$	$Q_B$	$T_A$ ( $Q_A + Q_B$ )	$T_B$ ( $\bar{Q}_A + Q_B$ )	$Q_A^+$	$Q_B^+$
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0
0	0	0	1	0	1

 So, the counter counts the sequence of 3 states as



Hence, the circuit is of a MOD-3 counter.

5. (c)  
2's complement representation of -29 is 11100011.


1	0	-1
1	1	0
0	1	+1
0	0	0
0	0	0
1	0	-1
1	1	0
1	1	0

Recorded pair is : 00 - 100 + 10 - 1.

6. (c)

$$f(A, B, C, D) = BD + A'B'C' + ACD + B'CD$$

(5, 7, 13, 15) (0, 1) (11, 15) (3, 11)

 

$$f(A, B, C, D) = \sum m(0, 1, 3, 5, 7, 11, 13, 15)$$

$$= BD + CD + A'D + A'B'C'$$

7. (c)

$$(11X1Y)_8 = (12C9)_{16}$$

$$001001 X 001 Y = 0001 \underbrace{0010}_{X} 1100 \underbrace{1001}_{Y}$$

These are missing in left side. Hence  $X = 3$  and  $Y = 1$ .  
So,  $X + Y = 3 + 1 = 4$

8. (a)

Characteristic equation for J-K flip flop:

$$Q_{n+1} = J_n Q'_n + K'_n Q_n$$

Characteristic equation for S-R flip flop:

$$Q_{n+1} = S_n + R'_n Q_n$$


9. (a)

**Note:** Clock is negative edge triggered, so when clock goes from 1 → 0 then output is changes.


CLK	$Q_1$ $D_1 = Z$	$Q_2$ $D_2 = Q_1$	$Q_3$ $D_3 = Q_2$	$Q_4$ $D_4 = Q_3$	Z
	1	0	1	0	0
1	0	1	0	1	1
2	1	0	1	0	0
3	0	1	0	1	1

Output Z for next 3 clock cycles = 101.  
 Hence option (a) is correct wave form for 101.

 10. (d)  
 To generate length S we need  $\log_2 S$  flip-flop.
11. (c)  
 Now,  $X > Y$  if  
 (a)  $X_2 = 1$   
 (b)  $X_2 = 0$  and  $X_1X_0 > Y_1Y_0$



 12. (c)
- $$F = A(\bar{A} + B)(\bar{A} + B + \bar{C})$$
- $$= (A + B\bar{B} + C\bar{C})(\bar{A} + B + C\bar{C})(\bar{A} + B + \bar{C})$$
- $$= (A + B + C)(A + B + \bar{C})(A + \bar{B} + C)(A + \bar{B} + \bar{C})(\bar{A} + B + C)(\bar{A} + B + \bar{C})$$
- POS (F) =  $M_0, M_1, M_2, M_3, M_4, M_5$   
 =  $\Pi(0, 1, 2, 3, 4, 5)$
- So, SOP (F) =  $(0, 1, 2, 3, 4, 5, 6, 7) - (0, 1, 2, 3, 4, 5)$   
 =  $\Sigma(6, 7)$
- So,  $F = \Sigma(6, 7)$  and  $F = \Pi(0, 1, 2, 3, 4, 5)$
13. (a)



Level changes at points are  $t = 20, 35, 50, 65, 80, 95$  ns

14. (b)

$$\begin{aligned}
 & [D' + AB' + A'C + AC'D + A'C'D]' \\
 &= [D' + AC'D + AB' + A'C + A'C'D]' \\
 &= [D' + AC' + AB' + A' [C + C'D]]' \\
 &= [D' + AC' + AB' + A' [C + D]]' \\
 &= [D' + AC' + AB' + A'C + A'D]' \\
 (\because D' + A'D &= D' + A') \\
 &= [D' + A' + AC' + AB' + A'C]' \\
 (\because A' + A'C &= A') \\
 (\because A' + AC' + AB' &= A' + A(C' + B') = A' + C' + B') \\
 &= [D' + A' + C' + B']' \\
 &= ABCD
 \end{aligned}$$

Hence, only 1 minterm is required.

15. (d)

Let,

$$\begin{array}{rcccc}
 A = & & a_2 & a_1 & a_0 \\
 B = & & & b_1 & b_0 \\
 \hline
 A \times B = & & a_2b_0 & a_1b_0 & a_0b_0 \\
 & b_1a_2 & b_1a_1 & b_1a_0 & \downarrow \\
 \hline
 & b_1a_2 & (a_2b_0 + a_1b_1) & (a_1b_0 + b_1a_0) & a_0b_0 \\
 & C_3 & C_2 & C_1 & C_0
 \end{array}$$

Number of AND gates required  $X = 6$

Number of one bit full adders required  $Y = 3$

$$X + Y = 6 + 3 = 9$$

16. (d)

Output of ExOR Gate =  $b_i \oplus b_{i+1}$

Initially  $Q = 0$  assume

So, After 1 clock,  $Z = b_7 \oplus b_0$

After 2 clock,  $Z = b_7 \oplus b_6$

After 3 clock,  $Z = b_6 \oplus b_5$

After 4 clock,  $Z = b_5 \oplus b_4$

After 5 clock,  $Z = b_4 \oplus b_3$

After 6 clock,  $Z = b_3 \oplus b_2$


After 7 clock,  $Z = b_2 \oplus b_1$

After 8 clock,  $Z = b_1 \oplus b_0$

Which is same as Binary to gray code converter.

17. (d)  
Test for Lockout

Present State			Present Input						Next State		
Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>	J <sub>2</sub>	K <sub>2</sub>	J <sub>1</sub>	K <sub>1</sub>	J <sub>0</sub>	K <sub>0</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
0	0	0	1	0	1	1	0	1	1	1	0
0	0	1	1	1	1	1	0	1	1	1	0
0	1	0	1	0	1	1	1	1	1	0	1
1	0	1	1	1	1	0	0	0	0	1	1

 

Hence, the counter does not enter into lockout state.

18. (a)  
After 1<sup>st</sup> clock tick:

$$x_0^+ = x_0$$

$$x_1^+ = x_0 \oplus x_1$$

$$x_2^+ = (x_0 + x_1) \oplus x_2$$

$$x_3^+ = (x_0 + x_1 + x_2) \oplus x_3$$

After 2<sup>nd</sup> clock tick:

$$(x_0^+)^+ = x_0^+ = x_0$$

$$(x_1^+)^+ = x_0^+ \oplus x_1^+ = x_0 \oplus x_0 \oplus x_1 = 0 \oplus x_1 = x_1$$

$$(x_2^+)^+ = (x_0^+ + x_1^+) \oplus x_2^+ = \underbrace{(x_0 + (x_0 \oplus x_1))}_A \oplus \underbrace{(x_0 + x_1)}_B \oplus x_2$$

x <sub>1</sub>	x <sub>0</sub>	A	B	A ⊕ B
		(x <sub>0</sub> + (x <sub>0</sub> ⊕ x <sub>1</sub> ))	(x <sub>0</sub> ⊕ x <sub>1</sub> )	
0	0	0	0	0
0	1	1	1	0
1	0	1	1	0
1	1	1	1	0

$$= 0 \oplus x_2 = x_2 \quad \text{[By using above truth table]}$$

$$(x_3^+)^+ = (x_0^+ + x_1^+ + x_2^+) \oplus x_3^+$$

$$= x_3 \text{ only}$$

So, after 2 clock tick Register R contain X only.

19. (b)

We know that, for Mod-N counter  $f_o = \frac{f_i}{N}$

$$f_o = \text{Output frequency} = 8 \text{ kHz}$$

$$f_i = \text{Input frequency} = 256 \text{ kHz}$$

$$\begin{aligned} \text{Mod } N &= \frac{f_i}{f_0} \\ &= \frac{256 \text{ kHz}}{8 \text{ kHz}} = 32 \end{aligned}$$

20. (a)

$$\begin{aligned} \text{Exponent} &= 1000\ 0101 = 133 \\ \text{Biased exponent} &= \text{Actual exponent} + \text{Bias} \\ \text{Actual exponent} &= \text{Biased exponent} - \text{Bias} \\ &= 133 - 127 = 6 \\ \text{Mantissa} &= 11010000000000000000 \\ \text{Number} &= 1.1101 \times 2^6 \\ &= -1110100 \\ &= (-116)_{10} \end{aligned}$$

21. (d)

- $S_1$  is incorrect, as mentioned in question would required five 4X1 MUX instead of three.
- $S_2$  is incorrect, as it is not always the case. For example, the function  $f(x, y, z) = \sum_m(2, 4, 5, 6)$  can have different PI when group differently in K-map.

22. (a)

Truth table for BCD to excess-3 code output:

Decimal Value	Input				Output				Decimal Value
	P	Q	R	S	P	Q	R	S	
0	0	0	0	0	0	0	1	1	3
1	0	0	0	1	0	1	0	0	4
2	0	0	1	0	0	1	0	1	5
3	0	0	1	1	0	1	1	0	6
4	0	1	0	0	0	1	1	1	7
5	0	1	0	1	1	0	0	0	8
6	0	1	1	0	1	0	0	1	9
7	0	1	1	1	1	0	1	0	10
8	1	0	0	0	1	0	1	1	11
9	1	0	0	1	1	1	0	0	12

K-map for P:  $f(P, Q, R, S) = \sum m(5, 6, 7, 8, 9) + d(10, 11, 12, 13, 14, 15)$

		RS			
	PQ	00	01	11	10
00					
01			1	1	1
11		X	X	X	X
10		1	1	X	X

$$\begin{aligned} &= P + QS + QR \\ &= P + Q(S + R) \end{aligned}$$

23. (b)

$$Y = \bar{S}_1\bar{S}_0I_0 + \bar{S}_1S_0I_1 + S_1\bar{S}_0I_2 + S_1S_0I_3$$

$$I_0 = I_3 = S_1 \text{ and } I_1 = I_2 = S_0$$

$$\begin{aligned} \text{So, } Y &= \bar{S}_1\bar{S}_0S_1 + \bar{S}_1S_0S_0 + S_1\bar{S}_0S_0 + S_1S_0S_1 \\ &= \bar{S}_1S_0 + S_1S_0 = S_0 \end{aligned}$$

So, whenever  $S_0 = B$ , output ( $Y$ ) =  $B$

So, option (b) is correct.

24. (b)

We consider the last full adder far worst case delay.

Time after which output carry bit becomes available from the last full adder.

$$\begin{aligned} &= \text{total number of full address} \times \text{carry propagation delay of full adder.} \\ &= 16 \times 12 \text{ ns} = 192 \text{ ns} \end{aligned}$$

Time after which output sum bit becomes available from the last full adder.

$$\begin{aligned} &= \text{time taken for its carry in to become available} + \text{sum propagation delay of full adder.} \\ &= \{\text{total number of full address before last full adder} \times \text{carry propagation delay of full adder}\} + \\ &\text{sum propagation delay of full adder.} \\ &= \{15 \times 12 \text{ ns}\} + 15 \text{ ns} = 195 \text{ ns} \end{aligned}$$

25. (d)

$$A \oplus B = 10101101 \oplus 01101100 = 11000001$$

Now convert above binary code to gray code.

Gray of  $(11000001)_2$  is  $(10100001)_2$

$$(10100001)_2 = (161)_{10}$$

26. (b)

CLK	$Q_0$	$Q_1$	$Q_2$	$J_0 K_0$	$J_1 K_1$	$J_2 K_2$	$\bar{Q}_1 \bar{Q}_2$ (2 input gate)
0	0	0	0	1 1	1 1	1 1	1 1
1	1	0	0	1 1	1 1	1 1	1 1
2	0	1	0	1 1	1 1	1 1	0 1
3	1	1	0	1 1	1 1	1 1	0 1
4	0	0	1	1 1	1 1	1 1	1 0
5	1	0	1	1 1	1 1	1 1	1 0
6	0	1	1	1 1	1 1	1 1	0 0

Now if we will use OR gate then the flip flop will be CLR and we will get mod-6 counter from (0 to 5).

27. (d)

All the above statements are correct.



28. (a)

Clock	S, I = Y	Q <sub>3</sub>	Q <sub>2</sub>	Q <sub>1</sub>	Q <sub>0</sub>
		0	0	0	0
1	1	1	0	0	0
2	1	1	1	0	0
3	1	1	1	1	0
4	1	1	1	1	1
5	0	0	1	1	1

← Required Content

Total 5 clock cycles are required.


29. (c)

$$\text{Output of MUX} = \bar{A}Q + A\bar{Q}$$

$$\text{Output of decoder, } S = \bar{A}Q + A\bar{Q}$$

$$R = \overline{\bar{A}Q + A\bar{Q}}$$

So,

 

In SRFF

$$\begin{aligned} Q_{n+1} &= S + \bar{R}Q_n \\ &= (A \oplus Q_n) + (\overline{\overline{A \oplus Q_n}})Q_n \\ &= A \oplus Q_n \end{aligned}$$

So,  $Q_{n+1}$  is excitation equation of T-flip flop. Thus, the circuit will function as T-flip flop.

30. (a)

Johnson counter with  $n$ -flip flops has  $2n$  state.

Here,  $n = 4$

So total state is = 8

$$\begin{aligned} &= n \times 2 + 0.1 \text{ ms} \\ &= 8 \times 2 + 0.1 = 16.1 \text{ ms} \end{aligned}$$

