

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612**ELECTRICAL ENGINEERING****ELECTRIC CIRCUITS****Duration : 1:00 hr.****Maximum Marks : 50**


Read the following instructions carefully

1. This question paper contains **30** objective questions. **Q.1-10** carry one mark each and **Q.11-30** carry two marks each.
2. Answer all the questions.
3. Questions must be answered on Objective Response Sheet (**ORS**) by darkening the appropriate bubble (marked **A, B, C, D**) using HB pencil against the question number. Each question has only one correct answer. In case you wish to change an answer, erase the old answer completely using a good soft eraser.
4. There will be **NEGATIVE** marking. For each wrong answer **1/3rd** of the full marks of the question will be deducted. More than one answer marked against a question will be deemed as an incorrect response and will be negatively marked.
5. Write your name & Roll No. at the specified locations on the right half of the **ORS**.
6. No charts or tables will be provided in the examination hall.
7. Choose the **Closest** numerical answer among the choices given.
8. If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that questions.
9. If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO


Q.No. 1 to Q.No. 10 carry 1 mark each

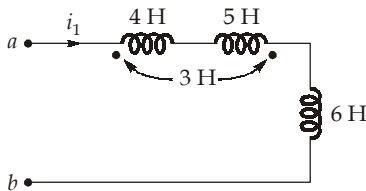Q.1 If $i_1 = 2 \cos 500t$ A in the network of given figure, then the value of the maximum energy stored in the network is




- (a) 18 J (b) 16 J
(c) 6 J (d) 42 J

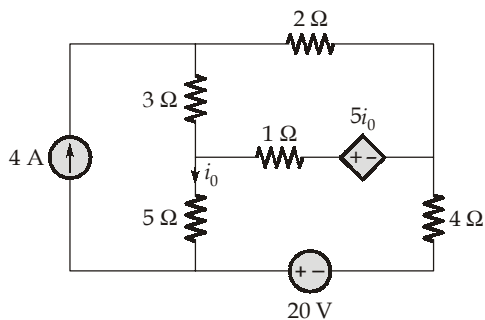Q.2 For the circuit shown in figure, the current i_0 is



- (a) -0.4705 A (b) 8.4705 A
(c) 3.4705 A (d) -2.3705 A

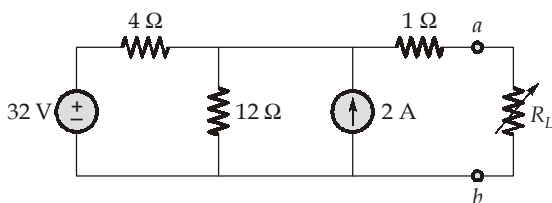Q.3 For the circuit shown in figure, the Thevenin voltage across the terminals a and b is



- (a) 20 V (b) 30 V
(c) -10 V (d) 15 V

Q.4 If the current through a 0.1 H inductor is $i(t) = 10t e^{-5t}$ A, then the energy stored at $t = 1$ sec is

- (a) 91×10^{-6} J
(b) 333×10^{-6} J
(c) 500×10^{-3} J
(d) 227×10^{-6} J


Q.5 A balance abc - sequence Y-connected source with $V_{an} = 100 \angle 10^\circ$ V is connected to a Δ -connected balanced load $(8 + 4j) \Omega$ per phase. The line current I_c is

- (a) $33.54 \angle 103.43^\circ$ (b) $58.1 \angle 103.43^\circ$
(c) $19.36 \angle -138.4^\circ$ (d) $41.3 \angle 133.43^\circ$

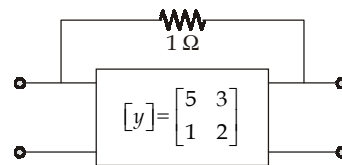Q.6 The y -parameters of a two-port network are


$$[y] = \begin{bmatrix} 5 & 3 \\ 1 & 2 \end{bmatrix} S$$

A resistor of 1Ω is connected across as shown in figure below. The new y -parameter would be




- (a) $\begin{bmatrix} 6 & 4 \\ 2 & 3 \end{bmatrix} S$ (b) $\begin{bmatrix} 6 & 2 \\ 0 & 3 \end{bmatrix} S$
(c) $\begin{bmatrix} 5 & 4 \\ 2 & 2 \end{bmatrix} S$ (d) $\begin{bmatrix} 4 & 4 \\ 2 & 1 \end{bmatrix} S$

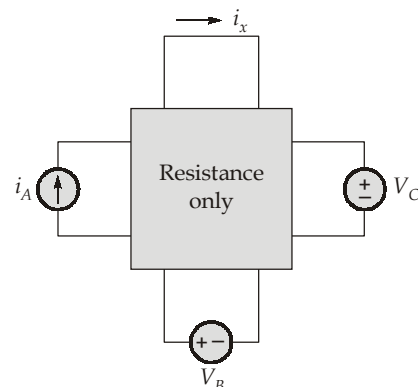Q.7 With sources i_A and V_B on in the circuit of figure and $V_C = 0$, $i_x = 20$ A, with i_A and V_C on and $V_B = 0$, $i_x = -5$ and finally, with all three sources on, $i_x = 12$ A. If the only source V_B is operating, then the value of i_x is




- (a) 17 A (b) -8 A
(c) 32 A (d) 7 A

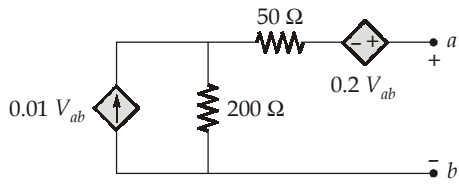Q.8 The network circuit is shown figure, the value of R_{th} across the terminals a and b is




- (a) -208.33Ω (b) 192Ω
 (c) -152Ω (d) 133.43Ω

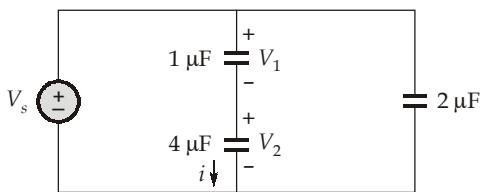Q.9 For the circuit shown in figure, $v_s = 100e^{-80t}$ and $v_1(0) = 20$ V. The value of $V_1(t)$ for $t \geq 0$ is



- (a) $-60 e^{-80t} + 80$ V (b) $100 e^{-80t} - 80$ V
 (c) $80 e^{-60t} - 60$ V (d) $80 e^{-80t} - 60$ V

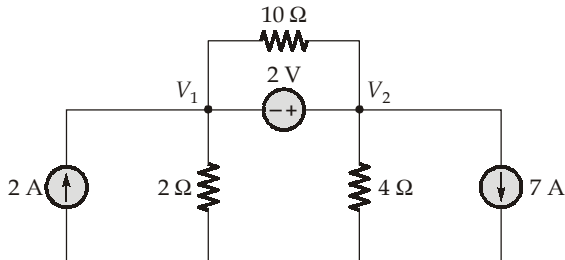
Q.10 For the circuit shown in figure, the node voltage V_2 is,



- (a) -3.33 V (b) -7.33 V
 (c) -5.33 V (d) -9.33 V


Q. No. 11 to Q. No. 30 carry 2 marks each

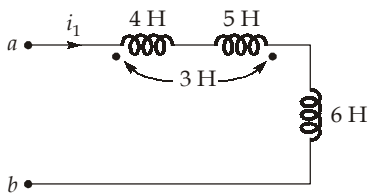Q.11 If $i_1 = 2 \cos 500t$ A in the network of given figure, then the value of the maximum energy stored in the network is




- (a) 18 J (b) 16 J
 (c) 6 J (d) 42 J

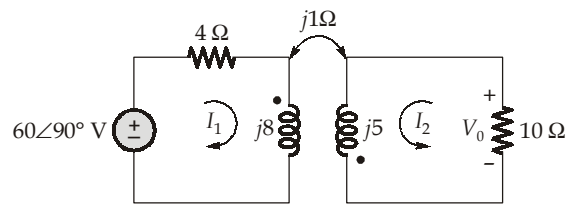Q.12 For the circuit shown in figure, voltage V_0 across the 10Ω resistance is




- (a) $-6j$ (b) $+8j$
 (c) $-16j$ (d) $9j$

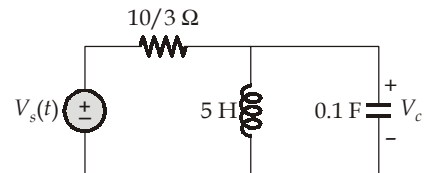Q.13 Consider the circuit shown in figure. Assume that at $t = 0$, -1 A flows through the inductor and $+5$ V is across the capacitor. If $V_s = 10 u(t)$ V, then the value of the voltage across the capacitor is



- (a) $(25e^{-t} - 20e^{-2t})u(t)$ V
 (b) $(17.5e^{-t} - 12.5e^{-2t})u(t)$ V
 (c) $(30e^t - 25e^{2t})u(t)$ V
 (d) $(35e^{-t} - 30e^{-2t})u(t)$ V

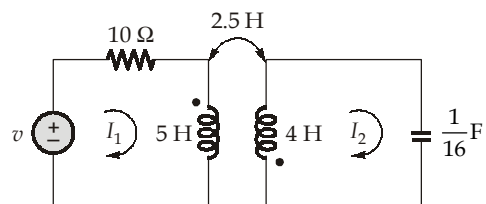Q.14 The circuit shown in figure, if the voltage $v = 60 \cos(4t + 30^\circ)$ V, then the energy stored in the coupled inductors at time $t = 1$ s, will be




- (a) 20.5 J (b) 28.5 J
 (c) 14.5 J (d) 42.5 J

Q.15 A parallel resonant circuit has impedance at $s = -50 \pm j1000s^{-1}$ and a zero at the origin. If $C = 1 \mu\text{F}$, then the value of L is


- (a) 9.89 H (b) 0.997 H
 (c) 99.79 H (d) 0.00997 H

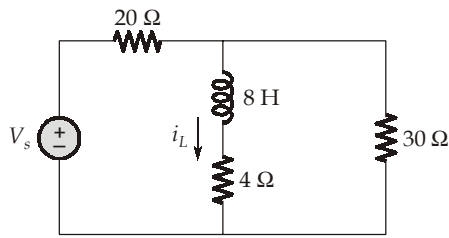Q.16 If $V_s = [-5 + 12 u(t) + 3 \delta(t)]$ V for the circuit shown. The expression of $i_L(t)$ for $t > 0$ is,




- (a) $\left(\frac{21}{80} - \frac{3}{80} e^{-2t}\right) u(t)$
- (b) $\left(\frac{31}{81} - \frac{21}{80} e^{-2t}\right) u(t)$
- (c) $\left(\frac{51}{80} - \frac{31}{80} e^{-2t}\right) u(t)$
- (d) $\left(\frac{3}{80} - \frac{21}{80} e^{-2t}\right) u(t)$

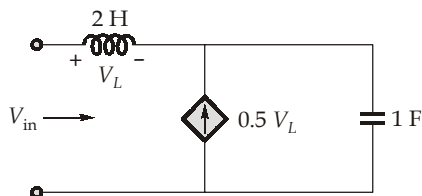Q.17 The input admittance of the circuit represents a parallel combination of a resistance R and an inductance L . If $\omega = 1$ rad/s then the value of R and L is




- (a) $R = 0.5 \Omega, L = 2$ H
- (b) $R = 0.5 \Omega, L = 0.5$ H
- (c) $R = 2 \Omega, L = 2$ H
- (d) $R = 2 \Omega, L = 0.5$ H

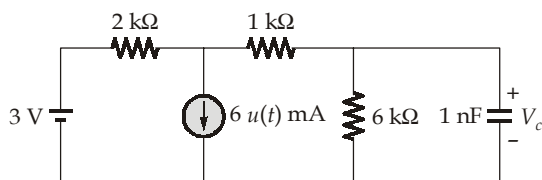Q.18 A network circuit is shown below. The value of V_c at $t = 2 \mu$ s is



- (a) -3.06 V
- (b) 12.01 V
- (c) -14.02 V
- (d) 6.07 V

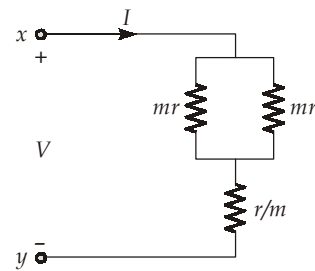Q.19 For the circuit current to be maximum the value of m will be



- (a) $\sqrt{2}$
- (b) $\sqrt{3}$
- (c) $\sqrt{5}$
- (d) $\sqrt{7}$


Q.20 A voltage waveform $v(t)$ can be expressed as,

$$v(t) = \begin{cases} 100(1 - e^{-10t}) \text{ V} & \text{for } 0 < t < 1 \\ 100e^{-10t} \text{ V} & \text{for } 1 < t < 2 \end{cases}$$

The rms value of the voltage wave upto $t = 2$ is


- (a) 65.25 V
- (b) 35.75 V
- (c) 31.25 V
- (d) 19.32 V

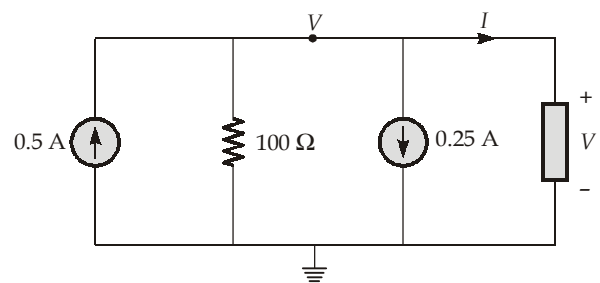Q.21 The power absorbed by the unknown element, if 0.5 A source supplies 1 W to the circuit.




- (a) 0.23 W
- (b) 0.46 W
- (c) 0.69 W
- (d) 0.26 W

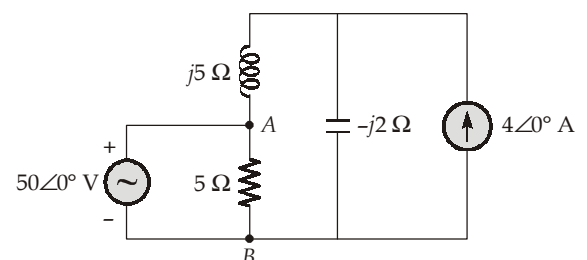Q.22 The voltage V_{AB} for the network shown below:



- (a) 0 V
- (b) $150 \angle 0^\circ$ V
- (c) $50 \angle 0^\circ$ V
- (d) $200 \angle 0^\circ$ V

Q.23 For the circuit shown below:

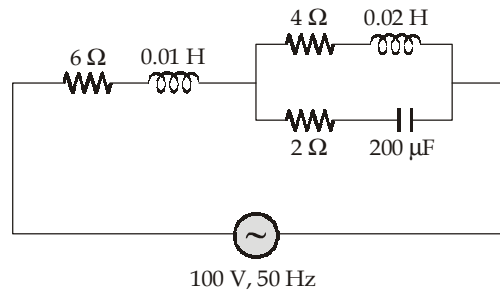


The input power factor is _____.

- (a) 0.899 (b) 0.86
(c) 0.60 (d) 0.30

Q.24 The relative heating effects of two current waves (having same peak value), one sinusoidal and the other, rectangular in shape will be _____.

- (a) 1 : 2 (b) 1 : $\sqrt{2}$
(c) 1 : $\sqrt{3}$ (d) 1 : 3


Q.25 For the circuit shown below.

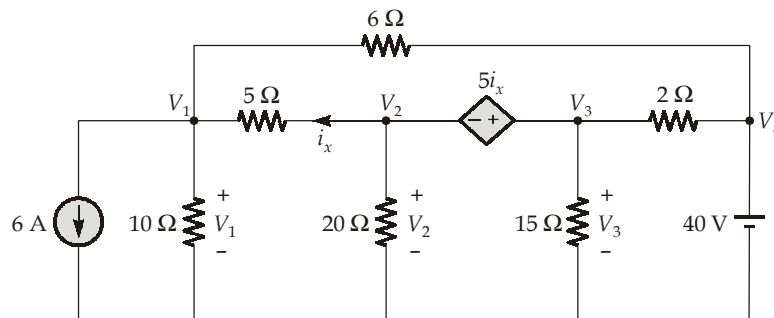

The node voltage V_3 will be _____ V.

- (a) 20 V (b) 30 V
(c) 50 V (d) 40 V

Q.26 For the circuit shown below:

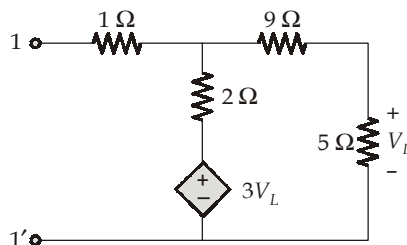

Thevenin's equivalent resistance of the circuit given from input terminal 1 - 1' will be _____ Ω.

- (a) 30 Ω (b) 29 Ω
(c) 28 Ω (d) 16 Ω

Q.27 A balanced 3-phase star-connected load draws 10 kW from a three-phase balanced systems of 400 V, 50 Hz while the line current is 75 A (leading power factor) then the capacitance of the load is _____ μF .

- (a) 183 (b) 1083
 (c) 3149 (d) 361

Q.28 A series RLC circuit resonate at 10 kHz, have a bandwidth of 1 kHz and draw 15.3 W from a 200 V generator operating at the resonant frequency of the current the capacitance of RLC circuit is

- (a) 416 pF (b) 610 pF
 (c) 2.61 pF (d) 201 pF


Q.29 A two-port network is described by the equations,

$$V_1 = 5I_1 + 2I_2 \text{ and } V_2 = 2I_1 + I_2$$

A load impedance (resistive) of 3Ω is connected at port 2, then the value of input impedance is _____ Ω .

- (a) 2Ω (b) 3Ω
 (c) 4Ω (d) 5Ω

Q.30 In the circuit shown below:

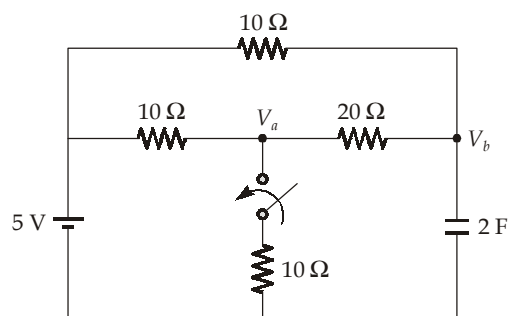

Steady state is reached with switch open. At $t = 0$, switch is closed then $V_a(0^+)$ is _____ V.

- (a) 2 V (b) 3 V
 (c) 5 V (d) 8 V





MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ELECTRIC CIRCUITS

ELECTRICAL ENGINEERING

Date of Test : 29/06/2024

ANSWER KEY >


- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (a) | 13. (d) | 19. (a) | 25. (b) |
| 2. (a) | 8. (a) | 14. (a) | 20. (a) | 26. (b) |
| 3. (b) | 9. (d) | 15. (b) | 21. (b) | 27. (b) |
| 4. (d) | 10. (c) | 16. (a) | 22. (c) | 28. (b) |
| 5. (a) | 11. (a) | 17. (c) | 23. (b) | 29. (c) |
| 6. (b) | 12. (a) | 18. (a) | 24. (a) | 30. (b) |

DETAILED EXPLANATIONS

1. (a)

$$\text{Energy stored maximum} = \frac{1}{2} L_{eq} i^2 = \frac{1}{2} \times 9 \times 2^2 = 18 \text{ J}$$

2. (a)

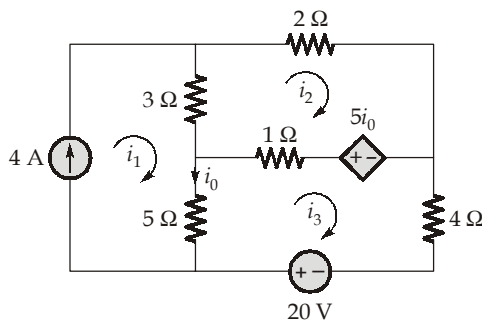

Apply mesh analysis,

$$i_1 = 4$$

$$i_0 = (i_1 - i_3) = 4 - i_3$$

$$3(i_2 - i_1) + 2i_2 - 5i_0 + (i_2 - i_3) = 0$$

$$6i_2 + 4i_3 = 32$$

... (i)

$$1(i_3 - i_2) + 5i_0 + 4i_3 - 20 - 5i_0 = 0$$

$$5i_3 - i_2 = 20$$

... (ii)


From equation (i) and (ii), we get

$$i_2 = 2.35 \text{ A};$$

$$i_3 = 4.4705 \text{ A}$$

$$i_0 = 4 - i_3 = -0.4705 \text{ A}$$

3. (b)

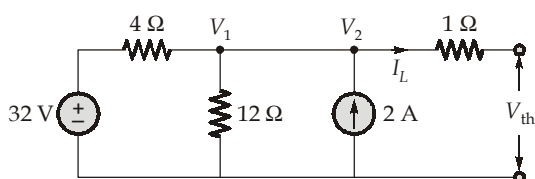

Apply node analysis,

$$\frac{V_1 - 32}{4} + \frac{V_1}{12} - 2 = 0$$

$$V_1 \left(\frac{1}{4} + \frac{1}{12} \right) = 10$$

$$V_1 \left(\frac{4}{12} \right) = 10$$

$$V_1 = \frac{120}{4} = 30 \text{ V}$$

The thevenin across a, b it is open circuited,

$$\therefore V_{th} = V_1 = 30 \text{ V}$$

4. (d)

$$i(t) = 10t e^{-5t}$$

$$\begin{aligned} \text{Energy stored, } E &= \frac{1}{2} Li^2 = \frac{1}{2} \times 0.1 \times (10t e^{-5t})^2 \\ &= \frac{0.1}{2} \times 100t^2 e^{-10t} = 5t^2 e^{-10t} \end{aligned}$$

At $t = 1$ sec,

$$\begin{aligned} E_{1 \text{ sec}} &= 5 \times 1 \times e^{-10} \\ &= \frac{5}{e^{10}} = 227 \times 10^{-6} = 227 \mu\text{J} \end{aligned}$$

5. (a)

$$Z_{\Delta} = (8 + 4j) \Omega$$

$$Z_Y = \frac{Z_{\Delta}}{3} = \left(\frac{8}{3} + \frac{4j}{3} \right) \Omega$$

$$V_{an} = 100 \angle 10^\circ \text{ V}$$

$$V_{cn} = 100 \angle 130^\circ \text{ V}$$

In star;

$$\begin{aligned} I_{c \text{ line}} = I_{c \text{ phase}} &= \frac{100 \angle 130^\circ}{(8 + 4j) / 3} \\ &= 33.54 \angle 103.43^\circ \text{ A} \end{aligned}$$

6. (b)

y -parameters of 1Ω resistor network are $\begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix}$

New y -parameter,

$$\begin{aligned} &= \begin{bmatrix} 5 & 3 \\ 1 & 2 \end{bmatrix} + \begin{bmatrix} 1 & -1 \\ -1 & 1 \end{bmatrix} \\ &= \begin{bmatrix} 6 & 2 \\ 0 & 3 \end{bmatrix} \text{S} \end{aligned}$$

7. (a)

Let,


$$\begin{aligned} i_x &= i_{xA} + i_{xB} + i_{xC} \\ i_{xA} + i_{xB} &= 20 \\ i_{xA} + i_{xC} &= -5 \\ i_{xA} + i_{xB} + i_{xC} &= 12 \\ i_{xA} &= 3 \text{ A;} \\ i_{xB} &= 17 \text{ A;} \\ i_{xC} &= -8 \text{ A} \end{aligned}$$

\therefore if only source V_B is operating,

then

$$i_x = i_{xB} = 17 \text{ A}$$

8. (a)

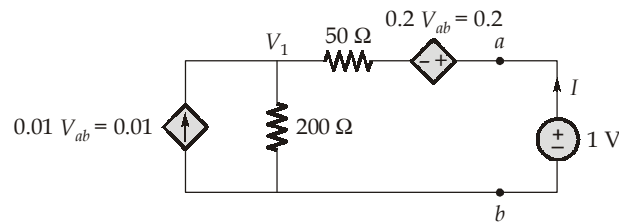

$$0.01 = \frac{V_1}{200} + \frac{V_1 - 1 + 0.2}{50}$$

$$0.01 = \frac{V_1}{200} + \frac{V_1}{50} - 0.016$$

$$V_1 = 0.026 \times 40 = 1.04 \text{ V}$$

$$I = \frac{1 - 0.2 - 1.04}{50} = -0.0048 \text{ A}$$

$$R_{th} = \frac{V}{I} = \frac{1}{-0.0048} = -208.33 \text{ } \Omega$$


9. (d)

$$C_{eq} = 1 \parallel 4 = \frac{4}{5} = 0.8 \text{ } \mu\text{F}$$

$$\begin{aligned} i &= C_{eq} \frac{dv}{dt} = 0.8 \frac{d}{dt} (100e^{-80t}) \times 10^{-6} \\ &= 0.8 \times 100 \times (-80)e^{-80t} \times 10^{-6} \\ &= -6.4 e^{-80t} \text{ mA} \end{aligned}$$

$$\begin{aligned} v_1(t) &= \frac{1}{C_1} \int_0^t i dt + V_1(0) \\ &= \frac{1}{1 \times 10^{-6}} \int_0^t -6.4e^{-80t} dt \times 10^{-3} + 20 \\ &= \frac{-6.4}{10^{-3}} \times \frac{e^{-80t}}{-80} \Big|_0^t + 20 \\ v_1(t) &= 80(e^{-80t} - 1) + 20 \\ &= (80e^{-80t} - 60) \text{ V} \end{aligned}$$

10. (c)

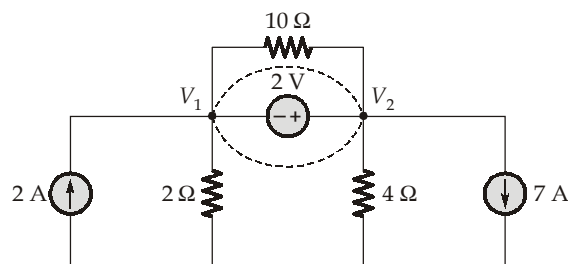


Using supernode method,

$$\begin{aligned}
 -2 + \frac{V_1}{2} + \frac{V_2}{4} + 7 &= 0 \\
 2V_1 + V_2 &= -20 \\
 V_1 - V_2 &= -2 \\
 V_1 &= -7.33 \text{ V} \\
 V_2 &= -5.33 \text{ V}
 \end{aligned}$$

11. (a)

$$\text{Energy stored maximum} = \frac{1}{2} L_{eq} i^2 = \frac{1}{2} \times 9 \times 2^2 = 18 \text{ J}$$

12. (a)

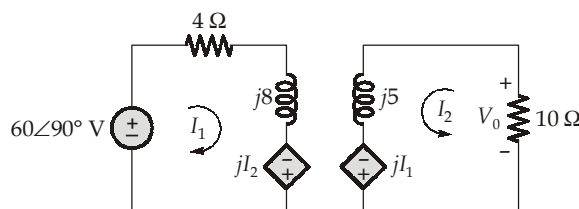


Apply KVL,

$$\begin{aligned}
 (10 + j5)I_2 - jI_1 &= 0 \\
 I_1 &= \frac{(10 + j5)}{j} I_2 = (5 - 10j)I_2 \\
 -60j + (4 + 8j)I_1 - jI_2 &= 0 \\
 (4 + 8j)(5 - 10j)I_2 - jI_2 &= 60j \\
 I_2 &= 0.6 \angle 90^\circ \\
 V_0 &= -10 \times I_2 \\
 &= -10 \times 0.6j = -6j
 \end{aligned}$$

13. (d)

$$\begin{aligned}
 i(0) &= -1 \text{ A} \\
 V(0) &= 5 \text{ V}
 \end{aligned}$$

Apply node analysis

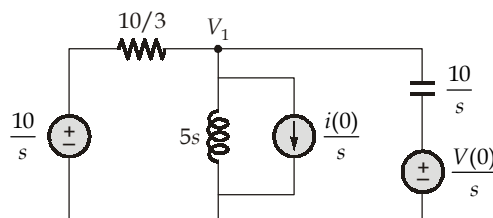

$$\frac{\left(V_1 - \frac{10}{s} \right)}{\frac{10}{3}} + \frac{V_1}{5s} - \frac{1}{s} + \frac{\left(V_1 - \frac{5}{s} \right)}{\left(\frac{10}{s} \right)} = 0$$

$$V_1 \left(\frac{3}{10} + \frac{1}{5s} + \frac{s}{10} \right) - \frac{10 \times 3}{s \times 10} - \frac{1}{s} - \frac{5}{s} \times \frac{s}{10} = 0$$

$$V_1 \left(\frac{3s + 2 + s^2}{10s} \right) = \left(\frac{3}{s} + \frac{1}{s} + \frac{0.5s}{s} \right)$$

$$V_1 = \frac{10s}{(s^2 + 3s + 2)} \times \frac{(0.5s + 4)}{s}$$

$$V_1 = \frac{(5s + 40)}{s^2 + 3s + 2} = \frac{5(s + 8)}{(s + 1)(s + 2)}$$

$$V_1 = 5 \left(\frac{7}{s + 1} - \frac{6}{s + 2} \right)$$

$$v_1(t) = (35e^{-t} - 30e^{-2t})u(t)$$


14. (a)

$$X_{L1} = j\omega L = j4 \times 5 = j20 \Omega$$

$$X_{L2} = j\omega L_2 = j4 \times 4 = j16 \Omega$$

$$X_C = \frac{1}{j\omega C} = \frac{16}{j4 \times 1} = -j4 \Omega$$
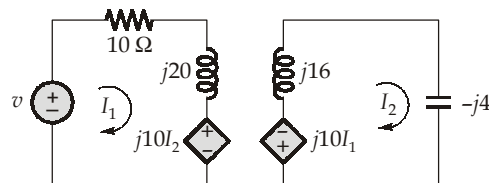
$$X_m = j\omega M = j \times 4 \times 2.5 = j10 \Omega$$



$$-60\angle 30^\circ + (10 + 20j)I_1 + j10I_2 = 0 \quad \dots(i)$$

$$(j16 - j4)I_2 + j10I_1 = 0$$

$$I_1 = -1.2I_2 \quad \dots(ii)$$

$$-(10 + j20) \times 1.2I_2 + j10I_2 = 60\angle 30^\circ$$

$$I_2 = 3.25\angle 160.6^\circ \text{ A}$$

$$I_2 = 3.25 \cos(4t + 160.6^\circ)$$

$$I_1 = 3.9 \cos(4t - 19.4^\circ)$$

At $t = 1$ sec,

$$4t = 4 \text{ rad} = 229.18^\circ$$

$$I_2 = 2.82 \text{ A}$$

$$I_1 = -3.38 \text{ A}$$

Total energy stored in the coupled inductor is

$$E = \frac{1}{2}L_1 I_1^2 + \frac{1}{2}L_2 I_2^2 + M I_1 I_2$$

$$E = \frac{1}{2} \times 5 \times (-3.38)^2 + \frac{1}{2} \times 4 \times (2.82)^2 - 2.5 \times 3.38 \times 2.82 = 20.5 \text{ J}$$

15. (b)

$$\text{T.F.} = \frac{s}{(s+50)^2 + (1000)^2} = \frac{s}{s^2 + 100s + 100.25 \times 10^4}$$

$$s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$$


$$\frac{1}{RC} = 100;$$

$$\frac{1}{LC} = 100.25 \times 10^4 = \frac{1}{L \times 1 \times 10^{-6}}$$

$$L = 0.9975 \text{ H}$$

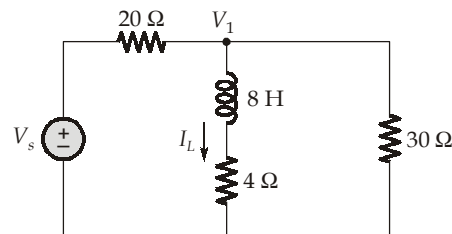16. (a)

$$V_s(s) = \frac{-5}{s} + \frac{12}{s} + 3 = \left(\frac{7}{s} + 3 \right)$$



$$\frac{(V_1 - V_s)}{20} + \frac{V_1}{8s+4} + \frac{V_1}{30} = 0$$

$$V_1 \left(\frac{1}{20} + \frac{1}{8s+4} + \frac{1}{30} \right) = \frac{1}{20} \left(\frac{7+3s}{s} \right)$$

$$V_1 \left(\frac{24s+12+60+16s+8}{60(8s+4)} \right) = \frac{1}{20s} (7+3s)$$

$$V_1 = \frac{7+3s}{20s} \times \frac{60(8s+4)}{(40s+80)}$$

$$= \frac{3(7+3s)(8s+4)}{s(40s+80)}$$

$$I_L = \frac{3(7+3s)(8s+4)}{s(40s+80)(8s+4)} = \frac{3}{s} \times \frac{(7+3s)}{40(s+2)}$$

$$I_L = \frac{3}{40} \left[\frac{7}{2s} + \frac{-1}{2(s+2)} \right]$$


$$i_L(t) = \frac{3}{40} \left(\frac{7}{2} - \frac{1e^{-2t}}{2} \right) u(t)$$

$$i_L(t) = \left(\frac{21}{80} - \frac{3}{80} e^{-2t} \right) u(t)$$

17. (c)

$$X_L = \omega L = 2$$

$$X_C = \frac{1}{1} = 1$$

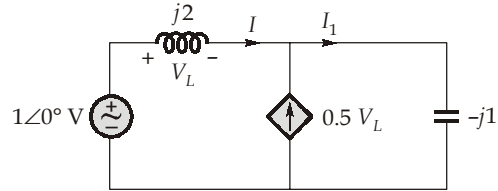

$$\begin{aligned} I &= 0.5 V_L + I_1 \\ &= -0.5 \times (j2)I + I_1 \\ I &= -jI + I_1 \end{aligned}$$

$$I(1 + j) = \frac{(1 - j2I)}{-j1}$$

$$I(-j + 1) = (1 - j2I)$$

$$I(1 + j) = 1$$


$$I = \left(\frac{1}{2} - \frac{j}{2} \right)$$

$$Y_{in} = I \times 1 = \left(\frac{1}{2} + \frac{1}{j2} \right) s$$

$$R = 2, L = 2$$



18. (a)

At $t < 0$,

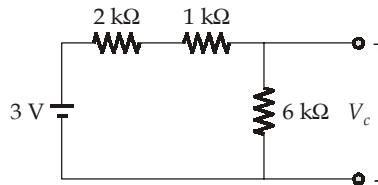

$$V_c(0^-) = 3 \times \frac{6}{(6+3)} = \frac{18}{9} = 2 \text{ V}$$

At $t > 0$,

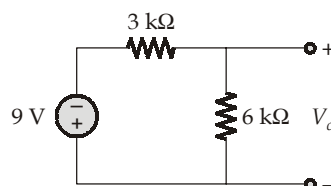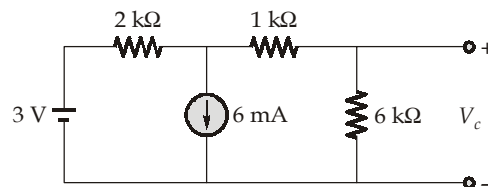

$$v_c(\infty) = \frac{6}{9} \times (-9) = -6 \text{ V}$$

$$v_c(t) = -6 + (2 + 6)e^{-t/\tau}$$

$$\tau = \frac{18}{9} \times 1 = 2 \mu\text{s}$$

$$V_c(t) = -6 + 8e^{-\frac{t}{2}}$$

$$V_c(2 \mu\text{s}) = -6 + 8e^{-1} = -3.06 \text{ V}$$

19. (a)

The equivalent resistance across $x-y$ is

$$R_{x-y} = \frac{mr}{2} + \frac{r}{m} = \frac{m^2r + 2r}{2m}$$

It may be noted that I will be maximum when R_{x-y} will be minimum,

$$\frac{\delta R_{x-y}}{\delta m} = 0$$

i.e., $2m(2mr) - 2(m^2r + 2r) = 0$

i.e., $m = \sqrt{2}$

20. (a)

$$(V_{\text{rms}})^2 = \frac{1}{T} \left[\int_0^{t_1} v^2 dt + \int_{t_1}^T v^2 dt \right]$$


$$= \frac{1}{2} \left[\int_0^1 10^4 (1 - 2e^{-10t} + e^{-20t}) dt + \int_1^2 10^4 e^{-20t} dt \right]$$

$$= (5000) \left[\left[(t + 0.2e^{-10t} - 0.05e^{-20t}) \right]_0^1 - \left(\frac{1}{20} \right) e^{-20t} \right]_1^2$$

$$= (5000) [1 + 0.2e^{-10} - 0.2 + 0.05 - 0.05e^{-40}]$$

$\therefore V_{\text{rms}} = 65.25 \text{ V}$

21. (b)

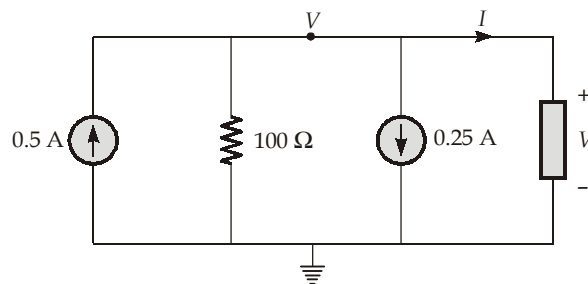

Voltage across 0.5 A current source is

$$V = \frac{\text{Power}}{\text{Current}} = \frac{1 \text{ W}}{0.5 \text{ A}} = 2 \text{ V}$$

Applying nodal analysis at node

$$0.5 = \frac{V}{100} + 0.25 + I$$


$$0.5 = \frac{2}{100} + 0.25 + I$$

$$I = 0.23 \text{ A}$$

Power absorbed by unknown element = $0.23 \times 2 = 0.46 \text{ W}$

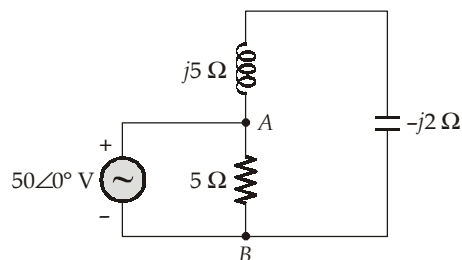
22. (c)

Step-I: When the $50\angle 0^\circ \text{ V}$ source is acting alone.



$$V'_{AB} = 50\angle 0^\circ + 0 \text{ V} = 50\angle 0^\circ \text{ V}$$

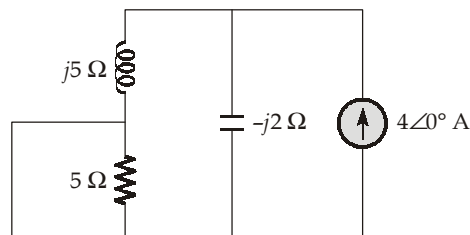Step-II: When the $4\angle 0^\circ \text{ A}$ source is acting alone.



$$V''_{AB} = 0 \text{ V}$$

By superposition theorem, $V_{AB} = V'_{AB} + V''_{AB}$
 $= 50\angle 0^\circ = 50\angle 0^\circ \text{ V}$

23. (b)

$$X_{L1} = 2\pi \times 50 \times 0.01 = 3.14 \Omega$$

$$X_{L2} = 2\pi \times 50 \times 0.02 = 6.28 \Omega$$

$$X_C = \frac{1}{2\pi \times 50 \times 200 \times 10^{-6}} = 15.92 \Omega$$

$$\bar{Z}_1 = 6 + j3.14 \Omega$$

$$\bar{Z}_2 = 4 + j6.28 \Omega$$

$$\bar{Z}_3 = 2 - j15.92 \Omega$$

$$\begin{aligned}\bar{Z} &= \bar{Z}_1 + \frac{\bar{Z}_2 \bar{Z}_3}{\bar{Z}_2 + \bar{Z}_3} \\ &= (6 + j3.14) + \frac{(4 + j6.28)(2 - j15.92)}{(4 + j6.28) + (2 - j15.92)} = 17.27 \angle 30.75^\circ \Omega\end{aligned}$$

Power factor = $\cos\phi = \cos(30.75^\circ) = 0.86$ (lagging)

24. (a)

RMS value of the rectangular wave = I_m


RMS value of sinusoidal current wave = $\frac{I_m}{\sqrt{2}}$

Heating effect due to rectangular current wave = $I_m^2 RT$

Heating effect due to sinusoidal current wave = $\left(\frac{I_m}{\sqrt{2}}\right)^2 RT$

$$\text{Relative heating effects} = \left(\frac{I_m}{\sqrt{2}}\right)^2 RT : I_m^2 RT = 1 : 2$$

25. (b)

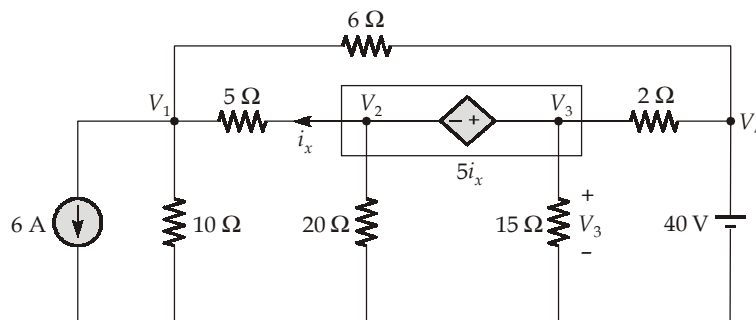

Nodes 2 and 3 form a super node:

$$\begin{aligned}V_3 &= 5i_x + V_2 \\ &= 5\left[\left(\frac{V_2 - V_1}{5}\right)\right] + V_2 = 2V_2 - V_1\end{aligned}$$

Applying KCL at node 1,

$$6 + \frac{V_1}{10} + \frac{V_1 - V_2}{5} + \frac{V_1 - V_4}{6} = 0$$

$$6 + \frac{V_1}{10} + \frac{V_1}{5} - \frac{V_2}{5} + \frac{V_1 - 40}{6} = 0$$

$$\frac{7}{15}V_1 - \frac{1}{5}V_2 = \frac{2}{3} \quad \dots(3)$$

Applying KCL for the super node:

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{V_3}{15} + \frac{V_3 - V_4}{2} = 0$$

$$\frac{V_2 - V_1}{5} + \frac{V_2}{20} + \frac{(2V_2 - V_1)}{15} + \frac{(2V_2 - V_1) - 40}{2} = 0$$


$$-\frac{23}{30}V_1 + \frac{83}{60}V_2 = 20 \quad \dots(4)$$

Solving equation (3) and (4),

$$\begin{aligned} V_1 &= 10 \text{ V} \\ V_2 &= 20 \text{ V} \\ V_3 &= 2V_2 - V_1 \\ &= 40 - 10 = 30 \text{ V} \end{aligned}$$

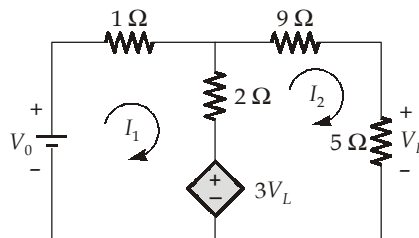26. (b)

Let us apply a voltage source V_0 at the input terminals such that the current in the loops be I_1 and I_2 .



Obviously,

$$V_L = R_L I_2 = 5I_2$$

\therefore The dependent voltage source is $3V_L = 15I_2$

Again applying KVL in loop-1,

$$\begin{aligned} V_0 &= 3I_1 + 15I_2 - 2I_2 \\ &= 3I_1 + 13I_2 \quad \dots(1) \end{aligned}$$

In loop-2,

$$\begin{aligned} 0 &= -2I_1 + (2 + 9 + 5) I_2 - 3V_L \\ 0 &= -2I_1 + 16I_2 - 15I_2 \end{aligned}$$

$$I_2 = 2I_1 \quad \dots(2)$$

$$V_0 = 3I_1 + 13 \times 2I_1$$

$$V_0 = 29I_1$$

$$\frac{V_0}{I_1} = R_{\text{input}} = 29 \Omega$$

27. (b)

$$Z_{ph} \text{ (Phase impedance)} = \frac{V_{ph}}{I_{ph}} = \frac{400}{75\sqrt{3}} = 3 \Omega$$

$$\left[\text{In star connection } I_{ph} = I_{\text{line}}, V_{ph} = \frac{V_L}{\sqrt{3}} \right]$$

$$\frac{\text{Power}}{\text{Phase}} = I_{ph}^2 R_{ph}$$

$$\frac{10 \times 10^3}{3} = (75)^2 R_{ph}$$

$$\therefore R_{ph} = \frac{10 \times 1000}{3 \times 75 \times 75} = 0.6 \Omega$$

$$\therefore X_{ph} = \sqrt{Z_{ph}^2 - R_{ph}^2} = \sqrt{3^2 - (0.6)^2} = 2.94 \Omega$$

As the current is leading, X_{ph} must be capacitive.

$$\therefore X_c = 2.94 \Omega$$

or,
$$\frac{1}{\omega C} = 2.94 \Omega$$

$$\therefore C = \frac{1}{2.94 \times 2\pi f} = \frac{1}{2.94 \times 2 \times \pi \times 50} = 1083 \mu\text{F}$$

28. (b)

For a series RLC circuit operating at resonance,

$$V_R = V = 200 \text{ V}$$

$$P_R = \frac{V^2}{R}$$

$$15.3 = \frac{(200)^2}{R}$$

$$R = \frac{200 \times 200}{15.3} = 2.61 \text{ k}\Omega$$

$$Q = \frac{f_0}{\Delta f} = \frac{10}{1} = 10$$

Now,
$$Q = \frac{\omega_0 L}{R}$$

$$10 = \frac{2\pi(10^4)(L)}{2.61 \times 10^3}$$

$$\therefore L = 416 \text{ mH}$$

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

$$10^4 = \frac{1}{2\pi\sqrt{416 \times 10^{-3} C}}$$

$$C = 610 \text{ pF}$$

29. (c)

$$V_1 = 5I_1 + 2I_2 \quad \dots(1)$$

$$V_2 = 2I_1 + I_2 \quad \dots(2)$$

and

$$V_2 = -I_2 R_L = -3I_2 \quad \dots(3)$$

From equation (2) and (3),

$$-3I_2 = 2I_1 + I_2$$

or,

$$-4I_2 = 2I_1$$


$$I_2 = -\frac{I_1}{2} \text{ put this value in equation (1)}$$

$$V_1 = 5I_1 + 2\left(-\frac{I_1}{2}\right) = 4I_1$$

$$\therefore Z_{\text{in}} = \frac{V_1}{I_1} = 4 \Omega$$

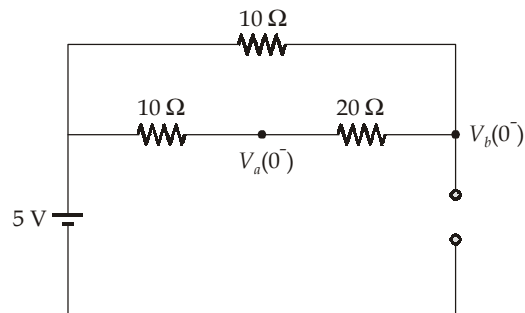30. (b)


At $t = 0^-$, the network attains steady state condition. Hence, the capacitor acts as an open-circuit.



$$V_b(0^-) = 5 \text{ V}$$

At $t = 0^+$, the capacitor acts as a voltage source of 5 V,

$$V_b(0^+) = 5 \text{ V}$$

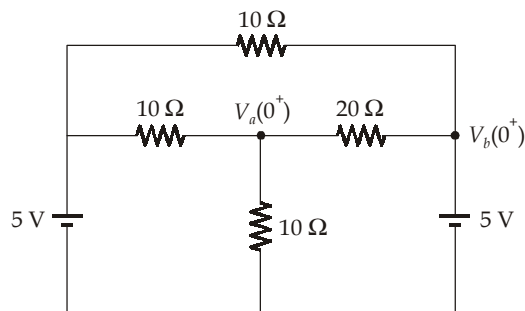

Writing KCL equation at $t = 0^+$

$$\frac{V_a(0^+) - 5}{10} + \frac{V_a(0^+)}{10} + \frac{V_a(0^+) - 5}{20} = 0$$

$$0.25 V_a(0^+) = 0.75$$

$$V_a(0^+) = 3 \text{ V}$$

