

**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

ELECTRONICS ENGINEERING
NETWORK THEORY**Duration : 1:00 hr.****Maximum Marks : 50**


Read the following instructions carefully

1. This question paper contains **30** objective questions. **Q.1-10** carry one mark each and **Q.11-30** carry two marks each.
2. Answer all the questions.
3. Questions must be answered on Objective Response Sheet (**ORS**) by darkening the appropriate bubble (marked **A, B, C, D**) using HB pencil against the question number. Each question has only one correct answer. In case you wish to change an answer, erase the old answer completely using a good soft eraser.
4. There will be **NEGATIVE** marking. For each wrong answer **1/3rd** of the full marks of the question will be deducted. More than one answer marked against a question will be deemed as an incorrect response and will be negatively marked.
5. Write your name & Roll No. at the specified locations on the right half of the **ORS**.
6. No charts or tables will be provided in the examination hall.
7. Choose the **Closest** numerical answer among the choices given.
8. If a candidate gives more than one answer, it will be treated as a **wrong answer** even if one of the given answers happens to be correct and there will be same penalty as above to that questions.
9. If a question is left blank, i.e., no answer is given by the candidate, there will be **no penalty** for that question.

DO NOT OPEN THIS TEST BOOKLET UNTIL YOU ARE ASKED TO DO SO


Q.No. 1 to Q.No. 10 carry 1 mark each

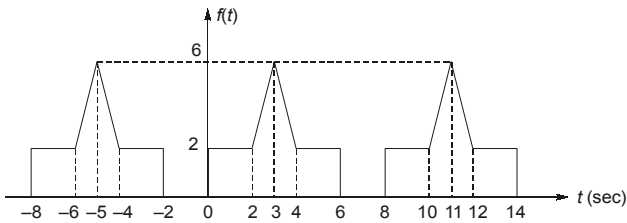Q.1 The average value of the periodic signal shown below is




- (a) 2 (b) 4
(c) 6 (d) 8

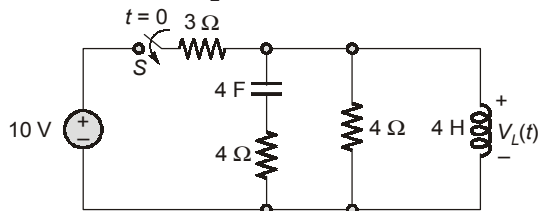Q.2 In the circuit shown in figure, the switch S is closed at time ($t = 0$). The voltage across the inductance ($V_L(t)$) at $t = 0^+$, is



- (a) 2 V (b) 4 V
(c) -6 V (d) 8 V


Q.3 Consider the circuit shown below

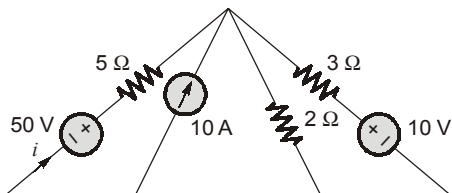

The current flowing through 50 V source is


- (a) 30 A (b) 20.66 A
(c) 5.48 A (d) 2.34 A

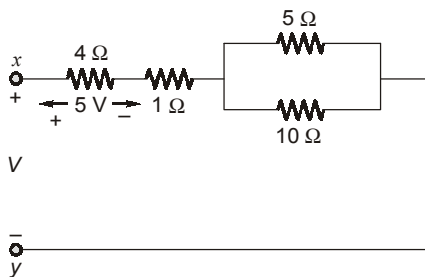Q.4 Determine the voltage that must be applied at $x - y$ terminal such that the voltage across 4Ω is 5 V.



- (a) 5 V (b) 10.417 V
(c) 20.123 V (d) 25.72 V

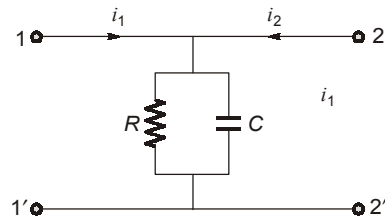Q.5 For the parallel RC circuit shown below, if $R = 1 \Omega$, and $C = 1$ F. The value of $Z_{21}(s)$ will be



- (a) $s + 1$
(b) $\frac{1}{s} + 1$
(c) $\frac{-1}{s + 1}$
(d) $1 - \frac{s}{s + 1}$


Q.6 If the current in a 20Ω resistor is given by

$$i = 4 + 5\sin\omega t - 3\cos 3\omega t$$

The power consumed by the resistor is

- (a) 1 kW (b) 1.865 W
(c) 660 W (d) 720 W

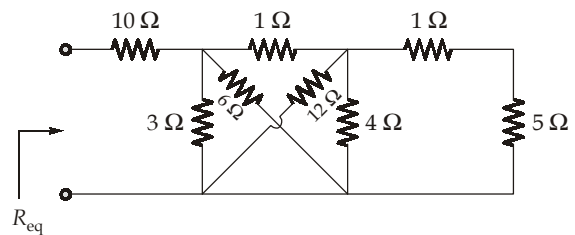
Q.7 Consider the circuit shown in the figure below:



the equivalent resistance (R_{eq}) is

- (a) 10.5 Ω (b) 11.2 Ω
(c) 22.4 Ω (d) 36.5 Ω

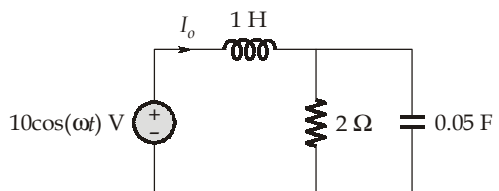Q.8 Consider the circuit shown in the figure below:




If the $I_o(j\omega)$ is current flowing in the circuit for particular value of angular frequency ω , then the

value of $\left| \frac{I_o(j)}{I_o(5j)} \right|$ is equal to

- (a) 2.1 (b) 3.6
(c) 4.2 (d) 8.8

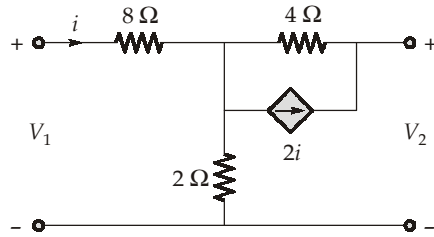
Q.9 Consider the circuit shown in the figure below:



the value of Y_{21} is equal to

- (a) -0.25 s (b) -0.5 s
(c) -0.75 s (d) -1 s

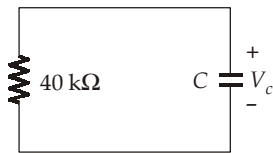Q.10 Consider the circuit shown in figure below:




Assume $V_c(0^-) = 5 \text{ V}$. If $v_c(t) = \frac{5}{e} \text{ V}$ at $t = 0.1$

sec, then the value of C is

- (a) $1.2 \mu\text{F}$ (b) $1.5 \mu\text{F}$
(c) $2.5 \mu\text{F}$ (d) $5 \mu\text{F}$

Q. No. 11 to Q. No. 30 carry 2 marks each


Q.11

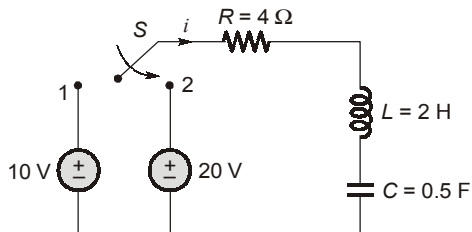

If the switch is at position '1' for a long time and at $(t = 0)$ it is moved to position '2', then the current $i(t)$ for $t > 0$ will be

- (a) $(5e^{-t} + 25e^t) \text{ A}$ (b) $(5 + 25te^{-t}) \text{ A}$
(c) $(5te^{-t}) \text{ A}$ (d) $(25te^{-t} + 5) \text{ A}$

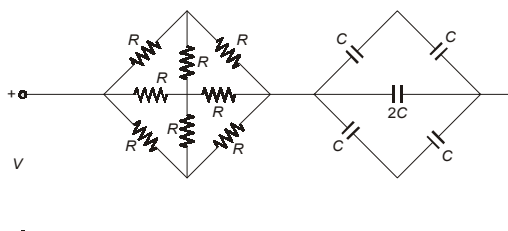Q.12 The time constant of the circuit shown below will be




- (a) RC (b) $2RC$
(c) $\frac{RC}{2}$ (d) $\frac{3RC}{2}$

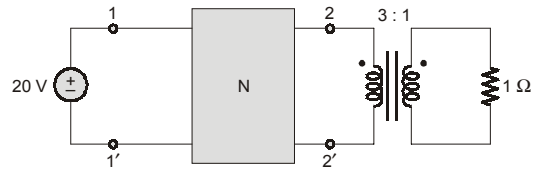Q.13 For the circuit shown below, the network N has


Z parameter matrix of $\begin{bmatrix} 4 & 8 \\ 1 & 3 \end{bmatrix}$. If the transformer

used in the circuit is ideal, then the power delivered to the 1Ω resistance will be



- (a) 55.56 mW (b) 2.25 W
(c) 4.5 W (d) None of these

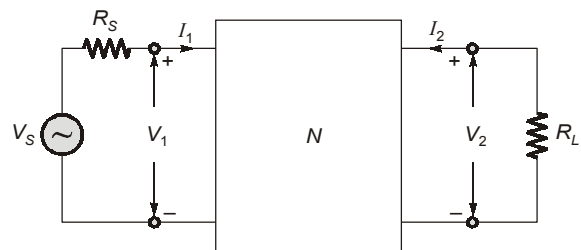Q.14 The hybrid parameter of the network N shown below are $h_{11} = 2 \Omega$, $h_{12} = 4$, $h_{21} = -5$ and $h_{22} = 2 \Omega$. The supply voltage, if the power dissipated in the load resistor $R_L (= 4 \Omega)$ is 25 W and R_s is given by 2Ω is




- (a) 11 V (b) 22 V
(c) 43 V (d) 58 V

Q.15 For a series RLC circuit the magnitude of frequency at which the drop across the capacitor is maximum will be


- (a) $\sqrt{\frac{1}{LC} - \left(\frac{RC}{L}\right)^2} \text{ rad/sec}$
(b) $\frac{1}{\sqrt{LC}} \text{ rad/sec}$
(c) $\sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} \text{ rad/sec}$
(d) $\sqrt{\frac{1}{LC} - R^2C^2} \text{ rad/sec}$

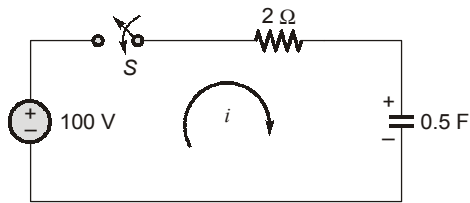Q.16 In below figure the capacitor initially has a charge of 10 C . The current in the circuit after two seconds the switch S is closed will be



- (a) 5.41 A (b) 7.21 A
(c) 8.31 A (d) 9.15 A


Q.17 Consider the circuit shown below

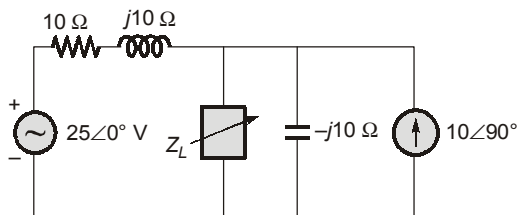

The maximum power absorbed by the load is

- (a) 390.625 W (b) 400.125 W
(c) 500.125 W (d) 350.625 W

Q.18 Consider the circuit shown below

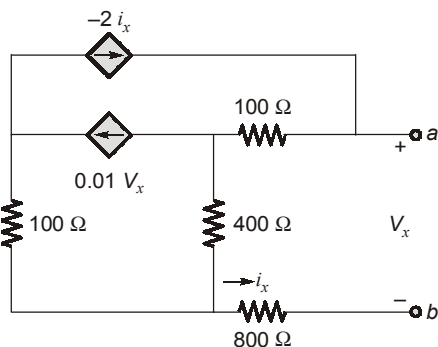

The Thevenin's equivalent resistance across the terminals a and b is

- (a) 10 Ω (b) 20 Ω
(c) 30 Ω (d) 60 Ω

Q.19 A series resonance circuit has a source frequency of 5 kHz and source impedance of $(2 + j4)\text{ Ω}$. The load impedance being $(10 - jX_C)\text{ Ω}$. The value of C such that the power consumed by the resistor is maximum is


- (a) 1.45 μF (b) 7.95 μF
(c) 2.84 μF (d) 9.87 μF

Q.20 The voltage applied to series R - L circuit at $t = t_0$ sec is given by $10\cos\left(\frac{t}{2} + 45^\circ\right)\text{ V}$. The value of resistance is 1 Ω and the value of inductance

is 2 H. The value of t_0 to obtain the transient free response is


- (a) $\frac{\pi}{4}$ sec (b) $\frac{\pi}{2}$ sec
(c) π sec (d) 2π sec

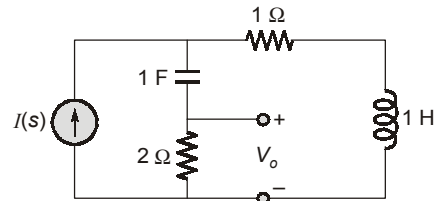Q.21 Find the transfer function $\frac{V_o(s)}{I(s)}$ for the network shown




- (a) $\frac{2s(s+1)}{s^2+3s+1}$ (b) $\frac{2(s+1)}{s^2+3s+1}$
(c) $\frac{8s(s+1)}{2s^2+6s+1}$ (d) $\frac{2s(s+1)}{2s^2+6s+1}$

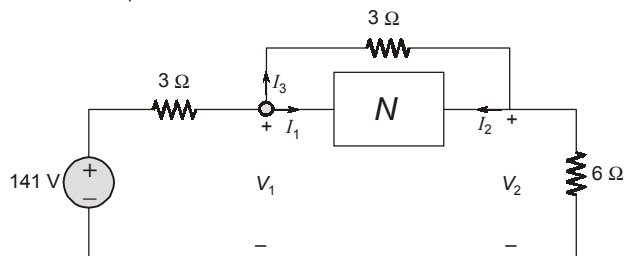Q.22 For the two port network N shown below in figure Z parameter matrix is $\begin{bmatrix} 2 & 1 \\ 1 & 4 \end{bmatrix}$. The value of I_1 in Amperes is




- (a) 12 (b) 21
(c) 24 (d) 28

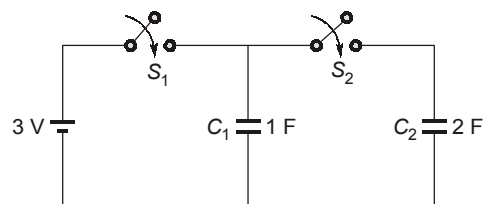Q.23 In the figure shown, all elements used are ideal. For time $t < 0$, S_1 remain closed and S_2 open. At $t = 0$, S_1 is opened and S_2 is closed. If the voltage V_{C_2} across the capacitor C_2 at $t = 0^-$ is zero, the voltage across the capacitor combination at $t > 0$ will be



- (a) 1/2 V (b) 1 V
(c) 3/2 V (d) 5/2 V

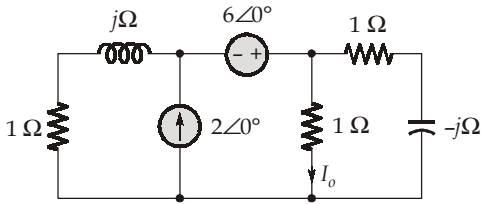
Q.24 Consider the circuit shown in the figure below:



The value of I_o is equal to


- (a) $5.831\angle 149.03^\circ$ (b) $2\angle 180^\circ$
(c) $6.913\angle 132.1^\circ$ (d) $2.915\angle -30.96^\circ$

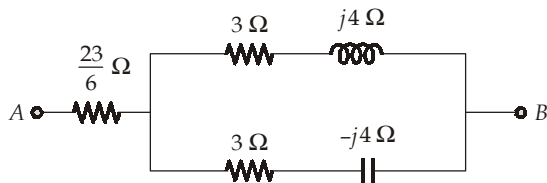Q.25 For the circuit shown below the equivalent impedance seen across the terminals A and B is



- (a) $5\ \Omega$ (b) $8\ \Omega$
(c) $j8\ \Omega$ (d) $(7 + j10)\ \Omega$

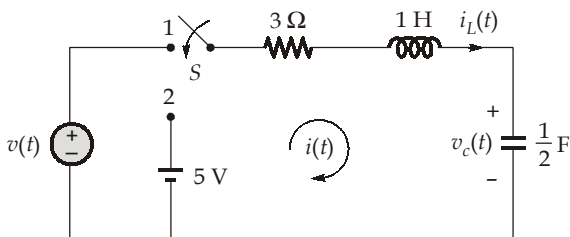Q.26 In the figure shown below, the switch S is moved from position 1 to 2 at time $t = 0$. Just before the switch is thrown, the initial conditions are $i_L(0^-) = 2\text{ A}$ and $V_C(0^-) = 2\text{ V}$. Then the current $i(t)$ for $t > 0$ is







- (a) $(e^t - e^{-2t})\text{ A}$ (b) $(e^{-t} - e^{-2t})\text{ A}$
(c) $(e^{-t} + e^{-2t})\text{ A}$ (d) $(e^t + e^{2t})\text{ A}$

Q.27 The resonant frequency of a series RLC circuit is 1.5 MHz with the resonating capacitor set at 150 pF . If the bandwidth is 10 kHz , then the effective resistance of the circuit would be (approximately)


- (a) $1.25\ \Omega$ (b) $2.25\ \Omega$
(c) $3.25\ \Omega$ (d) $4.71\ \Omega$

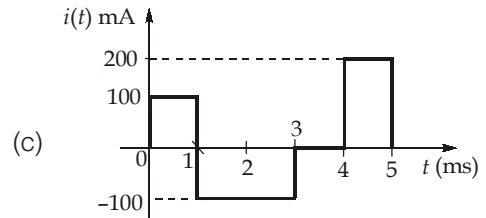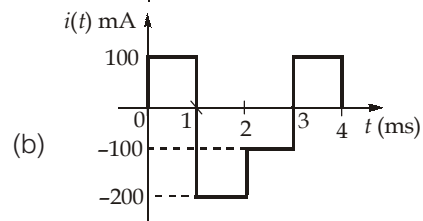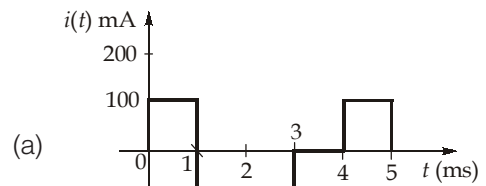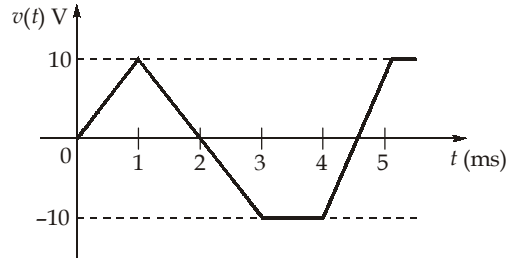Q.28 A voltage signal $v(t)$ is applied to a capacitor with capacitance equal to $10\ \mu\text{F}$. The voltage wave is shown in the figure below. Which of the following plot is correct for the current $i(t)$ through the capacitor?



(d) None of these

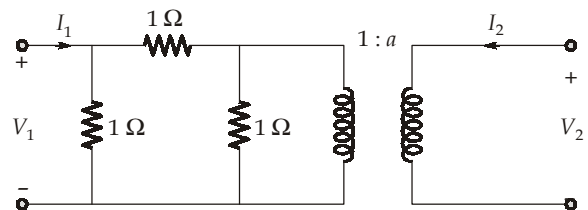Q.29 Consider the circuit shown in the figure below:



Assuming 'a' to be a positive non zero number, then which of the following statement is correct?

- (a) Z-parameter does not exist for all values of 'a'
(b) Z-parameter does not exist for 'a' = 3
(c) Z-parameter does not exist for 'a' = 8
(d) Z-parameter exists for all positive value of 'a'

Q.30 An RLC circuit along with its phase diagram is shown in figure below,

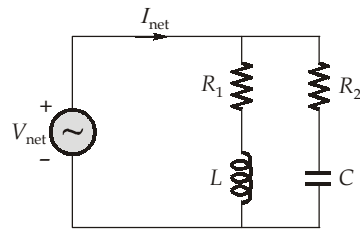


Figure -1

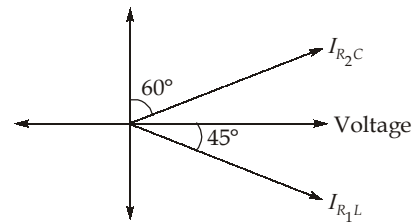


Figure -2

If $L = C$, then the minimum value of $R_1 + R_2$ is

- (a) 2.63Ω (b) 6.33Ω
 (c) 21.4Ω (d) 19Ω





MADE EASY

India's Best Institute for IES, GATE & PSUs

Delhi | Bhopal | Hyderabad | Jaipur | Pune | Kolkata

Web: www.madeeasy.in | E-mail: info@madeeasy.in | Ph: 011-45124612

NETWORK THEORY

ELECTRONICS ENGINEERING

Date of Test : 29/06/2024

ANSWER KEY >

- | | | | | |
|--------|---------|---------|---------|---------|
| 1. (a) | 7. (b) | 13. (b) | 19. (b) | 25. (b) |
| 2. (b) | 8. (a) | 14. (d) | 20. (c) | 26. (c) |
| 3. (c) | 9. (a) | 15. (c) | 21. (a) | 27. (d) |
| 4. (b) | 10. (c) | 16. (a) | 22. (c) | 28. (c) |
| 5. (d) | 11. (c) | 17. (a) | 23. (b) | 29. (d) |
| 6. (c) | 12. (b) | 18. (d) | 24. (d) | 30. (a) |

DETAILED EXPLANATIONS

1. (a)

The average value of periodic signal can be calculated by considering one time period


$$= \frac{\text{Total area under the graph for one period}}{T_0}$$

Total area under the graph for one period = Area 1 + Area 2 + Area 3 + Area 4

here Area 1 = Area 2 = Area 3 = Area 4 = 4

and $T_0 = 8 \text{ sec}$
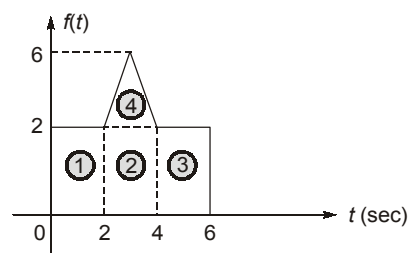
$$\text{Average value} = \frac{4 + 4 + 4 + 4}{8} = \frac{16}{8} = 2$$




2. (b)

Before closing the switch, the circuit was not energized, therefore, current through inductor and voltage across capacitor are zero.

After closing the switch, at $t = 0^+$ inductor acts as open-circuit and capacitor acts as short-circuit.

Equivalent circuit at $t = 0^+$

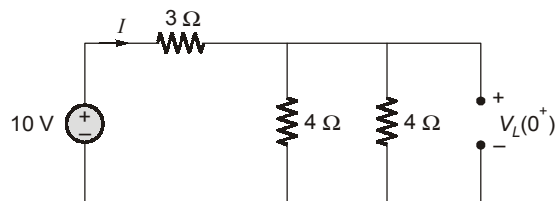


$$I = \frac{10}{3 + 4 \parallel 4} = 2 \text{ A}$$

$$V_L(0^+) = I \times (4 \parallel 4) = 2 \times 2 = 4 \text{ V}$$

3. (c)

using source transformation

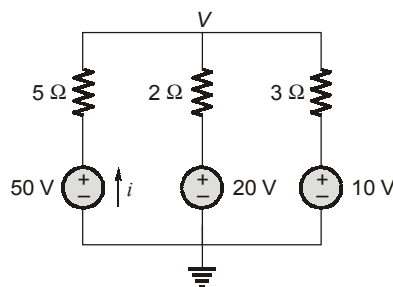

applying KCL at V

$$\frac{V-50}{5} + \frac{V-20}{2} + \frac{V-10}{3} = 0$$

$$\frac{6V-300+15V-300+10V-100}{30} = 0$$

$$31V-700 = 0$$


or

$$V = \frac{700}{31} = 22.58 \text{ V}$$

$$i = \frac{50-V}{5}$$

$$= \frac{50-22.58}{5} = 5.48 \text{ A}$$

4. (b)

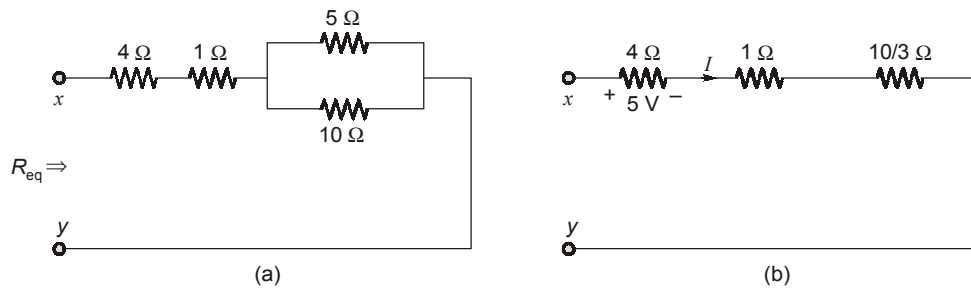

$$R_{eq} = 4 \Omega + 1 \Omega + (5 \parallel 10) \Omega$$

$$= 5 \Omega + \left(\frac{5 \times 10}{15} \right) \Omega$$

$$= 5 + \frac{10}{3} = \frac{25}{3} \Omega$$

Also from (b) $I = \frac{5}{4} \text{ A}$ (in series circuit current remains same)

$\therefore V_{xy} = \frac{5}{4} \times \frac{25}{3} = 10.417 \text{ V}$

5. (d)

Converting the network into s-domain


$$V_2(s) = I_1(s) \left(\frac{R \times \frac{1}{Cs}}{R + \frac{1}{Cs}} \right)$$

or

$$\frac{V_2(s)}{I_1(s)} = \frac{R}{RCs+1} = \frac{1}{\left(s + \frac{1}{RC} \right)}$$

$\therefore Z_{21}(s) = \frac{V_2(s)}{I_1(s)} = \frac{1}{\left(s + \frac{1}{RC} \right)} = \frac{1}{1(s+1)}$

$$Z_{21}(s) = \frac{1}{(s+1)}$$

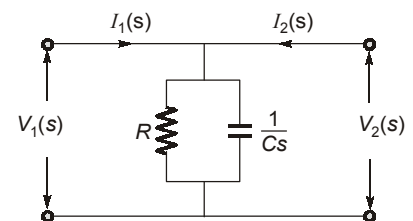


6. (c)

$$\begin{aligned}
 P &= P_0 + P_1 + P_2 \\
 &= 4^2 \times 20 + \left(\frac{5}{\sqrt{2}}\right)^2 \times 20 + \left(\frac{3}{\sqrt{2}}\right)^2 \times 20 \quad \left[\because I_{\text{rms}} = \frac{I_{\text{max}}}{\sqrt{2}} \right] \\
 &= (16 + 12.5 + 4.5) \times 20 = 660 \text{ W}
 \end{aligned}$$

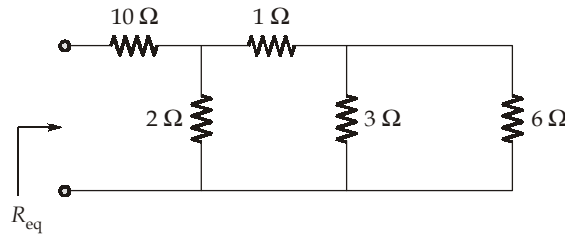7. (b)

The resistance $6 \Omega \parallel 3 \Omega$ and $12 \Omega \parallel 4 \Omega$ also 1Ω is in series with 5Ω , thus, the circuit can be redrawn as



$$\begin{aligned}
 \therefore R_{\text{eq}} &= 10 \Omega + 2 \Omega \parallel (1 + 3 \Omega \parallel 6 \Omega) \\
 R_{\text{eq}} &= 11.2 \Omega
 \end{aligned}$$

8. (a)

$$\begin{aligned}
 Z_L &= j\omega L = j\Omega \\
 Z_C &= \frac{1}{j\omega C} = \frac{1}{j(1)(0.05)} = -j20 \Omega
 \end{aligned}$$

$$\therefore Z_{\text{eq}} = j + 2 \parallel (-j20) = 1.98 + j0.802 \Omega$$

and

$$\begin{aligned}
 Z_L(j5) &= 5j\Omega \\
 Z_C(j5) &= -j4 \Omega
 \end{aligned}$$


$$\therefore Z_{\text{eq}}(j5) = j5 + 2 \parallel (-j4) = 1.6 + j4.2 \Omega$$

Now,

$$I(j\omega) \propto \frac{1}{Z(j\omega)}$$

$$\therefore \left| \frac{I_o(j)}{I_o(j5)} \right| = \left| \frac{Z(j5)}{Z(j)} \right| = \left| \frac{1.6 + j4.2}{1.98 + j0.802} \right| = 2.104$$

9. (a)

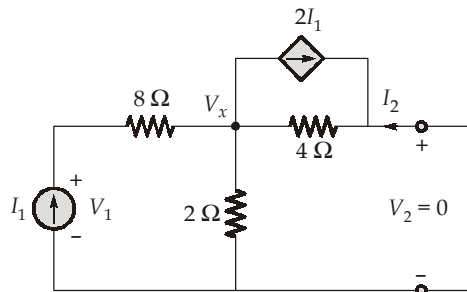

$$I_1 = \frac{V_x}{2} + \frac{V_x}{4} + 2I_1$$

$$-I_1 = 0.75V_x \quad \dots(i)$$

$$I_2 = -\frac{V_x}{4} - 2I_1 = -\frac{V_x}{4} + 1.5V_x = 1.25V_x$$

Now,

$$V_1 = 8I_1 + V_1$$

$$V_1 = -6V_x + V_x = -5V_x$$

∴

$$\frac{I_2}{V_1} = -\frac{1.25}{5} = -0.25 \text{ S}$$

10. (c)

Voltage across capacitor

$$V_c(t) = V_{\text{final}} + (V_{\text{initial}} - V_{\text{final}})e^{-t/RC}$$

$$= 0 + (5 - 0)e^{-t/RC}$$

But given,

$$V_c(t) = \frac{5}{e} = 5e^{-t/RC}$$


$$\frac{5}{e} = 5e^{-(0.1/40 \text{ k}\Omega \times C)}$$

$$\frac{0.1}{40 \text{ k}\Omega \times C} = 1$$

∴ $C = 2.5 \mu\text{F}$ (or) $2.5 \times 10^{-6} \text{ F}$

11. (c)


At ($t = 0^-$)

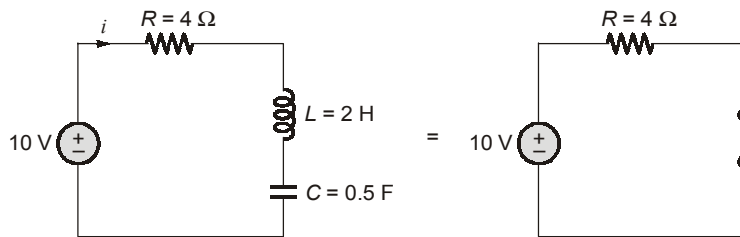

$$V_c(0^-) = 10 \text{ V}$$

$$i_L(0^-) = 0 \text{ A}$$

At ($t = 0^+$)

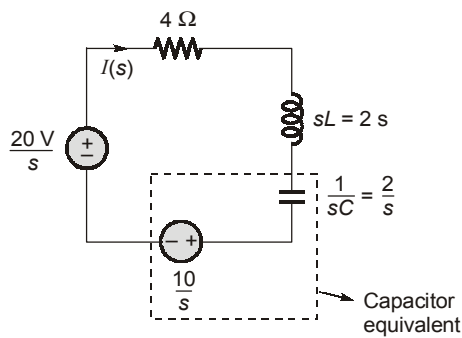


$$I(s) = \frac{10/s}{4 + 2s + \frac{2}{s}} = \frac{10/s}{\frac{4s + 2s^2 + 2}{s}} = \frac{10}{2(s^2 + 2s + 1)}$$

$$I(s) = \frac{5}{(s + 1)^2}$$


$$i(t) = 5te^{-t} u(t) \text{ A}$$

12. (b)

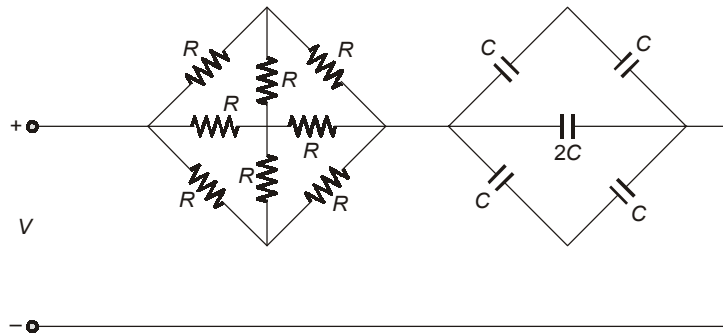


The time constant of an RC circuit is $\tau = R_{eq} C_{eq}$


Calculation of C_{eq}

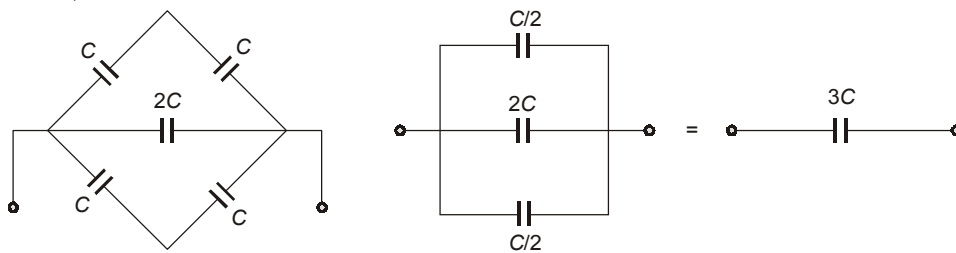

Calculation of R_{eq}

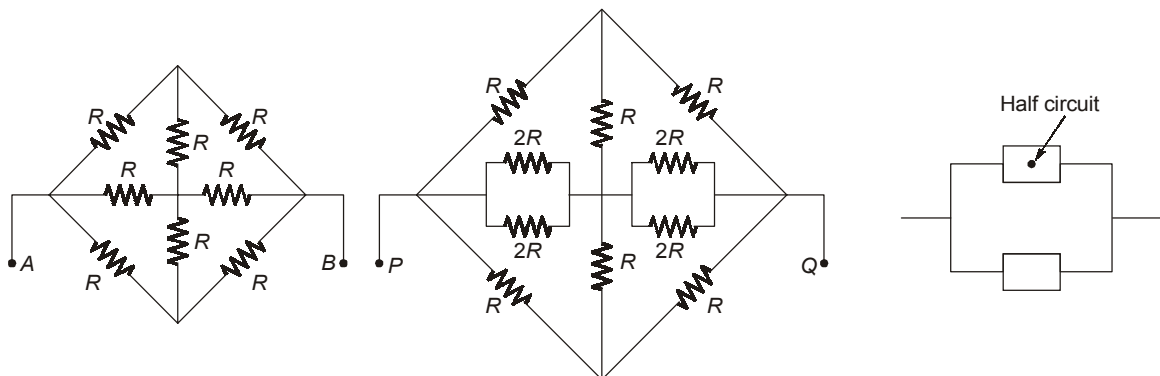

It is Wheatstone bridge.

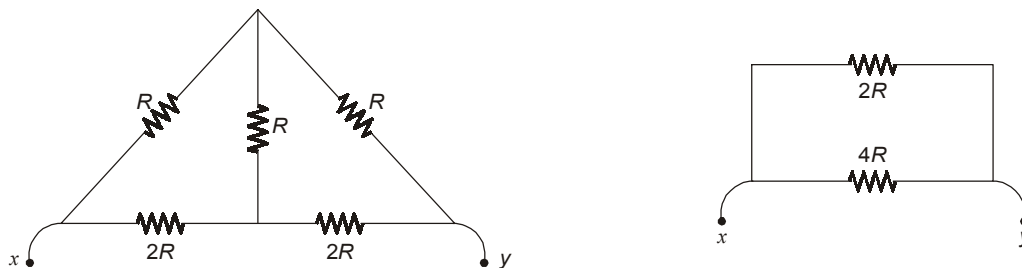

$$(R_{eq})_{\text{Half circuit}} = \frac{4R \times 2R}{6R} = \frac{4R}{3}$$

$$R_{eq} = (R_{eq})_{\text{Half circuit}} \parallel (R_{eq})_{\text{Half circuit}}$$

$$= \left(\frac{4R}{3}\right) \parallel \left(\frac{4R}{3}\right) = \left(\frac{2R}{3}\right)$$


\therefore

$$\tau = R_{eq} C_{eq}$$

$$= \frac{2R}{3} \times 3C = 2RC$$

13. (b)

Network 'N' can be replaced as

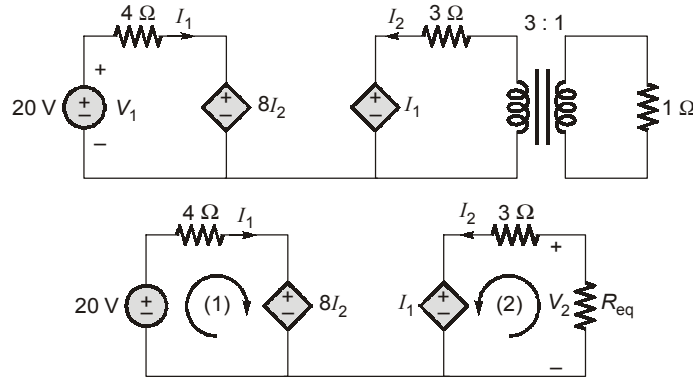

$$R_{eq} = (1) \times \left(\frac{3}{1}\right)^2 = 9 \Omega$$

Applying KVL at loop (1)

$$20 = 4I_1 + 8I_2$$

also

$$V_2 = -9I_2 = I_1 + 3I_2$$

⇒

$$I_1 = -12I_2$$

$$20 = 4(-12I_2) + 8I_2$$

$$20 = -40I_2$$

⇒

$$I_2 = -0.5 \text{ A}$$

$$I_1 = -12(-0.5) = 6 \text{ A}$$

Now,

$$\frac{I_{\text{primary}}}{I_{\text{secondary}}} = \frac{1}{3}$$

⇒


$$3I_{\text{primary}} = I_{\text{secondary}}$$

$$3(-I_2) = I_3$$

⇒

$$I_3 = 1.5 \text{ A}$$
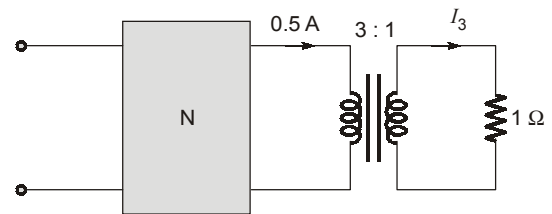
$$\begin{aligned} \text{Power delivered to } 1 \Omega &= (I_3)^2 \times R_L = (1.5)^2 \times 1 \\ &= 2.25 \text{ Watts} \end{aligned}$$



14. (d)

The *h*-parameter

$$V_1 = 2I_1 + 4V_2$$

$$I_2 = -5I_1 + 2V_2$$

Power dissipated in R_L

$$P_L = \frac{V_2^2}{R_L} = 25 \text{ W}$$

∴

$$V_2 = \sqrt{25 \times 4} = 10 \text{ V}$$

∴

$$V_2 = -I_2 R_L$$

∴

$$I_2 = -2.5 \text{ A}$$

substituting the values

we get

$$V_1 = 2I_1 + 40$$

$$-2.5 = -5I_1 + 20$$

∴

$$I_1 = 4.5 \text{ A} \quad \text{and}$$

$$V_1 =$$

49 V

$$\therefore I_1 = \frac{V_s - V_1}{2} = 4.5$$

$$\Rightarrow V_s = 58 \text{ V}$$

15. (c)

For series RLC circuit,

$$Z = \sqrt{R^2 + (X_L - X_C)^2}$$

The circuit current

$$I = \frac{V}{Z}$$


 \therefore The drop across the capacitor C

$$V_C = IX_C = \frac{V}{Z} X_C$$

$$\text{i.e. } V_C^2 = \frac{V^2 X_C^2}{Z^2} = \frac{V^2}{(\omega C)^2 \left[R^2 + \left(\omega L - \frac{1}{\omega C} \right)^2 \right]}$$

For maximum voltage drop

$$\begin{aligned} V_{C\max} &= \frac{dV_C}{d\omega} = 0 \\ &= \sqrt{\frac{1}{LC} - \frac{R^2}{2L^2}} \text{ rad/sec} \end{aligned}$$

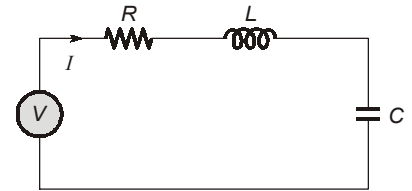**16. (a)**

Using KCL

$$100 = R \frac{dQ}{dt} + \frac{Q}{C}$$

$$100C = RC \frac{dQ}{dt} + Q$$

$$\int_{Q_0}^Q \frac{dQ}{100C - Q} = \frac{1}{RC} \int_0^t dt$$

$$(-\ln(100C - Q))_{Q_0}^Q = \frac{t}{RC}$$

$$\ln \frac{(100C - Q)}{(100C - Q_0)} = -\frac{t}{RC}$$

$$100C - Q = (100C - Q_0) e^{-t/RC}$$

$$i = \frac{dQ}{dt} = \left(\frac{100C - Q_0}{RC} \right) e^{-t/RC} = \left(\frac{50 - 10}{1} \right) e^{-t/RC}$$


$$i = 40 e^{-t/RC}$$

at $t = 2 \text{ sec}$

$$i = 40 e^{-2} = 5.413 \text{ A}$$


17. (a)

Z_{Th} :

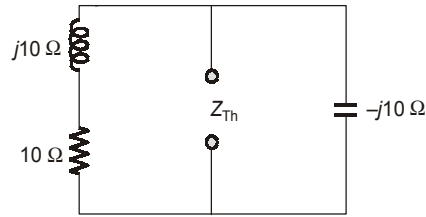

$$Z_{Th} = \frac{(10 + j10)(-j10)}{10 + j10 - j10} = 10 - j10$$

V_{Th} :

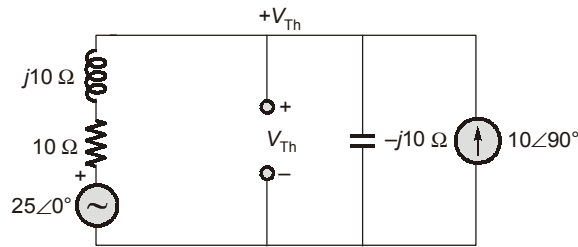

$$\frac{V_{Th} - 25}{10 + j10} + \frac{V_{Th}}{-j10} = 10\angle 90^\circ$$

$$\frac{V_{Th}}{10 + j10} - \frac{25}{10 + j10} - \frac{V_{Th}}{j10} = 10j$$

$$(V_{Th})j10 - 250j - 10V_{Th} - 10jV_{Th} = -100(10 + 10j)$$

$$j10V_{Th} - 250j - 10V_{Th} - 10jV_{Th} = -1000(1 + j)$$

$$-10V_{Th} = -1000 - 1000j + 250j$$


$$-10V_{Th} = -1000 - 750j$$

$$V_{Th} = 100 + j75$$

$$Z_L = Z_{Th}^* = 10 + j10$$

$$P_{max} = \frac{|V_{Th}|^2}{4\text{Re}\{Z_{Th}\}} = \frac{(\sqrt{100^2 + 75^2})^2}{4 \times 10} = 390.625 \text{ W}$$

18. (d)

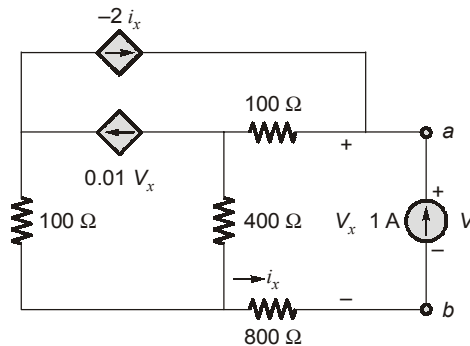

$$V = 100(1 - 2i_x) + 400(1 - 2i_x - 0.01V_x) + 800i_x$$

$$i_x = 1 \text{ A and } V_x = V$$

$$5V = 1300 - 1000 = 300$$

$$V = 60 \text{ V}$$

∴

and

$$R_{Th} = 60 \Omega$$

19. (b)

Given,

$$\begin{aligned} f_0 &= 5 \text{ kHz} \\ Z &= Z_{\text{source}} + Z_{\text{load}} \\ &= 2 + j4 + 10 - jX_C \\ &= [12 + j(4 - X_C)] \Omega \end{aligned}$$

at resonance, imaginary part of Z is zero.

$$\therefore X_L = X_C$$

$$\therefore X_C = \frac{1}{\omega_0 C} = 4$$

$$\text{or } C = 7.95 \mu\text{F}$$

As at resonance current is maximum and thus, maximum power transferred to R .

20. (c)

Condition for Transient free response is given by

$$\omega t_0 = \tan^{-1}\left(\frac{\omega L}{R}\right) - \theta + \frac{\pi}{2}$$


$$\text{here, } \omega = \frac{1}{2}, \quad \theta = 45^\circ$$

$$\frac{t_0}{2} = \tan^{-1}\left(\frac{\frac{1}{2} \times 2}{1}\right) - \frac{\pi}{4} + \frac{\pi}{2}$$

$$\frac{t_0}{2} = \frac{\pi}{2}$$

$$t_0 = \pi = 3.1416 \text{ sec}$$

21. (a)

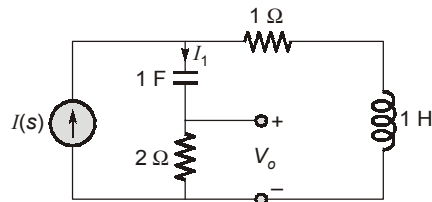


$$I_1(s) = \frac{I(s)(1+s)}{\frac{1}{s} + 2 + 1 + s} = \frac{I(s)(s+1)s}{s^2 + 3s + 1}$$

$$V_o(s) = 2I_1(s) = \frac{I(s)2s(s+1)}{s^2 + 3s + 1}$$

$$\frac{V_o(s)}{I(s)} = \frac{2s(s+1)}{s^2 + 3s + 1}$$

22. (c)

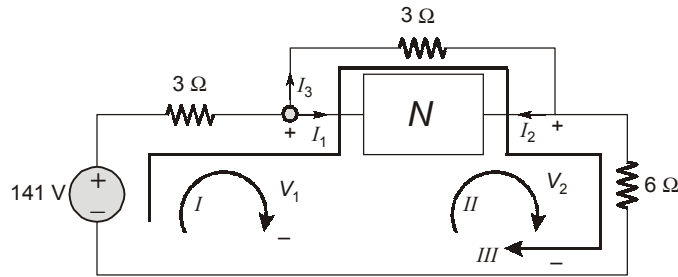

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 & 1 \\ 1 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \Rightarrow \begin{aligned} V_1 &= 2I_1 + I_2 \\ V_2 &= I_1 + 4I_2 \end{aligned}$$

Applying KVL

Loop I

$$\begin{aligned} 3(I_1 + I_3) + V_1 &= 141 \\ 3I_1 + 3I_3 + 2I_1 + I_2 &= 141 \\ 5I_1 + I_2 + 3I_3 &= 141 \end{aligned} \quad \dots(i)$$

Loop II

$$\begin{aligned} V_2 &= (I_3 - I_2) \cdot 6 \\ V_2 &= I_1 + 4I_2 \\ I_1 + 4I_2 &= 6I_3 - 6I_2 \\ I_1 + 10I_2 - 6I_3 &= 0 \end{aligned} \quad \dots(ii)$$

Loop III


$$\begin{aligned} 3(I_1 + I_3) + 3I_3 + 6(I_3 - I_2) &= 141 \\ 3I_1 - 6I_2 + 12I_3 &= 141 \end{aligned} \quad \dots(iii)$$

By equation (i), (ii) and (iii)

$$I_1 = 24 \text{ A} \quad I_2 = 1.5 \text{ A} \quad I_3 = 6.5 \text{ A}$$

23. (b)

At $t = 0^-$ S_1 is closed. S_2 is open

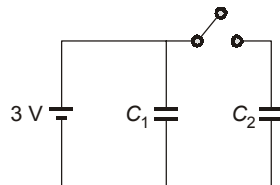


C_1 gets charged upto 3 V charge stored in C_1

$$Q_0 = C_1 V = 1 \times 3 = 3 \text{ C}$$

Voltage across C_2 is zero at $t = 0^-$, so no charge stored in C_2 .

At $t > 0$, S_1 is open and S_2 is closed.

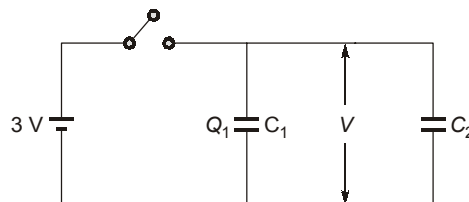charge stored (Q_0) initially in C_1 gets redistributed between C_1 and C_2



Let Charge stored in $C_1 = Q_1$

Charge stored in $C_2 = Q_2$

According to conservation of charge

$$Q_1 + Q_2 = Q_0 = 3 \quad \dots(1)$$

Voltage across C_1 = Voltage across C_2

$$\frac{Q_1}{C_1} = \frac{Q_2}{C_2} \Rightarrow \frac{Q_1}{1} = \frac{Q_2}{2}$$

$$Q_2 = 2Q_1 \quad \dots(2)$$

from (1) and (2)

$$Q_1 = 1 \text{ C}$$


and

$$Q_2 = 2 \text{ C}$$

$$\therefore \text{Voltage across the combination} = \frac{Q_1}{C_1} = \frac{1}{1} = 1 \text{ V}$$

24. (d)

Applying KCL on supernode

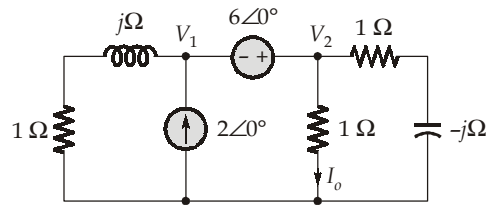

$$\frac{V_1}{1+j} - 2 + \frac{V_2}{1} + \frac{V_2}{1-j} = 0$$

and

$$V_1 + 6 = V_2$$

$$\therefore \begin{bmatrix} 0.5 - 0.5j & 1.5 + 0.5j \\ 1 & -1 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 2 \\ -6 \end{bmatrix}$$

$$\therefore V_2 = \frac{\begin{bmatrix} 0.5 - 0.5j & 2 \\ 1 & -6 \end{bmatrix}}{\begin{bmatrix} 0.5 - 0.5j & j0.5 + 0.5j \\ 1 & -1 \end{bmatrix}}$$

$$V_2 = \frac{5.83095 \angle 149.036^\circ}{2 \angle 180^\circ}$$

$$V_2 \approx 2.915 \angle -30.96^\circ$$

Thus,

$$I_o = \frac{V_2}{1\Omega} = 2.915 \angle -30.96^\circ$$

25. (b)


$$\begin{aligned} Z_{AB} &= \left(\frac{23}{6} \right) + [(3 + j4) \parallel (3 - j4)] \\ &= \frac{23}{6} + \frac{(3 + j4)(3 - j4)}{6} = \frac{23 + 25}{6} = \frac{48}{6} \Omega = 8 \Omega \end{aligned}$$

$$\therefore Z_{AB} = 8 \Omega$$

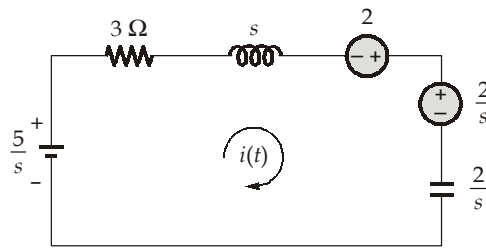26. (c)

At $t = 0$, switch is closed

For $t > 0$, the circuit in s-domain becomes,



Applying KVL, we get,

$$\frac{5}{s} - \frac{2}{s} + 2 = \left(3 + s + \frac{2}{s} \right) I(s)$$

$$I(s) = \frac{2s + 3}{(s + 1)(s + 2)}$$

Using partial fractions, $I(s) = \frac{1}{(s + 1)} + \frac{1}{(s + 2)}$

or $i(t) = L^{-1}[I(s)] = (e^{-t} + e^{-2t}) \text{ A ; for } t > 0$

27. (d)

Given, $f = 1.5 \text{ MHz}$
 $C = 150 \text{ pF}$
 $\text{BW} = 10 \text{ kHz}$

For series *RLC* circuit, $Q = \frac{f_o}{\text{BW}} = \frac{1.5 \times 10^6}{10 \times 10^3} = 150$

$$Q = \frac{1}{\omega RC}$$

$$\frac{1}{150} = 2\pi \times 1.5 \times 10^6 \times 150 \times 10^{-12} \times R$$

$$R = \frac{10^6}{2\pi \times 1.5 \times 150 \times 150} = 4.71 \Omega$$

28. (c)

For a capacitor $i(t) = \frac{cdv(t)}{dt} = 10 \times 10^{-6} \frac{dv(t)}{dt} \times 10^3 \text{ A}$
 $= 10^{-2} \frac{dv(t)}{dt} \text{ A} = 10 \frac{dv(t)}{dt} \text{ mA}$

29. (d)

Now, applying KCL at node A, we get,


$$I_1 = V_1 + (V_1 - V_1')$$

$$= 2V_1 - V_1'$$

$$I_1 = 2V_1 - \frac{1}{a}V_2$$

For I_2 , we can write
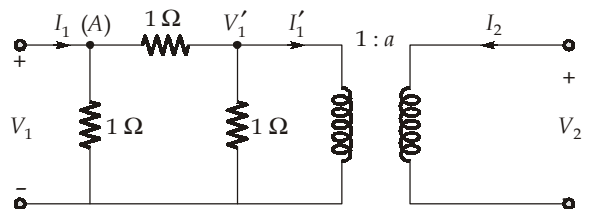
$$I_2 = -\frac{1}{a}I_1' = -\frac{1}{a}[-V_1' + (V_1 - V_1')]$$



$$= -\frac{1}{a}V_1 + \frac{2}{a^2}V_2$$

$$\therefore \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 2 & -\frac{1}{a} \\ -\frac{1}{a} & \frac{2}{a^2} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

For the Z-parameter to not exist.

$$|Y| = 0$$

$$\therefore |Y| = \frac{4}{a^2} - \frac{1}{a^2} = \frac{3}{a^2}$$

$$\therefore |Y| \neq 0$$

Thus, no such value exist for which $|Y| = 0$.

30. (a)

From phasor, we can write

$$\tan 30^\circ = \frac{X_C}{R_2}$$

$$\Rightarrow R_2 = X_C \sqrt{3} = \frac{\sqrt{3}}{\omega C}$$

$$\tan 45^\circ = \frac{X_L}{R_1}$$

$$\Rightarrow R_1 = X_L = \omega L$$

$$R_1 R_2 = \frac{\sqrt{3}}{\omega C} \times \omega L = \frac{L}{C} \sqrt{3}$$

$$R_1 R_2 = \sqrt{3} = 1.732$$

we know

$$\frac{R_1 + R_2}{2} \geq \sqrt{R_1 R_2}$$

as arithmetic mean \geq geometric mean ; (for non-negative real numbers)

$$R_1 + R_2 \geq 2\sqrt{\sqrt{3}}$$

$$R_1 + R_2 \geq 2(3)^{1/4}$$

Minimum value of $R_1 + R_2 = 2.63 \Omega$

