

# POSTAL Book Package

# 2023

## Electrical Engineering Conventional Practice Sets

### Analog Electronics

### *Contents*

Sl.	Topic	Page No.
1.	Diode Circuits .....	2 - 25
2.	BJT-Characteristics and Biasing .....	26 - 51
3.	BJT as an Amplifier .....	52 - 71
4.	FET Biasing and Basic FET Amplifiers .....	72 - 91
5.	Frequency Response of Amplifiers .....	92 - 108
6.	Differential Amplifiers .....	109 - 117
7.	Feedback Amplifiers .....	118 - 133
8.	Large Signal Amplifier .....	134 - 147
9.	Operational Amplifier .....	148 - 189
10.	Signal Generators and Waveform Shaping Circuits .....	190 - 215




**MADE EASY**  
Publications

**Note:** This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.

## Diode Circuits

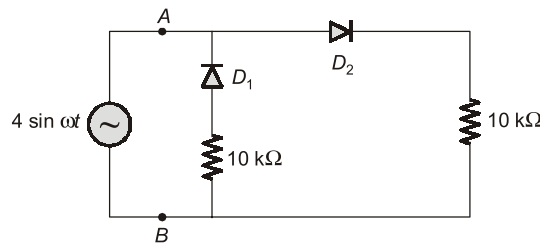**Q1** A voltage source  $V_{AB} = 4 \sin \omega t$ , is applied across the terminals  $A$  and  $B$  of the circuit. The diodes are assumed to be ideal. Find the impedance offered by the circuit across the terminals  $A$  and  $B$  in kilo ohm.



**Solution:**

In +ve half cycle  $D_1$  – off (R.B.)

$D_2$  – on (F.B.)

∴ Equivalent circuit will be


∴

$$V_{AB} = 4 \sin \omega t$$

$$I_{AB} = \frac{V_{AB}}{10 \text{ k}\Omega}$$

∴
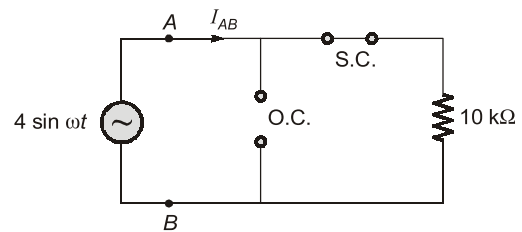
$$R_i = \frac{V_{AB}}{I_{AB}} = 10 \text{ k}\Omega$$



For –ve half cycle,

$D_1$  on,  $D_2$  off


Equivalent circuit,

$$V_{AB} = 4 \sin \omega t$$


$$I_{AB} = \frac{4 \sin \omega t}{10 \text{ k}\Omega}$$

∴
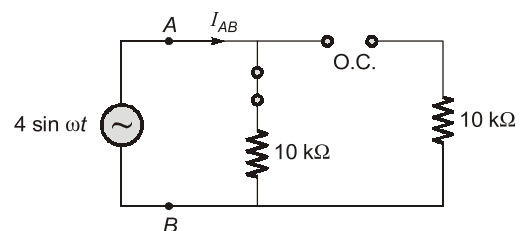
$$\frac{V_{AB}}{I_{AB}} = R_i = 10 \text{ k}\Omega$$



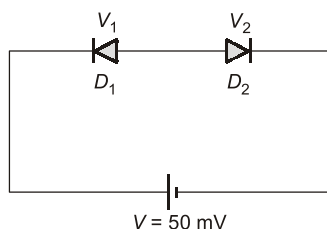**Q2** Two ideal and identical junction diodes are connected as shown in Figure. If the current through the reverse-biased diode is  $I_0$  and is constant, explain the circuit operation when both the diodes are connected in forward-biased condition. Assume  $V_T = 25 \text{ mV}$ ,  $V_\gamma = 0.7 \text{ V}$  and  $\eta = 1$  for the diodes.



**Solution:**

**Case 1:** Diode  $D_1$  is in reverse bias where as  $D_2$  is forward biased.

At Node 'a'

$$I_1 + I_2 = 0$$

$$I_1 = -I_2$$

$$I_S \left( e^{-\frac{V_1}{\eta V_T}} - 1 \right) = -I_S \left( e^{\frac{+V_2}{\eta V_T}} - 1 \right)$$

$$e^{-\frac{V_1}{\eta V_T}} + e^{\frac{V_2}{\eta V_T}} = 2$$

Also,

$$V_2 = 50 - V_1$$

$$\therefore e^{-\frac{V_1}{\eta V_T}} + e^{\frac{50 - V_1}{\eta V_T}} = 2$$

$$e^{-\frac{V_1}{\eta V_T}} \left[ 1 + e^{\frac{50}{\eta V_T}} \right] = 2$$

$$e^{-\frac{V_1}{V_T}} = \frac{2}{1 + e^2}$$

$$e^{-\frac{V_1}{V_T}} = \frac{2}{3.39} = 0.24$$


Putting in  $I_1$ ,

$$I_1 = I_0 = I_S \left[ e^{-\frac{V_1}{V_T}} - 1 \right]$$

$$I_1 = I_0 = -0.76 I_S$$

-ve sign denotes that direction of current will be opposite to the assumed direction.

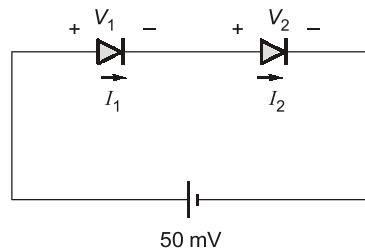**Case 2:** Both the diodes are forward biased.



As both diodes are ideal and identical hence voltage drop across both diodes will be same.


$$\therefore V_1 = V_2 = 25 \text{ mV}$$

$$\text{Now, } I_1 = I_2 = I_S \left( e^{\frac{V_1}{V_T}} - 1 \right) = I_S \left( e^{\frac{25}{25}} - 1 \right) = 1.72 I_S$$

$$\frac{I_1}{I_0} = \frac{1.72 I_S}{0.76 I_S} = 2.26$$

$$\therefore I_1 = 2.26 I_0$$

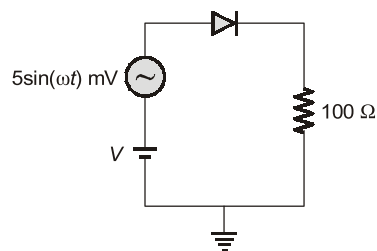**Q3** A DC current of  $26 \mu\text{A}$  flows through the circuit shown. The diode in the circuit is forward biased and it has an ideality factor of one. At the quiescent point, the diode has a junction capacitance of  $0.5 \text{ nF}$ . Its neutral region resistances can be neglected. Assume that the room temperature thermal equivalent voltage is  $26 \text{ mV}$ .



For  $\omega = 2 \times 10^6 \text{ rad/s}$ , the amplitude of the small-signal component of diode current.

**Solution:**

The small-signal equivalent model of the given circuit can be drawn as shown below.

Given that,


$$\omega = 2 \times 10^6 \text{ rad/sec}$$

$$C_j = 0.5 \text{ nF}$$

$$I_{DC} = 26 \mu\text{A}$$

$$V_T = 26 \text{ mV}$$

$$\eta = 1$$

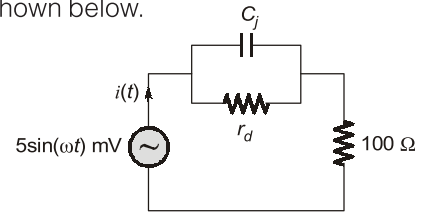

Since, small signal incremental diode resistance,  $r_d = \frac{\eta V_T}{I_{DC}} = \frac{26 \text{ mV}}{26 \mu\text{A}} = 1 \text{ k}\Omega$

and impedance due to junction capacitance,  $\frac{1}{\omega C_j} = \frac{1}{2 \times 10^6 \times 0.5 \times 10^{-9}} \Omega = 1 \text{ k}\Omega$

So, total impedance of the circuit will be,

$$Z = \left( r_d \parallel \frac{1}{j\omega C_j} \right) + 100 \Omega$$

$$\left( r_d \parallel \frac{1}{j\omega C_j} \right) = \frac{(1000)(-j1000)}{1000 - j1000} \Omega = \frac{-j(1+j)}{2} \text{ k}\Omega = \frac{1}{2}(1-j) \text{ k}\Omega = (500 - j500) \Omega$$



$\therefore$

$$Z = 600 - j500 \Omega$$

$$|Z| = 100\sqrt{36 + 25} = 100\sqrt{61} \Omega$$


$$I_m = \frac{V_m}{|Z|} = \frac{5 \text{ mV}}{100\sqrt{61} \Omega} = \frac{50}{\sqrt{61}} \mu\text{A} = 6.40 \mu\text{A}$$

**Q4** Assuming forward voltage drop across diodes to be 0.7 V, draw the transfer characteristic of the clipper circuit shown in figure.

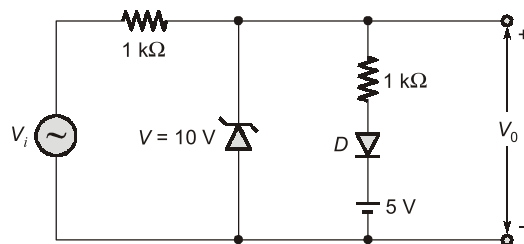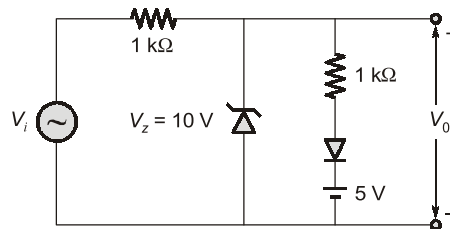**Solution:**

When  $V_i$  is +ve and  $V_i > 5.7 \text{ V}$

Assume diode is conducting,

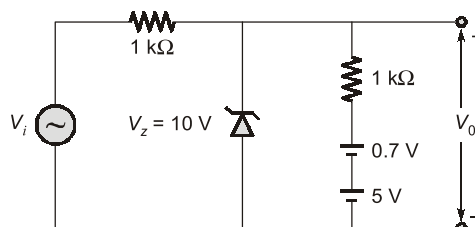

Assume the zener diode is reverse biased and having voltage less than breakdown voltage

$$V_i - I(1 \text{ k}\Omega) - I(1 \text{ k}\Omega) - 0.7 - 5 = 0$$

$$V_i - I(2 \text{ k}\Omega) - 5.7 = 0$$

$$I(2 \text{ k}\Omega) = V_i - 5.7$$

$$I = \left( \frac{V_i - 5.7}{2 \text{ k}\Omega} \right)$$

$$V_o = 5.7 + 1 \times I$$

$$= 5.7 + \left( \frac{V_i - 5.7}{2} \right) = \left( \frac{5.7 + V_i}{2} \right)$$

When,

$$V_i < 5.7 \text{ V}$$

$$V_o = V_i$$

If,

$$5.7 < V_i < 14.3$$

( $\because$  Diode is in off state)

$$V_o = \left( \frac{5.7 + V_i}{2} \right)$$

Diode conducts and zener diode is reverse biased,

When,

$$V_i > 14.3 \text{ V}$$

$\Rightarrow$

$$V_o = 10 \text{ volts}$$


Breakdown occurs in zener diode.

When,


$$V_i < 0 \text{ V}$$

$$V_o = -0.7 \text{ V}$$

**Transfer characteristics:**

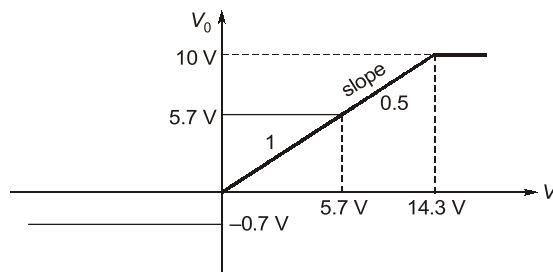

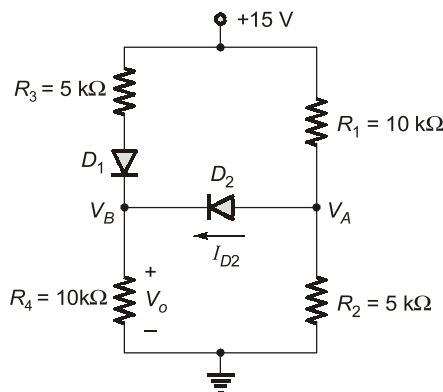**Q5** Determine the current  $I_{D2}$  and the voltage  $V_o$  in the multidiode circuit shown in the figure below. Assume that, cut-in voltage  $V_\gamma = 0.7 \text{ V}$  for each diode.



**Solution:**

To begin, initially assume that, both the diodes  $D_1$  and  $D_2$  are in their conducting state.

By applying KCL at A and B nodes, we have

$$\frac{15 - V_A}{10} = I_{D2} + \frac{V_A}{5}$$

...(i)

$$\text{and } \frac{15 - (V_B + 0.7)}{5} + I_{D2} = \frac{V_B}{10} \quad \dots(\text{ii})$$

We note that  $V_B = V_A - 0.7$ . Combining the two equations and eliminating  $I_{D2}$ , we find

$$V_A = 7.62 \text{ V} \quad \text{and} \quad V_B = 6.92 \text{ V}$$

From equation (i) above, we obtain

$$\frac{15 - 7.62}{10} = I_{D2} + \frac{7.62}{5} \Rightarrow I_{D2} = -0.786 \text{ mA}$$

We assumed that  $D_2$  was ON, so a negative current is inconsistent with that initial assumption.


Now assume that diode  $D_2$  is OFF and  $D_1$  is ON. To find the node voltages, we can simply use voltage divider principle as

$$V_A = \left( \frac{5}{5 + 10} \right) (15) = 5 \text{ V}$$


$$\text{and } V_B = V_o = \left( \frac{10}{10 + 5} \right) (15 - 0.7) = 9.53 \text{ V}$$

These voltages show that diode  $D_2$  is indeed reverse biased so that  $I_{D2} = 0$ .

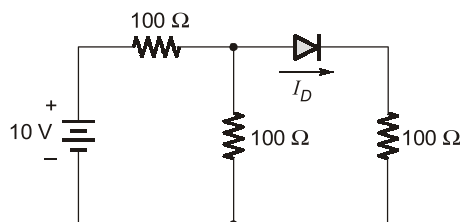**Q6** Find the diode current  $I_D$  in the circuit shown below when the diode has cut in voltage,  $V_y = 0.7 \text{ V}$  and forward resistance,  $R_f = 25 \Omega$ .





**Solution:**

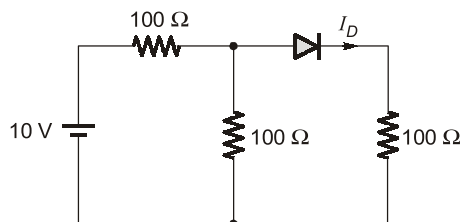

**Given :** Diode cut-in voltage = 0.7 V and diode forward resistance = 25 Ω

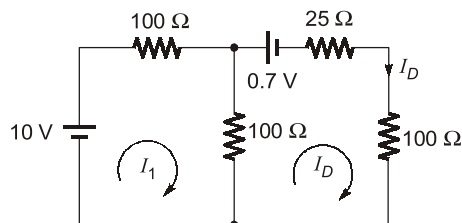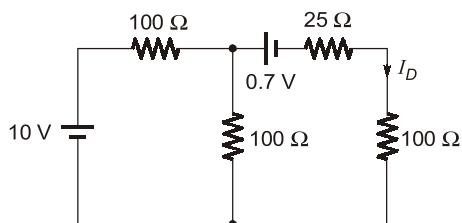Replacing the diode with its equivalent, we get,



$$\text{Using KVL, } 10 - 100I_1 - 100(I_1 - I_D) = 0 \quad \dots(\text{i})$$

$$-0.7 - 125I_D + 100(I_1 - I_D) = 0 \quad \dots(\text{ii})$$

Solving equation (i) and (ii)

$$10 - 200I_1 - 100I_D = 0 \quad \dots(\text{iii})$$

$$-0.7 - 225I_D + 100I_1 = 0 \quad \dots(\text{iv})$$