

POSTAL Book Package

2023

Electrical Engineering

Conventional Practice Sets

Power Electronics

Contents

Sl. Topic	Page No.
1. Power Semi-conductor Diode and Transistor	2
2. Diode Rectifiers	6
3. Thyristors	14
4. Thyristor Commutation Techniques	24
5. Phase Controlled Rectifiers	31
6. Choppers	55
7. Inverters	73
8. Resonant Converters	94
9. Power Semiconductor Drives	98
10. Switched Mode Power Supply (SMPS)	114
11. Miscallenaous	118




MADE EASY
Publications

Note: This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.

Power Semi-conductor Diode and Transistor

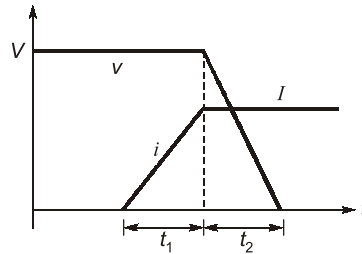Q1 The voltage across and current through a power semiconductor device switching transients are shown in the figure. Deduce the expression for the energy lost in the ON/OFF transition in terms of V , I , t and t_2 .



Solution:

During t_1 interval voltage is constant (V), while current starts increasing. Thereafter, in t_2 interval voltage starts decreasing and becomes zero and current becomes constant (I), so the transition is turn on.

During t_1 interval:

$$\text{Power loss} = vi$$

$$\text{Energy loss, } E_1 = \int vi dt [= E_1(\text{Say})]$$

$\therefore v$ is constant in this interval,

\therefore

$$\begin{aligned} E_1 &= V \cdot \int i dt \\ &= V(\text{Area under } i\text{-}t \text{ curve in } t_1) \end{aligned}$$

or

$$E_1 = V \left[\frac{1}{2} I t_1 \right] = \frac{1}{2} V I t_1$$

During t_2 interval:

$$\text{Power loss} = vi$$

$$\text{Energy loss, } E_2 = \int vi dt$$

$\therefore i$ is constant in the interval ($=I$)

\therefore

$$\begin{aligned} E_2 &= I \cdot \int v dt \\ &= I(\text{Area under } v\text{-}t \text{ curve in } t_2) \end{aligned}$$

or


$$E_2 = I \left(\frac{1}{2} V t_2 \right) = \frac{1}{2} V I t_2$$

Therefore, total energy lost during ON transition,


$$E_{\text{lost}} = E_1 + E_2 = \frac{1}{2} V I t_1 + \frac{1}{2} V I t_2$$

or,
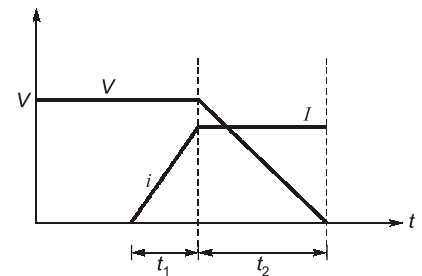
$$E_{\text{lost}} = \frac{1}{2} V I (t_1 + t_2)$$



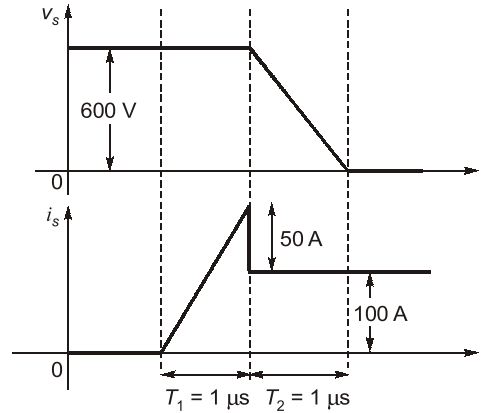Q2 If the voltage (V_s) across and current (i_s) through a power semiconductor switch during turn-on process are shown in the figure below, then calculate the energy dissipated during the turn-on process.



Solution:

We know that,

$$\text{Energy} = \int_0^t v_i dt$$

Here,

$$\text{Energy} = E_I + E_{II} + E_{III}$$

$$= V \cdot 0 + \int_{t_1}^{t_2} V \cdot i_s dt + \int_{t_2}^{t_3} v_s \cdot I_2 dt$$


$$= 0 + V \int_0^{T_1} i_s dt + I_2 \int_0^{T_2} v_s dt$$

$$= V \left[\frac{1}{2} I_1 T_1 \right] + I_2 \left[\frac{1}{2} V T_2 \right]$$


$$= 600 \left[\frac{150}{2} \times 1 \times 10^{-6} \right] + 100 \left[\frac{600}{2} \times 1 \times 10^{-6} \right]$$

$$= 75000 \times 10^{-6} \text{ J}$$
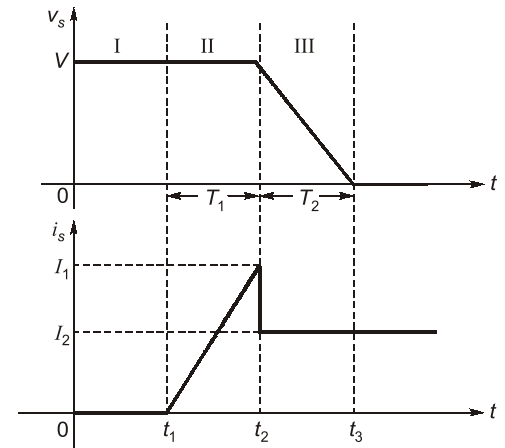
$$\therefore \text{Energy} = 75 \text{ mJ}$$



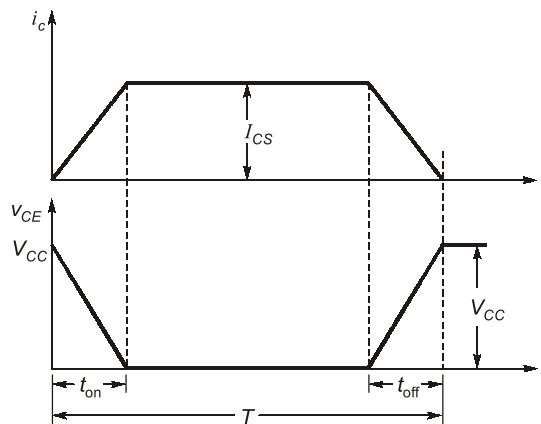Q3 Find the energy loss during switch-on and off intervals of a power transistor with switching characteristics as shown in the figure. Where $I_{CS} = 80 \text{ A}$, $V_{CC} = 220 \text{ V}$, $t_{on} = 1.5 \text{ ms}$ and $t_{off} = 4 \text{ ms}$. Also determine the average power loss in the transistor if switching frequency is 2 kHz .



Solution:

From the switching characteristics given in the figure above.

$$\begin{aligned}
 \text{Energy loss during turn-on } (E_{\text{loss(on)}}) &= \int_0^{t_{\text{on}}} i_c \cdot v_{CE} dt \\
 &= \int_0^{t_{\text{on}}} \left[\frac{I_{CS}}{t_{\text{on}}} \right] t \cdot \left(V_{CC} - \frac{V_{CC}}{t_{\text{on}}} t \right) dt \\
 &= \int_0^{t_{\text{on}}} \frac{I_{CS} V_{CC}}{t_{\text{on}}} \cdot t dt - \int_0^{t_{\text{on}}} \frac{I_{CS} V_{CC}}{t_{\text{on}}^2} \cdot t^2 dt \\
 &= \frac{I_{CS} V_{CC}}{t_{\text{on}}} \cdot \frac{t_{\text{on}}^2}{2} - \frac{I_{CS} V_{CC}}{t_{\text{on}}^2} \cdot \frac{t_{\text{on}}^3}{3} = \frac{I_{CS} V_{CC}}{6} \cdot t_{\text{on}}
 \end{aligned}$$

$$\therefore E_{\text{loss(on)}} = \frac{80 \times 220}{6} \times 0.15 \times 10^{-3} \text{ Watt-sec.}$$

$$E_{\text{loss(on)}} = 0.44 \text{ Watt-sec.}$$

Similarly,
$$E_{\text{loss(off)}} = \frac{I_{CS} V_{CC}}{6} \cdot t_{\text{off}}$$

or
$$E_{\text{loss(off)}} = \frac{80 \times 220}{6} \times 0.4 \times 10^{-3} \text{ Watt-sec.}$$

$$\therefore E_{\text{loss(off)}} = 1.17 \text{ Watt-sec.}$$

Average power loss in the power transistor for switching frequency of 2 kHz

= (Energy loss in ON and OFF switching) \times Switching frequency

$$= \frac{I_{CS} V_{CC}}{6} (t_{\text{on}} + t_{\text{off}}) \times f$$

$$= (0.44 + 1.17) \times 2 \times 10^3 = 3.22 \text{ kW}$$

Q4 For a power diode, the reverse recovery time is 3.9 μs and the rate of diode-current decay is 50 A/ μs . For a softness factor of 0.3, calculate the peak inverse current and storage charge.

Solution:

Given, Reverse recovery time (t_{rr}) = 3.9 μs

$$\text{Softness factor } \left(\frac{t_5}{t_4} \right) = 0.3$$

$$\therefore t_5 = 0.3 t_4$$

$$t_{rr} = t_4 + t_5 = 3.9 \mu\text{s}$$

$$\text{or, } 1.3 t_4 = 3.9 \mu\text{s}$$


$$\text{or, } t_4 = 3 \mu\text{s}$$

Given,
$$\frac{di}{dt} = 50 \text{ A}/\mu\text{s}$$

The peak inverse current I_{RM} can be expressed as:

$$I_{RM} = t_4 \frac{di}{dt} = 3 \times 50 \text{ Amp.}$$

or,
$$I_{RM} = 150 \text{ Amp.}$$

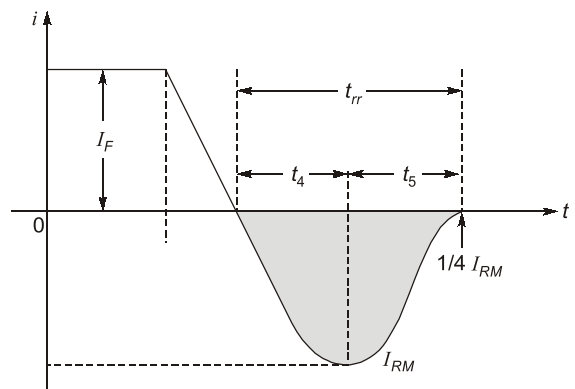

Assuming reverse recovery characteristic to be triangular,

$$\text{Storage charge } (Q_R) = \frac{1}{2} I_{RM} \cdot t_{rr} = \frac{1}{2} \times 150 \times 3.9 \mu\text{C}$$

$$Q_R = 292.5 \mu\text{C}$$

$$\therefore I_{RM} = 150 \text{ A and } Q_R = 292.5 \mu\text{C}$$

Q5 For the circuit shown in figure below, determine:

- (a) Power loss in the on-state
- (b) Power loss during the turn-on interval.

MOSFET parameters are: $t_r = 2 \text{ ms}$, $R_{DS(on)} = 0.2 \Omega$, duty cycle (D) = 0.7 and $f = 30 \text{ kHz}$.

Solution:

When MOSFET is on:

Drain current,

$$I_D = \frac{V_{DS}}{R_L + R_{DS(on)}}$$

$$= \frac{100}{12 + 0.2} = 8.197 \text{ A}$$

Switching period,

$$T = \frac{1}{f} = \frac{1}{30 \times 10^3} = 33.333 \mu\text{sec}$$

$$\text{Duty cycle } (D) = \frac{t_{on}}{T}$$

$$\therefore \text{ on time is given by, } t_{on} = D \cdot T = 0.7 \times 33.333 \times 10^{-6}$$

$$= 23.3331 \mu\text{s}$$

(a) Energy loss during on state,

$$E_{on} = I_D^2 R_{DS(on)} \cdot t_{on}$$

$$= (8.197)^2 \times 0.2 \times (23.3331 \times 10^{-6})$$

$$= 313.554 \mu\text{J}$$

Now, power loss during on state,

$$P_{on} = E_{on} \cdot f$$

$$= 313.554 \times 10^{-6} \times 30 \times 10^3$$

$$= 9.4066 \text{ W}$$

(b) Energy loss during the turn-on [assuming triangular switching on characteristic]

$$E_{\text{turn-on}} = \frac{V_{DS} \cdot I_D \cdot t_r}{6} = \frac{100 \times 8.197}{6} \times 2 \times 10^{-6}$$

$$= 273.233 \mu\text{J}$$

Power loss during turn-on,

$$P_{\text{turn-on}} = E_{\text{turn-on}} \cdot f = 273.233 \times 10^{-6} \times 30 \times 10^3$$

$$= 8.197 \text{ W}$$

