



**MADE EASY**

India's Best Institute for IES, GATE & PSUs

Important Questions  
for **GATE 2022**


**ELECTRONICS  
ENGINEERING**

**Day 3 of 8**

**Q.51 - Q.75 (Out of 200 Questions)**

**Control Systems  
and Analog Circuits**

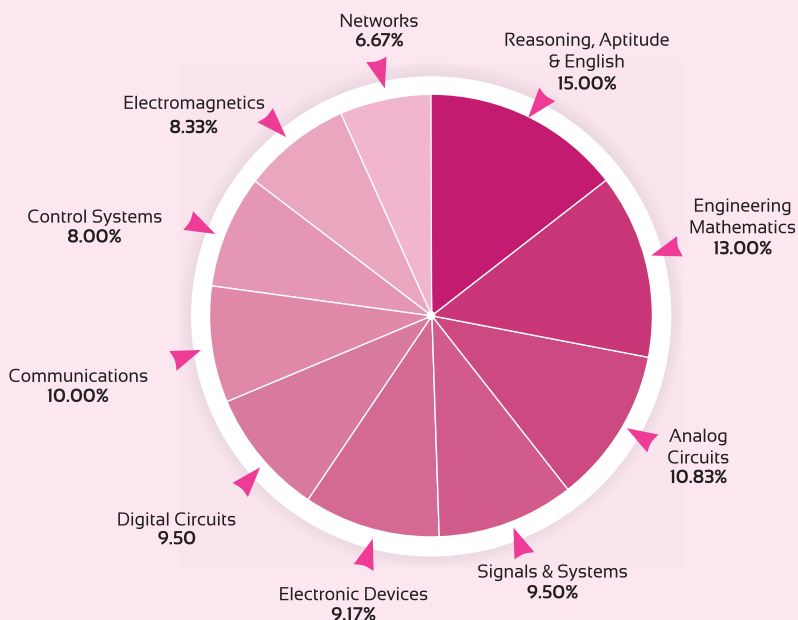
**SUBJECT-WISE WEIGHTAGE ANALYSIS OF GATE SYLLABUS**



Subject	Average % (last 5 yrs)*
Reasoning, Aptitude & English	15.00%
Engineering Mathematics	13.00%
Analog Circuits	10.83%
Signals & Systems	9.50%
Electronic Devices	9.17%
Digital Circuits	9.50%
Communications	10.00%
Control Systems	8.00%
Electromagnetics	8.33%
Networks	6.67%
<b>Total</b>	<b>100%</b>

## Control Systems and Analog Circuits

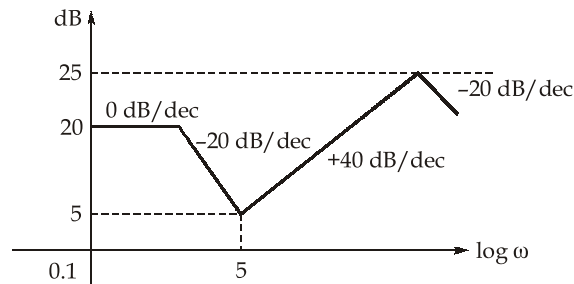**Q.51** Consider the Bode plot shown in the figure below,



the transfer function is,

- |   |  |
|---|--|
| <p>(a) <math>\frac{35(s+5)^2}{(s+0.89)(s+22.32)^3}</math></p> <p>(c) <math>\frac{281.37(s+5)^3}{(s+1)(s+15)^3}</math></p> | <p>(b) <math>\frac{281.37(s+5)^3}{(s+0.89)(s+15.81)^3}</math></p> <p>(d) <math>\frac{35(s+5)^3}{(s+1)(s+22.32)^3}</math></p> |
|---|--|

**Q.52** The open loop transfer function of a unity feedback control system is given by

$$G(s) = \frac{K}{s(0.1s+1)}$$

The value of  $K$  such that the resonance peak becomes 1.25 is \_\_\_\_\_.

**Q.53** The open loop transfer function of a control system is given by

$$G(s) = \frac{K}{s(1+s)(1+0.1s)}$$

The value of gain  $K$  for which the gain margin of the system is 20 dB is


- |          |          |
|----------|----------|
| (a) 1.10 | (b) 10   |
| (c) 11   | (d) 12.1 |

**Q.54** The open loop transfer function of a unity feedback control system is given as

$$G(s) = \frac{K}{s^2}$$

The value of system gain  $K$  for which point  $+j2$  lie on the root locus is \_\_\_\_\_.

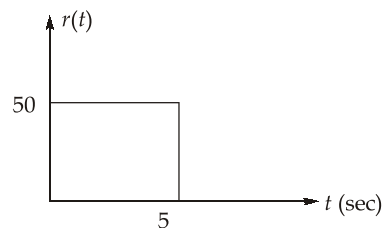**Q.55** The steady state error of a unity feedback linear control system for a unit step input is 0.5. The steady state error of the same system, for a pulse input as shown in the figure below is



- |          |              |
|----------|--------------|
| (a) zero | (b) 12       |
| (c) 25   | (d) infinite |

**Q.56** An uncompensated open loop transfer function of a system is given by

$$G(s)H(s) = \frac{100}{s(s+1)}$$

In order for the velocity error constant of compensated system to be 10, the required compensator is given by

$$G_c(s) = \frac{(s+10)}{(s+a)}$$

then the value of 'a' is \_\_\_\_\_.

**Q.57** The transfer function of a control system is given as

$$G(s) = \frac{10}{s(s+2)}$$

A first order compensator is designed in a unity feedback configuration so that the poles of the compensated system are located at -1, -3 and -5. The transfer function of the compensator is,


- |                                 |                                |
|---------------------------------|--------------------------------|
| (a) $\frac{0.9(s+4)}{(s+7)}$    | (b) $\frac{10(s+3)}{(s+5)}$    |
| (c) $\frac{0.9(s+1.67)}{(s+7)}$ | (d) $\frac{10(s+1.67)}{(s+5)}$ |

**Q.58** A unity negative feedback system has an open loop transfer function

$$G(s)H(s) = \frac{K(s+2)}{s(s-1)}$$

The value of system gain  $K$  for which the stable closed loop system has critically damped response is \_\_\_\_\_.

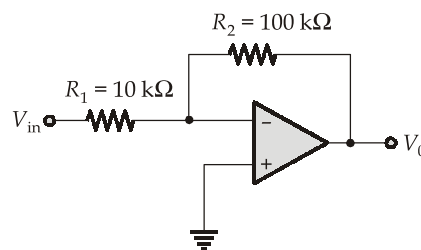
**Q.59** Consider an ideal inverting op-amp circuit as seen in the figure below:




Both the resistances  $R_1$  and  $R_2$  are constructed with a tolerance of 5%, then the range in which the gain of the amplifier can approximately vary is

- |                      |                      |
|----------------------|----------------------|
| (a) $-9 < G_v < -10$ | (b) $-8 < G_v < -11$ |
| (c) $-9 < G_v < -11$ | (d) $-8 < G_v < -10$ |

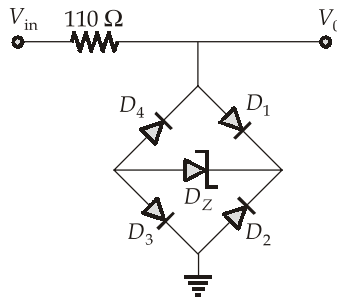
**Q.60** Consider the circuit shown in the figure below.



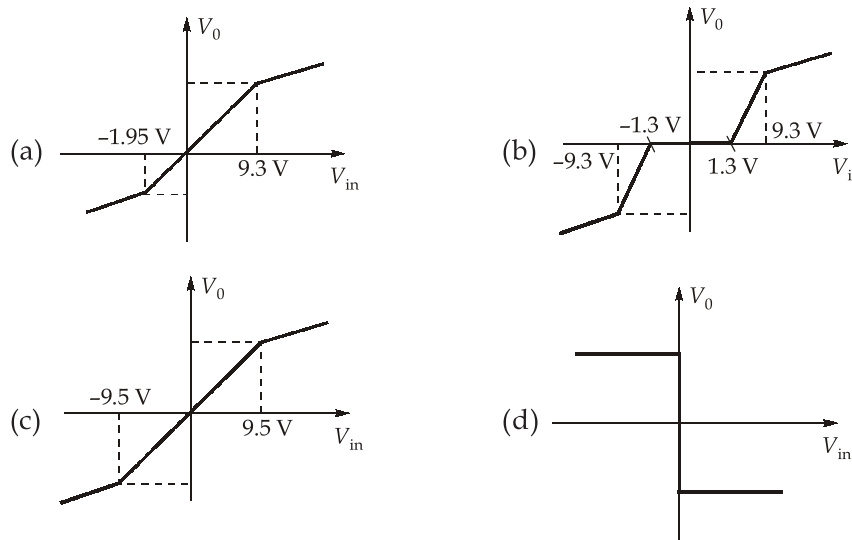The diodes shown in the figure are identical and could be modeled as a constant voltage source of  $V_D = 0.65$  V along with a forward resistance  $r_D = 20$   $\Omega$ . The Zener diode can also be modeled with a voltage drop  $V_z = 8.2$  V along with a resistance of  $r_z = 20$   $\Omega$  when reverse biased, then the transfer characteristic curve can be represented as



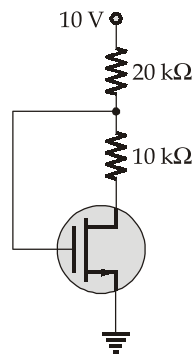**Q.61** Consider the transistor circuit shown in the figure below.



The transistor has parameter  $\frac{\mu_n C_{ox} W}{2L} = 12.5$  mA/V<sup>2</sup> and  $V_T = 1$  V, then the value of  $V_{DS}$  is equal to \_\_\_\_\_ V.

**Q.62** Consider the clamper circuit shown below.

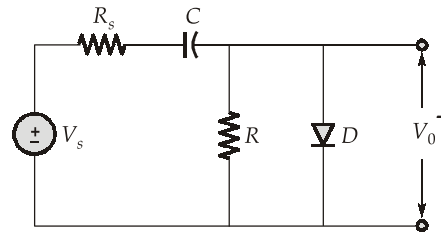
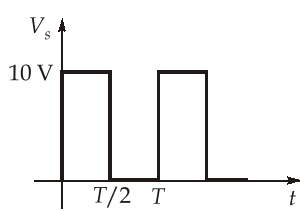


Figure 1


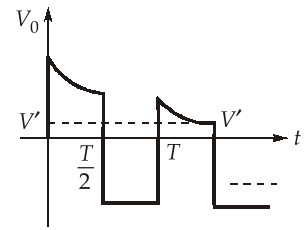


Figure 2

The diode  $D$  has a small signal forward resistance  $R_f = 100 \Omega$ . The value of  $R_s = 100 \Omega$ ,  $R = 100 \text{ k}\Omega$  and  $C = 1 \mu\text{F}$ . The input to the circuit is a square wave  $V_s(t)$  with amplitude of 10 V and frequency of 5 kHz. The output of the circuit is drawn in figure 2 which is created by neglecting the forward drop across the diode and the current flowing through resistance  $R$ , then the value of  $V'$  is equal to \_\_\_\_\_ V.

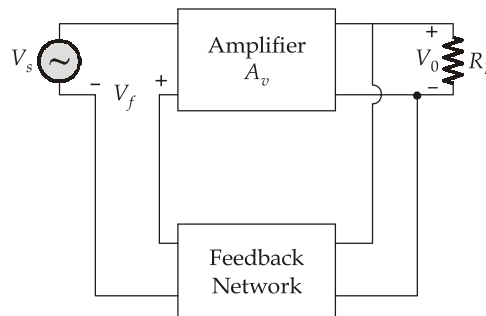
**Q.63** Consider the block diagram of a feedback network shown in the figure below.



The circuit is operated by having an input voltage  $V_s = 100 \text{ mV}$ ,  $V_f = 95 \text{ mV}$  and giving an output voltage  $V_0 = 10 \text{ V}$ . Then the value of voltage gain  $A_v$  and feedback factor  $\beta$  is equal to

- (a)  $A_v = 200$  and  $\beta = 0.837$                       (b)  $A_v = 2 \times 10^3$  and  $\beta = 0.0095$   
 (c)  $A_v = 100$  and  $\beta = 0.095$                       (d)  $A_v = 3 \times 10^3$  and  $\beta = 0.0635$

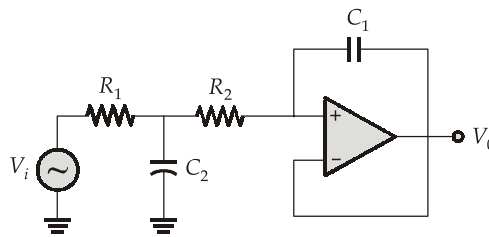
**Q.64** Consider the active filter circuit shown in the figure below.



Then the transfer function of the filter can be given as  
 (Assume the op-amp to be ideal)

- (a)  $\frac{1}{(1 + sR_1C_2)(1 + \Delta R_2C_1)}$                       (b)  $\frac{1 - sR_1C_2}{1 + sR_2C_1}$   
 (c)  $\frac{(1 + sR_2C_1)}{(1 + sR_1C_2)}$                       (d)  $\frac{1}{1 + sR_1C_2}$

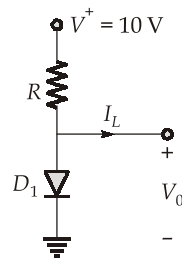
**Q.65** Consider the circuit shown in the figure below.



The value of  $I_L$  is sufficiently small so that the corresponding change in regulator output voltage  $\Delta V_0$  is small enough to justify using small signal model. The value of  $R$  is selected such that at no load the voltage across the diode is 0.7 V. Then the magnitude of  $I_D$  that results in a load


regulation  $\left(\frac{\Delta V_0}{V_0}\right) = 5 \text{ mV/mA}$  is equal to \_\_\_\_\_ mA. [Assume  $\eta = 1$  and  $V_T = 0.025 \text{ V}$ ]

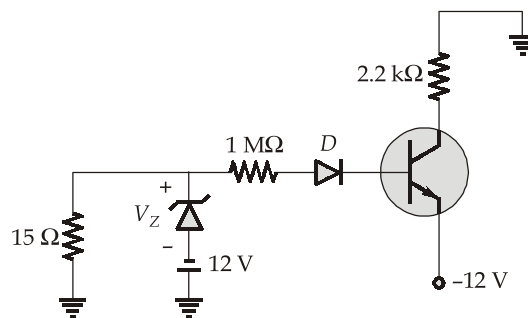**Q.66** Consider the transistor circuit shown in the figure below.



The forward drop of BJT and the diode is equal to 0.7 V and the Zener breakdown voltage  $V_z = 5 \text{ V}$ . If  $\beta = 30$  and  $V_{CE(\text{sat})} = 0.2 \text{ V}$ , then the current through collector is equal to \_\_\_\_\_ mA.

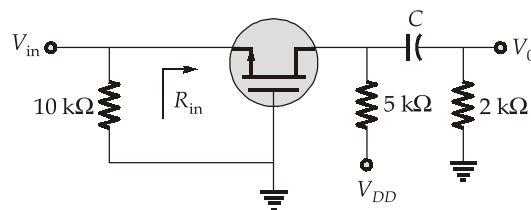**Q.67** Consider the transistor circuit shown in the figure below.



Assume the transistor is biased in saturation region with  $g_m = 5 \text{ mA/V}$ . Then the value of input resistance  $R_{in}$  is equal to

- |                  |                  |
|------------------|------------------|
| (a) 500 $\Omega$ | (b) 250 $\Omega$ |
| (c) 200 $\Omega$ | (d) 728 $\Omega$ |



**Q.71** Consider the op-amp circuit shown in the figure below.

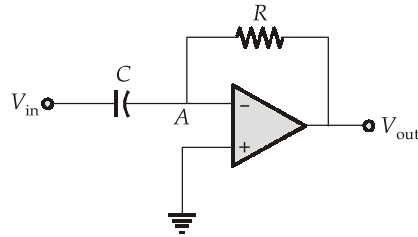


Figure (1)


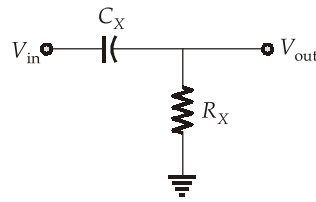


Figure (2)

The op-amp is an ideal op-amp except having a finite open loop gain of  $A_0$ . The above circuit can be modeled as a high pass filter as shown in figure 2. Then the condition for which the poles of figure 1 and figure 2 will coincide can be given as

- (a)  $C_X = A_0 C_1$  and  $R_X = R_1/A_0$       (b)  $C_X = (1 + A_0)C_1$  and  $R_X = R_1(1 + A_0)$   
 (c)  $C_X = (1 + A_0)$  and  $R_X = R_1$       (d)  $C_X = C_1/(1 + A_0)$  and  $R_X = R_1$

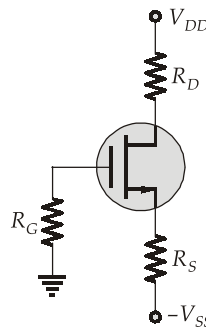
**Q.72** A MOS transistor is biased at a drain current of  $I_D$ , with  $K = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} = 100 \mu\text{A/V}$  and  $V_T = 1 \text{ V}$  as shown in the figure below.



The value of  $k$  varies  $\pm 10\%$  of the actual value, then the value of  $R_S$  that would result in  $I_D = 100 \mu\text{A}$  with a variability of  $\pm 1\%$  is equal to

- (a) 35 k $\Omega$       (b) 45 k $\Omega$   
 (c) 55 k $\Omega$       (d) 65 k $\Omega$

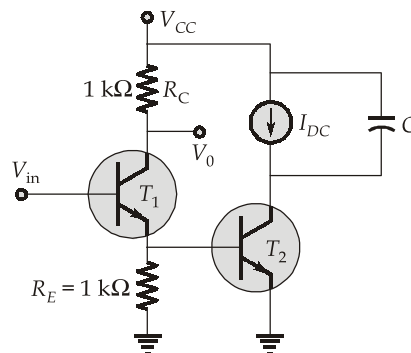**Q.73** Consider the circuit shown in the figure below.




The transistors  $T_1$  and  $T_2$  are identical with  $\beta = 100$ . They are biased in such a way that  $g_{m1} = 5 \text{ mA/V}$  and  $g_{m2} = 100 \text{ mA/V}$ . The magnitude of small signal voltage gain of the amplifier

$A_v = \left| \frac{V_0}{V_{in}} \right|$  is equal to \_\_\_\_\_ V/V.



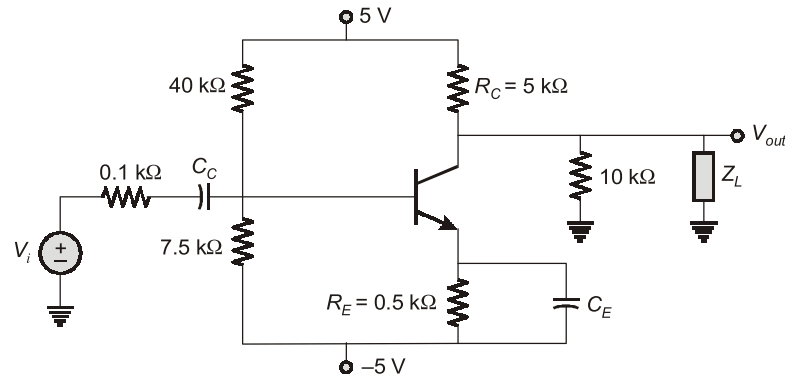
Q.74 Consider the common emitter circuit as shown in the figure below:



A load is connected to the transistor with  $Z_L = \frac{-j \times 10^{12}}{30\pi f} \Omega$ . Due to this load a cut-off frequency of the circuit is  $f_{H'}$  where  $f_{H'} = \frac{1}{2\pi\tau_L}$ . Then the value of  $\tau_L$  is \_\_\_\_\_ nsec.

### Multiple Select Questions (MSQ)

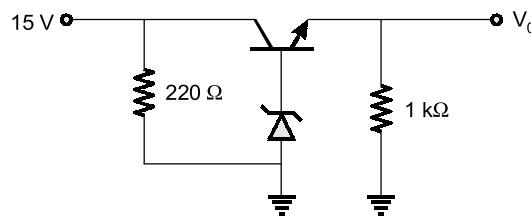Q.75 In the regulator circuit shown below,  $V_z = 12 \text{ V}$ ,  $\beta = 50$ ,  $V_{BE} = 0.7 \text{ V}$ .



Then which of the following is/are correct?


- (a) Current through zener diode is 13.41 mA.
- (b) Output voltage ( $V_0$ ) is 11.3 V.
- (c) Current through zener diode is 15.63 mA.
- (d) Output voltage ( $V_0$ ) is 10.7 V.

■■■■

### Detailed Explanations

51. (b)

The given Bode plot is

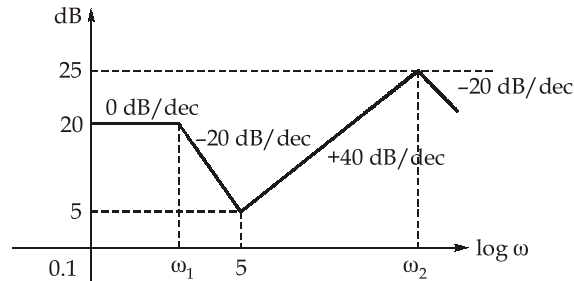

Here, at frequency  $\omega_1$  the slope of the line changes from 0 dB/dec to -20 dB/dec hence,

$$G_1(s) = \frac{1}{\left(1 + \frac{s}{\omega_1}\right)}$$

where,  $\omega_1$  can be calculated as,

$$-20 = \frac{20 - 5}{\log \omega_1 - \log 5}$$

$$-20 = \frac{-15}{\log\left(\frac{5}{\omega_1}\right)}$$

$$\log\left(\frac{5}{\omega_1}\right) = \frac{15}{20}$$

$$\omega_1 = \frac{5}{5.623} = 0.89 \text{ rad/sec}$$

At the corner frequency of 5 rad/sec the slope of the line again changes to +40 dB/dec hence,

$$G_2(s) = \left(1 + \frac{s}{5}\right)^3$$

Now, at corner frequency of  $\omega_2$  the slope of the line changes to -20 dB/dec.

$$\therefore G_3(s) = \frac{1}{\left(1 + \frac{s}{\omega_2}\right)^3}$$

where,  $\omega_2$  can be calculated as

$$40 \text{ dB/dec} = \frac{25 - 5}{\log \omega_2 - \log 5}$$

$$40 = \frac{20}{\log\left(\frac{\omega_2}{5}\right)}$$

$$\log\left(\frac{\omega_2}{5}\right) = \frac{1}{2}$$

$$\begin{aligned}\omega_2 &= 5 \times 3.16 \\ &= 15.81 \text{ rad/sec}\end{aligned}$$

∴ Overall transfer function becomes,

$$\begin{aligned}T(s) &= K \times G_1(s) \times G_2(s) \times G_3(s) \\ &= \frac{K\left(1 + \frac{s}{5}\right)^3}{\left(1 + \frac{s}{0.89}\right)\left(1 + \frac{s}{15.81}\right)^3}\end{aligned}$$

$$\therefore 20 \log K = 20$$

$$\therefore K = 10$$

and therefore, 
$$T(s) = \frac{10 \times 0.89 \times 15.81^3 (s+5)^3}{5^3 (s+0.89)(s+15.81)^3} = \frac{281.37(s+5)^3}{(s+0.89)(s+15.81)^3}$$

52. (12.5) (12 to 13)

Resonance peak,

$$M_r = \frac{1}{2\xi\sqrt{1-\xi^2}}$$

Here, 
$$G(s) = \frac{K}{s(1+0.1s)}$$

$$\therefore T(s) = \frac{K}{s+0.1s^2+K} = \frac{10K}{s^2+10s+10K}$$

On comparing with second order transfer function, we have,

$$2\xi\omega_n = 10$$

$$\omega_n = \sqrt{10K}$$

Now, 
$$M_r = \frac{1}{2\xi\sqrt{1-\xi^2}} = 1.25$$

$$\therefore 4\xi^2(1-\xi^2) = \left(\frac{1}{1.25}\right)^2 = 0.64$$

$$\xi^4 - \xi^2 + 0.16 = 0$$

$$\xi^2 = 0.8 \text{ and } 0.2$$

$$\therefore \xi = 0.89 \text{ and } 0.447$$

For 
$$\xi = 0.447$$

$$\omega_n = \frac{10}{2\xi} = \frac{10}{2 \times 0.447} = 11.18$$

and 
$$K = \frac{\omega_n^2}{10} = 12.5$$

53. (a)

$$\begin{aligned} G(s) &= \frac{K}{s(1+s)(1+0.1s)} \\ &= \frac{K}{s(1+s+0.1s+0.1s^2)} \\ &= \frac{K}{(0.1s^3 + 1.1s^2 + s)} \end{aligned}$$

converting  $s = j\omega$  we get,

$$G(j\omega) = \frac{K}{-1.1\omega^2 + j\omega(1-0.1\omega^2)}$$

at the phase crossover frequency  $\omega_{PC}$  the imaginary part is zero, hence, by putting  $\omega = \omega_{PC}$  in the imaginary part and equating it to zero, we get,

$$\omega_{PC} (1 - 0.1\omega_{PC}^2) = 0$$

$$1 - 0.1\omega_{PC}^2 = 0$$

$$\omega_{PC} = \sqrt{10} = 3.162 \text{ rad/sec}$$

$$\therefore GM = 20 \text{ dB}$$

$$\therefore 20 \log GM = 20 \text{ dB}$$

$$GM = 10$$

Hence,  $\frac{1}{|G(j\omega)|_{\omega=\omega_{PC}}} = 10$

$$\frac{1}{0.0909K} = 10$$

or  $K = \frac{1}{0.0909 \times 10} = 1.101$

54. (4)

$$\frac{K}{s^2} + 1 = 0$$

$$\Rightarrow \frac{K}{(j2)^2} + 1 = 0$$

$$\Rightarrow -\frac{K}{4} + 1 = 0$$

$$\Rightarrow K = 4$$

55. (a)

The steady state error can be calculated as

$$e_{ss} = \lim_{s \rightarrow 0} \frac{sR(s)}{1 + G(s)H(s)}$$

For unit step input,  $R(s) = \frac{1}{s}$

$$e_{ss} = \lim_{s \rightarrow 0} \frac{1}{1 + G(s)} = 0.5 \quad (\text{given})$$

or

$$\frac{1}{1 + G(0)} = 0.5$$

$$1 + G(0) = 2$$

$$G(0) = 1 \quad \dots(i)$$

For the given input,

$$r(t) = 50 [u(t) - u(t - 5)]$$

$$R(s) = 50 \left[ \frac{1}{s} - \frac{1}{s} e^{-5s} \right]$$

$$R(s) = 50 \left( \frac{1 - e^{-5s}}{s} \right)$$

$\therefore$  Steady state error

$$e_{ss}' = \lim_{s \rightarrow 0} \frac{s \times 50(1 - e^{-5s})}{s(1 + G(s))}$$

$$= \frac{50(1 - e^0)}{1 + G(0)} = 25(1 - 1) = 0$$

56. (100)

$$(K_V)_{\text{uncompensated}} = \lim_{s \rightarrow 0} sG(s)H(s)$$

$$= \lim_{s \rightarrow 0} \frac{100}{(s+1)} = 100$$

$$(K_V)_{\text{compensated}} = \lim_{s \rightarrow 0} s \times G(s)H(s) \times G_c(s)$$

$$= \lim_{s \rightarrow 0} s \times \frac{100}{s(s+1)} \times \frac{(s+10)}{(s+a)}$$


$$10 = \frac{100 \times 10}{a} \quad \text{or} \quad a = 100$$

57. (c)

Let us assume that the transfer function of the compensator is

$$G_c(s) = \frac{K(s+a)}{(s+b)}$$

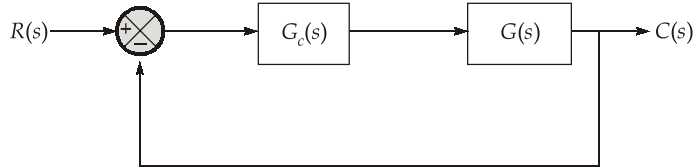∴ The block diagram of the system can be drawn as



$$\begin{aligned} \frac{C(s)}{R(s)} &= \frac{G_c(s)G(s)}{1 + G_c(s)G(s)} \\ &= \frac{\frac{K(s+a)}{(s+b)} \times \frac{10}{s(s+2)}}{1 + \frac{K(s+a)}{(s+b)} \times \frac{10}{s(s+2)}} \\ &= \frac{10K(s+a)}{s(s+2)(s+b) + 10K(s+a)} \\ &= \frac{10K(s+a)}{s^3 + 2s^2 + s^2b + 2bs + 10Ks + 10Ka} \end{aligned}$$

Characteristic equation is

$$s^3 + (2+b)s^2 + (2b+10K)s + 10Ka = 0 \quad \dots(i)$$

according to the question the new characteristic equation is

$$\begin{aligned} (s+1)(s+3)(s+5) &= 0 \\ (s^2 + s + 3s + 3)(s+5) &= 0 \\ s^3 + s^2 + 3s^2 + 3s + 5s^2 + 20s + 15 &= 0 \\ s^3 + 9s^2 + 23s + 15 &= 0 \end{aligned} \quad \dots(ii)$$

From equation (i) and (ii)

$$\begin{aligned} 2+b &= 9 \\ \Rightarrow b &= 7 \\ 2b+10K &= 23 \\ 10K &= 23-14 \\ 10K &= 9 \\ \Rightarrow K &= 0.9 \\ \text{and } 10Ka &= 15 \\ \Rightarrow a &= \frac{15}{10} \times \frac{10}{9} = 1.67 \end{aligned}$$

$$\therefore G_c(s) = \frac{0.9(s+1.67)}{(s+7)}$$

58. (9.89) (9.50 to 10.00)

The characteristic equation of the closed loop system is

$$1 + G(s)H(s) = 0$$

$$1 + \frac{K(s+2)}{s(s-1)} = 0$$

$$s^2 + (K-1)s + 2K = 0 \quad \dots(i)$$

Using Routh's tabular form, we have,

$s^2$	1	2K
$s^1$	K-1	0
$s^0$	2K	

For system to be stable,

$$K - 1 > 0$$

or  $K > 1$

∴ On comparing equation (i) with standard characteristic equation, we have

$$\omega_n = \sqrt{2K}$$

and  $2\xi\omega_n = (K-1)$

For  $\xi = 1$ ,

$$2 \times \omega_n = (K-1)$$

or  $2 \times \sqrt{2K} = (K-1)$

or  $4(2K) = K^2 - 2K + 1$

$$K^2 - 10K + 1 = 0$$

∴  $K = 0.10$  and  $9.89$

∴  $K > 1$  for stable operation.

∴  $K = 9.89$  is the valid answer.

59. (c)

$$\text{Gain} = \frac{R_L}{R_1} = \frac{-R_2(1 \pm x\%)}{R_1(1 \pm x\%)}$$

$$\begin{aligned} \therefore G_{\max} &= \frac{-R_2(1+x\%)}{R_1(1-x\%)} = \frac{-R_L \left(1 + \frac{5}{100}\right)}{R_1 \left(1 - \frac{5}{100}\right)} \\ &= \frac{-100(1+0.05)}{10(1-0.05)} = -10 \times \frac{1.05}{0.95} \approx -11 \text{ V/V} \end{aligned}$$

$$G_{\min} = \frac{-R_L \left(1 - \frac{5}{100}\right)}{R_1 \left(1 + \frac{5}{100}\right)} = -10 \times \frac{0.95}{1.05} \approx -9 \text{ V/V}$$

60. (c)

The diodes  $D_1, D_3$  and  $D_z$  will limit the voltage for positive cycle and diodes  $D_2, D_4$  and  $D_z$  will limit the output voltage in the (negative) cycle.

**Note :** The Zener diode will always be in reverse biased for both the cases.

$$\therefore V_{in} = V_{out}$$

$$\text{for } -(0.65 \times 2 + 8.2) < V_{in} < (0.65 \times 2 + 8.2)$$


$$-9.5 < V_{in} < 9.5$$

$$\text{and } V_{out} = kV_{in} + b \text{ for } |V_{in}| > 9.5$$

Hence, only figure (c) is according to the given conditions.

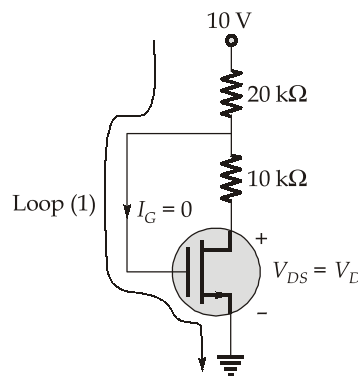61. 3.10 (2.80 to 2.40)

Applying KVL in drain to source loop, we get,



$$10 - (30 \text{ k})I_D - V_{DS} = 0$$

$$\therefore V_{DS} = 10 - 30I_D \quad (\text{Assuming } I_D \text{ to be in mA})$$

$$\text{now, } I_D = \frac{\mu_n C_{ox} W}{2L} (V_{GS} - V_T)^2$$

Applying KVL in loop (1), we get,

$$V_{GS} = 10 - 20I_D$$

$$I_D = 12.5 \times 10^{-3} [10 - 20I_D - 1]^2$$

On solving, we get,  $I_D = 1 \text{ mA}$  and  $0.2 \text{ mA}$

Now,  $V_{GS} = 10 - 20I_D = 10 - 20 \times 1 = -10$  which is not possible

Hence  $I_D = 0.2 \text{ mA}$

$$\therefore V_{DS} = 10 - 30 \times 0.2$$

$$= 10 - 6 = 4 \text{ V}$$

$$\text{and } V_{GS} = 10 - 20 \times 0.2 = 6 \text{ V}$$

$$\therefore V_{DS} < V_{GS} - V_T$$

Hence, MOS is working in linear region.

$$\text{Thus, } I_D = \frac{\mu_n C_{ox} W}{2L} [2(V_{GS} - V_T)V_{DS} - V_{DS}^2]$$

$$I_D = 12.5 \times 10^{-3} [2 \times (10 - 20I_D - 1)(10 - 30I_D) - (10 - 30I_D)^2]$$




Thus the equation reduces to

$$300I_D^2 - 420I_D + 80 = 0$$

$$\begin{aligned} \therefore I_D &= 1.17 \text{ mA}, 0.23 \text{ mA} \\ \therefore I_D &= 0.23 \text{ mA} \\ \therefore V_{DS} &= 10 - 30 \times 0.23 = 3.1 \text{ V} \end{aligned}$$

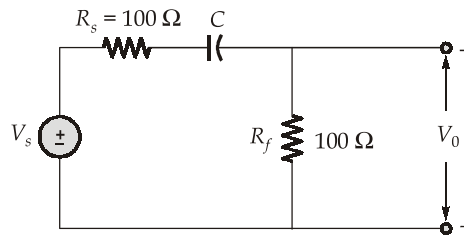**62. 1.84 (1.60 to 2.00)**

The capacitor is initially uncharged hence for the first positive cycle the circuit can be redrawn as



$$\therefore V_0 = 10 \times \frac{100}{100 + 100} = 5 \text{ V}$$

thus for  $t = 0$ ,  $V_0 = 5 \text{ V}$

Now, the capacitor will start charging with time constant  $\tau$

$$\therefore \tau = (100 + 100) \times 1 \times 10^{-6} = 200 \text{ } \mu\text{F}$$

$$\therefore V_0 \left[ t = \frac{T}{2} \right] = 5 \cdot e^{-\frac{T}{2\tau}} = 5e^{-1/2} = 3.03 \text{ V}$$

Thus for (positive) cycle, the value of  $V_0 = V_s - V_c$


Where  $V_s = \text{Input voltage} = 0 \text{ V}$

$V_c = \text{Voltage across capacitor} = -3.94 \text{ V}$

Now, for the second cycle, the amplitude will again be equal to 3.03 V.

$$\therefore V_0 \left[ t = \frac{3T}{2} \right] = 3.03 e^{-1/2} = 1.837 \approx 1.84 \text{ V}$$

$$V' = 1.84 \text{ V}$$

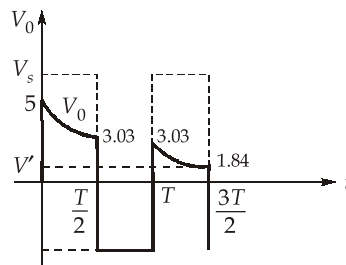

63. (b)

$$A_v = \frac{V_0}{V_i}$$

now,


$$V_i = V_s - V_f = 100 - 95 = 5 \text{ mV}$$

$$A_v = \frac{10}{5} \times 10^3 = 2 \times 10^3 \text{ V/V}$$

and

$$\beta = \frac{V_f}{V_0} = \frac{95 \times 10^{-3}}{10} = 9.5 \times 10^{-3} \text{ V/V}$$

64. (d)

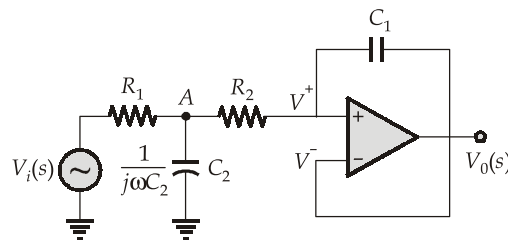

In ideal op-amp  $V^+ = V^-$

So,  $V^+ = V^- = V_0$  (Due to virtual grounding)

(Since the voltage drop across capacitor is zero, thus there will be no current flowing through capacitor  $C_1$  and thus no current will flow through  $R_2$ )

$\therefore V_A = V_0(s)$

Applying KCL at node A,


$$\frac{V_0(s) - V_i(s)}{R_1} + \frac{V_0(s) - 0}{1/j\omega C_2} = 0$$

$$\text{So, } V_0(s) \left[ \frac{1 + j\omega C_2 R_1}{R_1} \right] = \frac{V_i(s)}{R_1}$$

$$\frac{V_0(s)}{V_i(s)} = \frac{1}{1 + j\omega R_1 C_2}$$

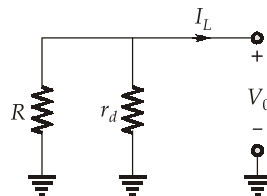65. 4.987 (4.50 to 5.50)

Drawing the small signal equivalent of the circuit, we get,



$$\therefore \Delta V_0 = -I_L (R \parallel r_d)$$

$$\frac{\Delta V_0}{I_L} = -R \parallel r_d$$

$$\frac{\Delta V_0}{I_L} = -\frac{1}{\frac{1}{R} + \frac{1}{r_d}}$$

now, 
$$r_d = \frac{\eta V_T}{I_D} = \frac{V_T}{I_D} \quad [:\eta = 1]$$

and 
$$R = \frac{V^+ - 0.7}{I_D}$$

thus, 
$$\frac{\Delta V_0}{I_L} = \frac{-1}{\frac{I_D}{V^+ - 0.7} + \frac{I_D}{V_T}}$$


$$\frac{\Delta V_0}{I_L} = -\frac{V_T}{I_D} \cdot \frac{V^+ - 0.7}{V^+ - 0.7 + V_T}$$

$$\therefore -\frac{V_T}{I_D} \cdot \frac{V^+ - 0.7}{V^+ - 0.7 + V_T} = \frac{5 \times 10^{-3}}{10^{-3}}$$

$$-\frac{0.025}{I_D} \cdot \frac{10 - 0.7}{10 - 0.7 + 0.025} = 5$$

$$|I_D| = \frac{0.025}{5} \times \frac{10 - 0.7}{10 - 0.7 + 0.025} = 4.987 \text{ mA}$$

66. 0.108 (0.08 to 0.12)

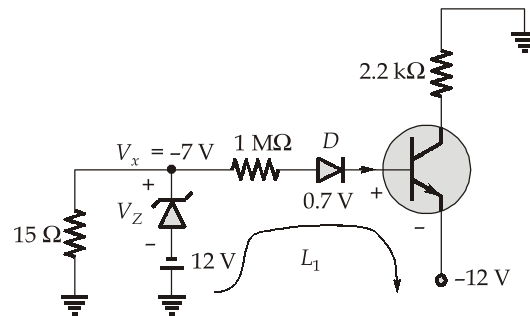

Applying KCL in loop ' $L_1$ ' we get,


$$12 - 5 + 1 \times I_B + 0.7 + 0.7 - 12 = 0$$

$$I_B = 3.6 \mu\text{A}$$

$$I_C = 30 \times 3.6 \mu\text{A}$$

$$= 108 \mu\text{A} = 0.108 \text{ mA}$$

67. (c)

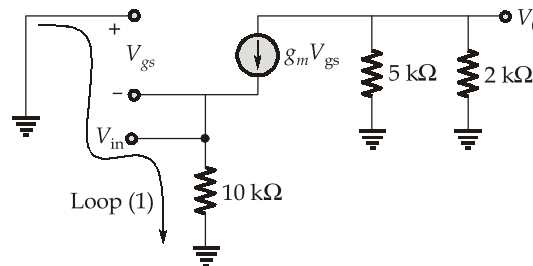

Applying KVL in loop (1), we get,

$$V_{in} + V_{gs} = 0$$

$$\begin{aligned} \text{now,} \quad V_{in} &= -V_{gs} \\ i_{in} &= g_m V_{gs} \\ \therefore R_{in} &= \frac{V_{in}}{i_{in}} = \frac{V_{gs}}{g_m V_{gs}} = \frac{1}{g_m} = \frac{1}{5 \times 10^{-3}} = 200 \Omega \end{aligned}$$

68. (a)

$$\begin{aligned} \text{Let,} \quad R'_1 &= R_1 \parallel R_C \\ \therefore G' &= \frac{-R_2/R_1}{1 + \frac{1}{A} \left( 1 + \frac{R_2}{R_1} \right)} \quad [ \because 'A' \text{ is finite} ] \end{aligned}$$

$$\begin{aligned} \text{Expected Gain} \quad G &= \frac{-R_2}{R_1} \\ \therefore \text{We are asked condition for } G' &= G. \end{aligned}$$

$$\therefore \frac{-R_2/R'_1}{1 + \frac{1}{A} \left( 1 + \frac{R_2}{R'_1} \right)} = \frac{-R_2}{R_1}$$

$$\frac{1}{R_1} + \frac{1}{R_1 A} \left[ 1 + \frac{R_2}{R'_1} \right] = \frac{1}{R'_1}$$

$$\text{now,} \quad R'_1 = \frac{R_1 R_C}{R_1 + R_C}$$


$$\therefore \frac{R_1 + R_C}{R_1 R_C} = \frac{1}{R_1} \cdot \left[ 1 + \frac{R_2 \left( \frac{R_1 + R_C}{R_1 R_C} \right)}{A} \right]$$

$$(R_1 + R_C)A = AR_C + R_C + \frac{R_2}{R_1} (R_1 + R_C)$$

$$R_1 A = R_C + GR_1 + GR_C \quad \left[ \because \frac{R_2}{R_1} = G \right]$$

$$\therefore R_C = \frac{A - G}{1 + G} R_1$$

69. 11.28 (11.00 to 11.50)

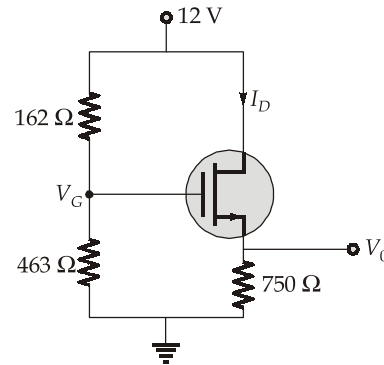

$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T)^2$$

$$\frac{8.88 - V_{GS}}{750 \Omega} = 4 \times 10^{-3} (V_{GS} - 1.5)^2$$

$$3V_{GS}^2 - 8V_{GS} - 2.13 = 0$$

$$\therefore V_{GS} = 2.91 \text{ V}, -0.243 \text{ V}$$

$$V_{GS} = 2.91 \text{ V}$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_T) = 2 \times 4 \times 10^{-3} (2.91 - 1.5)$$


$$g_m = 11.28 \text{ mA/V}$$

70. 0.6 (0.40 to 0.80)

$$V_{\text{out}} = V^+$$

Since op-amp is used as a voltage buffer  $V_0 = V^+$


Thus,  $V^+(0)$  can be given as

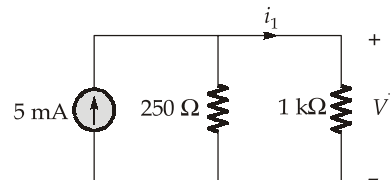

$$i_1 = \frac{250}{250 + 1000} \times 5 \times 10^{-3} \text{ A} = \frac{250}{1250} \times 5 \times 10^{-3}$$

$$i_1 = 1 \text{ mA}, \quad \therefore V^+(0^+) = 1 \times 10^3 \times 1 \times 10^{-3} = 1 \text{ V}$$

At  $t = \infty$ , we have

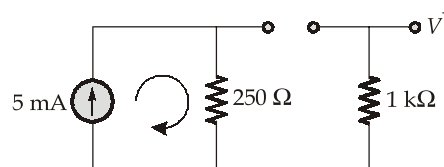

Thus,  $V^+(\infty) = 0 \text{ V}$

Time constant,  $\tau = R_{\text{eq}} C$

$$R_{\text{eq}} = 250 + 1000 = 1250 \Omega$$

$$\begin{aligned} \therefore \tau &= 1250 \times 8 \times 10^{-3} \text{ sec} \\ &= 10 \text{ sec} \end{aligned}$$

$$\therefore V^+(t) = V^+(\infty) + (V^+(0^+) - V^+(\infty))e^{-t/\tau} = V^+(0) \cdot e^{-t/\tau} = e^{-t/10} \text{ Volts}$$

for  $t = 5 \text{ sec}$

$$V^+(5) = \exp\left[-\frac{5}{10}\right] \text{ Volts} = \exp\left[-\frac{1}{2}\right] = \exp(-0.5)$$

$$V_0 = V^+(5 \text{ sec}) = 0.6 \text{ Volts}$$

71. (d)

For figure 2, we have

$$\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{R_X}{R_X + \frac{1}{sC_X}} = \frac{(R_X C_X)s}{s(R_X C_X) + 1}$$

From figure 1 applying KCL at input node A, we get,

$$\frac{V_{\text{in}} - V_A}{1/sC_1} = \frac{V_X - V_{\text{out}}}{R_1}$$

now,

$$V_A = \frac{-V_{\text{out}}}{A_0}$$

$$\therefore \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{-(R_1 C_1)s}{1 + \frac{1}{A_0} + \frac{R_1 C_1 s}{A_0}}$$

$\therefore$  Equating the poles of the two system, we get,

$$\frac{1}{R_X C_X} = \frac{A_0 + 1}{R_1 C_1}$$

$$C_X = C_1$$

$$\therefore R_X = \frac{R_1}{1 + A_0}$$

or

$$R_X = R_1$$

$$C_X = \frac{C_1}{1 + A_0}$$

72. (b)

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{GS} - V_T)^2$$

$$= K(V_{GS} - V_T)^2$$

now,  $V_G = 0$  and  $V_s = +I_D R_S - V_{SS}$

$$\therefore I_D = K(V_{SS} - I_D R_S - V_T)^2$$

$$\frac{\partial I_D}{\partial K} = (V_{SS} - I_D R_S - V_T)^2 + 2K(V_{SS} - I_D R_S - V_T)(-R_S) \cdot \frac{\partial I_D}{\partial K}$$

$$\frac{\partial I_D}{\partial K} = \frac{I_D}{K} - 2R_S \sqrt{\frac{I_D}{K}} \cdot K \frac{\partial I_D}{\partial K}$$

$$\therefore \frac{\partial I_D / I_D}{\partial K / K} = \frac{1}{1 + 2R_S \sqrt{I_D K}}$$

now, given  $K = 100 \mu\text{A/V}$ ,  $\frac{\Delta K}{K} = 10\%$ ,  $V_T = 1 \text{ V}$ ,  $I_D = 100 \mu\text{A}$  and  $\frac{\Delta I_D}{I_D} = 1\%$


$$\frac{1}{10} = \frac{1}{1 + \left(2\sqrt{100 \times 10^{-3} \times 100 \times 10^{-3} \times 10^{-6}}\right) R_S}$$

$$1 + \left(2\sqrt{10 \times 10^{-3} \times 10^{-6}}\right) R_S = 10$$

$$R_S = 45 \text{ k}\Omega$$

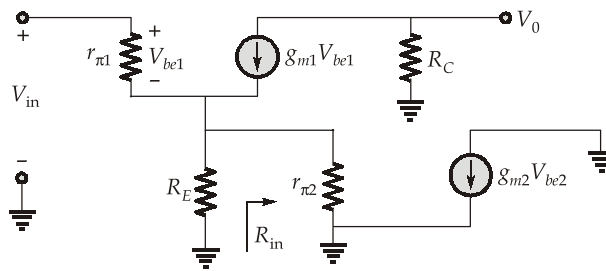73. (1.428) (1.30 to 1.60)

Drawing small signal equivalent circuit of the circuit, we get,




$$R_{in} = r_{\pi 2} = \frac{\beta}{g_{m2}} = \frac{100}{100 \times 10^{-3}} = 1 \text{ k}\Omega$$

Thus,

$$\begin{aligned} R'_E &= R_E \parallel r_{\pi 2} \\ &= 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega \\ &= 0.5 \text{ k}\Omega = 500 \Omega \end{aligned}$$

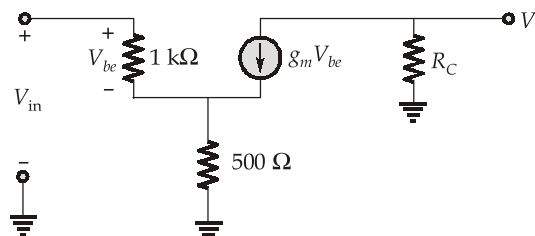now, the equivalent circuit can be drawn as




$$\text{Thus, } \left| \frac{V_0}{V_{in}} \right| = \frac{g_{m1} R_C}{1 + g_{m1} R'_E} = \frac{5 \times 10^{-3} \times 1 \times 10^3}{1 + 500 \times 5 \times 10^{-3}} = 1.428 \text{ V/V}$$

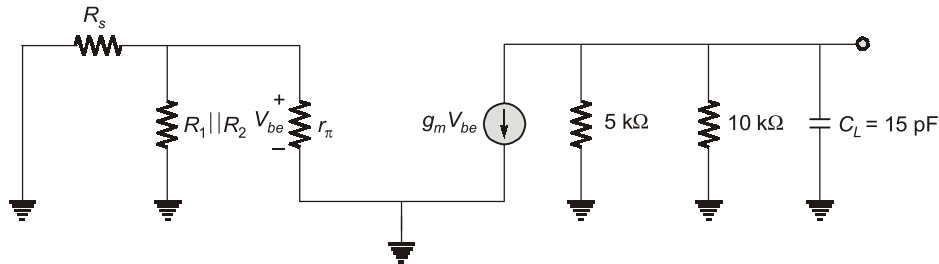74. (50)

$$\therefore Z = \frac{-j \times 10^{12}}{30\pi f} = \frac{1}{2\pi f (15 \times 10^{-12})} \Omega$$

$\therefore$  The value of the load is 15 pF and it is purely capacitive  
now drawing the small signal model for the circuit and shorting all the capacitors and sources, we get



Now, current source can be open circuited. Thus

$$\begin{aligned} \tau_L &= (5 \text{ k}\Omega \parallel 10 \text{ k}\Omega) \cdot 15 \times 10^{-12} \\ &= \frac{50}{15} \times 15 \times 10^{-9} = 50 \text{ nsec} \end{aligned}$$

75. (a, b)

$$V_0 = V_z - V_{BE} = 12 - 0.7 = 11.3 \text{ V}$$

$$V_{CE} = V_i - V_0 = 15 - 11.3 = 3.7 \text{ V}$$

$$I_{220 \Omega} = \frac{15 - 12}{220} = 13.63 \text{ mA}$$

$$I_{1 \text{ k}\Omega} = \frac{V_0}{1} \text{ mA} = \frac{11.3}{1} \text{ mA}$$

$$= 11.3 \text{ mA}$$

$$I_C = I_{1 \text{ k}\Omega}$$

$$I_B = \frac{I_C}{\beta} = \frac{11.3}{50} \text{ mA}$$

$$= 0.226 \text{ mA}$$

$$\therefore I_z = I_{220 \Omega} - I_B = 13.636 - 0.226 = 13.41 \text{ mA}$$

