

# POSTAL Book Package

# 2021

## Instrumentation Engineering

### Objective Practice Sets

#### Electrical Circuits

*Contents*

Sl.	Topic	Page No.
1.	Circuit Element and Energy Sources .....	2 - 9
2.	Network Laws, Mesh and Nodal Analysis .....	10 - 26
3.	Network Theorems .....	27 - 41
4.	Circuit Transient and Laplace Transform Analysis .....	42 - 63
5.	Graph Theory .....	64 - 69
6.	Resonance .....	70 - 78
7.	Two Port Network .....	79 - 98
8.	Network Function and Network Synthesis .....	99 - 109
9.	Miscellaneous .....	110 - 123



**MADE EASY**  
Publications

**Note:** This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.


# 1

## CHAPTER

# Circuit Element and Energy Sources

- Q.1** The equivalent star impedance of a balanced delta connected load of value  $6 + j9 \Omega$  is given by  
 (a)  $9 + j6 \Omega$       (b)  $2 + j3 \Omega$   
 (c)  $18 + j27 \Omega$       (d)  $6 - j9 \Omega$

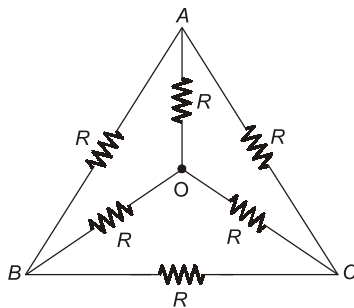
- Q.2** The effective resistance between the terminals A and B in the circuit shown in the figure is



- (a)  $R$       (b)  $R - 1$   
 (c)  $\frac{R}{2}$       (d)  $\frac{6}{11}R$


- Q.3** A network contains only independent current sources and resistors. If the values of all resistors are doubled, the values of the node voltages  
 (a) will become half  
 (b) will remain unchanged  
 (c) will become double  
 (d) cannot be determined unless the circuit configuration and the values of the resistors are known

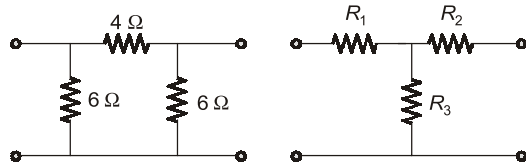- Q.4** The value of  $R_1$ ,  $R_2$  and  $R_3$  of the equivalent net 'T' network for the given  $\pi$  network will be such that




- |                   |               |               |
|-------------------|---------------|---------------|
| $R_1$             | $R_2$         | $R_3$         |
| (a) $2.25 \Omega$ | $1.5 \Omega$  | $1.5 \Omega$  |
| (b) $1.5 \Omega$  | $1.5$         | $2.25 \Omega$ |
| (c) $2.25 \Omega$ | $1.5 \Omega$  | $2.25 \Omega$ |
| (d) $1.5 \Omega$  | $2.25 \Omega$ | $1.5 \Omega$  |

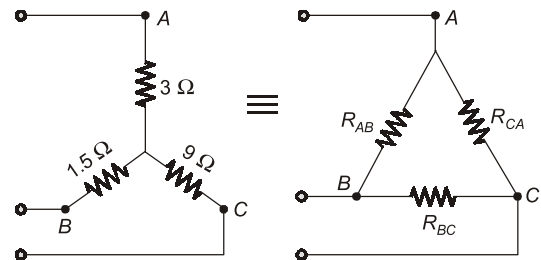- Q.5** For the equivalent @ figure circuit shown in the given figure, the values of  $R_{AB}$  and  $R_{BC}$  are respectively




- (a)  $5 \Omega$  and  $15 \Omega$       (b)  $15 \Omega$  and  $30 \Omega$   
 (c)  $30 \Omega$  and  $5 \Omega$       (d)  $20 \Omega$  and  $35 \Omega$

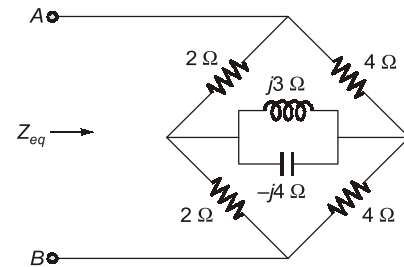- Q.6** In the circuit of figure. The equivalent impedance seen across terminals A, B is \_\_\_\_\_  $\Omega$ .



- Q.7** If each branch of a delta circuit has impedance  $Z/\sqrt{3}$  then, each branch of the equivalent Y circuit has impedance.  
 (a)  $\frac{Z}{\sqrt{3}}$       (b)  $\frac{Z}{3\sqrt{3}}$   
 (c)  $3\sqrt{3}Z$       (d)  $Z/3$

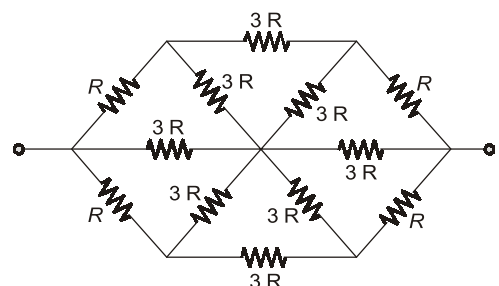- Q.8** The equivalent resistance between terminals A and B for the circuit shown is:



**Q.25 Assertion (A):** Inductors carrying steady direct currents act as effective short circuits with zero voltage across it.

**Reason (R):** The voltage induced across an inductance is proportional to the rate of change of current  $di/dt$ .

- (a) Both A and R are true, and R is the correct explanation of A.
- (b) Both A and R are true, but R is not a correct explanation of A.
- (c) A is true, but R is false.
- (d) A is false, but R is true.




**Answers      Circuit Element and Energy Sources**


1. (b)    2. (c)    3. (c)    4. (b)    5. (a)    6. (2.67)    7. (b)    8. (c)    9. (b)  
 10. (b)    11. (c)    12. (d)    13. (a)    14. (c)    15. (b)    16. (c)    17. (a)    18. (d)  
 19. (a)    20. (b)    21. (d)    22. (d)    23. (c)    24. (a)    25. (a)

**Explanations      Circuit Element and Energy Sources**

**1. (b)**

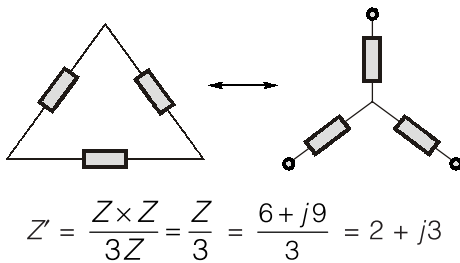

**2. (c)**

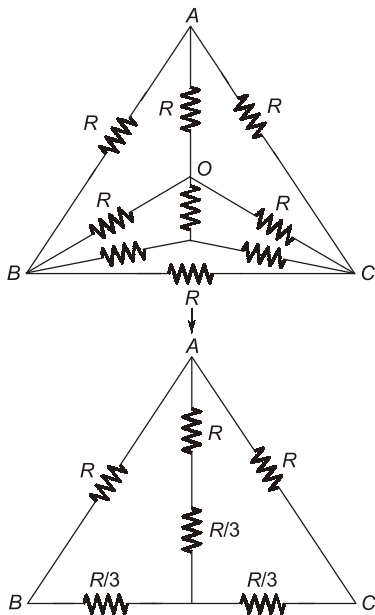

$$R_{AB} = R \left\| \left( \frac{R}{3} + \left( \frac{4R}{3} \parallel \frac{4R}{3} \right) \right) \right\| = \frac{R}{2}$$

**3. (c)**

Since the network contains only independent current sources, so changing resistors in the same proportion the current through each branch will remain same but node voltages will change in the same proportion. Hence, doubling all resistors, node voltages will be doubled.


**4. (b)**

$$R_1 = \frac{4 \times 6}{4 + 6 + 6} = \frac{24}{16} = 1.5 \Omega$$

$$R_2 = \frac{6 \times 4}{16} = 1.5 \Omega$$

$$R_3 = \frac{6 \times 6}{16} = 2.25 \Omega$$

**5. (a)**

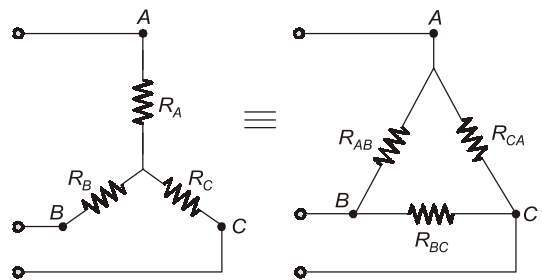

$$R_{AB} = R_A + R_B + \frac{R_A R_B}{R_C}$$

$$R_{AB} = 3 + 1.5 + \frac{3 \times 1.5}{9}$$

$$= 3 + 1.5 + 0.5 = 5 \Omega$$

$$R_{BC} = 9 + 1.5 + \frac{9 \times 1.5}{3}$$


$$= 9 + 1.5 + 4.5 = 15 \Omega$$

$$R_{CA} = R_A + R_C + \frac{R_A R_C}{R_B}$$

$$= 3 + 9 + \frac{3 \times 9}{1.5} = 30 \Omega$$

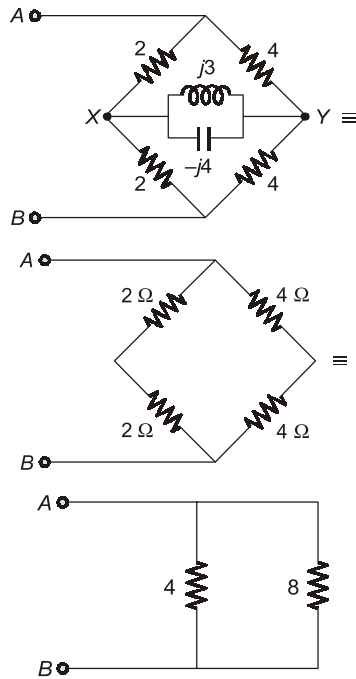
**6. Sol.**

The above circuit is a wheatstone bridge circuit, thus no current will flow through branch XY.



$$Z_{eq} = 8 || 4 = \frac{8 \times 4}{12} = \frac{8}{3} = 2.67 \Omega$$

**7. (b)**

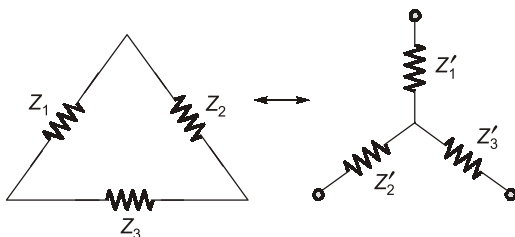

$$Z'_1 = \frac{Z_1 Z_2}{Z_1 + Z_2 + Z_3}$$

$$Z'_2 = \frac{Z_1 Z_3}{Z_1 + Z_2 + Z_3}$$


$$Z'_3 = \frac{Z_2 Z_3}{Z_1 + Z_2 + Z_3}$$

$$Z'_1 = \frac{\frac{Z}{\sqrt{3}} \times \frac{Z}{\sqrt{3}}}{\frac{Z}{\sqrt{3}} + \frac{Z}{\sqrt{3}} + \frac{Z}{\sqrt{3}}}$$

$$= \frac{\frac{Z^2}{(\sqrt{3})^2}}{\frac{3Z}{\sqrt{3}}} = \frac{Z^2 \sqrt{3}}{3Z \times 3}$$

$$\Rightarrow Z'_1 = \frac{Z}{3\sqrt{3}}$$

**8. (c)**

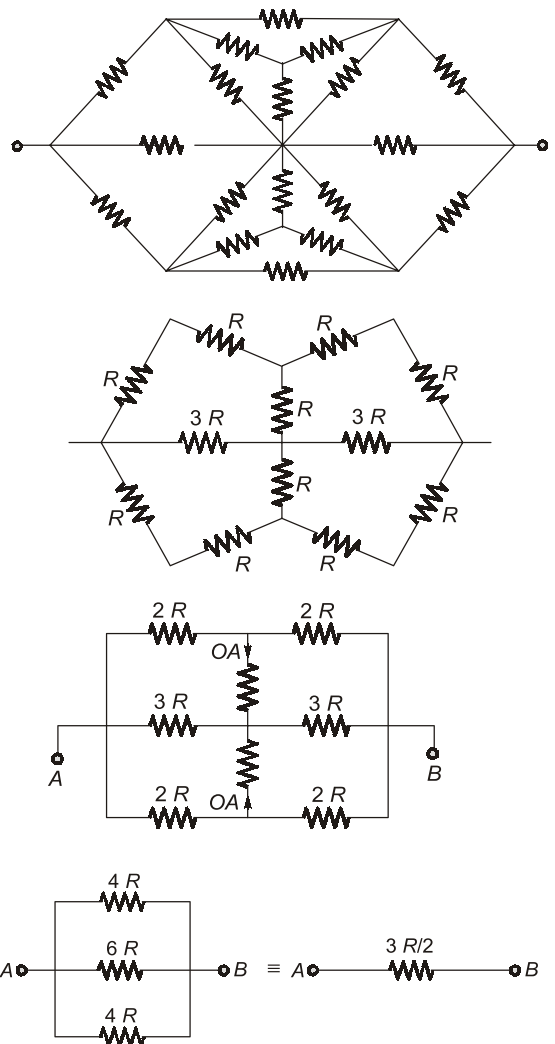

**9. (b)**

$$R_A = \frac{R_b R_c}{R_a + R_b + R_c} = K \cdot \left( \frac{R_c R_b}{R_a + R_b + R_c} \right)$$


$$R_B = \frac{R_a R_c}{R_a + R_b + R_c} = K \cdot \left( \frac{R_a R_c}{R_a + R_b + R_c} \right)$$

with 'a' and 'b' doubled,

$$R' = \frac{\rho (2a + 2b)}{2 (2a - 2b)^2}$$

$$= \frac{\rho (a + b)}{4 (a - b)^2} = \frac{R}{2}$$

**24. (a)**

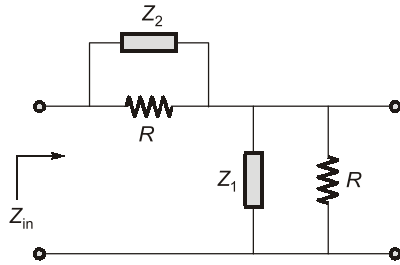

$$Z_{in} = R$$

$$\frac{Z_{in}}{R} = \frac{Z_1}{R + Z_1} + \frac{Z_2}{R + Z_2}$$

$$\frac{R}{R} = 1 = \frac{Z_1}{R + Z_1} + \frac{Z_2}{R + Z_2}$$

$$1 - \frac{Z_1}{R + Z_1} = \frac{Z_2}{R + Z_2}$$

$$\frac{R}{R + Z_1} = \frac{Z_2}{R + Z_2}$$

$$Z_2 = R$$

$$Z_1 = Z_2 = R$$

**25. (a)**

$$V_L \propto \frac{di}{dt}; \quad V_L = L \frac{di}{dt}$$

For d.c.  $\frac{di}{dt} = 0 \Rightarrow v = 0$

Inductor acts as short-circuit.

