

POSTAL Book Package

2021

Electronics Engineering Conventional Practice Sets

Electronic Devices and Circuits

Contents

Sl.	Topic	Page No.
1.	Basic Semiconductor Physics	2 - 15
2.	PN Junction and Circuits	16 - 36
3.	Bipolar Junction Transistor	37 - 57
4.	Field Effect Transistor	58 - 71
5.	Power Switching Devices and Circuits	72 - 77
6.	Introduction to IC Fabrication	78 - 80



MADE EASY
Publications

Note: This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.


Power Switching Devices and Circuits

Practice Questions : Level-I

 Q.1 What are SCRs? Draw the symbol and its V - I characteristics. Explain its operation.

Solution:

- SCR is a thyristor family member.
- SCR is a 4 layer solid state device with 3 terminals (A, K and G) and having 3 junctions.
- Unidirectional device.




- In SCR internal regions are relatively lightly doped when compared to outermost layer.
- The equivalent circuit of SCR can be represented by one PNP transistor and one NPN transistor connected back to back.
- SCR is a latch.
- Bi-stable device i.e. having stable ON and OFF states.
- SCR can handle large amount of power with a very small amount of power consumption.
- If anode is given a negative voltage with respect to Cathode, then SCR will never conduct.

Current operation of SCR:

Also called Gate operation of SCR


If I_G is kept zero and let $V_{AA} < V_{BO}$

- Junctions J_1 and J_3 are FB and J_2 is RB.
- Internal resistance of SCR is very large ($\geq 1 \text{ M}\Omega$).
- The function of Gate is trigger the SCR by sending a proper I_G .
- Once SCR is triggered by sending proper I_G , the SCR will be losing total control on I_A and SCR will continue to remain in ON STATE.
- Once SCR is ON, it will not respond to the Gate.
- SCR can be switched OFF by using any one of the following methods:
 - (i) Disconnect V_{AA} .
 - (ii) Give anode a negative voltage with respect to cathode.
 - (iii) Reduce V_{AA} so that I_A reduces and falls below certain value of current I_H (Holding current) and SCR will go to OFF.

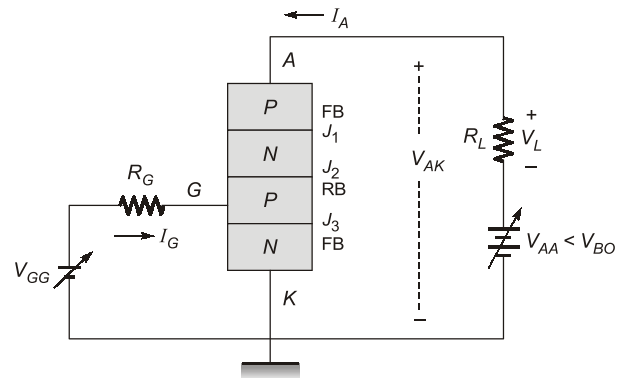

- The firing voltage of SCR $\propto \frac{1}{I_G}$ i.e. by applying larger values of I_G we can trigger the SCR.

 V_I characteristic of SCR is given below:




Q2 Use the device to design a simple circuit to generate a continuous sawtooth wave of amplitude 100 volts, and repetitive frequency of 500 Hz. The following data is available regarding the four layer diode: $V_{BO} = 100 \text{ V}$, $I_A = 20 \text{ A}$, $I_H = 20 \text{ mA}$.

Solution:

The circuit to generate a continuous sawtooth wave using a four layer $p-n-p-n$ diode is shown here.

When the diode is OFF, it is effectively open and capacitor C charges to 200 V through R_1 & R_2 . When $V_D = V_0$ reaches V_{BO} ($= 100 \text{ V}$), the diode turns ON and acts like a (say $1 \text{ V} = V_H$) battery. The capacitor now discharges to V_H through R_2 . When $i_D = i_0$ reaches the holding current $I_H = 20 \text{ mA}$, the diode switches off and C begins to charge again also, $I_A = 20 \text{ A}$.

 

When diode is ON:

$$V_0 = V_{\infty} - (V_{\infty} - V_1)e^{-t/T_{ON}}$$

$$V_{\infty} = 1 \text{ V and } V_1 = 100 \text{ V}$$

where

$$\therefore V_0 = 1 + 99e^{-t/T_{ON}} \quad \dots(i)$$

where

$$T_{ON} = R_2 C$$

Now,


$$i_0 = C \frac{dV_0}{dt}$$

\Rightarrow

$$i_0 = \frac{-99}{T_{ON}} e^{-t/T_{ON}}$$

At
 
$$t = T_2, i_0 = -20 \times 10^{-3} \text{ A} \quad (\text{Given})$$



When diode is OFF:

$$V_0 = V_\infty - (V_\infty - V_1)e^{-t/T_{OFF}}$$

where $V_\infty = 200 \text{ V}$ and $V_1 = 1.1 \text{ V}$

$$T_{OFF} = (R_1 + R_2)C \approx RC$$

At $t = T_1$, $V_0 = 100 \text{ V}$

$$\therefore \text{Repetitive frequency} = f = \frac{1}{T_1 + T_2} = 500 \text{ Hz}$$

After solving all the above equations we get,

$$R_1 = 1 \text{ M}\Omega, R_2 = 100 \Omega \text{ and } C = 5 \mu\text{F}.$$

Q3 For an SCR, the gate cathode characteristic has a straight-line slope of 130. For trigger source voltage of 15 volt and allowable gate power dissipation of 0.5 watts. Determine the Gate-source resistance?

Solution:

Here given that, Power = $V_g I_g = 0.5 \text{ Watt}$... (i)

and $\frac{V_g}{I_g} = 130$... (ii)

So, $130 I_g^2 = 0.5$ [From equation (i) and (ii)]

or $I_g^2 = \frac{0.5}{130}$

or $I_g = \sqrt{3.846 \times 10^{-3}} = 0.062 \text{ A}$

$\therefore I_g = 62 \text{ mA}$

So, gate voltage = $V_g = 130 I_g$

$\Rightarrow V_g = 8.06 \text{ volt}$


In the SCR, for the Gate circuit we have,

$$E_s = I_g R_s + V_g = 0.062 \times R_s + 8.06$$

or $\frac{15 - 8.06}{0.062} = R_s$

\therefore Gate-source resistance (R_s) = 111.94Ω

 Q4 Thyristor shown in the figure has $I^2 t$ rating of $20 \text{ A}^2 \text{ sec}$. If terminal 'A' get short circuited to the ground. Calculate the fault clearance time so that SCR is not damaged.



Solution:

The worst possible fault current should be considered for calculating the fault clearance time. Maximum fault current occurs when source voltage is at its peak value = $230\sqrt{2}$ volt, when terminal 'A' gets shorted circuited to the ground, the resistance offered to source is equal to,

$$\frac{10 \times 1}{11} + (1) = \frac{21}{11} \Omega$$

Assuming maximum fault current = $\frac{230\sqrt{2} \times 11}{21} \text{ A}$, which is to remain constant during the short clearance time (t_c) we get,

$$\int_0^{t_c} i^2 dt = \int_0^{t_c} \left(\frac{230\sqrt{2} \times 11}{21} \right)^2 \cdot dt = 20 \text{ A}^2$$

or
$$t_c = 20 \left[\frac{21}{230\sqrt{2} \times 11} \right]^2 \times 1000 \text{ ms}$$

$\Rightarrow t_c = 0.6892 \text{ m-sec}$

Practice Questions : Level-II

Q5 For an SCR, gate-cathode characteristic is given by the equation,

$$V_g = 1 + 10 I_g$$

The Gate source voltage is a rectangular pulse of 15 V with 20 μ -sec duration. For an average gate power dissipation of 0.3 Watt and a peak gate-drive power of 5 Watt.

Calculate:

- the resistance to be connected in series with the SCR gate.
- the triggering frequency.
- the duty cycle of the triggering pulse.

Solution:

(a) For an SCR, we have given,

$$V_g = 1 + 10 I_g \quad \dots(i)$$

For pulse-triggering of SCRs during pulse-on period, we have

$$(\text{peak-gate voltage}) \times (\text{peak-gate current}) = \text{peak-gate drive power i.e. } P_{gm} \quad \dots(ii)$$

As the gate rectangular pulse width is 20 μ -sec (i.e. less than 100 μ -sec), so there is no any dc data will be applicable. Had the gate pulse width been more than 100 μ -sec, the relation given,

$$V_g = 1 + 10 I_g$$

$$V_g \times I_g = (1 + 10 I_g) I_g$$

$\Rightarrow 10 I_g^2 + I_g = 0.3 \text{ Watt}$, will holds good but as the dc data not applied here, we should note that:

$$(1 + 10 I_g) \times I_g = 5$$

$$\Rightarrow 10 I_g^2 + I_g - 5 = 0 \quad \dots(iii)$$

$$\therefore I_g = 0.659 \text{ A or } -0.759 \text{ A}$$

So, we get the value of $I_g = 0.659 \text{ A}$

Hence, amplitude of the current pulse = 0.659 A

Now, during the pulse-ON period,

$$E_s = I_g + I_g R_s$$

$$= I_g R_s + (10 I_g + 1)$$

[From equation (i)]

$$\Rightarrow R_s = \frac{E_s - V_g}{I_g} = \frac{15 - 1 - (10 \times 0.659)}{0.659}$$

$$\therefore R_s = 11.24 \Omega$$


(b) Since,
$$P_{gm} = \frac{P_{gaV}}{fT} \quad \text{[Here, } T = 20 \mu\text{-sec]}$$

and Triggering frequency $(f) = \frac{P_{gaV}}{T \times P_{gm}}$

$$\Rightarrow f = \frac{0.3 \times 10^6}{20 \times 5} = 3 \text{ kHz}$$

(c) Duty cycle = $d = fT = 3 \times 10^3 \times 20 \times 10^{-6} = 0.06$

- Q6** A relaxation oscillator using an UJT as shown in figure below, is to be designing for triggering of an SCR. The data of an UJT is $\eta = 0.72$, $I_P = 0.6 \text{ mA}$, $V_P = 18 \text{ V}$, $V_V = 1 \text{ V}$, $I_V = 2.5 \text{ mA}$, $R_{BB} = 5 \text{ k}\Omega$, normal leakage current with emitter open = 4.2 mA , firing frequency is 2 kHz . Then for $C = 0.04 \text{ }\mu\text{F}$, determine the value of R , R_1 and R_2 .

 **Solution:**

In an UJT, the time required (T) for a capacitor (C) to charge from initial voltage ' V_V ' to peak point voltage ' V_P ' through a large resistor ' R ' can be obtained as:

$$T = \frac{1}{f} = RC \ln \left(\frac{1}{1 - \eta} \right) \quad \dots(i)$$

$$\Rightarrow R = \frac{1}{f C \ln \left(\frac{1}{1 - \eta} \right)} = \frac{10^6}{2000 \times 0.04 \times \ln(3.57)}$$

$$\therefore R = 9.82 \text{ k}\Omega$$

As, V_D is not given so,

$$V_P = \eta V_{BB}$$

$$\Rightarrow V_{BB} = \frac{V_P}{\eta} = \frac{18}{0.72} = 25 \text{ V}$$

$$\text{we know that, } R_2 = \frac{10^4}{\eta V_{BB}} = \frac{10^4}{0.72 \times 25} = 555.5 \text{ }\Omega$$

As given that, emitter is open,

$$\text{So, } V_{BB} = \text{normal leakage current } (R_1 + R_2 + R_{BB})$$

$$\Rightarrow R_1 + R_2 + R_{BB} = \frac{25 \times 10^3}{4.2} = 5.95 \times 10^3 \text{ }\Omega$$

$$\Rightarrow R_1 = (5952.38 - 5000 - 555.5) \text{ }\Omega$$

$$\therefore R_1 = 397 \text{ }\Omega$$

- Q7** What are Opto-isolators? Where do they find application? Discuss their propagation delay, operating voltage range and power dissipation.

Solution:

The opto-isolators which is also called opto-coupler are the device which are optically coupled but electrically isolated that incorporate many characteristics.

\Rightarrow A schematic arrangement of opto-coupler is given below:

