

# POSTAL Book Package

# 2021

## Instrumentation Engineering

### Objective Practice Sets

#### Measurements

#### *Contents*

Sl. Topic	Page No.
1. Static and Dynamic Characteristics, Error Analysis .....	2 - 7
2. Galvanometers, Voltmeters and Ammeters .....	8 - 16
3. Measurement of Resistance, Potentiometer, AC & DC Bridges .....	17 - 26
4. Measurement of Energy and Power .....	27 - 31
5. Digital Voltmeter (DVM) and Q-meter .....	32 - 35
6. Cathode Ray Oscilloscope .....	36 - 39



**MADE EASY**  
Publications

**Note:** This book contains copyright subject matter to MADE EASY Publications, New Delhi. No part of this book may be reproduced, stored in a retrieval system or transmitted in any form or by any means. Violators are liable to be legally prosecuted.

# Galvanometers, Voltmeters and Ammeters

- Q.1** Match **List-I (Instrument)** with **List-II (Property/use)** and select the correct answer using the codes. Given below the lists :
- List-I**
- PMMC
  - Moving Iron
  - Thermocouple
  - Electrostatic type
- List-II**
- Square law type scale
  - Very good high frequency response
  - Linear scale over the entire range
  - Voltmeter
- Codes:**
- |     | A | B | C | D |
|-----|---|---|---|---|
| (a) | 4 | 1 | 2 | 3 |
| (b) | 3 | 2 | 1 | 4 |
| (c) | 4 | 2 | 1 | 3 |
| (d) | 3 | 1 | 2 | 4 |
- Q.2** The voltage of a circuit is measured by a voltmeter having a finite resistance which is half of the output resistance of the circuit. The voltmeter will measure
- higher value of voltage
  - lower value of voltage
  - exact value of voltage
  - it will measure zero
- Q.3** An ac voltmeter has a range of 0-600 mV and its accuracy is 0.5% of the f.s.d. (full scale deflection). If the input voltage to the instrument is 200 mV, the output of the instrument would be
- 201 mV
  - 199 mV
  - Between 199 and 201 mV
  - Between 197 and 203 mV
- Q.4** The deflection angle of the pointer of an ideal moving iron ammeter is  $25^\circ$  for 2 A dc current. If a current of  $2 \sin(314)t$  A is passed through the ammeter then the deflection angle is \_\_\_\_\_ degree.
- Q.5** Which one of the following measuring instruments would consume the LOWEST power from the source during measurement?
- Permanent magnet moving coil
  - Electronic multimeter
  - Electrostatic instrument
  - Moving iron instrument
- Q.6** In a moving-iron meter, the deflecting torque is proportional to
- square of the current through the coil
  - current through the coil
  - sine of the current through the coil
  - square-root of the current through the coil
- Q.7** Which of the following statements is true?
- Deflection type instruments are more sensitive as compared with null type of instruments.
  - Deflection type instruments are less sensitive as compared to the null type of instruments.
  - Null type of instruments are more suited for measurement in dynamic conditions as compared with the deflection type of instruments.
  - All of the above.
- Q.8** A voltmeter of 0-1 volt range is desired to measure 0-100 volt. The value of series resistance  $R_s$  required, if the sensitivity of the voltmeter is  $1\text{k}\Omega/\text{V}$  is \_\_\_\_\_  $\text{k}\Omega$ .

**Q.9** If a current of  $3\sin(\pi t)$  amperes is passed through a moving iron ammeter, the ammeter deflection angle is  $135^\circ$ . The applied dc current if the deflection of the pointer is  $30^\circ$  is \_\_\_\_\_ A dc.

**Q.10** A moving iron voltmeter is connected across the voltage source whose instantaneous value is  $v(t) = 5 + 10 \cos(314t + 30^\circ)$ . The reading of the meter is

- (a) 15 V                      (b) 5 V  
(c)  $\sqrt{125}$  V                (d)  $\sqrt{75}$  V

**Q.11** The inductance of MI type of instrument is given by

$$L = 10 - 5\theta - 2\theta^2 \mu\text{H}$$

Where,  $\theta$  is deflection in radians. The spring constant for the instrument,  $k$  is  $24 \times 10^{-6}$  Nm/rad. The magnitude of deflection for an input current of 5 amperes is \_\_\_\_\_ rad.

**Q.12** The current in a circuit consist of a dc component of 10 A superimposed on a 50 Hz. Sinusoidal component of rms value of 10 A. The reading shown by a PMMC ammeter will be

- (a)  $10\sqrt{2}$  A                (b) 0 A  
(c) 10 A                      (d)  $\left(10 + \frac{10}{\pi}\right)$  A

**Q.13** An ammeter of range 0 to 1 A is used to measure current in the range of 0 to 100 A. If internal resistance of the ammeter is  $1000 \Omega$ . The value of shunt resistance required is \_\_\_\_\_  $\Omega$

**Q.14** The deflection angle of the pointer of an ideal moving iron ammeter is  $30^\circ$  for 1.5 ampere dc current. If a current of  $2 \sin(314t)$  amperes is passed through the ammeter then the deflection angle is \_\_\_\_\_ degree.


**Q.15** The sensitivity of a PMMC instrument is  $10 \text{ k}\Omega/\text{V}$ . If this instrument is used in a rectifier type voltmeter with half waves rectification. What would be the sensitivity ?

- (a)  $10 \text{ k}\Omega/\text{V}$                 (b)  $9 \text{ k}\Omega/\text{V}$   
(c)  $4.5 \text{ k}\Omega/\text{V}$               (d)  $22.2 \text{ k}\Omega/\text{V}$

**Q.16** A voltmeter of 0 - 1 volt range is desired to measure 0 - 20 volt. The value of resistance required to be connected with the voltmeter if the sensitivity of the voltmeter is  $1.5 \text{ k}\Omega/\text{V}$ , is

- (a)  $28.5 \text{ k}\Omega$  in parallel  
(b)  $28.5 \text{ k}\Omega$  in series  
(c)  $12.5 \text{ k}\Omega$  in parallel  
(d)  $12.5 \text{ k}\Omega$  in series

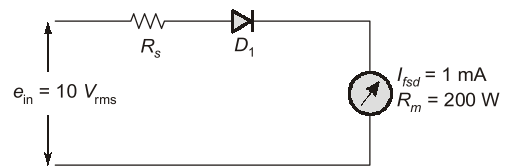**Q.17** Calculate the value of the multiplier resistor for a  $10 V_{\text{rms}}$  range on the voltmeter as shown in the figure given below. Assuming forward resistance of the diode is zero and the reverse resistance is infinite.





- (a)  $2.3 \text{ k}\Omega$                       (b)  $3.3 \text{ k}\Omega$   
(c)  $4.3 \text{ k}\Omega$                       (d)  $5.3 \text{ k}\Omega$

**Q.18** A 10 V Full-scale voltmeter having  $100 \text{ k}\Omega/\text{V}$  sensitivity is used to measure the output of a photovoltaic cell having an internal resistance of  $1 \text{ M}\Omega$ . The voltmeter reads 5 V. The voltage generated by the photovoltaic cell is.

- (a) 5 V  
(b) 10 V  
(c) Greater than 5 V but less than 10 V  
(d) Greater than 10 V

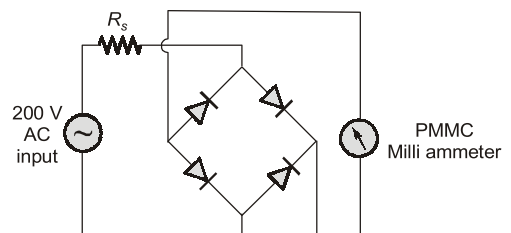**Q.19** A rectifier type ac voltmeter consists of a series resistance  $R_s$ , an ideal full-wave rectifier bridge and a PMMC instrument as shown in the figure. The internal resistance of the instrument is  $200 \Omega$  and a full scale deflection is produced by a dc current of 1 mA. The value of  $R_s$  required to obtain full scale deflection with an ac voltage of  $200 \text{ V}$  (rms) applied to the input terminal, is



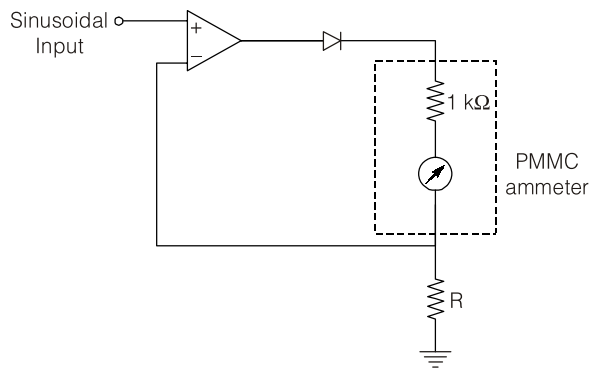

- Q.41** An ac voltmeter using full-wave rectification and having a sinusoidal input has an ac sensitivity equal to
- (a) 1.414 times dc sensitivity
  - (b) dc sensitivity
  - (c) 0.90 times dc sensitivity
  - (d) 0.707 times dc sensitivity

- Q.42** Match List-I (Parameter to be measured) with List-II (Instrument to be used) and select the correct answer using the code given below the lists:

**List-I**

- A. Average value of current
- B. RMS value of current
- C. Frequency of a wave
- D. Strain gauge resistance

**List-II**

- 1. Self-balancing bridge
- 2. Wien bridge
- 3. PMMC ammeter
- 4. Moving-iron ammeter

**Codes:**

	A	B	C	D
(a)	3	4	2	1
(b)	2	1	3	4
(c)	3	1	2	4
(d)	2	4	3	1

- Q.43** What is the series resistance required to extend the 0-100 V range of a 20000 Ω/V meter to 0-1000 V?
- (a) 10 MΩ
  - (b) 16 MΩ
  - (c) 18 MΩ
  - (d) 20 MΩ




**Answers Galvanometers, Voltmeters and Ammeters**

1. (d)    2. (b)    3. (d)    5. (d)    6. (a)    7. (b)    10. (d)    12. (c)    15. (c)  
 16. (b)    17. (c)    18. (b)    19. (a)    20. (a)    21. (a)    22. (b)    23. (b)    24. (b)  
 25. (c)    26. (d)    27. (c)    28. (a)    29. (b)    30. (b)    31. (d)    32. (d)    34. (c)  
 36. (d)    38. (c)    39. (a)    41. (c)    42. (a)    43. (c)

**Explanations Galvanometers, Voltmeters and Ammeters**

1. (d)  
 PMMC → linear scale  
 Moving iron → square law scale  
 Thermocouple → good high frequency response  
 Electrostatic → voltmeter

2. (b)

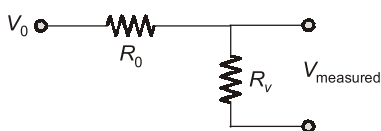

$$V_{\text{measured}} = \frac{R_v}{R_v + R_0} \cdot V_0$$

since  $(R_v + R_0)$  is more compared to  $R_v$   
 $\therefore V_{\text{measured}}$  is lower than  $V_0$

3. (d)

$$\text{Deviation} = 600 \times \frac{0.5}{100} = 3$$

Thus, for an input of 200 mV, the output of the instrument will lie in the range  $200 \pm 3$  = between 197 and 203 mV.

36. (d)

Moving-iron meter and thermocouple meter have square-law response so do not have linear scale.

37. (0.002)

$$I_m = 10 \text{ mA}$$

$$R_m = \frac{100}{10} = 10 \Omega$$

$$\text{Shunt multiplying factor} = \frac{50}{10 \times 10^{-3}} = 5000$$

$$\text{Shunt resistance} = \frac{10}{5000 - 1} = 0.002 \Omega$$

38. (c)

Reading of ac ammeter = rms value


$$\text{rms value} = I_{\max} \sqrt{\alpha}$$

where,  $\alpha$  = duty cycle

$$\alpha = \frac{1}{2}$$

$$\text{rms value} = 100 \text{ mA} \sqrt{\frac{1}{2}} \cong 71 \text{ mA}$$

40. (22.5)

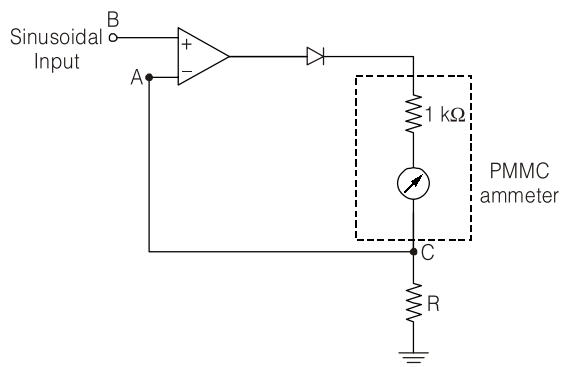

$$V_B = V_{\text{avg}} = \frac{200\sqrt{2}}{\pi} = 90 \text{ mV}$$

$$V_A = V_B$$

(By the concept of virtual ground)

$$\therefore V_A = 90 \text{ mV}$$

Also, it can be observed that  $V_C = V_B$  at point 'C'

$$V_C = I_R$$

$$90 \times 10^{-3} = 4 \times 10^{-3} \times R$$

$$R = \frac{90}{4} = 22.5 \Omega$$

41. (c)

For full-wave rectifier type of instruments,

$$V_{\text{avg}} = 0.9 V \text{ where } V = V_m / \sqrt{2}$$

43. (c)

Initial resistance =  $20000 \times 100 = 2 \text{ M}\Omega$

Final resistance =  $20000 \times 1000 = 20 \text{ M}\Omega$

$\therefore$  Series resistance =  $20 - 2 = 18 \text{ M}\Omega$

