

ESE

MADE EASY **WORKBOOK** 2026



**Detailed Explanations of
Try Yourself Questions**

Electrical Engineering
Microprocessors



1

Basics of Intel 8085, Intel 8086 and other Microprocessors

T1. (b)

In 8085 lower order address bus and data bus are multiplexed to reduce the no. of pins and demultiplexing is done using ALE pin which is when 1 then lower order byte work as address and when 0 work as data.

T2. (b)

The first machine cycle of any instruction is opcode fetch cycle.

T3. (c)

T4. (d)

STA 16-bit address → Store the content of accumulator at 16-bit address.

T5. (b)


Ready → 0 ; microprocessor with for I/O
1 ; indicates I/O is ready for communication

■■■■

2

8085 Programming

T1. Sol.

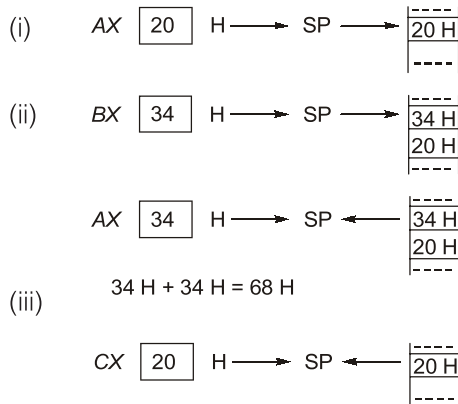

Contents of registers.

AX = 68 H
 BX = 34 H
 CX = 20 H

T2. Sol.

Infinite.

T3. (c)

RST 6.5 and RST 5.5 both are Maskable interrupt.

address location of RST 5.5

$$= (8 \times 5.5)_{10} = (44)_{10} = (2C)_{16}$$

XTHL → is a instruction which exchanges top of stack with HL pair.

SID is signal used for serial input data.

T4. (b)

AC ⇒ Auxiliary carry flags status is used only in DAA {DAS}

Decimal adjust after additions {subtraction}

All conditional jumps are short jumps $z = 1$ if data is same when compared.

T5. (a)

SI, DI i.e. source index and destination index registers are used for extra segment (or) alternate data segment.

■■■■

3

8085 Microprocessor Interfacing and Applications

T1. Sol.


Total Memory of 8085 = 2^{16} bytes

Size of one page = $256 = 2^8$ bytes

Number of pages = $\frac{2^{16}}{2^8} = 2^8 = 256$ pages

T2. (d)

1 KB memory is interfaced

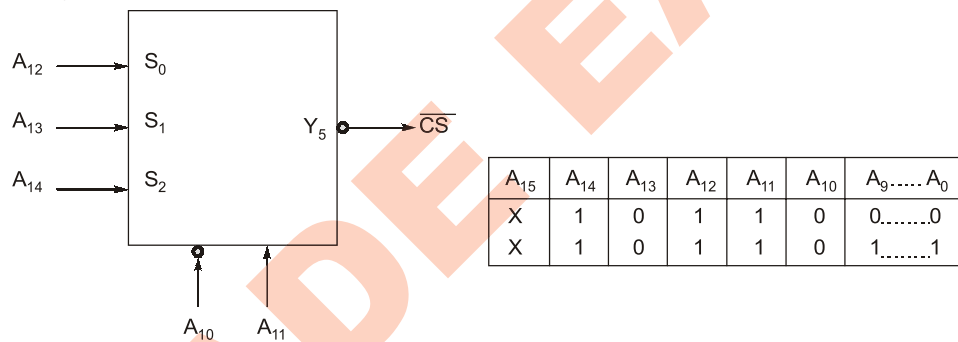

If $A_{15} = 0 \Rightarrow 5800 \text{ H to } 5 \text{ BFFH}$

If $A_{15} = 1, \Rightarrow \text{D800H to DBFFH}$

T3. Sol.

8085 is an 8 bit microprocessor with 8 bit address lines for I/O devices. So, in I/O mapped I/O mode, 8085 can have at most $2^8 = 256$ input devices and 256 output devices. Their addresses will lie in the range from 00000000 to 11111111.

T4. (d)

Find whether I/O is I/O mapped I/O or memory mapped I/O.

As per the question $\overline{\text{IO}/\overline{\text{M}}}$ signal is connected to $\overline{\text{G}_{2\text{A}}}$ i.e. $\text{IO}/\overline{\text{M}} = 0$, hence I/O is allocated address as memory mapped I/O i.e. it has 16-bit address. As it is given in question to access data from I/O, it is an I/P device so instruction must be 'LDA', hence the answer is LDA F8F8H.

By considering the lines A_{15} to A_0 , the address F8F8H can be obtained.

T5. Sol.

As per the memory map given

F400H – F7FFH, the decoder input lines values can be found i.e. A_{12} , A_{11} and A_{10} .

A_{15}	A_{14}	A_{13}	A_{12}	A_{11}	A_{10}	A_9	A_8	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
1	1	1	1	0	1	0	0	0	0	0	0	0	0	0	0
F				4				0				0H			

$\therefore A_{12} A_{11} A_0$ are 10 1 is 5.

Decoding logic of decoder:

Input			Output
C	B	A	
A_{12}	A_{11}	A_0	
0	0	0	Y_0
0	0	1	Y_1
	$\vdots$		
1	0	1	Y_5
1	1	0	Y_6
1	1	1	Y_7

$\therefore Y_5$ output is connected to the chip select line of memory.

■■■■